

Name:

Id#

COE 202, Term 162
Fundamentals of Computer Engineering

Quiz# 3

Date: Thursday, March 23

Q1. Simplify the following Boolean function **F** together with the don't care condition **d** in (1) sum-of-products and (2) product-of-sums form. In your solution, identify prime implicants and essential prime implicants for each case.

$$F(W, X, Y, Z) = \sum m(0, 1, 2, 3, 7, 8, 10), d(W, X, Y, Z) = \sum m(5, 6, 11, 15)$$

Q2. Convert the circuit given below using minimum number of only 2-input NOR gates and inverters.

