

COE 202, Term 102
Fundamentals of Computer Engineering

Quiz# 3

Date: Saturday, April 16

Q1.

- (i) Simplify the following Boolean functions **F** together with the don't care conditions **d**, into minimal sum-of-products expressions. Identify all the prime implicants and the essential prime implicants.

$$F(A, B, C, D) = \sum m(0, 6, 7, 8, 9), \quad d(A, B, C, D) = \sum m(1, 2, 5, 10, 12, 13, 14, 15)$$


	CD			
	00	01	11	10
AB				
00	1	X	0	X
01	0	X	1	1
11	X	X	X	X
10	1	1	0	X

Prime Implicants: $C'D, CD', BC, BD, B'C', B'D', AC', AD'$

There are no essential prime implicants.

$$F = B'C' + BC$$

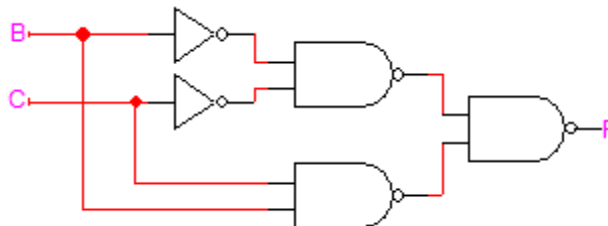- (ii) Show an implementation of the function using minimal number of NAND gates.



(iii) Show an implementation of the function using minimal number of NOR gates.

		CD			
		00	01	11	10
AB	00	1	X	0	X
	01	0	X	1	1
	11	X	X	X	X
	10	1	1	0	X

$$F' = B'C + BC' \Rightarrow F = F'' = (B+C')(B'+C)$$

