

Name: KEY

Id#

COE 202, Term 121  
Digital Logic Design

Quiz# 3

Date: Saturday, Nov. 10

Q1. For the Boolean function  $F(W, X, Y, Z) = \sum m(0, 1, 2, 3, 7, 8, 10)$ ,  $d(W, X, Y, Z) = \sum m(5, 6, 11, 15)$  shown in the k-map below:

WX \ YZ	00	01	11	10
00	1	1	1	1
01	0	x	1	x
11	0	0	x	0
10	1	0	x	1



- (i) Identify all the prime implicants and the essential prime implicants of F.
- (ii) Simplify the Boolean function **F** into a minimal sum-of-products expression.

Prime implicants:  $\bar{w}\bar{x}$ ,  $\bar{x}\bar{z}$ ,  $\bar{w}z$ ,  $\bar{w}y$ ,  $y\bar{z}$ ,  $\bar{x}y$

Essential prime implicants:  $\bar{x}\bar{z}$

$$F = \bar{x}\bar{z} + \bar{w}z$$

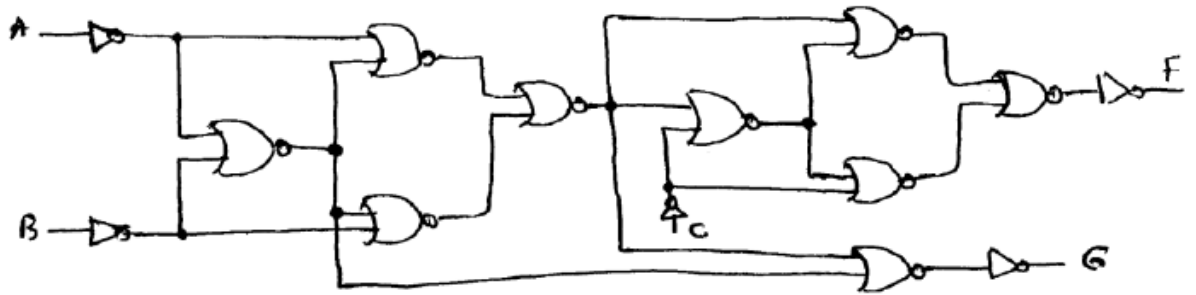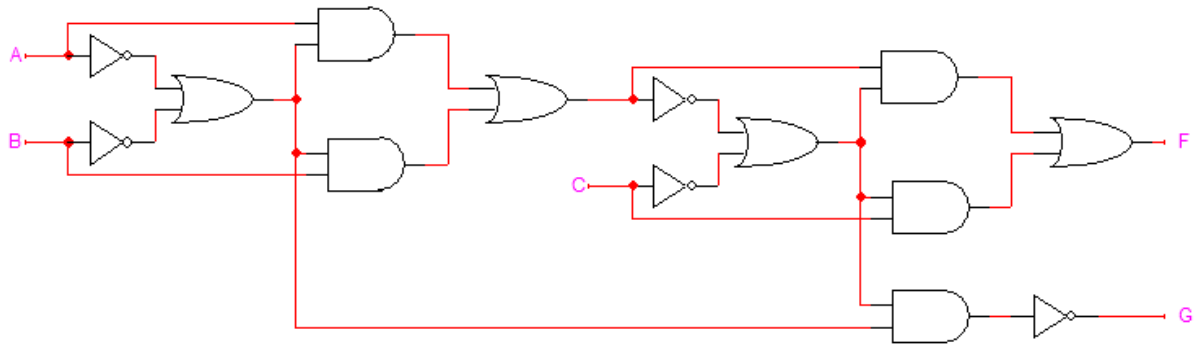**Q2.** Implement the logic circuit given below using only NOR and NOT gates



**Q3.** Design a 3-bit decremter using only basic gates (AND, OR, and NOT). The circuit takes a 3-bit unsigned number  $I = I_2I_1I_0$  as input and generates a 3-bit output number  $Z = Z_2Z_1Z_0$  and a **Valid** output  $V$ . Whenever  $I > 0$  the output  $Z = I - 1$  and  $V = 1$ . If  $I = 0$ , the output is invalid which is indicated by an output  $V = 0$ . Derive the simplified Boolean expressions of all outputs.

$I_2$	$I_1, I_0$		00	01	11	10	
			X	0	0	1	
			1	0	0	1	

$Z_0 = \overline{I_0}$

$I_2$	$I_1, I_0$		00	01	11	10	
			X	0	1	0	
			1	0	1	0	

$Z_1 = \overline{I_1}\overline{I_0} + I_1I_0$

$I_2$	$I_1, I_0$		00	01	11	10	
			X	0	0	0	
			1	0	1	1	

$Z_2 = I_2 \cdot (I_0 + I_1)$

$I_2$	$I_1$	$I_0$	$Z_2$	$Z_1$	$Z_0$	$V$
0	0	0	X	X	X	0
0	0	1	0	0	0	1
0	1	0	0	0	1	1
0	1	1	0	1	0	1
1	0	0	0	1	1	1
1	0	1	1	0	0	1
1	1	0	1	0	1	1
1	1	1	1	1	0	1

$V = \text{Max\_Term } \Phi$   
 $V = I_2 + I_1 + I_0$