

Name:

Id#

COE 202, Term 162
Fundamentals of Computer Engineering

Quiz# 3 Solution

Date: Thursday, March 23

Q1. Simplify the following Boolean function **F** together with the don't care condition **d** in (1) sum-of-products and (2) product-of-sums form. In your solution, identify prime implicants and essential prime implicants for each case.

$$F(W, X, Y, Z) = \sum m(0, 1, 2, 3, 7, 8, 10), d(W, X, Y, Z) = \sum m(5, 6, 11, 15)$$

Sum of products:

wx \ yz	00	01	11	10
00	1	1	1	1
01	0	X	1	X
11	0	0	X	0
10	1	0	X	1

Prime implicants: $\bar{w}\bar{x}, \bar{x}\bar{z}, \bar{w}z, \bar{w}y, yz, \bar{x}y$

Essential prime implicants: $\bar{x}\bar{z}$

$$F = \bar{x}\bar{z} + \bar{w}z$$

Product of sums:

wx \ yz	00	01	11	10
00	0	0	0	0
01	1	X	0	X
11	1	1	X	1
10	0	X	X	0

Prime implicants: $x\bar{y}, x\bar{z}, wx, wz$

Essential prime implicants: wz

$$\bar{F} = wz + x\bar{z}$$

$$F = \bar{F} = (\bar{w} + \bar{z})(\bar{x} + z)$$

Q2. Convert the circuit given below using minimum number of only 2-input NOR gates and inverters.

