

Name:

Id#

COE 202, Term 132
Digital Logic Design

Quiz# 4

Date: Tuesday, April 15

Q1. Determine the decimal value of the 7-bit binary number (1011010) when interpreted as:

An unsigned number	A signed-magnitude number	A signed-1's complement number	A signed-2's complement number


ii. Represent the decimal value (- 21) in binary using a total of 7 bits in the following notations:

A signed-magnitude number	A signed-1's complement number	A signed-2's complement number

iii. Perform the following signed-2's complement arithmetic operations in binary using 5 bits. All numbers given are represented in the signed-2's complement notation. Indicate clearly the carry values from the last two stages. For each of the three operations, check and indicate whether overflow occurred or not.

	a. $\begin{array}{r} 01101 \\ +10110 \\ \hline \end{array}$	b. $\begin{array}{r} 01010 \\ -11001 \\ \hline \end{array}$	c. $\begin{array}{r} 11010 \\ -00100 \\ \hline \end{array}$
Overflow Occurred? (Yes/No)			

 (B) Consider the 2's complement 4-bit adder/subtractor hardware shown (FA = full adder).



i. Fill in the spaces in the table below.



Inputs			Outputs			
A	B	Control	S (binary)	C ₄	C ₃	Overflow
0111	0101	0				
1010	1101	1				

ii. What type of 4-bit adder is used in this design? (Circle the correct answer):

- Carry-ripple adder
- Carry-look-ahead adder

(C) Consider a 2-bit version of the hardware above which is shown below. Shown also is full adder used. Given that each basic gate (i.e. AND, OR, NOT) has a delay of τ ns and the XOR gate has a delay of 3τ :

The Full Adder (FA)

  

i. Express, as a function of τ , the longest time interval needed for the hardware to perform an operation on the two 2-bit numbers.

ii. If such an operation must be performed in no longer than 33 ns, calculate the maximum basic gate delay allowed.