

Name: KEY

Id#

COE 202, Term 121
Digital Logic Design

Quiz# 4


Date: Monday, Dec. 10

Q1. Design a JK flip flop using a T flip flop.

Q	\bar{Q}	K	Q^+	T
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1


$\bar{Q}K$	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$T = \bar{Q}\bar{J} + QK$$

 

Q2. Given the following synchronous sequential circuit with two inputs {X, Y} and one output {Z}:

 - (i) Derive the state table of the circuit.
- (ii) Show the state diagram of the circuit.
- (iii) Is the circuit Mealy or Moore?
- (iv) Determine the output sequence for the input sequence $XY = \{00, 01, 10, 11, 00\}$. Note that 00 is the start of the sequence. Assume that the machine is reset to the state 0.




(i) $z = x \oplus y \oplus Q$

$D = xy + Q(x \oplus y)$

State Table:

Q	x	y	Q ⁺	z
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(ii) State Diagram:

 

(iii) The circuit is Mealy because the output Z depends on the inputs and current state Q .

(iv) $0 \xrightarrow[0]{00} 0 \xrightarrow[1]{01} 0 \xrightarrow[1]{10} 0 \xrightarrow[0]{11} 1 \xrightarrow[1]{00} 0$

Thus, the output sequence produced

is $\{0, 1, 1, 0, 1\}$.

