 


COE 202, Term 122
 Digital Logic Design

Quiz# 4

Date: Monday, April 8

Q1. We would like to design an adder to add the 8-bit constant 10101010 to an arbitrary 8-bit number. The adder is to be designed using four identical adder modules, each of which will add 2 bits of the number to the constant (10) and a carry from the next lower pair of bits and produce 2 bits of the sum and the carry to the next bits. A block diagram of part of this design is shown below:



The problem each 2-bit adder solves is:

		c
	a	b
+	1	0
	y	s t

- (i) Show a truth table for the 2-bit adder (it has three inputs: a, b, and c, and it has three outputs: y, s, and t), and find minimal SOP expressions for each output.
- (ii) Compute the delay from the c-input of each module to the y output of that module and the total delay for the 8 bits. Assume that the delay of a gate is related to the number of inputs i.e. the delay of an inverter is 1, the delay of a 2-input gate is 2, etc.

(i)

a	b	c	y	s	t
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	1	0

a	bc	00	01	11	10
0		0	0	1	0
1		1	1	0	1

$$y = a + bc$$

a	bc	00	01	11	10
0		1	1	0	1
1		0	0	1	0

$$s = \bar{a}\bar{b} + \bar{a}c + abc$$

a	bc	00	01	11	10
0		0	1	0	1
1		0	1	0	1

$$t = \bar{b}c + b\bar{c}$$

(ii) Delay from the c-input of each module to the y-output of the module = $2 + 2 = 4$

Since the first block does not have a carry in, a carry is generated when $a = 1$. Thus, the delay of $y = 2$.

For the 2nd block & 3rd block, each will add a delay of 4. Thus, the delay of the carry out of the 3rd block is $2 + 4 + 4 = 10$

For the 4th block, the delay across the s output is the largest which is $10 + 3 + 3 = 16$. Thus, the longest delay across the circuit is 16.

Q2.

(i) Determine the decimal value of the 7-bit binary number (1011010) when interpreted as:

An unsigned number	A signed-magnitude number	A signed-1's complement number	A signed-2's complement number
90	-26	-37	-38

(ii) Represent the decimal value (-21) in binary using a total of 7 bits in the following notations:

A signed-magnitude number	A signed-1's complement number	A signed-2's complement number
1010101	1101010	1101011

(iii) Perform the following signed-2's complement arithmetic operations in binary using 5 bits. All numbers given are represented in the signed-2's complement notation. Indicate clearly the carry values from the last two stages. For each of the three operations, check and indicate whether overflow occurred or not.

	$\begin{array}{r} \text{a. } 01101 \\ +10110 \\ \hline \textcircled{1}00011 \end{array}$	$\begin{array}{r} \text{b. } 01010 \\ -11001 \\ \hline \textcircled{1}11010 \\ +00111 \\ \hline \textcircled{0}10001 \end{array}$	$\begin{array}{r} \text{c. } 11010 \\ -00100 \\ \hline \textcircled{1}11010 \\ +11100 \\ \hline \textcircled{1}10110 \end{array}$
Overflow Occurred? (Yes/No)	No	Yes	No