

Name: KEY

Id#

COE 202, Term 132
Digital Logic Design

Quiz# 4

Date: Tuesday, April 15

Q1. Determine the decimal value of the 7-bit binary number (1011010) when interpreted as:

An unsigned number	A signed-magnitude number	A signed-1's complement number	A signed-2's complement number
90	-26	-37	-38


ii. Represent the decimal value (-21) in binary using a total of 7 bits in the following notations:

A signed-magnitude number	A signed-1's complement number	A signed-2's complement number
1010101	1101010	1101011

iii. Perform the following signed-2's complement arithmetic operations in binary using 5 bits. All numbers given are represented in the signed-2's complement notation. Indicate clearly the carry values from the last two stages. For each of the three operations, check and indicate whether overflow occurred or not.

$ \begin{array}{r} 01010 \\ \text{a. } \begin{array}{r} \overset{1}{\leftarrow} 01101 \quad +13 \\ +10110 \quad +(-10) \\ \hline 00011 \quad +3 \checkmark \end{array} \end{array} $	$ \begin{array}{r} \text{b. } \begin{array}{r} 01010 \quad +10 \\ -11001 \quad 00111 \quad -(-7) \\ \hline \quad \quad \quad +17 \end{array} \\ \text{c. } \begin{array}{r} \overset{0}{\leftarrow} 01010 \\ +00111 \\ \hline 10001 \quad \times 15 \end{array} \end{array} $	$ \begin{array}{r} \text{c. } \begin{array}{r} 11010 \quad 00110 \quad -6 \\ -00100 \quad \quad \quad -(-4) \\ \hline \quad \quad \quad -10 \\ \overset{1}{\leftarrow} 11010 \\ +11100 \\ \hline 10110 \\ = -01010 \\ = -10 \checkmark \end{array} \end{array} $	
Overflow Occurred? (Yes/No)	No	Yes	NO

 (B) Consider the 2's complement 4-bit adder/subtractor hardware shown (FA = full adder).



i. Fill in the spaces in the table below.

Inputs			Outputs			
A	B	Control	S (binary)	C ₄	C ₃	Overflow
0111	0101	0	1100	0	1	1
1010	1101	1	1101	0	0	0

Handwritten binary calculations:

$$\begin{array}{r} 0111 \\ + 0101 \\ \hline 1100 \end{array}$$



$$\begin{array}{r} 1010 \\ - 1101 \\ \hline 1101 \end{array}$$

ii. What type of 4-bit adder is used in this design? (Circle the correct answer):

- Carry-ripple adder
- Carry-look-ahead adder

b. Consider a 2-bit version of the hardware above which is shown below. Shown also is full adder used. Given that each basic gate (i.e. AND, OR, NOT) has a delay of τ ns and the XOR gate has a delay of 3τ :

The Full Adder (FA)

  

i. Express, as a function of τ , the longest time interval needed for the hardware to perform an operation on the two 2-bit numbers.

$$(3 + 3 + 2 + 3)\tau = 11\tau$$

ii. If such an operation must be performed in no longer than 33 ns, calculate the maximum basic gate delay allowed.

$$33 \text{ ns} / 11 = 3 \text{ ns}$$