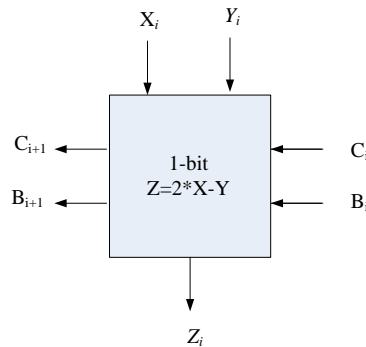


COE 202, Term 141
Digital Logic Design

Quiz# 4

Date: Thursday, Nov. 20

Q1 It is required to design a circuit to compute the equation $Z=2*X-Y$, where X and Y are two n -bit unsigned numbers. The circuit can be designed in a modular manner where it is designed for one bit and replicated n times. A 1-bit circuit block diagram is given below:




The meaning of the values of B_i and C_i is given in the table below:

B_i	C_i	Meaning
0	0	There is no carry or borrow
0	1	There is a carry of 1
1	0	There is a borrow of 1
1	1	This condition does not occur

For example, if $X_i=1$ and $Y_i=1$, then we should have $Z_i=1$, $B_{i+1}=0$ and $C_{i+1}=0$. If $X_i=0$ and $Y_i=1$, then we should have $Z_i=1$, $B_{i+1}=1$ and $C_{i+1}=0$.

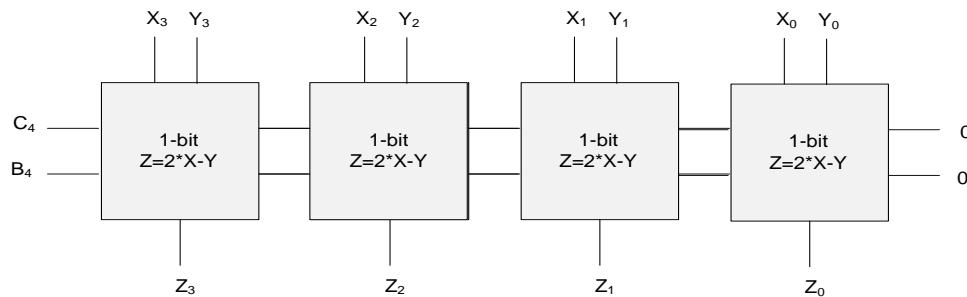The figure below shows how a 4-bit $Z=2*X-Y$ circuit is implemented using 4 copies of the basic 1-bit cell.



Derive the truth table for the basic one-bit cell. Derive the equation for the Z output only.

Truth Table:

X_i	Y_i	B_i	C_i	B_{i+1}	C_{i+1}	Z_i
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	1	0	1
0	0	1	1	X	X	X
0	1	0	0	1	0	1
0	1	0	1	0	0	0
0	1	1	0	1	0	0
0	1	1	1	X	X	X
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	0	0	1
1	0	1	1	X	X	X
1	1	0	0	0	0	1
1	1	0	1	0	1	0
1	1	1	0	0	0	0
1	1	1	1	X	X	X

$x_i y_i$ $B_i C_i$

	00	01	11	10
00	0	1	X	1
01	1	0	X	0
11	1	0	X	0
10	0	1	X	1

$$Z_i = \bar{y}_i C_i + \bar{y}_i B_i + y_i \overline{B_i C_i}$$

$$= \bar{y}_i (B_i + C_i)$$

$$+ y_i \overline{(B_i + C_i)}$$

$$= y_i \oplus (B_i + C_i)$$