

Name:

Id#

COE 202, Term 102
Fundamentals of Computer Engineering

Quiz# 5 (Take Home)

Due date: Saturday, May 7, 2011

Q.1. It is required to design a 4-bit arithmetic and logic unit that has two 4-bit inputs $A=A_3A_2A_1A_0$ and $B=B_3B_2B_1B_0$ and one **6-bit output** $C= C_5C_4C_3C_2C_1C_0$. The circuit implements the following functions based on the values of the four selection inputs S3, S2, S1 and S0.

S3 S2 S1 S0	Function
0 0 0 0	$C = A + B$
0 0 0 1	$C = A - B$
0 0 1 0	$C = A+1$
0 0 1 1	$C = A-1$
0 1 0 0	$C = A+ 2$
0 1 0 1	$C = A - 2$
0 1 1 0	$C = B$
0 1 1 1	$C = -B$
1 0 0 0	$C = 2B$
1 0 0 1	$C = 3B$
1 0 1 0	$C = 4B$
1 0 1 1	$C = A \text{ and } B$
1 1 0 0	$C = A \text{ or } B$
1 1 0 1	$C = A \text{ xor } B$
1 1 1 0	$C = A \text{ xnor } B$
1 1 1 1	$C = \text{not } B$

- (i) Show the block diagram design of your circuit using MSI components like Adder, Multiplexor, as needed.
- (ii) Model your design in logic works.
- (iii) Test your design and verify its correctness by simulation. Show snapshots of your simulation to demonstrate its correctness. For each function, test at least 4 input combinations of your choice to demonstrate correct functionality.

Submit your solution as a word document along with the circuits in one zipped file.