

**Name:**

**Id#**

**COE 202, Term 112  
Digital Logic Design**

**Quiz# 5**

Date: Wednesday, April 25

**Q1.** Design a rising edge-triggered D flip-flop using a rising edge-triggered JK flip flop.

**Q2.** A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following equations:

$$D_A = X \bar{Y} + X A \qquad D_B = X \bar{B} + X A \qquad Z = B$$

- (i) Draw the logic diagram of the circuit.
- (ii) Derive the state table.
- (iii) Derive the state diagram.