

Name:

Id#

COE 202, Term 141  
Digital Logic Design

Quiz# 5

Date: Thursday, Nov. 27

Q1 a. Fill in all blank cells in the two tables below.

Binary	Equivalent decimal value with the binary interpreted as:				
	Unsigned number	Signed-magnitude number	Signed-1's complement number	Signed-2's complement number	BCD number
10000000					

Decimal	Binary representation in 8 bits:		
	Signed-magnitude notation	Signed-1's complement notation	Signed-2's complement notation
- 75			

b. Using 2's-complement signed arithmetic in 5 bits, do the following operations **in binary**. Show all your work, and:


- Verify that you get the expected decimal results.
- Check for overflow and mark clearly any overflow occurrences.

(i)	(ii)
00111 - 10101 _____	10110 - 10011 _____

c. Consider the signed 2's complement arithmetic operation A - B in 6 bits. With B = 101100, the largest value allowed for A in order to avoid the occurrence of overflow is (\_\_\_\_\_)2.

**Q2** Assume that the delay of a 2-input XOR gate is 3ns while the delay of other gates is equal to the gate's number of inputs, i.e. the delay of an inverter is 1ns, the delay of a 2-input AND gate is 2ns, the delay of a 2-input OR is 2ns, the delay of a 3-input AND gate is 3ns, the delay of a 3-input OR gate is 3ns, etc.

 (a) **(6 points)** A 4-bit **Ripple Carry Adder (RCA)** is given below:



Determine and compute the **longest delay** in the **4-bit Ripple Carry Adder (RCA)**.

(b) **(4 points)** Show the design of a **2-bit Carry Look-Ahead Adder (CLA)** by drawing its logic diagram.

(c) **(3 points)** Using the delay assumptions given in the beginning of the question, determine and compute the **longest delay** in the **2-bit Carry Look-Ahead Adder (CLA)**.