

COE 202, Term 102
Fundamentals of Computer Engineering

Quiz# 5 (Take Home)


Due date: Saturday, May 7, 2011

Q.1. It is required to design a 4-bit arithmetic and logic unit that has two 4-bit inputs $A=A_3A_2A_1A_0$ and $B=B_3B_2B_1B_0$ and one **6-bit output** $C= C_5C_4C_3C_2C_1C_0$. The circuit implements the following functions based on the values of the four selection inputs S3, S2, S1 and S0.

S3 S2 S1 S0	Function
0 0 0 0	$C = A + B$
0 0 0 1	$C = A - B$
0 0 1 0	$C = A+1$
0 0 1 1	$C = A-1$
0 1 0 0	$C = A+ 2$
0 1 0 1	$C = A - 2$
0 1 1 0	$C = B$
0 1 1 1	$C = -B$
1 0 0 0	$C = 2B$
1 0 0 1	$C = 3B$
1 0 1 0	$C = 4B$
1 0 1 1	$C = A \text{ and } B$
1 1 0 0	$C = A \text{ or } B$
1 1 0 1	$C = A \text{ xor } B$
1 1 1 0	$C = A \text{ xnor } B$
1 1 1 1	$C = \text{not } B$

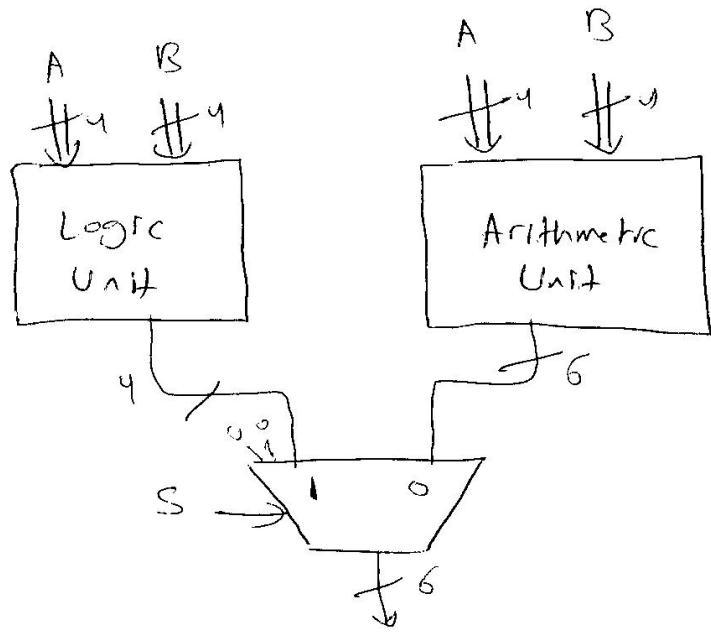- (i) Show the block diagram design of your circuit using MSI components like Adder, Multiplexor, as needed.
- (ii) Model your design in logic works.
- (iii) Test your design and verify its correctness by simulation. Show snapshots of your simulation to demonstrate its correctness. For each function, test at least 4 input combinations of your choice to demonstrate correct functionality.

We partition the design of the Arithmetic & Logic Unit into arithmetic unit and logic unit and we select between their outputs as shown below:




We design the select function as follows:


	$S_3 S_2$	$S_1 S_0$	00	01	11	10
00			0	0	0	0
01			0	0	0	0
11			1	1	1	1
10			0	0	1	0

$$S = S_3 S_2 + S_3 S_1 S_0$$

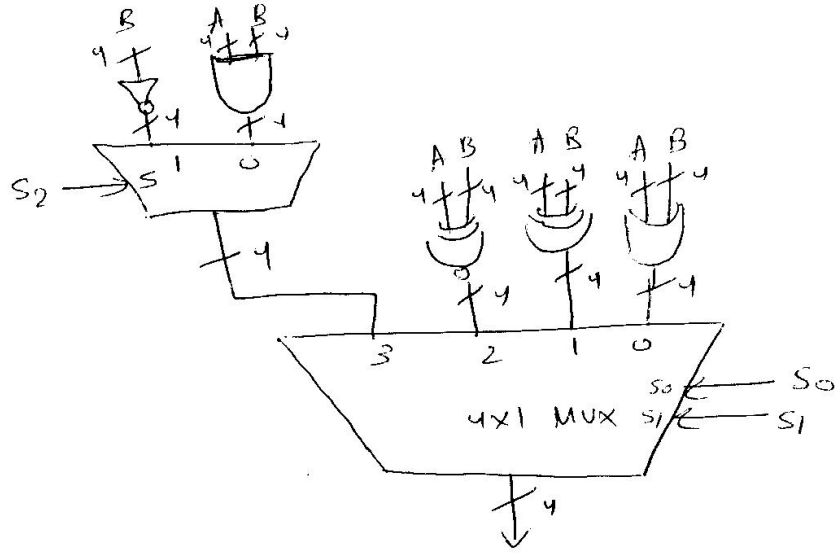Next, we design the logic unit as follows:



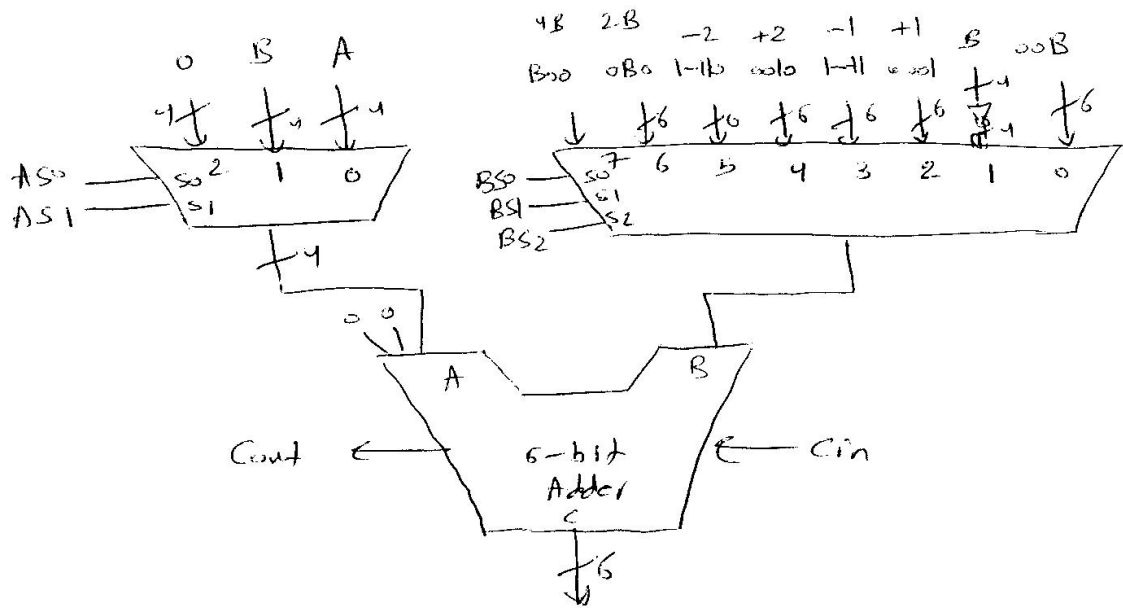The Arithmetic unit is designed as follows using one 6-bit adder:



After that, we need to find out the equations for C_{in} , A_{S1} , A_{S0} , B_{S2} , B_{S1} , and B_{S0} .

C_{in}

$S_3 S_2$	$S_1 S_0$			
	00	01	11	10
00	0	1	0	0
01	0	0	1	0
11	0	0	0	0
10	0	0	0	0

$$\begin{aligned}
 C_{in} &= \overline{S_3} S_2 S_1 S_0 + \overline{S_3} \overline{S_2} \overline{S_1} S_0 \\
 &= \overline{S_3} S_0 (S_2 S_1 + \overline{S_2} \overline{S_1}) \\
 &= \overline{S_3} S_0 (S_1 \oplus \overline{S_2})
 \end{aligned}$$

A_{S1}

$S_3 S_2$	$S_1 S_0$			
	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	0	0	0
10	1	0	0	1

$$A_{S1} = \overline{S_3} S_2 S_1 + S_3 \overline{S_2} \overline{S_0}$$

A_{S0}

$S_3 S_2$	$S_1 S_0$			
	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	1	0	0

$$A_{S0} = S_3 \overline{S_2} \overline{S_1} S_0$$

BS2

	$S_3 S_2$	$S_1 S_0$			
		00	01	11	10
00		0	0	0	0
01		1	1	0	0
11		0	0	0	0
10		1	1	0	1

$$BS2 = \overline{S_3} S_2 \overline{S_1} + S_3 \overline{S_2} \overline{S_1} + S_3 \overline{S_2} \overline{S_0}$$

BS1

	$S_3 S_2$	$S_1 S_0$			
		00	01	11	10
00		0	0	1	1
01		0	0	0	0
11		0	0	0	0
10		1	1	0	1

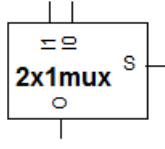
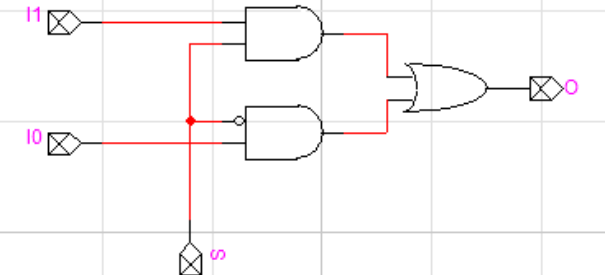
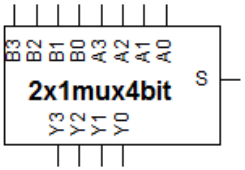
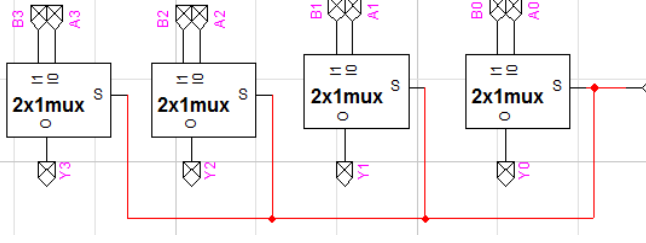

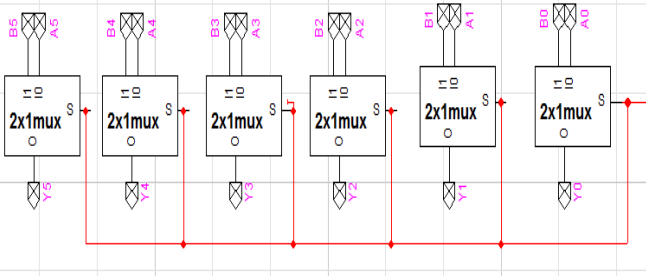
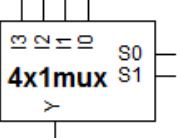
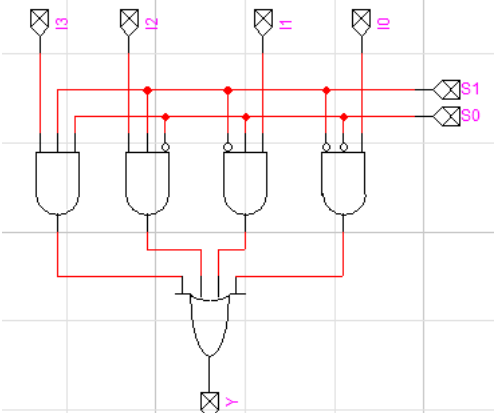
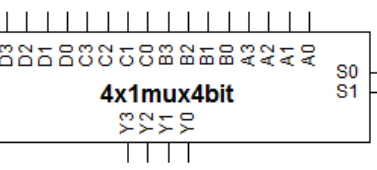
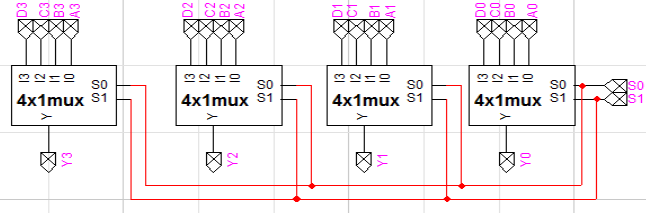
$$BS1 = \overline{S_3} \overline{S_2} S_1 + S_3 \overline{S_2} \overline{S_0} + S_3 \overline{S_2} \overline{S_1}$$

BS0



	$S_3 S_2$	$S_1 S_0$			
		00	01	11	10
00		0	1	1	0
01		0	1	1	0
11		0	0	0	0
10		0	0	0	1

$$BS0 = \overline{S_3} S_0 + S_3 \overline{S_2} S_1 \overline{S_0}$$



The design has been implemented in logic works and the following devices were created:

Device Name	Device Symbol	Logic Diagram
2x1 mux		
2x1 mux4bit		
2x1 mux6bit		
4x1 mux		
4x1 mux4bit		



8x1mux

  



8x1mux6bit

  


6bitadder

  


LogicUnit

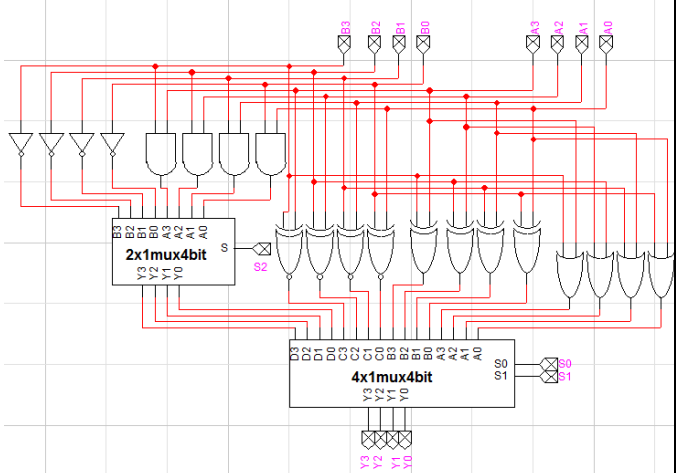 

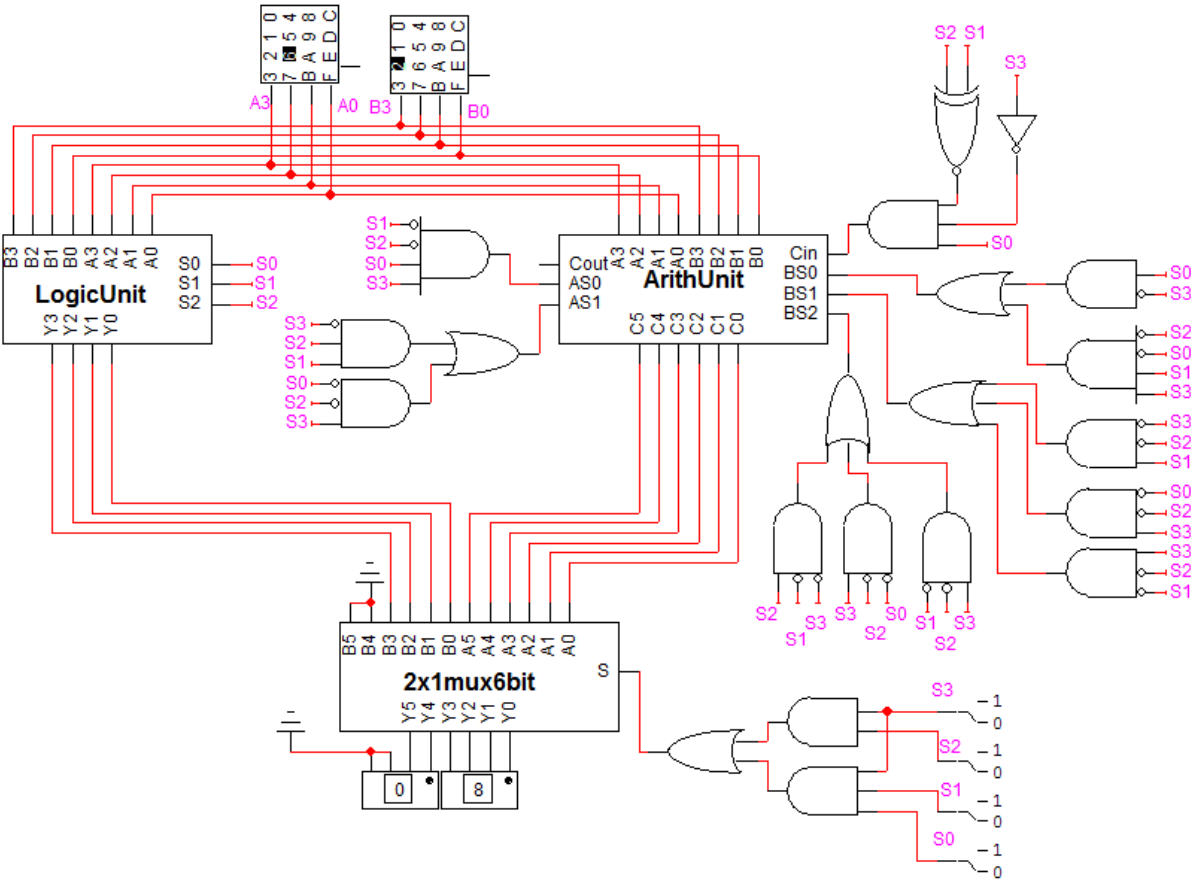
The whole ALU after integrating all the components and adding input and output is shown below:



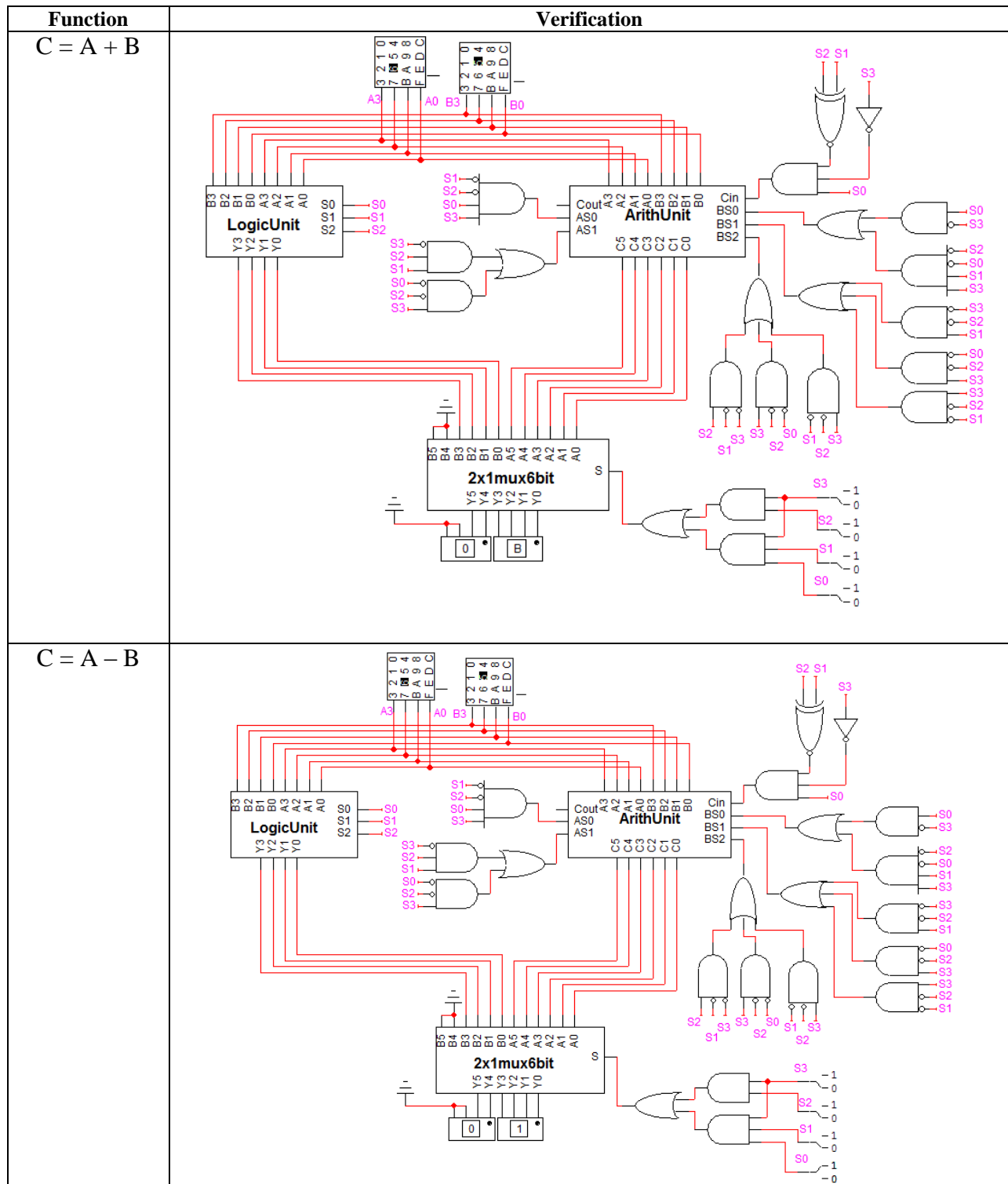
We will show next Verification of correct functionality of the ALU by setting A=6 and B=5:




$C = A + 1$

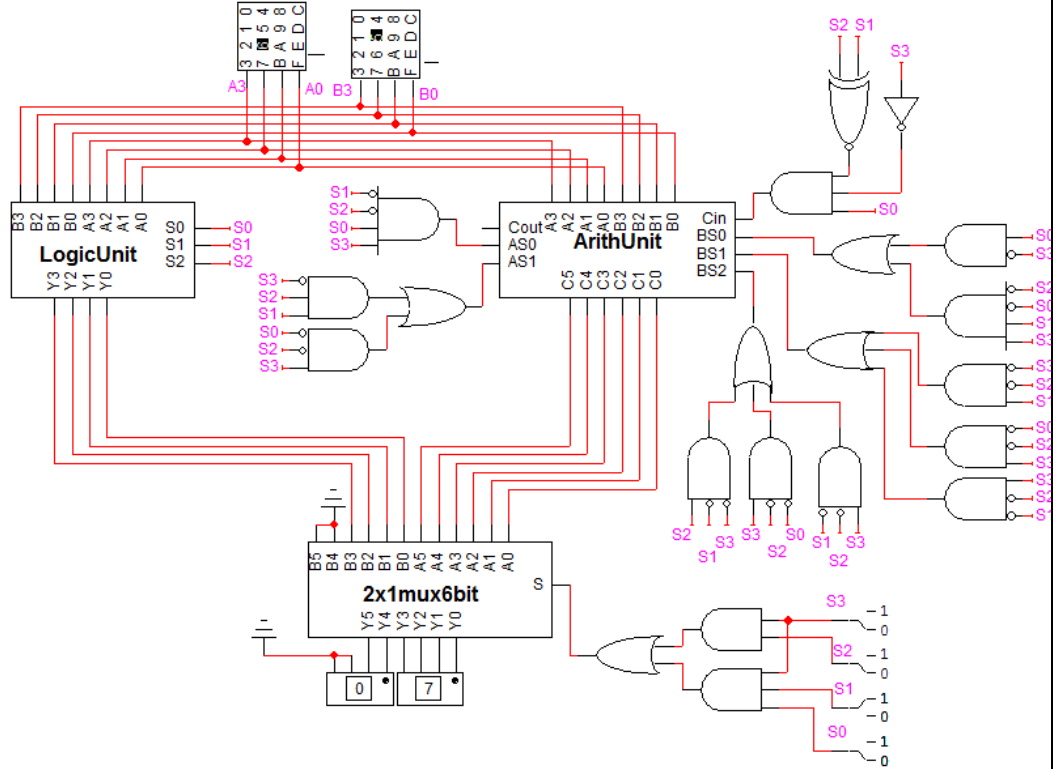


$C = A - 1$

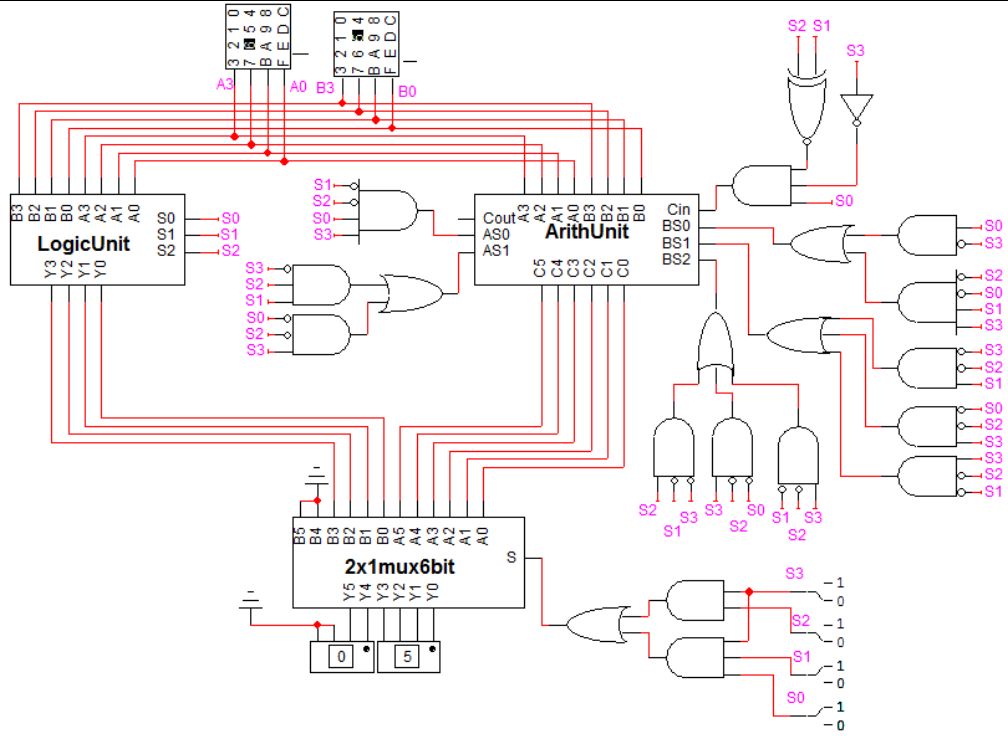


$$C = A + 2$$

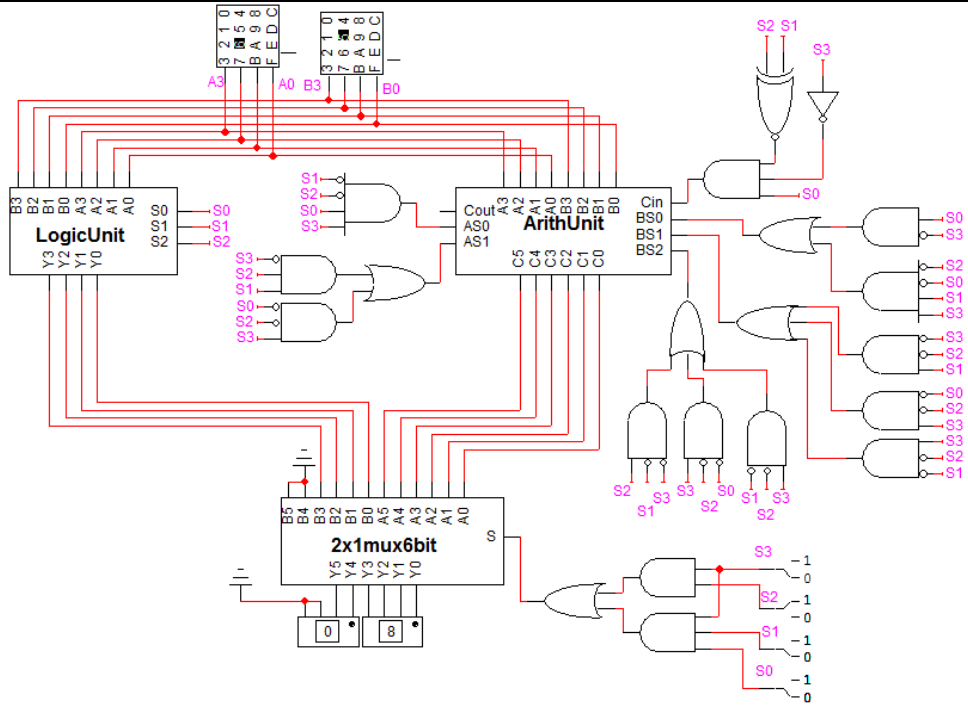


$$C = A - 2$$

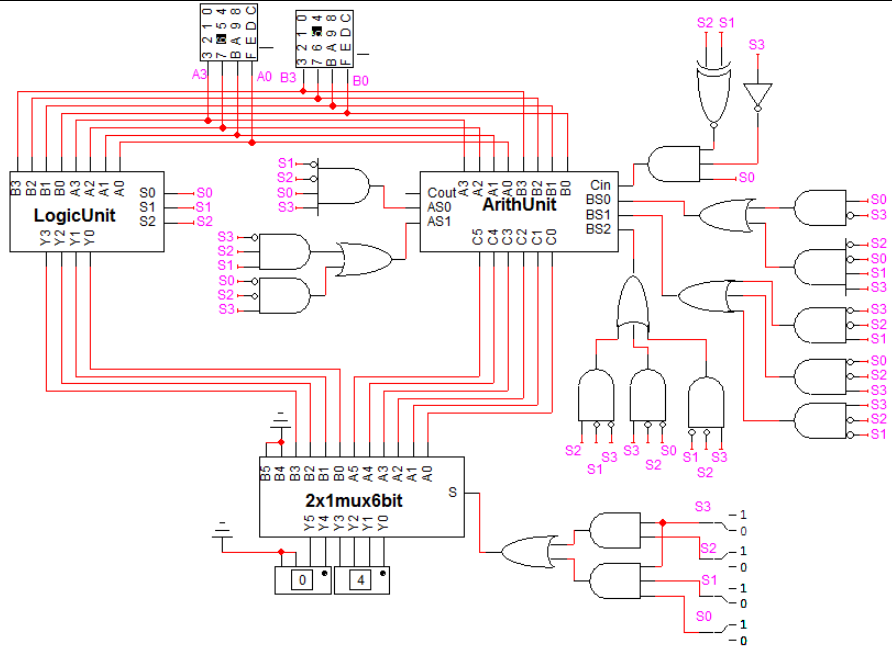


$C = B$

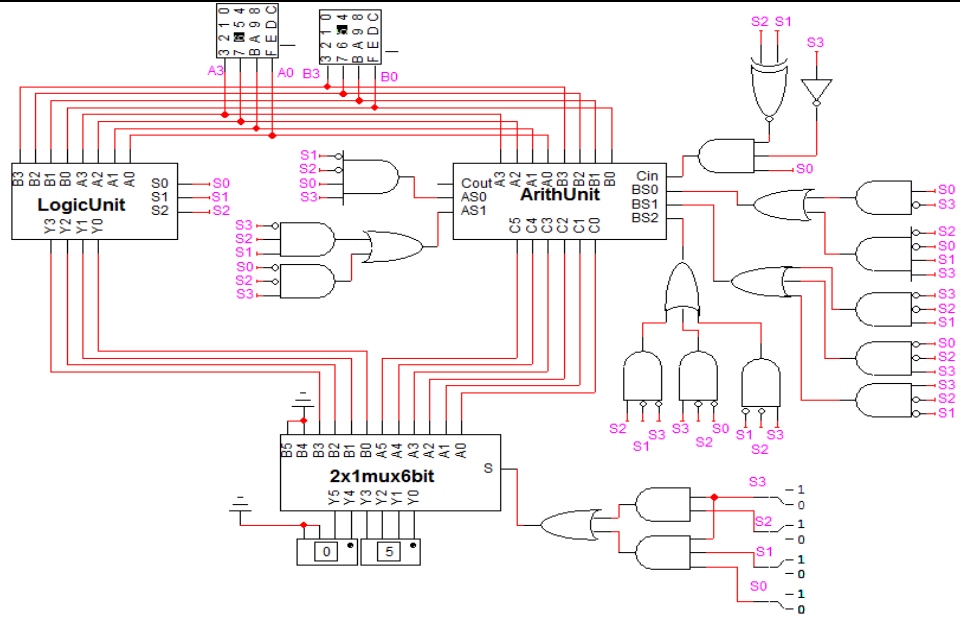


$C = -B$

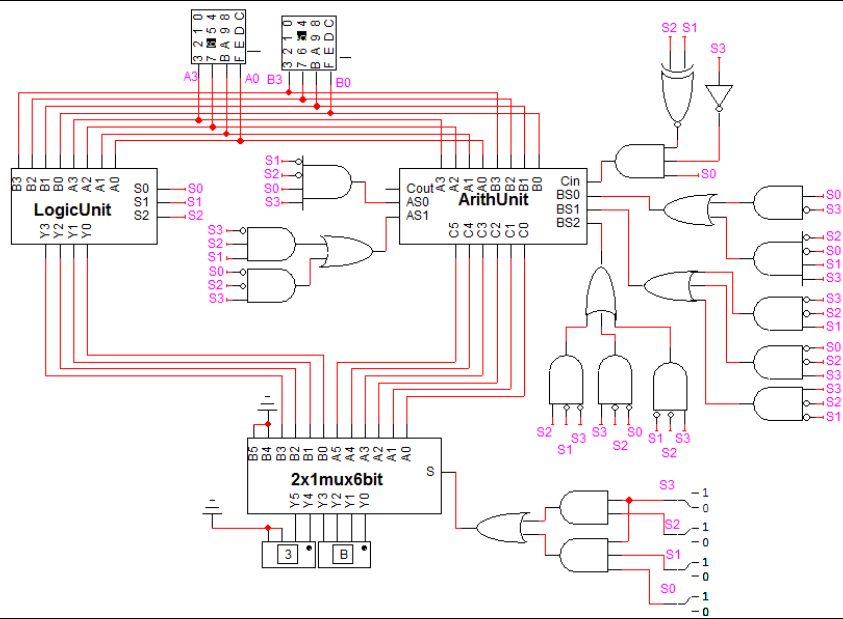


C = 2B

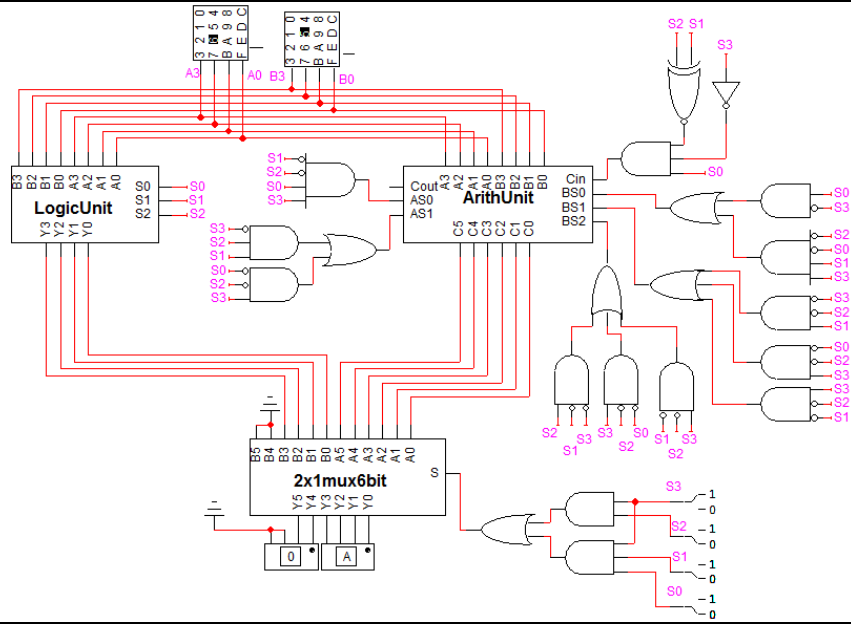


C = 3B

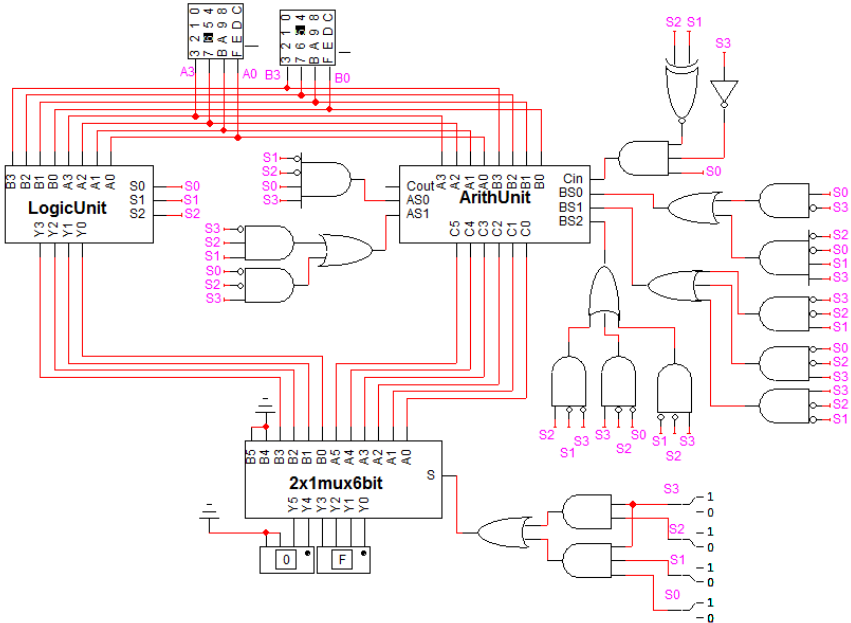


C = 4B

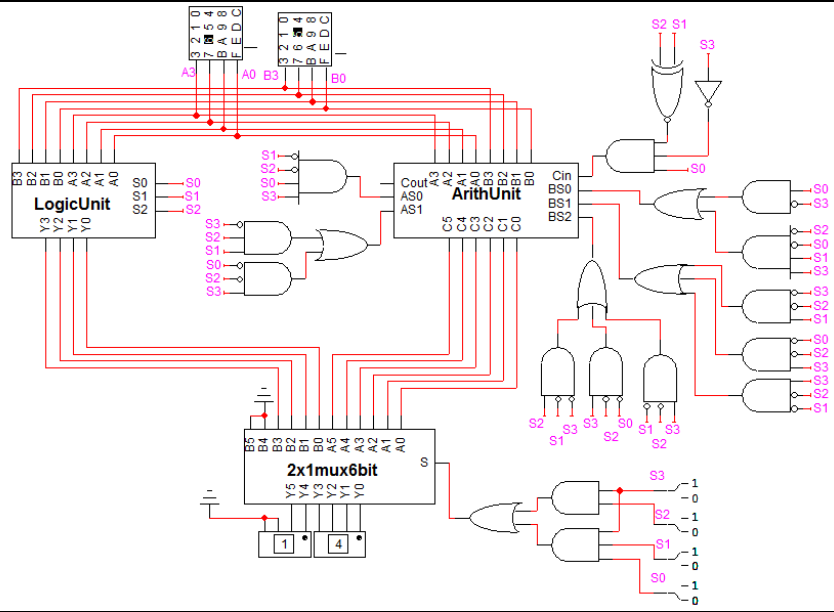


C = A and B

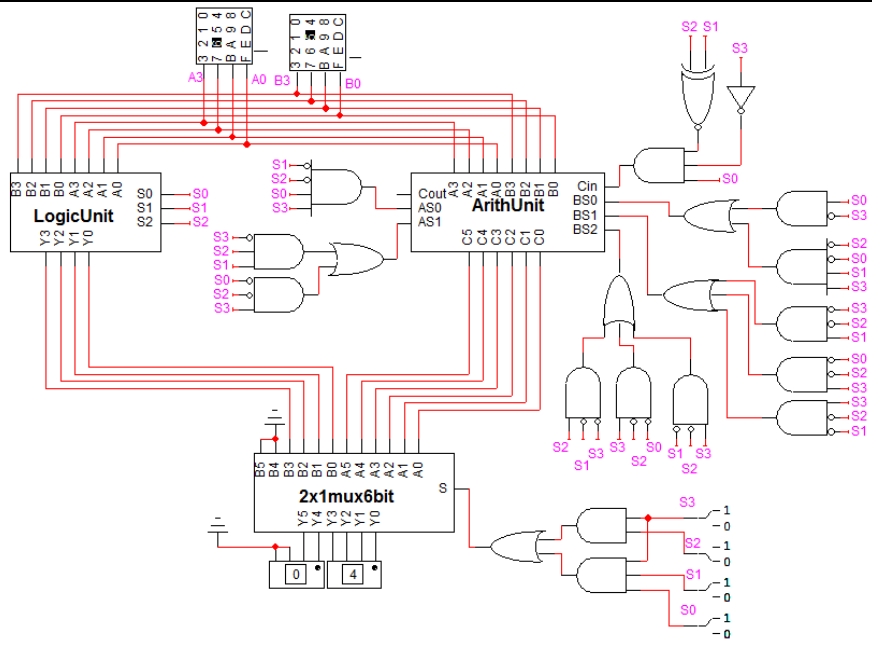


C = A or B

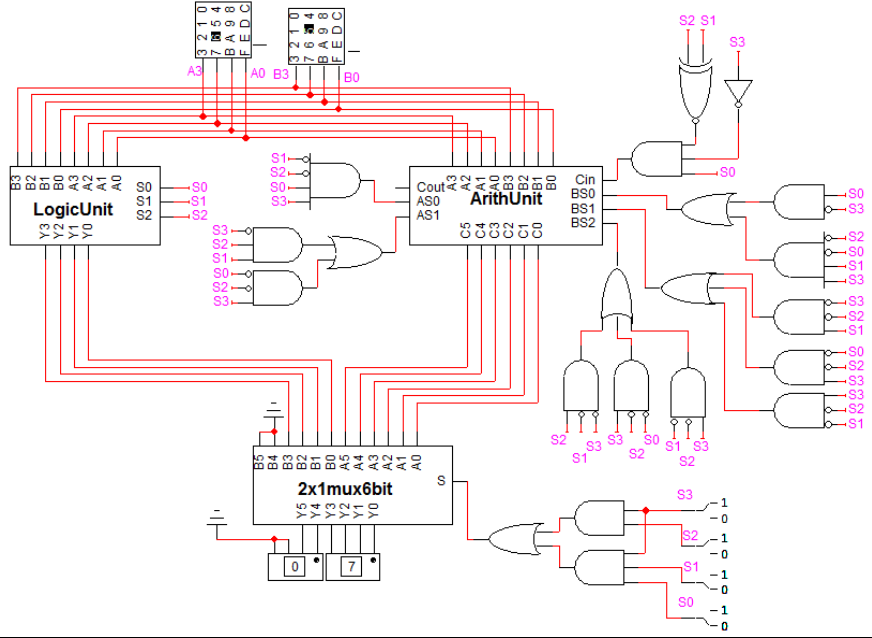

C = A xor B

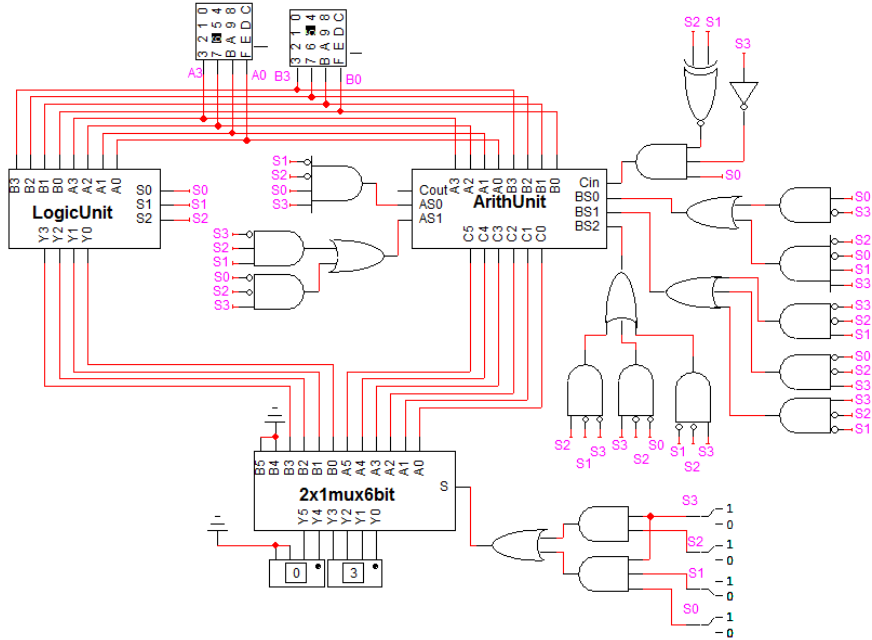

$C = A \text{ xnor } B$

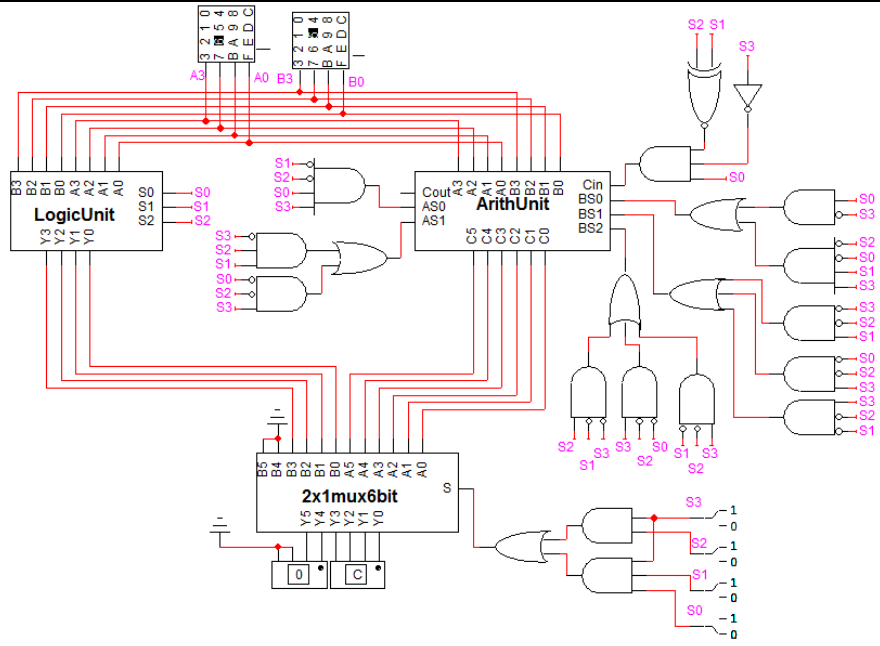

$C = \text{not } B$

