

Name: KEY

Id#

COE 202, Term 112
Digital Logic Design

Quiz# 5

Date: Wednesday, April 25


Q1. Design a rising edge-triggered D flip-flop using a rising edge-triggered JK flip flop.

State Table:

Current State (Q)	Input (D)	Next State (Q)	J	K
0	0	0	0	X
0	1	1	1	X
1	0	0	X	1
1	1	1	X	0

$$J = D$$

$$K = D'$$

 


Q2. A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following equations:

$$D_A = X' Y + X A$$

$$D_B = X' B + X A$$

$$Z = B$$

 (i) Draw the logic diagram of the circuit.




(ii) Derive the state table.

State Table:

Current state AB	Next state				output Z
	$xy=00$ AB	$xy=01$ AB	$xy=10$ AB	$xy=11$ AB	
00	00	10	00	00	0
01	01	11	00	00	1
10	00	10	11	11	0
11	01	11	11	11	1

(iii) Derive the state diagram.

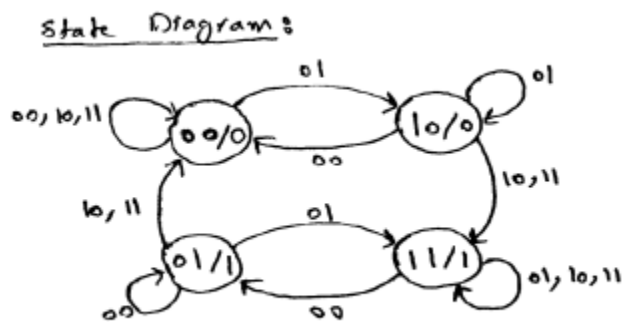

* Note that this circuit has a Moore model.

* Note that this circuit has several synchronizing sequence. For example, {00, 11} synchronizes it to state 00.