

COE 202, Term 121
Digital Logic Design

Quiz# 5


Date: Saturday, Dec. 22

Q1. The state table of a sequential circuit which has a single input X and two outputs, which are the flip flop outputs, is given below.


Current State	Next State X=0	Next State X=1
S0	S0	S1
S1	S1	S2
S2	S2	S0

- (i) Implement the sequential circuit using D-FFs and the smallest number of gates possible assuming the state assignment: S0=00, S1=01, and S2=10. Minimize your equations using K-map method.
- (ii) Draw the circuit diagram.


Current State		Next State X=0		Next state X=1	
F ₁	F ₀	F ₁	F ₀	F ₁	F ₀
0	0	0	0	0	1
0	1	0	1	1	0
1	0	1	0	0	0

 


$$D_1 = \bar{x} F_1 + x F_0$$

 
 
$$D_0 = \bar{x} F_0 + x \bar{F}_1 \bar{F}_0$$



 Q2. It is required to design a sequential circuit that receives two unsigned numbers X and Y serially and computes the output $Z=X-Y$ serially, assuming that $X \geq Y$. Derive the state diagram for your circuit assuming **Mealy** model.



Q3. It is required to design a sequential circuit that receives a serial input X and produces a serial output Z . The output Z will be 1 when the circuit detects the sequence 1010 assuming overlapping sequence detection. Derive the state diagram for your circuit assuming **Moore** model.

