

Name: KEY

Id#


COE 202, Term 122  
Digital Logic Design

Quiz# 5


Date: Monday, April 29

Q1.

 
- (i) Design a D-Latch using only NAND gates and inverters.



 - (ii) Design a D-Latch using only a 2x1 Multiplexer.



 - (iii) Design a **rising-edge** triggered D flip flop using only D-Latches and inverters.




Q2. Design a falling-edge triggered JK flip flop using a rising-edge triggered D flip flop. Show the design steps.

Q	J	K	Q <sup>+</sup>	D
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0


JK	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$D = J\bar{Q} + \bar{K}Q$$

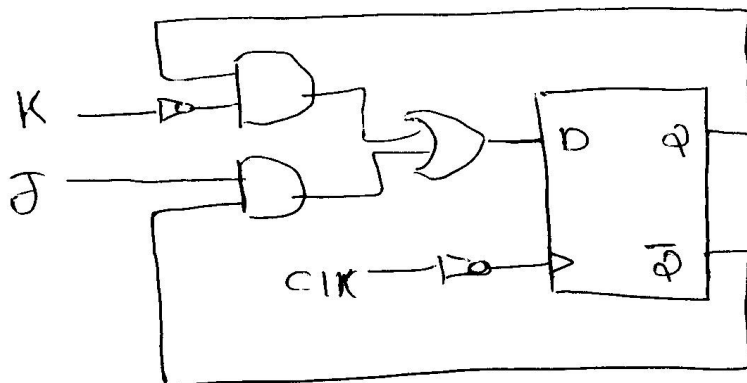

**Q3.**

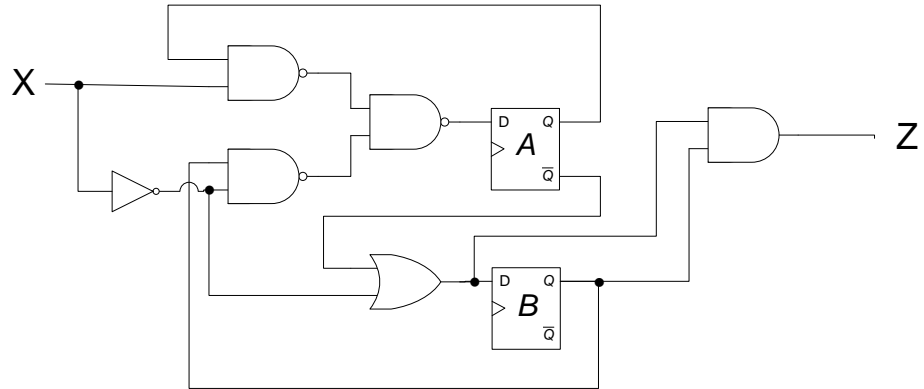- (i) Derive the state table and state diagram for the following circuit with a single input X, and a single output Z and determine whether the circuit is Mealy or Moore:




The circuit is Mealy since the output depends on both the current state and the input.

$$D_A = \overline{(\overline{XQ_A})(\overline{XQ_B})} = XQ_A + \overline{X}Q_B$$

$$D_B = \overline{Q_A} + \overline{X}$$

$$Z = Q_B(\overline{Q_A} + \overline{X}) = \overline{Q_A}Q_B + \overline{X}Q_B$$

$Q_A$	$Q_B$	$X$	$Q_A^+$	$Q_B^+$	$Z$
0	0	0	0	1	0
0	0	1	0	1	0
0	1	0	1	1	1
0	1	1	0	1	1
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	0

 

- (ii) Complete the following waveform for the positive-edge triggered circuit that implements the state diagram provided below. Assume the circuit is initially at the state  $Q_1Q_0 = 00$ .

