

Name: KEY

Id#

COE 202, Term 132
Digital Logic Design
Quiz# 5



Date: Tuesday, May 6

Question 1.



(13 points)

  - a. In the circuit shown, A is a D-type latch and B is a D-type flip flop. For the input waveforms given for the clock signal (Clk) and the input X, accurately draw the resulting waveforms at outputs Q_A and Q_B .

Assume that both Q_A and Q_B are initially at 0.



  - b. The state diagram shown is for a sequential circuit that has a single input X and a single output Y. The circuit uses two positive edge triggered D-type flip flops Q1 and Q0.
- i. Starting with the circuit in state $Q_1Q_0=11$, complete the missing waveforms in the timing diagram below.



- ii. Let the circuit be in state 00 with input X held permanently at 0. The circuit will end up being stuck at state 11. This state transition requires a minimum time duration of 1.5 ms.

$$3 \times T = 3 \times 0.5 \text{ ms}$$

Question 2.

(12 Points)

Consider the sequential circuit opposite and then answer the following questions:

a. Is the circuit Mealy or Moore?


Mealy

b. Provide logical expressions for the flip flop D inputs and the external output

$$D_{Q_0} = Q_1$$

$$D_{Q_1} = Q_0 Q_1 + X$$

$$Y = Q_0 Q_1 + X$$

 

c. Give both the state table and the state diagram. Use the layout given below for the state diagram. Note: Q0 represents the LSB of the binary value of the state.

Q_1	Q_0	X	Q_1^+	Q_0^+	Y
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

