

Name: KEY

Id#

COE 202, Term 141  
Digital Logic Design

Quiz# 5

Date: Thursday, Nov. 27

Q1 a. Fill in all blank cells in the two tables below.

Binary	Equivalent decimal value with the binary interpreted as:				
	Unsigned number	Signed-magnitude number	Signed-1's complement number	Signed-2's complement number	BCD number
10000000	128	-0	-127	-128	80

Decimal	Binary representation in 8 bits:		
	Signed-magnitude notation	Signed-1's complement notation	Signed-2's complement notation
- 75	11001011	10110100	10110101

b. Using 2's-complement signed arithmetic in 5 bits, do the following operations **in binary**. Show all your work, and:

- Verify that you get the expected decimal results.
- Check for overflow and mark clearly any overflow occurrences.


(i)	(ii)
00111 (+7) - <u>10101 (-11)</u> ----- 00111 (+7) + 01011 (+11) ----- 10010 (-14)	10110 (-10) - <u>10011 (-13)</u> ----- 10110 (-10) + 01101 (+13) ----- 00011 (+3)
Overflow, we added two positive numbers and we got negative result.	No overflow.

c. Consider the signed 2's complement arithmetic operation A - B in 6 bits. With B = 101100, the largest value allowed for A in order to avoid the occurrence of overflow is (01011)<sub>2</sub>.


A- B = A + 2's comp. B = A + 01100 = A + 20. The largest positive value without overflow is +31. Thus A+20=31 => A=11

**Q2** Assume that the delay of a 2-input XOR gate is 3ns while the delay of other gates is equal to the gate's number of inputs, i.e. the delay of an inverter is 1ns, the delay of a 2-input AND gate is 2ns, the delay of a 2-input OR is 2ns, the delay of a 3-input AND gate is 3ns, the delay of a 3-input OR gate is 3ns, etc.

 (a) **(6 points)** A 4-bit **Ripple Carry Adder (RCA)** is given below:




 Determine and compute the **longest delay** in the **4-bit Ripple Carry Adder (RCA)**.




The longest delay is **19 ns** which is along the path from {A0 B0} across the propagate XOR gate until the Cout signal.

 (b) (4 points) Show the design of a **2-bit Carry Look-Ahead Adder (CLA)** by drawing its logic diagram.



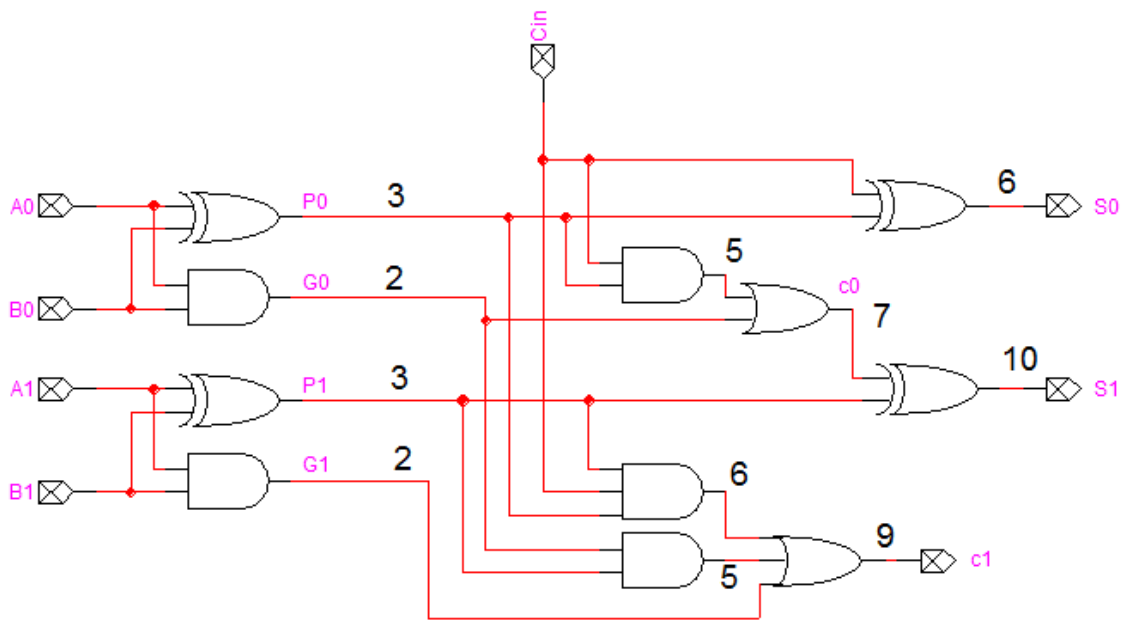(c) (3 points) Using the delay assumptions given in the beginning of the question, determine and compute the **longest delay** in the **2-bit Carry Look-Ahead Adder (CLA)**.



The longest delay is **10 ns** which is along the path from {A0 B0} across the propagate XOR gate until the S1 signal.