


## DIGITAL SYSTEM TESTING COE -545

### Lecture – 17 Built-In Self-Test (BIST)


 
### Introduction

- DFT will Improve CUT Testability (Controllability & Observability) → Still requires expensive ATE to Perform the Test
- To Reduce Test Cost → CUT is Designed to Test Itself → Include On-Chip Logic to Generate TV's and Evaluate Response → Built-In Self Test (**BIST**)
- V. Agrawal defines BIST as a DFT technique in which testing (test generation and test application) is accomplished through built-in hardware features
- BIST = BIT (Built in test) + self test



## BIST Merits

### Advantages

- **Accessability of Internal Nodes (not Possible with External ATE)**
- **At-Speed Test** → Test is applied @ Chip Own Speed
- **Reduced Test Cost** (No Expensive ATE)
- **In-Field Testing** is Possible

### Disadvantages

- **Area Overhead**
- **Performance Overhead**




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 3



## BIST Classification

 

COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 4

  
 
## Linear Feedback Shift Register



- **Linear** → Preserves (Follows) the Principle of *SuperPosition*
- Response to a Linear Composition of Stimuli = Linear Combination of Individual Responses to each Stimuli
- Let  $\mathbf{R}_i$  = Response of a Linear CUT to Input Stimuli  $S_i$ , and
- Let  $\mathbf{P}$  = The Linear CUT Function
- Let  $a_1, a_2$  = Constants
- Thus  $\mathbf{R}_1 = \mathbf{P}(S_1)$  and  $\mathbf{R}_2 = \mathbf{P}(S_2)$
- $a_1\mathbf{R}_1 + a_2\mathbf{R}_2 = a_1 \mathbf{P}(S_1) + a_2 \mathbf{P}(S_2) = \mathbf{P}(a_1S_1 + a_2S_2)$
- A **Linear Logic Circuit** Can be Constructed from the following basic Components:-


  
## Linear Feedback Shift Register (LFSR)


- A **Linear** Logic Circuit Can be Constructed from the following basic Components:-
  - Unit Delay Elements ( D-FFs)
  - Modulo-2 Adders (XOR Gate)
  - Modulo-2 Constant Multiplier ( $0 \rightarrow$  No Connection,  $1 \rightarrow$  Connection)
- Analyzing these circuits, all *operations* are “**Modulo 2**”




 
## LFSR Type 1 (External XOR)

- Thus,  $G(x)$  is Function of:
  - The Input Sequence
  - The Initial State of the Register
  - The Denominator Polynomial  $P(x) = 1 + \sum_{i=1}^n C_i x^i$
  - $P(x)$  is Called the Characteristic Polynomial of the LFSR



### SPECIAL CASES

#### 1. LFSR as Pseudo Random Test Pattern Generator (PRTPG)



- By Initializing the LFSR to 0000001 with no Input Sequence ( $I_m$ ) → We get a Pseudo Random Pattern Output

#### 2. LFSR as a Signature Analyzer (SA)

- By Initializing the LFSR to All 0's and Applying the Output Sequence of the CUT to the Input of the LFSR ( $I_m$ ) → The Sequence is Compressed into One Signature
  
## LFSR Type 1 (External XOR)

- The pattern produced by an LFSR is Periodic with a Max Period of  $2^n - 1$ , where  $n$  is the number off FFs in the LFSR = The degree of the C/C. Polynomial C/C. Polynomial  $P(x)$
- C/C. Polynomials which have maximal length are known as primitive polynomials
- Autonomous LFSRs with no I/P sequence (with  $I_m=0$ ), Serve as PRTPG.
- PRTPG Produce Sequences that are deterministic (not random) but the generated sequence has properties that have some properties of Random signals, e.g.:
  - Has  $(2^{n-1})$  1's and  $(2^{n-1}-1)$  0's
  - One Run of  $n$  Consecutive 1's and one run of  $(n-1)$  0's
- By Initializing the LFSR to All 0's and Applying the Output Sequence of the CUT to the Input of the LFSR ( $I_m$ ) → The Sequence is Compressed into One Signature



### LFSR Type 1 (External XOR)

	$Q_1 = Q_3 \oplus Q_4$	$Q_2$	$Q_3$	$Q_4$
1	0	0	0	1
2	1	0	0	0
3	0	1	0	0
4	0	0	1	0
5	1	0	0	1
6	1	1	0	0
7	0	1	1	0
8	1	0	1	1
9	0	1	0	1
10	1	0	1	0
11	1	1	0	1
12	1	1	1	0
13	1	1	1	1
14	0	1	1	1
15	0	0	1	1
	0	0	0	1

COE – KFUPM


- $P(x) = 1 + x^3 + x^4$
- Produced Sequence is Maximal  $\rightarrow$  Period = 15
- Each Output has 8-1's & 7-0's
- Single Run of 4-1's, && Single Run of 3-0's
- Single run of 2-1's & Single Run of 2-0's
- Two Runs of a Single 1 && Two Runs of Single 0
- Output Sequence is the Same for all  $Q$ 's

Dr. Alaaeldin Amin (COE 545)      Slide Number 13
 
### LFSR Type 1 (External XOR)

- $P(x) = 1 + x^3 + x^4$
- Output Sequence  $G(x) = 1 / P(x)$   
 $= x^{-4} + x^{-5} + x^{-6} + x^{-7} + x^{-9} + x^{-4} + x^{-11}$   
 $+ x^{-12} + x^{-15}$
- Note  $x^2$  is an output bit Coming out Earlier than  $x^1$  by one Clock Period
- $G(x) = 100110101111000$

$$\begin{array}{r}
 x^{-4} + x^{-5} + x^{-6} + x^{-7} + x^{-9} + x^{-4} + x^{-11} + x^{-12} + x^{-15} \\
 \hline
 I + x^3 + x^4 \\
 \hline
 I + x^{-1} + x^{-4} \\
 \hline
 x^{-1} + x^{-4} \\
 \hline
 x^{-1} + x^{-2} + x^{-5} \\
 \hline
 x^{-1} + x^{-4} \\
 \hline
 x^{-2} + x^{-4} + x^{-5} \\
 \hline
 x^{-2} + x^{-3} + x^{-6}
 \end{array}$$



Output Sequence

Slide Number 14

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

## LFSR's

Dr. Alaaeldi & min  
CCE, KFPM

### Theorem:

- An LFSR PRTPG Produces a *Periodic* Sequence  $\{a_n\}$ , such that the **Period** is the *smallest* integer  $k$  for which  $P(x)$  *Divides*  $(1 + x^k)$ .

## Previous Example:

$$(1+x^{15})/(1+x^3+x^4) = x^{11}+x^{10}+x^9+x^8+x^6+x^4+x^3+1$$

Thus  $k=15$  is the Period for the LFSR with

$$P(x) = (1 + x^3 + x^4)$$

## Exercise:

Prove that an LFSR with  $P(x) = (1 + x^2 + x^4)$  is not Primitive →  
 i.e. Period < 15

# Reciprocal Polynomials

- Let  $P(x)$  be a C/C Polynomial; Define the Reciprocal Polynomial  $\mathbf{P}^*(x) = x^n \mathbf{P}(1/x)$
  - An LFSR with  $\mathbf{P}^*(x)$  C/C Polynomial Generates the Sequence  $\{b_n\}$  which is the same as  $\{a_n\}$  Generated by  $P(x)$  but in Reverse Order  $\rightarrow b_i = a_{n-i}$
  - Example  $P(x) = (1 + x^3 + x^4) \rightarrow \mathbf{P}^*(x) = (1 + x + x^4)$
  - $G^*(x) = 1/(1 + x + x^4)$ 

$$= x^{-4} + x^{-7} + x^{-8} + x^{-10} + x^{-12} + x^{-13} + x^{-14} + x^{-15}$$

A diagram illustrating a 3D molecular structure. It features several atoms represented by spheres: red spheres for oxygen (O) and purple spheres for nitrogen (N). The structure shows the spatial arrangement of atoms and the formation of covalent bonds between them, indicated by dashed lines connecting the spheres. A large black arrow points from the bottom right towards the top left, suggesting a movement or flow within the molecule.

## P(x) Output Sequence



## P\*(x) Output Sequence

### LFSR as a Signature Analyzer

- Initial Stat = ALL 0's
- The Signature of a Sequence is the Pattern Left in the LFSR after the Last bit of Input  $I(x)$  has been Sampled  $G(x) = I(x)/P(x)$  under Zero Initial State
- $I(x) = Q(x). P(x) + R(x) \rightarrow$  Where  $R(x)$  is the Signature of  $I(x)$
- Let's Assume Having Two Input Sequences  $I(x)$  and  $I'(x)$ , where
  - $I(x)$  = Error Free Sequence
  - $I'(x) = I(x) + e(x)$  where  $e(x)$  is the Error Sequence (Polynomial)

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 17

### LFSR as a Signature Analyzer

- The error will not be Detected if  $I(x)$  &  $I'(x)$  Have the Same Signature
- $I(x) = Q(x). P(x) + S(x)$
- $I'(x) = Q'(x). P(x) + S(x)$
- Thus  $e(x) = I'(x) - I(x) = P(x)(Q'(x) - Q(x))$
- For the error Signal not to be Detected it must be a Multiple of the C/C Polynomila of the LFSR  $P(x) \rightarrow$  (i.e.,  $P(x)$  Divides  $e(x)$ )
- For an Input Sequence of  $k$ -Bits, Assuming all Possible Patterns to be Equally Likely  $\rightarrow$  The Probability of Failing to Detect an Error (Aliasing) is given by:

$$\frac{\# \text{ of Undetectable errors}}{\text{Total Number of Possible Errors}}$$

$$= \frac{2^{k-n} - 1}{2^k - 1}$$

Only 1 Seq is Correct

- For Long Sequences, i.e.  $k > n$
- Aliasing Probability  $\approx 2^{-n}$
- Aliasing Probability Only Depends on the Length of the LFSR
- For an LFSR of 16-Bits  $\rightarrow$  Aliasing Probability  $\approx 0.0015\%$
- For an LFSR of 8-Bits  $\rightarrow$  Aliasing Probability  $\approx 0.4\%$

Dr. Alaaeldin Amin – Computer  
Engineering Department - KFUPM

Page 9

### LFSR Type 2 (Internal XOR)

- The C/C Polynomial of this LFSR is Given by

$$P(x) = 1 + \sum_{i=1}^n C_i x^i$$

*Dr. Alaaeldin Amin  
COE, KFUPM*

- In This Case the Signature Remainder is Given By Dividing the Input Sequence by the Reciprocal Polynomial  $P^*(x)$
- $G(x) = Q(x) \cdot P^*(x) + S(x) \rightarrow$  where  $S(x)$  is the Signature



*COE – KFUPM      Dr. Alaaeldin Amin (COE 545)      Slide Number 19*



### Multiple Input Signature Register (MISR)



- Used to Test CUTs with Multiple Outputs ( $m$ )
  - Use One LFSR per Output → Costly ( $m$  LFSRs)
  - Use one LFSR  $m$  Times → Long Test Application Time (Costly!!)
  - Use a MISR → Parallel Signature Analyzer
- A MISR of  $n$ -Stages Has a Probability of Aliasing (error Masking) of  $2^{-n}$  for Equally Likely Patterns and Long Data Sequences
- An Error Sequence  $e(x)$  is Masked if it is Multiple of the C./C Polynomial  $P(x)$

*Dr. Alaaeldin Amin  
COE, KFUPM*

  *COE – KFUPM      Dr. Alaaeldin Amin (COE 545)      Slide Number 20*



  


  
 
## BIST CASE STUDY Partial TMS32010 DSP Chip

**OBJECTIVE:**  
*Incorporation of BIST Structure*

- ❖ 8 X 8 Bit Multiplier ⇒ 880 Gates
- ❖ 16-Bit ALU (5 Control Inputs + Carry\_In) ⇒ 354 Gates
- ❖ 1255 SSF in the Multiplier
- ❖ 574 SSF in the ALU



Portion of the TMS32010 DSP Chip


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 27
 
## BIST CASE STUDY Partial TMS32010 DSP Chip

- Two Test Sessions Required
  - Multiplier Test Sessions (BILBO = MISR)
  - ALU Test Sessions ( BILBO = PRPG )
- Addition of Two PRPG For ALU (16 Bit & 6-Bit)
- 20 Different Fault Simulation Runs with Different LFSR Seed Values
- Simulation Stopped After Fault Coverage Reaches 100%
  - Average # of Patterns 2177
  - Minimum # of Patterns 830
  - Maximum # of Patterns 3619
  - Fault Coverage = 100%



(a) BILBO BIST STRUCTURE


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 28
 
## BIST CASE STUDY Partial TMS32010 DSP Chip

- R3 Unmodified
- 22-Bit PRPG For ALU (16 Bit & 6-Bit)
- Response Data of Multiplier Used As Test Input to ALU
- Only ONE Test Session Required
- 20 Different Fault Simulation Runs with Different LFSR Seed Values
- Simulation Stopped After Fault Coverage Saturated At 64.5%
  - Average # of Patterns > 3000
  - Fault Coverage = 64 %



(b) Portion of the TMS32010 DSP Chip


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 29
 
## BIST CASE STUDY Partial TMS32010 DSP Chip

- R3 Extended as 38-Bit MISR (First 22\_Bits Inputs =0) or ALU (16 Bit & 6-Bit)
- Only ONE Test Session Required
- 20 Different Fault Simulation Runs with Different LFSR Seed Values
- Simulation Stopped After Fault Coverage Reaches 100%
  - Average # of Patterns 1457
  - Minimum # of Patterns 634
  - Maximum # of Patterns 2531
  - Fault Coverage = 100%



(c) Portion of the TMS32010 DSP Chip


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 30
 
## BIST CASE STUDY Partial TMS32010 DSP Chip

- R3 & R4 Are MISR
- Only ONE Test Session Required
- Least Hardware BIST Configuration
- 20 Different Fault Simulation Runs with Different LFSR Seed Values
- Simulation Stopped After Fault Coverage Reaches 100%
  - Average # of Patterns 1387
  - Minimum # of Patterns 721
  - Maximum # of Patterns 2121
  - Fault Coverage = 100%



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 31