


# **Bridging faults and $I_{ddq}$ testing**

---

**Kent Lam**  
**University of Alberta**  
**Department of Electrical and Computer Engineering**

*April 03, 2000*

1



## **Outline:**


---

- \* **Bridging faults**
- \* **What is  $I_{ddq}$  testing?**
- \* **Why  $I_{ddq}$  testing?**
- \* **Example**
- \* **Results**
- \* **Disadvantages**
- \* **Conclusion**
- \* **Future work**
- \* **References**

2
 
## Bridging faults

- \* **Definition: A bridging fault occurs when two leads in a logic network are connected accidentally**
- \* **Most common defect in Integrated Circuits (up to 30%)**



3

## Bridging faults (cont.)

- \* **Can be divided into three classes**
  - **Bridging within a logic element**
  - **Bridging between logical nodes without feedback**
  - **Bridging between logical nodes with feedback**



4

## What is $I_{ddq}$ testing?

- \* **The test of quiescent supply current ( $I_{ddq}$ )**
- \* **Faults and defects will result in elevated  $I_{ddq}$  current**
- \* **Built-in current sensor can be used**

5

## Why $I_{ddq}$ testing?



- \* **Stuck-at fault model has problems in representing CMOS failure modes (bridging faults, stuck-on faults, etc..)**
- \* **In the case of bridging faults, one logic value does not always dominate the other, therefore, cannot be tested by logic testing (depends on bridging resistance)**

6

## I<sub>ddq</sub> tests for bridging faults

\* An example

a=1, b=0      a=0, b=0

  

7

## I<sub>ddq</sub> tests for bridging faults (cont.)

\* **General rule for identifying I<sub>ddq</sub> tests for a bridging fault between nodes x and y:**

- *An input vector T is an I<sub>ddq</sub> test for (x,y) if and only if T(x) not equal to T(y)*

8

## Results - Comparison between Stuck-fault testing and $I_{ddq}$ testing

### \* International Symposium on Circuits and Systems (ISCAS) benchmarks

Name	# Transistors	# nodes	# inputs	# outputs	# gates	# gate types
C17	26	21	5	2	6	1
C432	728	421	36	7	174	12
C499	1396	822	41	32	180	7
C880	1164	657	60	26	304	12
C1355	1768	949	41	32	577	10
C1908	2058	1132	33	25	332	13

9

## •Results (cont.)

Name	Patterns	Faults	Missed	% Detected
C17	6	74	1	98.7%
C432	53	3968	174	95.6%
C499	58	7806	362	95.4%
C880	67	7909	99	98.8%
C1355	87	12103	62	99.5%
C1908	108	14023	338	97.6%

**Stuck fault patterns**

Name	Patterns	Faults	Missed	Coverage
C17	5	74	0	100.00%
C432	40	3968	56	98.59%
C499	99	7806	1	99.99%
C880	27	7909	2	99.97%

**Current sensing**

\* **Current test detects a higher percentage of bridging faults than stuck fault testing**

10

## Results (cont.)

- \* **Detecting faults using current sensing is easier than in stuck fault testing**
  - **Inputs need not be propagated to outputs**
  - **Transistor sizing is not a factor in current testing**

11

## Disadvantages

- \* **Slow, because have to wait for circuit to be stable to measure current**
- \* **Overhead in chip area for current monitor circuit**
- \* **Different leakage current limit for different circuits**

12

## Conclusion


- \* **Very effective technique, more accurate model**
- \* **Provide higher fault coverage than logic testing**

13

## Future work
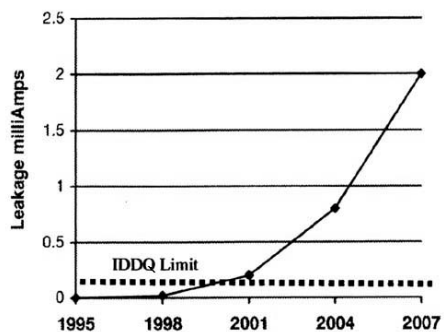
### Limitation of $I_{ddq}$ testing

- \* **As technology shrinks, leakage current increase**
- \* **Classical  $I_{ddq}$  testing will fail below 0.18 micron ?**
- \* **Delta- $I_{ddq}$ ,  $I_{ddt}$ , current signatures, power consumption analysis?**



14



## References

---

- \* **K. Baker, "SIA Roadmaps: Sunset Boulevard for Iddq", IEEE ITC, Jan. 1999, pp. 1121.**
- \* **K. C. Y. Mei, "Bridging and Stuck-At-Faults", IEEE Trans. On Computers, Vol. C-23, No. 7, pp. 720-727 July, 1974.**
- \* **S. Chakravarty and P. Thadikaran, "A Study of Iddq Subset Selection Algorithms for Bridging Faults", IEEE ITC, Feb. 1994, pp. 403-412.**
- \* **T. M. Storey and W. Maly, "CMOS Bridging Fault Detection", IEEE ITC, Jan. 1990, pp. 842-851.**