

# Fault Equivalence, Dominance & Collapsing

- **Definition:** If  $T_a$  is the set of *ALL* TVs which Detect Fault *a*, and  $T_b$  is the set of *ALL* TVs which Detect some other Fault *b*; the Two Faults *a*, and *b* are said to be **Equivalent** IFF  $T_a = T_b$ .
- In Other Words, *Two Faults* are **Equivalent** IFF *any* test detecting *one*, *also* detects *the Other* and vice versa


## Fault Equivalence

- **Lemma:** If faults *a* and *b* are equivalent then the corresponding faulty functions  $F_a$  and  $F_b$  are identical.
- Let  $tl \in T_a \rightarrow tl \in T_b$  (Since  $T_a = T_b$ )
- $F(tl) \oplus F_a(tl) = 1$  &&  $F(tl) \oplus F_b(tl) = 1$
- The above Equations are Valid  $\forall tl \in T_a (= T_b)$ , **Thus**
- $[F(tl) \oplus F_a(tl)] \oplus [F(tl) \oplus F_b(tl)] = 0 \rightarrow F_a(tl) \oplus F_b(tl) = 0$
- Thus  $F_a = F_b$
- **Definition:** *Two Faults* are **Equivalent** IFF *They Result in the Same Faulty Function*

## Fault Equivalence

- Fault Equivalence is an Equivalence Relationship, i.e. it is
  - Reflexive  $\rightarrow T_a = T_a$
  - Symmetric (  $T_a = T_b \rightarrow$  Reflexive  $\rightarrow T_b = T_a$  )
  - Transitive : Thus  
(  $T_a = T_b$  &&  $T_b = T_c \rightarrow$  Reflexive  $\rightarrow T_a = T_c$  )
- ***Thus, Equivalent Faults are Grouped into Equivalence Classes***
- ***Only One Fault of Each Class Need Be Included In the Fault List***


## Fault Equivalence (Example)

 

### 3-Input AND Gate

- ***Faults ( A/0 , B/0, C/0, F/1 ) are All Detectable by the single TV ( t = 111/0 )  $\rightarrow$  All 4 Faults Are Equivalent***


# Equivalence Rules

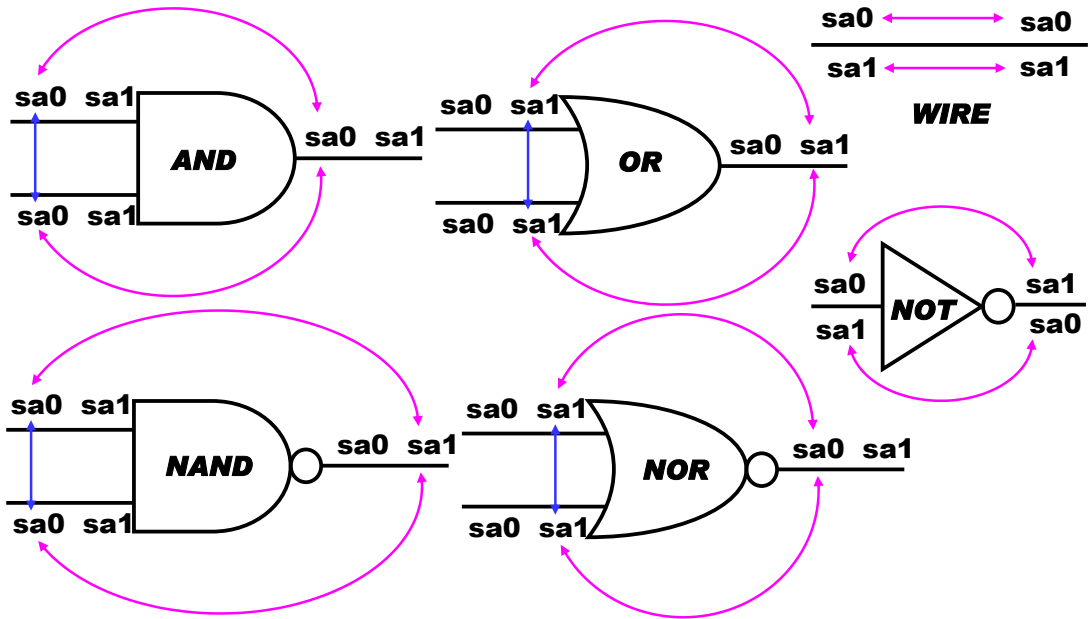

Fault Equivalence Indicated By Blue or Violet lines with Two-Way Arrows
 
# Equivalence Rules

For, Multi-Output Functions, All Faulty Outputs Must Be Identical to Establish Equivalence




Fault	Test ( $a \rightarrow x, y$ )	Faulty Output Functions
$a/0$	$1 \rightarrow 1/0, 1/0$	$(x = 0, y = 0)$
$x/0$	$1 \rightarrow 1/0, 1$	$(x = 0, y = a)$
$y/0$	$1 \rightarrow 1, 0/1$	$(x = a, y = 0)$
$x/0 \ \&\& \ y/0$	$1 \rightarrow 1/0, 1/0$	$(x = 0, y = 0)$

Multiple Fault


Single Faults at the STEM and Fanout Nodes  
Are Not Equivalent

# Equivalence Example

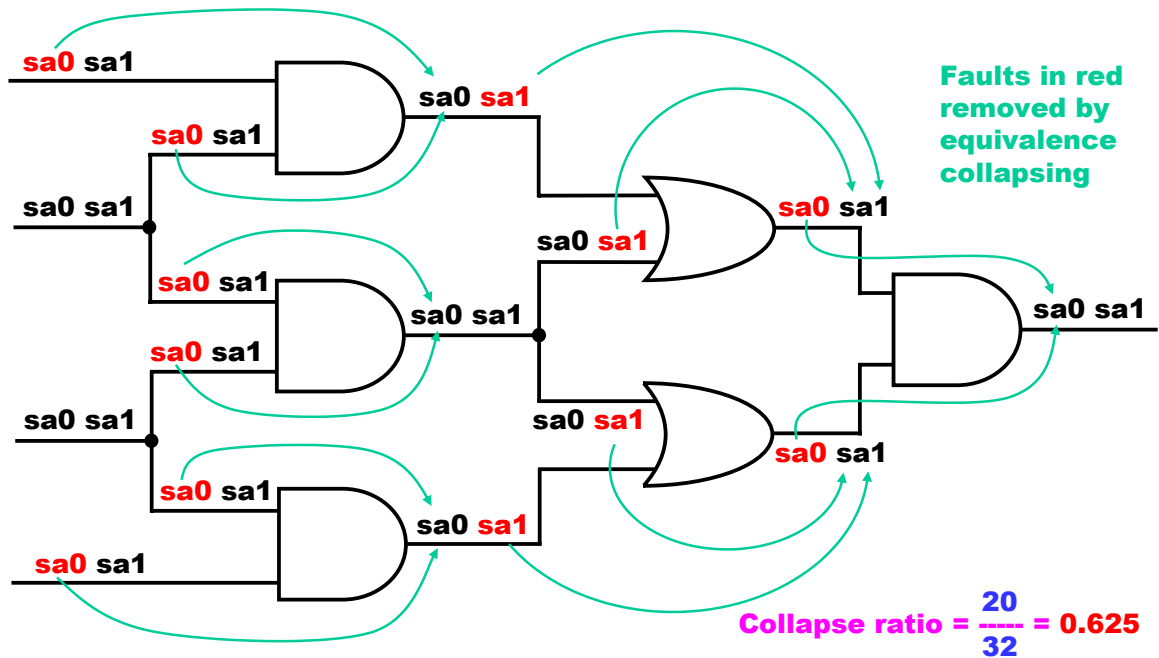
 
# Fault Dominance

- **Definition:** If  $T_a$  is the set of ALL TVs which Detect Fault  $a$ , and  $T_b$  is the set of ALL TVs which Detect some other Fault  $b$ ; Fault  $a$  is Said to Dominate Fault  $b$  IFF  $T_b \subseteq T_a$ .




- In other words, IF all TVs of some fault  $b$  also detect another fault  $a$ , then  $a$  is said to dominate  $b$ .
- If two faults dominate each other then they are equivalent.

# Fault Dominance (Example)

## 3-Input AND Gate

<b>Fault</b>	<b>Detecting TVs</b>
A/1	011/1
B/1	101/1
C/1	110/1
F/0	{011/1,101/1,110/1, 010/1, 001/1,100/1, 000/1}

 

**Obviously F/0 Dominates A/1, B/1 and C/1**

**Note Dominant Faults Need Not Be Included in The Fault List**


## Fault Collapsing

- Only One Fault From Each Class of Equivalent Faults Need Be Included In The Fault list (*Equivalence Fault Collapsing*)
- Only Dominated Faults Need Be Included In the Fault list (*Dominance Fault Collapsing*)
- For an  $n$ -input gate, at most  $n+1$  faults need to be considered out of the Possible  $2(n+1)$  Faults (exactly  $n+1$  faults for AND, OR, NAND, NOR, and Inverter Gates).

# Fault Collapsing (Example)

## 3-Input NAND Gate

TV		Detected	
ABC	F	Faults	
1 1 1	0	$A/0 \equiv B/0 \equiv C/0 \equiv F/1$	
0 1 1	1	$A/1 \subset F/0$	
1 0 1	1	$B/1 \subset F/0$	
1 1 0	1	$C/1 \subset F/0$	

 

- For NAND Gate with  $n$  I/Ps, Only  $(n+1)$  Faults Need Be Considered
- When dominance fault collapsing is used, it is sufficient to consider only the input faults  $\{A/0, A/1, B/1, C/1\}$


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 12
 
## Fault Collapsing Example

- 1  $\{A/0, B/0, H/0\}$
- 2  $\{C/1, D/1, F/1, G/0\}$
- 3  $\{E/0, G/0, V/0\}$
- 4  $\{H/1, V/1, Z/1\}$
- 5  $\{F/0, G/1\}$
- 6  $A/1 \subset H/1$ , thus  $A/1$  can represent  $H/1$  and all its equivalent faults in class 4
- 7  $C/0 \subset F/0$ , thus  $C/0$  can represent  $F/0$  and all its equivalent faults in class 5
- 8  $V/0 \subset Z/0$ , but  $V/0$  belongs to equivalence class 3, which has been merged into class 2. Any fault from this class is dominated by  $Z/0$ .
- 9  $B/1 \subset H/1$
- 10  $D/0 \subset F/0$
- 11  $E/1 \subset V/1$
- $\{A/0, A/1, B/1, C/0, C/1, D/0, E/1\}$



In a Fanout-Free circuit (Tree-like with no fanout nodes), PI faults form a dominance collapsed fault set.

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 13

# Fanout-Free Circuits

- This is a special class of circuits that are easy to test

Definition 1: Every line  $x$  has a maximum fanout of one gate.

Definition 2: There is just one path from every line  $x$  to the primary output

- Every logic circuit can be decomposed into a set of fanout-free subcircuits separated by fanout points


Definition 3: A set of tests  $T = \{t_1, t_2, \dots, t_k\}$  is **complete** if it detects (covers) all detectable SSL faults in the circuit

## Theorem

- In an fanout-free circuit, every test set that detects all SSL faults on primary inputs is **complete**.
 
# Checkpoints

- Primary inputs and fanout branches of a combinational circuit are called *checkpoints*.
- Checkpoint theorem: A test set that detects all single (multiple) stuck-at faults on all checkpoints of a combinational circuit, also detects all single (multiple) stuck-at faults in that circuit.




# Classes of Stuck-at Faults

- Following classes of single stuck-at faults are identified by fault simulators:
  - ❑ *Potentially-detectable fault* -- Test produces an unknown (X) state at *primary output* (PO); detection is probabilistic, usually with 50% probability.
  - ❑ *Initialization fault* -- Fault prevents initialization of the faulty circuit; can be detected as a potentially-detectable fault.
  - ❑ *Hyperactive fault* -- Fault induces much internal signal activity without reaching PO.
  - ❑ *Undetectable(Redundant) fault* -- No test exists for the fault.
  - ❑ *Untestable fault* -- Test generator is unable to find a test.
  - ❑ Some faults are detected by lots of tests—”easy” faults
  - ❑ Some faults are detected by few tests—”hard” faults
  - ❑ Some input patterns detect no faults
  - ❑ The number of tests needed for a *complete test set* is often a small fraction of the total number of input patterns available
  - ❑ Finding a minimal test set is hard and usually impractical

## Combinational Circuit Testing
 
### Basic Definitions


- Let fault  $f$  change output  $Z(X)$  of a circuit  $C$  to  $Z_f(X)$ .
- A TV  $t$  detects  $f$  if  $Z(t) \neq Z_f(t) \rightarrow Z(t) \oplus Z_f(t) = 1$
- Fault  $f$  is Undetectable or Redundant if  $Z(t) = Z_f(t) \quad \forall t$ .
- If the fault line  $x$  s-a-d is undetectable, then  $x$  and circuits feeding  $x$  can be removed from the circuit.






# Combinational Circuit Testing

## Another Example

 

## Redundancy

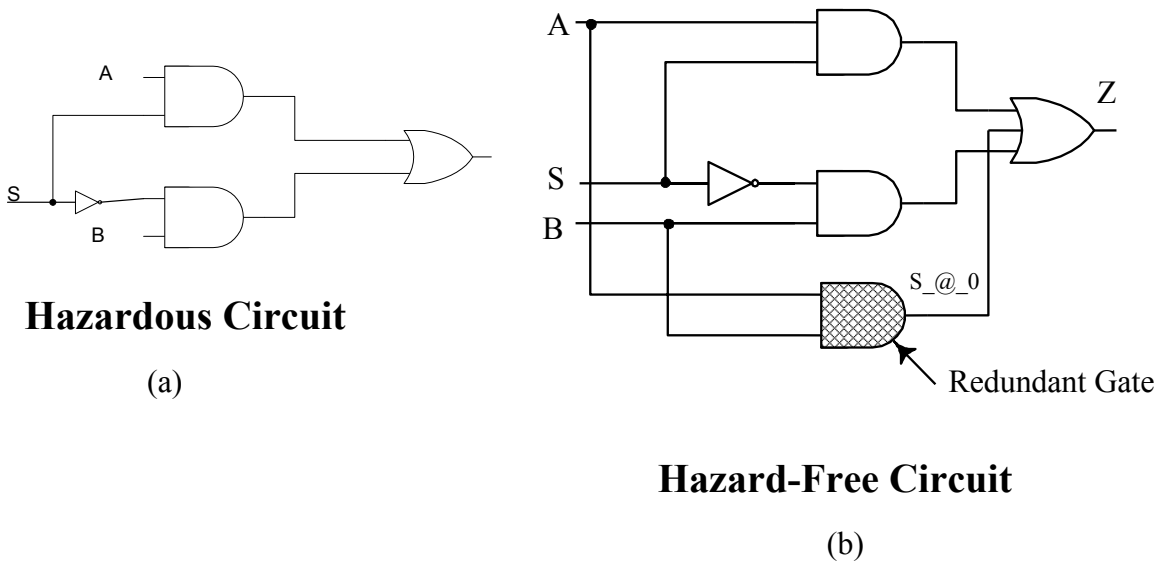

# Combinational Circuit Testing

## Basic Definitions (cont'd)

- A set of tests  $T = \{t_1, t_2, \dots, t_k\}$  is **complete** if it detects (covers) all detectable SSL faults in the circuit
- We can represent any test set  $\{t_1, t_2, \dots, t_k\}$  by the Boolean function whose minterms are  $\{t_1, t_2, \dots, t_k\}$ .
- **Example**, the function  $Z(a,b,c,d) = a'bd' + abcd$  denotes the 3-member test set  $\{0100, 0110, 1111\}$ .
- The set of all tests for fault  $f$  is expressed by the Boolean function  $(Z(x) \oplus Z_f(x))$

## Boolean Difference

- **Shannon's Expansion Theorem:**

$$F(X_1, X_2, \dots, X_n) = X_2 \bullet F(X_1, 1, \dots, X_n) + \overline{X_2} \bullet F(X_1, 0, \dots, X_n)$$

- **Boolean Difference (partial derivative):**

$$\frac{\partial F_j}{\partial g} = F_j(1, X_1, X_2, \dots, X_n) \oplus F_j(0, X_1, \dots, X_n)$$

- **Fault Detection Requirements for g stuck-at 0:**

$$G(X_1, X_2, \dots, X_n) = 1$$

$$\frac{\partial F_j}{\partial g} = F_j(1, X_1, X_2, \dots, X_n) \oplus F_j(0, X_1, \dots, X_n) = 1$$