

DIGITAL SYSTEM TESTING

COE -545


Lecture – 05

Test Generation (Boolean Difference)

Combinational Circuit Testing

Basic Definitions

 
- Let fault f change output $Z(X)$ of a circuit C to $Z_f(X)$.
- A TV t detects f if $Z(t) \neq Z_f(t) \rightarrow Z(t) \oplus Z_f(t) = 1$
- Fault f is Undetectable or Redundant if $Z(t) = Z_f(t) \quad \forall t$.
- If the fault *line x s-a-d* is undetectable, then x and circuits feeding x can be *removed* from the circuit.




S_@_1

Combinational Circuit Testing

Another Example

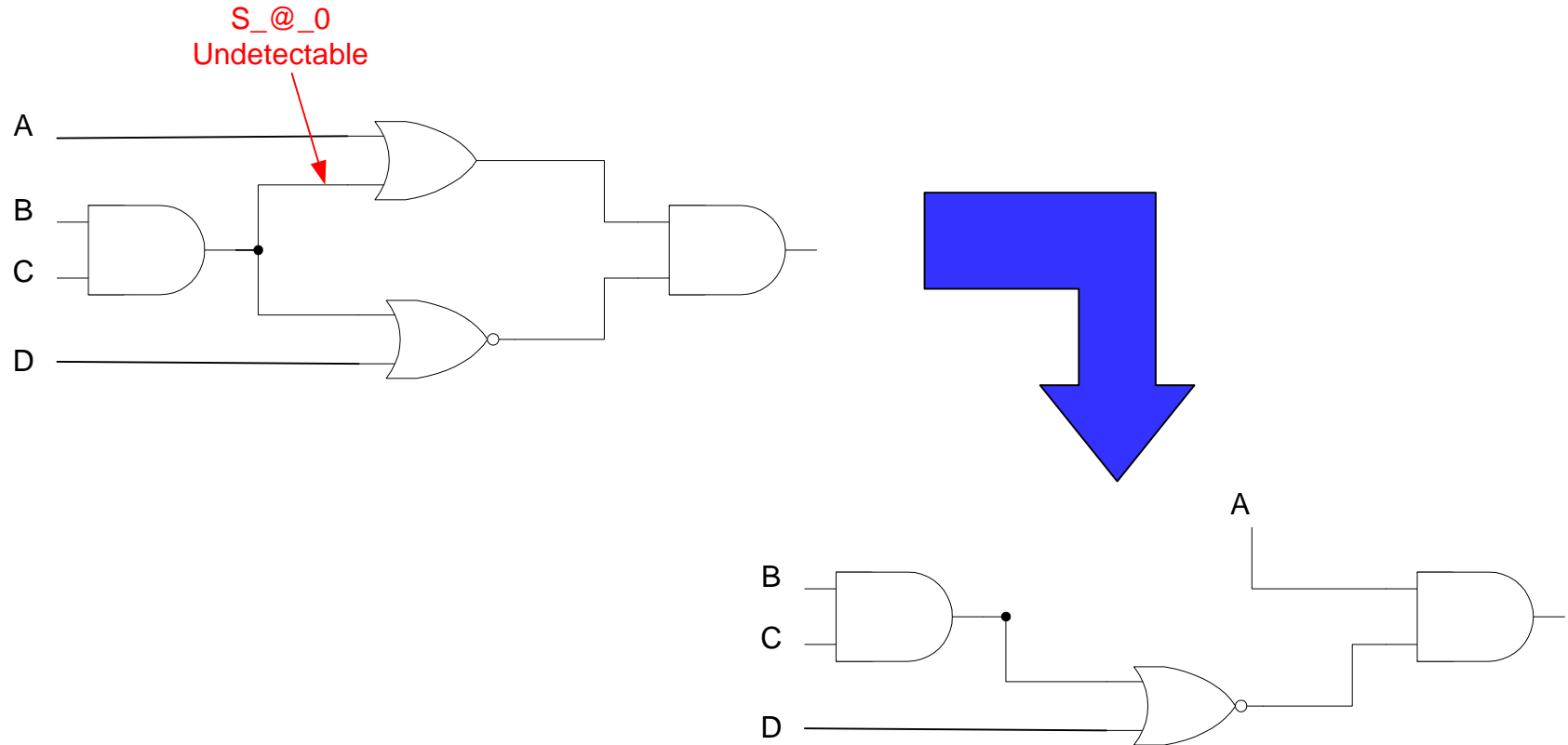


Redundancy

 

Hazardous Circuit

(a)

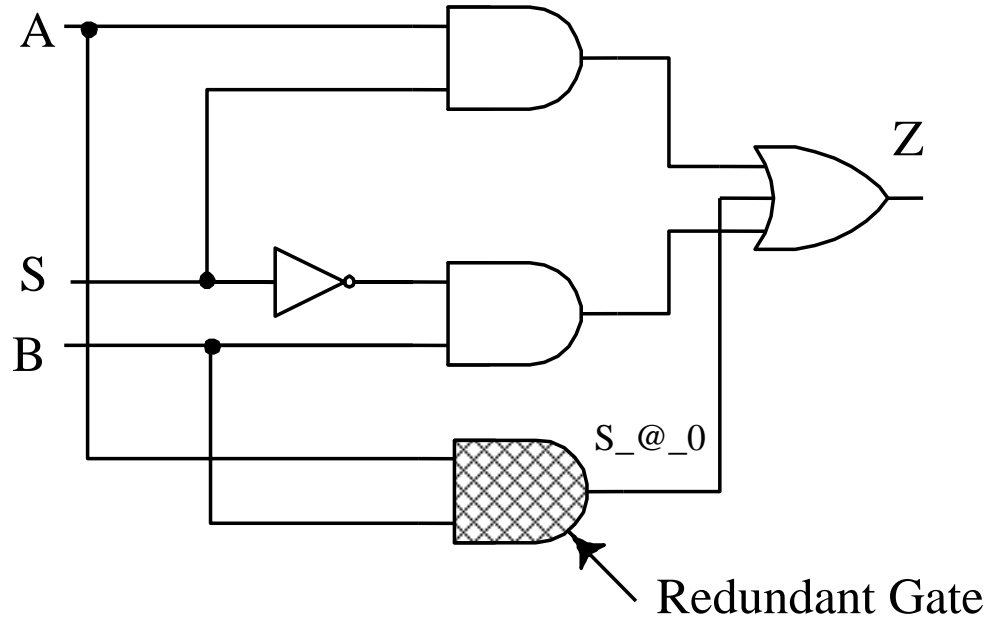

Hazard-Free Circuit

(b)

Combinational Circuit Testing

Basic Definitions (cont'd)

- A set of tests $T = \{t_1, t_2, \dots, t_k\}$ is complete if it detects (covers) all detectable SSL faults in the circuit
- We can represent any test set $\{t_1, t_2, \dots, t_k\}$ by the Boolean function whose minterms are $\{t_1, t_2, \dots, t_k\}$.
- Example, the function $Z(a,b,c,d) = a'bd' + abcd$ denotes the 3-member test set $\{0100, 0110, 1111\}$.

- The set of all TVs for fault f is expressed by the Boolean function $(Z(x) \oplus Z_f(x))$

Example

- Fault-Free Fun = $F(a,b,c) = (a + b)(b + c)$
- Fault = $b/0$
- Faulty Fun = $F_{\alpha} = ac$
- TVs Detecting this Fault Should Satisfy: $(F \oplus F_{\alpha}) = 1$
- Thus, $(a + b)(b + c) \oplus ac = B(A' + C')$
- This represents 2 possible Tests
- TV set for $a/1 = \{01x, x10\} \rightarrow \{010, 011, 110\}$

Boolean Difference Method

- Fault-Free Fun= $F(x_1, x_2, \dots, x_n)$
- Assuming a SSL Fault $x_i/1$
- $F_\alpha = F(x_i=1) = F(x_1, x_2, \dots, 1, \dots, x_n) = F_i(1)$
- Assuming a SSL Fault $x_i/0$
- $F_\alpha = F(x_i=0) = F(x_1, x_2, \dots, 0, \dots, x_n) = F_i(0)$
- According to Shannon's Expansion Theorem:

$$F(x_1, x_2, \dots, x_n) = x_i F_i(1) + \bar{x}_i F_i(0)$$

- Thus, the Test Set to Detect $x_i/0$ corresponds to :

$$T_0 = x_i (F_i(1) \oplus F_i(0)) , \text{ Likewise}$$

- The Test Set to Detect $x_i/1$ corresponds to :

$$T_1 = \bar{x}_i (F_i(1) \oplus F_i(0))$$

Boolean Difference Method

- The Expression $(F_i(1) \oplus F_i(0))$ is Termed the Boolean Difference of F wrt x_i , or (dF/dx_i)
- Thus, the Test Set to Detect $x_i/0$ corresponds to :

$$T_0 = x_i \cdot (dF/dx_i)$$

The Test Set to Detect $x_i/1$ corresponds to :

$$T_1 = \bar{x}_i \cdot (dF/dx_i)$$

Notes:

- The x_i 's are Primary Inputs
- A Fault on some PI (x_i) is Undetectable iff


$$F_i(1) = F_i(0)$$

OR

$$dF/dx_i = 0$$

Which Means that **F is INDEPENDENT OF x_i**

Example

 

- Fault = **a/1**
- Fault-Free Fun= $F(a,b,c,d) = (a + bc)(b' + c')d'$
- $\mathbf{T}(a/1) = a'.dF/da$
- $dF/da = [1(b' + c')d' \oplus bc(b' + c')d']$
 $= b'd' + c'd'$
- So $\mathbf{T}(a/1) = a'b'd' + a'c'd'$
- Test set for a/1 = $\{00x0, 0x00\} = \{0000, 0010, 0100\}$

Boolean Difference Method

- Boolean Difference (BD) has the following Properties:

$$1. d\bar{F}/dx_i = dF/dx_i$$


$$2. d/dx_i[dF/dx_j] = d/dx_j[dF/dx_i]$$

$$3. d[F(X) \oplus G(X)]/dx_i = dF/dx_i \oplus dG/dx_i$$

$$4. d[F(X).G(X)]/dx_i = F.dG(X)/dx_i \oplus G.dF(X)/dx_i \oplus dF(X)/dx_i .dG(X)/dx_i$$

$$5. d[F(X) + G(X)]/dx_i = \bar{F}.dG/dx_i \oplus \bar{G}.dF/dx_i \oplus (dF/dx_i).(dG/dx_i)$$

Example

 

- Fault = $\beta/0$
- $\mathbf{T}(\beta/0) = \beta(\mathbf{X}).dF(x, \beta)/d\beta$
 - $\beta(\mathbf{X}) = a + bc$ $F(x, \beta) = (b' + c')d' \beta$
- $dF/d\beta = (b' + c')d'$
- So $\mathbf{T}(\beta/0) = ab'd' + ac'd'$
- Test set for $\beta/0 = \{1000, 1010, 1100\}$

Test Generation Schemes

- BD method is more Theoretical → Too Complex to Use for Practical Circuits
- Need a More Practical Approach
- **Deterministic Test Generation**
 - Fault- Oriented ATG
 - Fault Independent ATG
- **Random Test Generation**
 - Combined Deterministic and Random Test Generation
- **ATG Systems**
- **Conclusions**

Classification & Problems


Testing

- **Off- Line**
- **Edge- Pin**
- **Stored- Pattern**
- **Full Comparison of the Output Results**

General Problems for TG:


- **Cost of Generating the Test**
- **Quality of the Generated Test**
- **Cost of Applying the Test**

Deterministic Test Generation

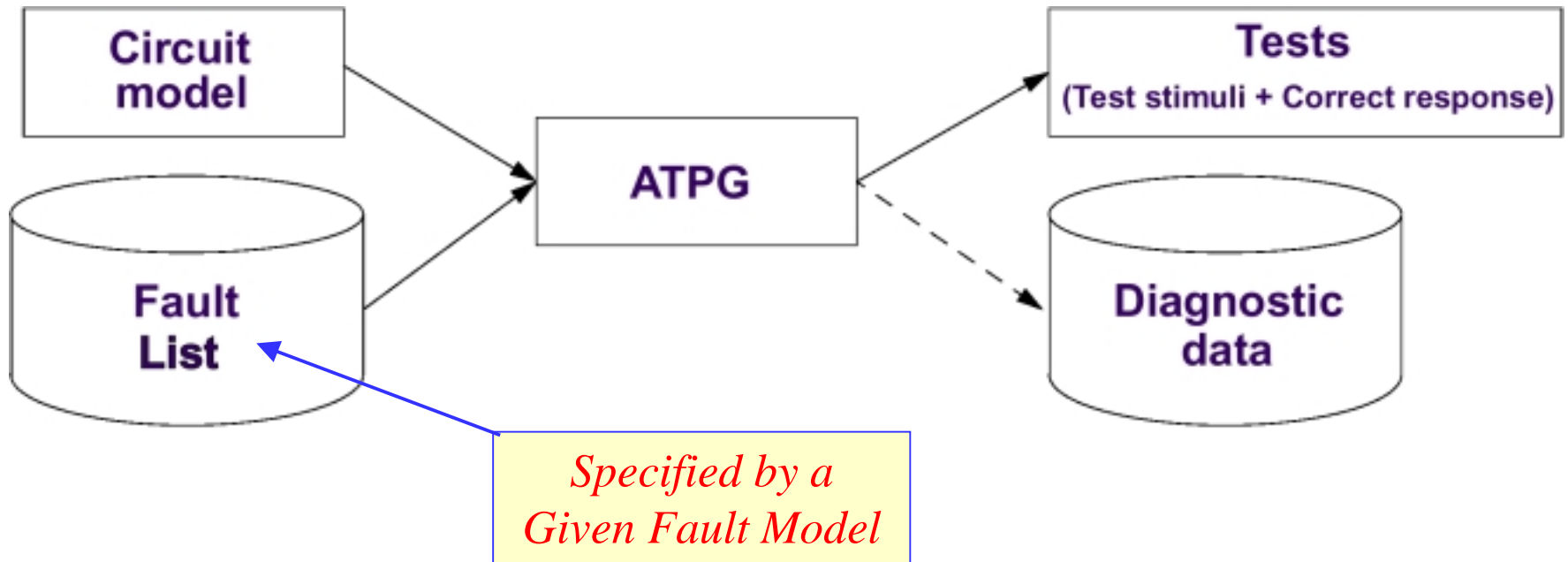

- **Manual / Automatic**
 - **Automatic Test Pattern Generation (ATPG)**
- **Deterministic ATPG Can Be Fault- Oriented / Fault-Independent**

Fault-Oriented ATPG

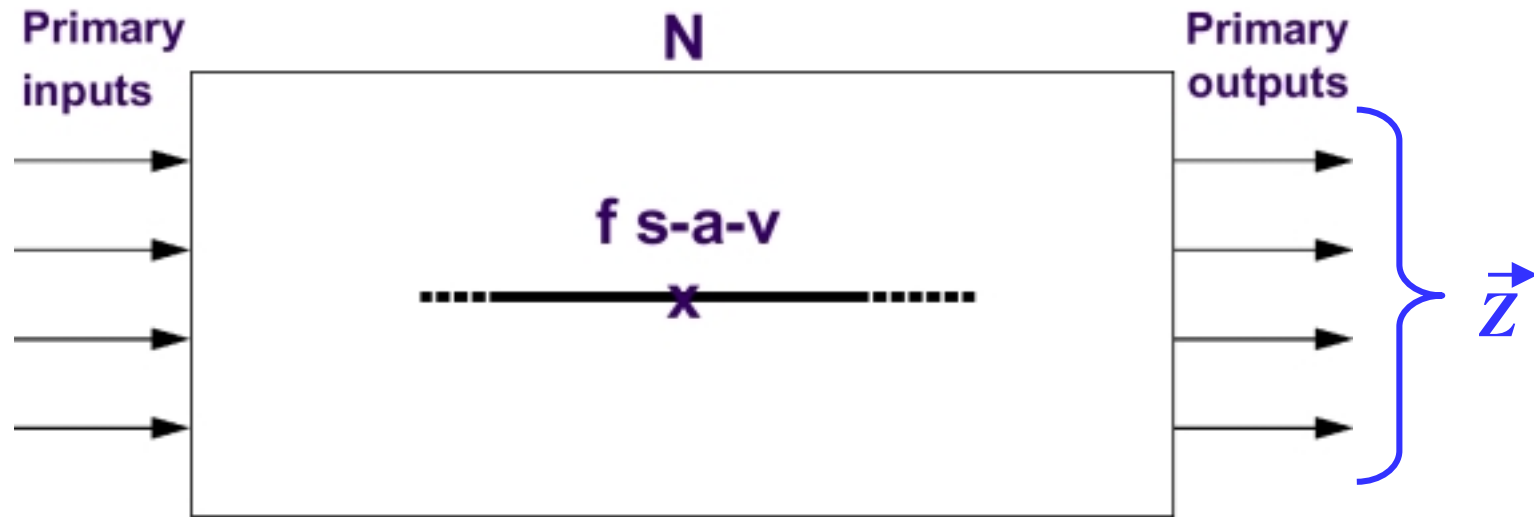

- Targets a Particular Fault $f \in \{ \text{Fault List} \}$

➤ Finds a TV t which Detects f

$$\square \quad t \text{ Detects } f \iff Z(t) \neq Z_f(t) \iff Z(t) \oplus Z_f(t) = 1$$


TV Generation

- **Two** Steps Are Necessary to Generate TV t which Detects Fault f :
 - Fault Activation/excitation/provoking: Effecting a Different Value \bar{v} at the Faulty Line x When x Is Stuck at v .
 - Fault Propagation: Propagating Error to an Observable PO

Definitions

- A *Line* whose Value under TV t Changes in the Presence of Fault f is Said to Be Sensitized to the Fault f by the Test t
- A Path Composed of Sensitized Lines Is Called a Sensitized Path


Single Path Sensitization

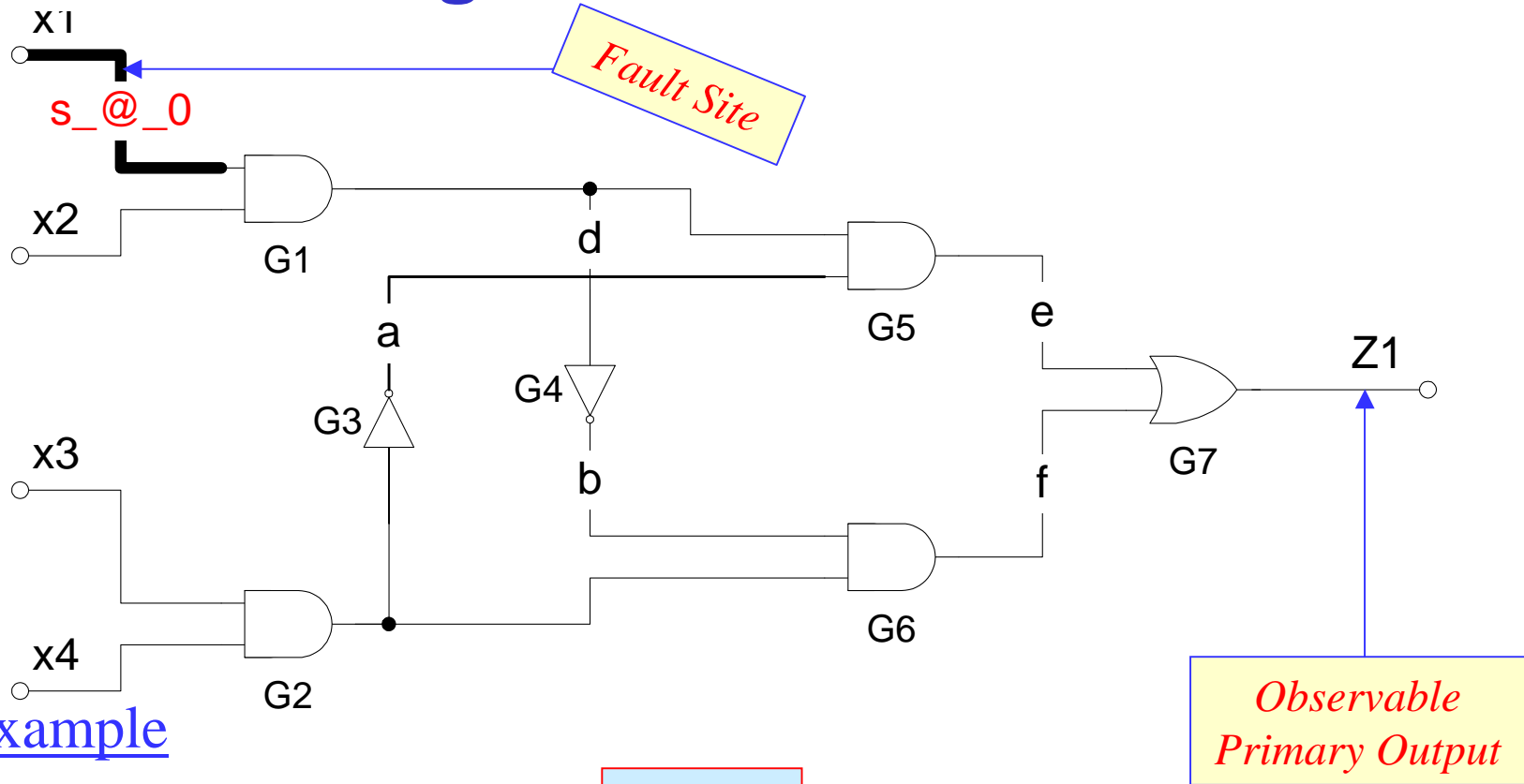

Example

1. Fault Activation \rightarrow **X1=1**
2. Fault Propagation \rightarrow 2 Possible Options (Paths)
 - Option 1: $G_1 - G_5 - G_7$
 - Option 2: $G_1 - G_4 - G_6 - G_7$


Single Path Sensitization *Option 1*

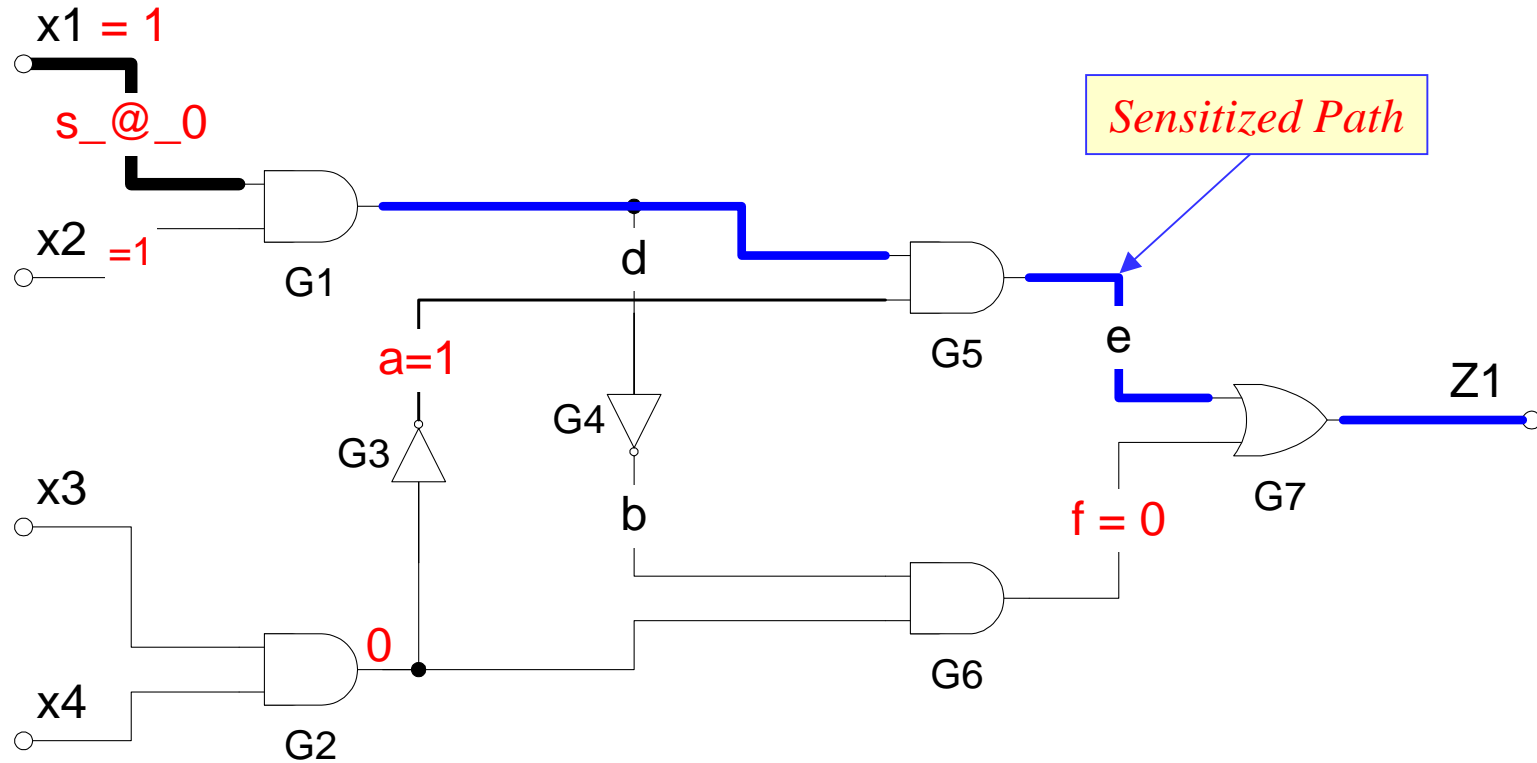

Example

1. Fault Activation $\rightarrow X1=1$
2. Fault Propagation : G1 – G5 – G7 \rightarrow *Two Possible TVs*
 - T1 = 110X , 1
 - T2 = 11X0 , 1

Single Path Sensitization *Option 2*

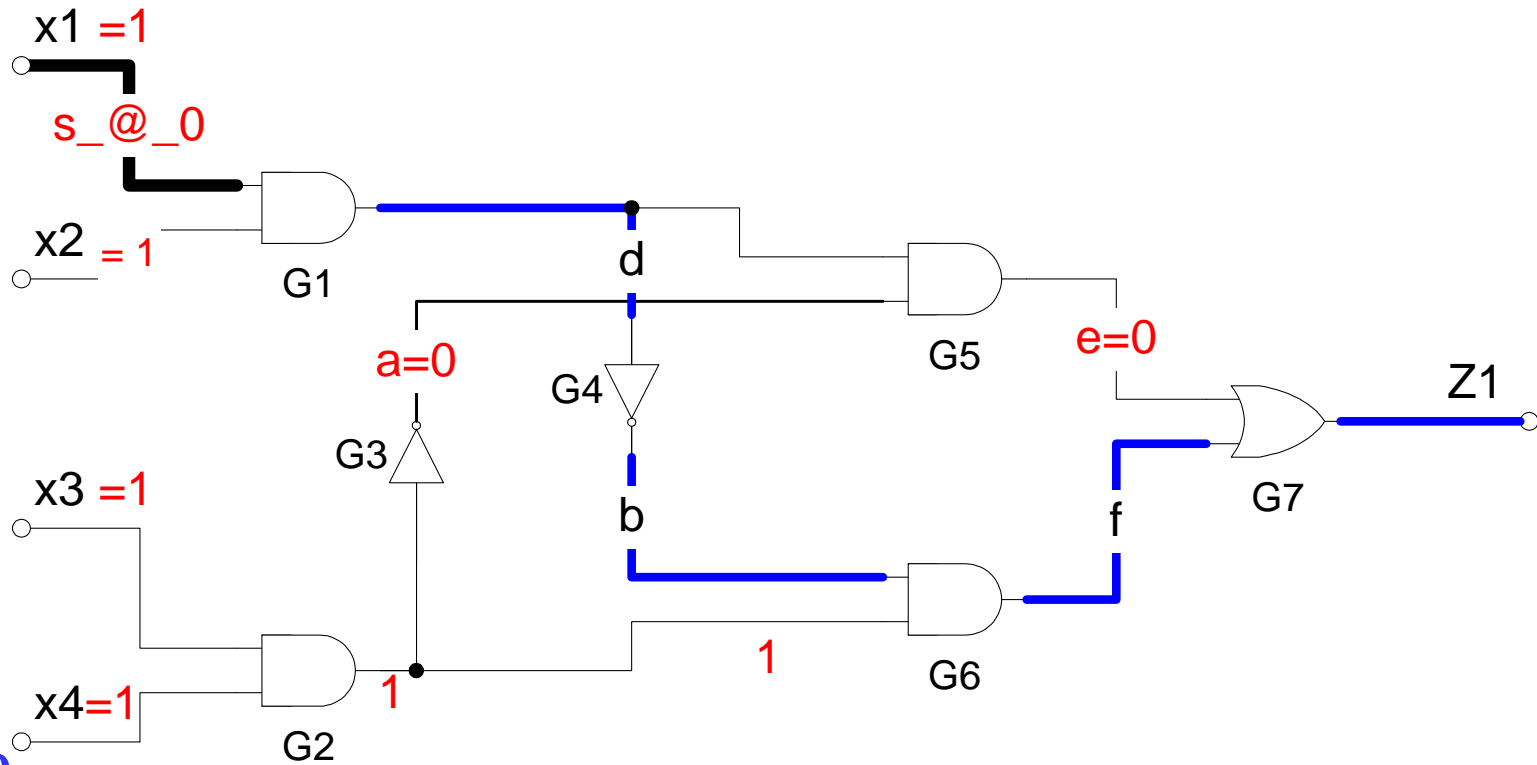

Example

1. Fault Activation $\rightarrow X1=1$


2. Fault Propagation : G1 – G4 – G6 - G7

\rightarrow *One Possible TV* $\rightarrow T = 1111, 0$


Multiple Path Sensitization

Major *Problem* with Single Path Sensitization

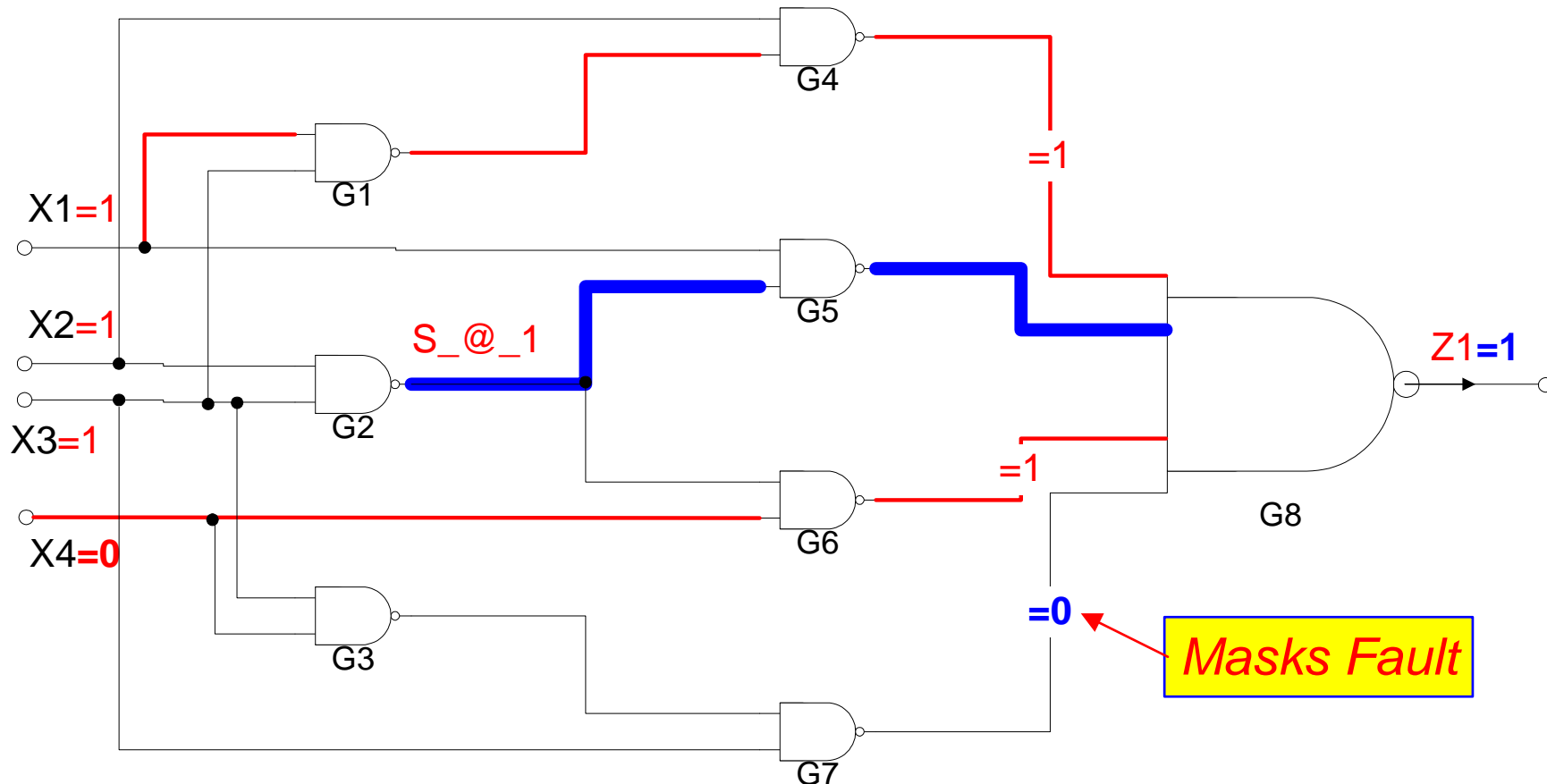- A TV May not be Possible to Generate for Some *Testable* Faults if Only One Path is Sensitized at a Time



Multiple Path Sensitization

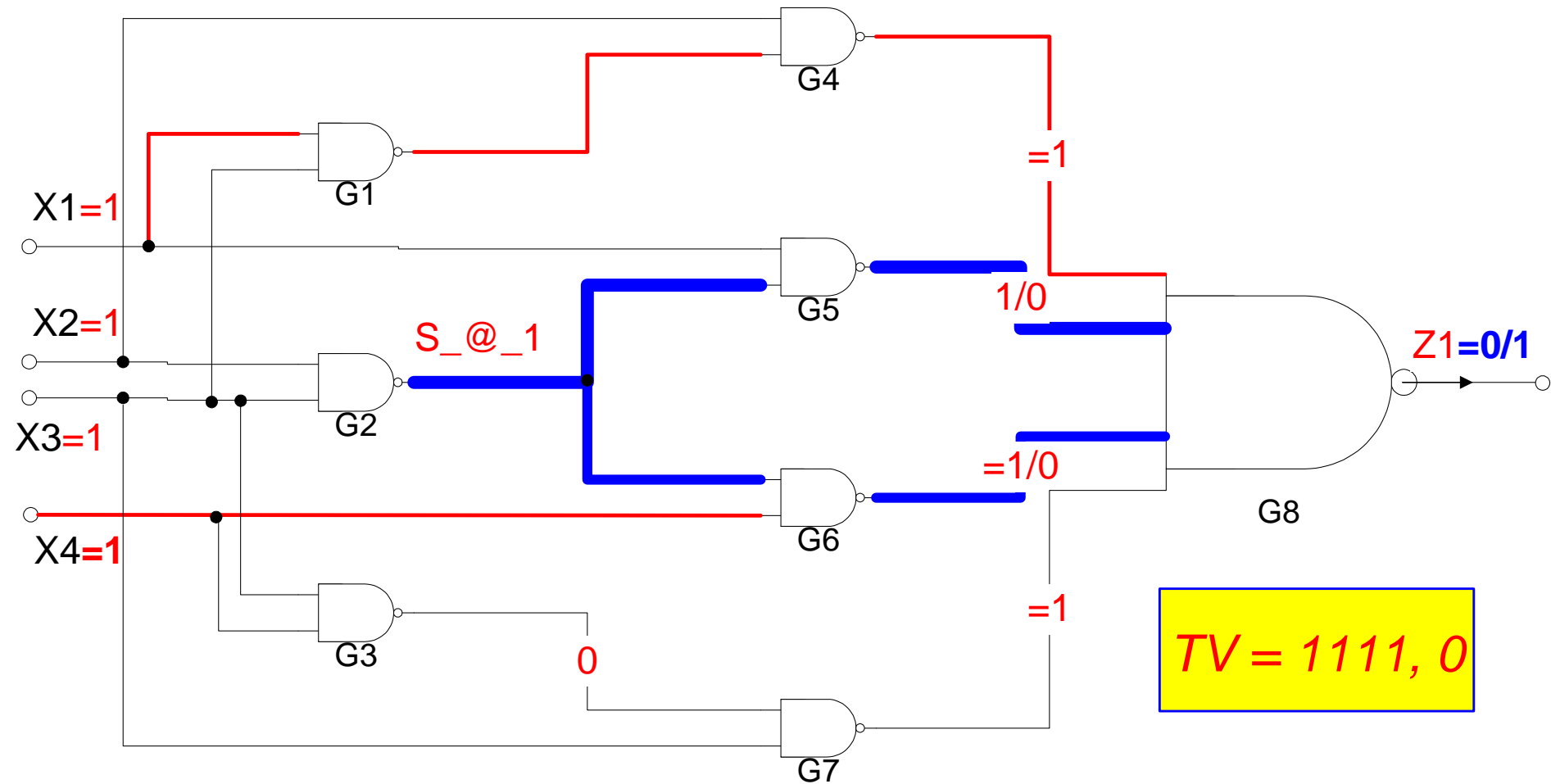

The D-Algorithm

- An Algorithmic Approach which Generates a TV for a Given Fault if One Exists
- Multiple Path Sensitization
- 5-Valued Logic { 0, 1, X, D, \bar{D} }
- **D**: A Line is Assigned a **D** value if it has a value **1** in the **Fault-Free** Circuit but has a **0** Value in the **Faulty** Circuit.
(**D** \approx S_@_0)
- **\bar{D}** : A Line is Assigned a **\bar{D}** value if it has a value **0** in the **Fault-Free** Circuit but has a **1** Value in the **Faulty** Circuit.
(**\bar{D}** \approx S_@_1)
- D / \bar{D} Follow Rules of Boolean Algebra


The D-Algorithm

$\mathbf{D + D = D}$	$\overline{\mathbf{D}} + \overline{\mathbf{D}} = \overline{\mathbf{D}}$
$\mathbf{D . D = D}$	$\overline{\mathbf{D}} . \overline{\mathbf{D}} = \overline{\mathbf{D}}$
$\overline{\mathbf{D}} + \mathbf{D} = \mathbf{1}$	$\mathbf{D} . \overline{\mathbf{D}} = \mathbf{0}$
$\mathbf{D} . \mathbf{1} = \mathbf{D}$	$\overline{\mathbf{D}} . \mathbf{1} = \overline{\mathbf{D}}$
$\mathbf{D} . \mathbf{0} = \mathbf{0}$	$\overline{\mathbf{D}} . \mathbf{0} = \mathbf{0}$
$\mathbf{D} + \mathbf{1} = \mathbf{1}$	$\overline{\mathbf{D}} + \mathbf{1} = \mathbf{1}$
$\mathbf{D} + \mathbf{0} = \mathbf{D}$	$\overline{\mathbf{D}} + \mathbf{0} = \overline{\mathbf{D}}$


\bullet	$\mathbf{0}$	$\mathbf{1}$	\mathbf{D}	$\overline{\mathbf{D}}$	\mathbf{x}
$\mathbf{0}$	0	0	0	0	0
$\mathbf{1}$	0	1	D	$\overline{\mathbf{D}}$	x
\mathbf{D}	0	D	D	0	x
$\overline{\mathbf{D}}$	0	$\overline{\mathbf{D}}$	0	$\overline{\mathbf{D}}$	x
\mathbf{x}	0	X	x	x	x

**AND Operation of the
5-Valued D-Calculus**

Example - Single Path Sensitization

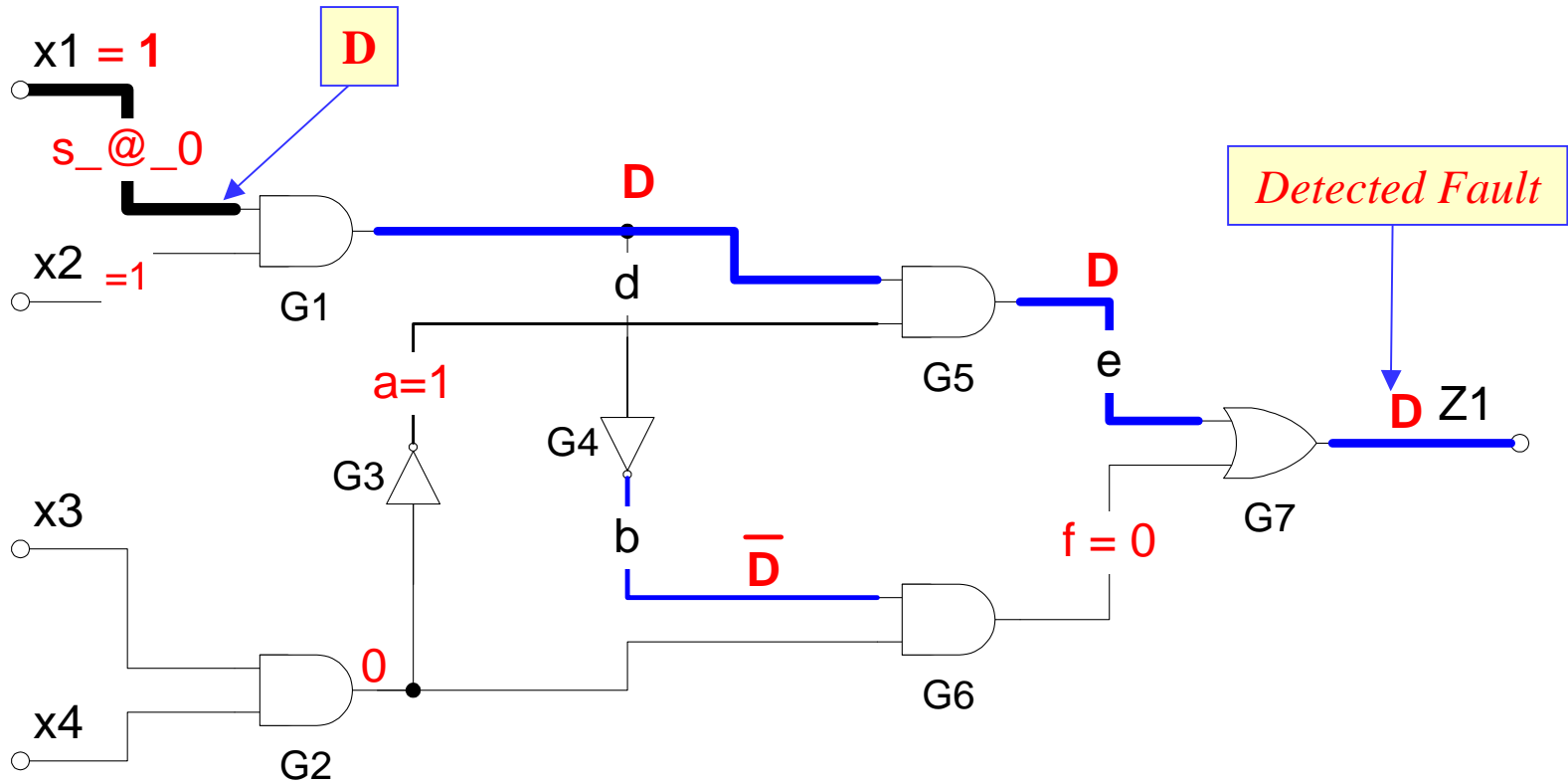

Example - Multiple Path Sensitization

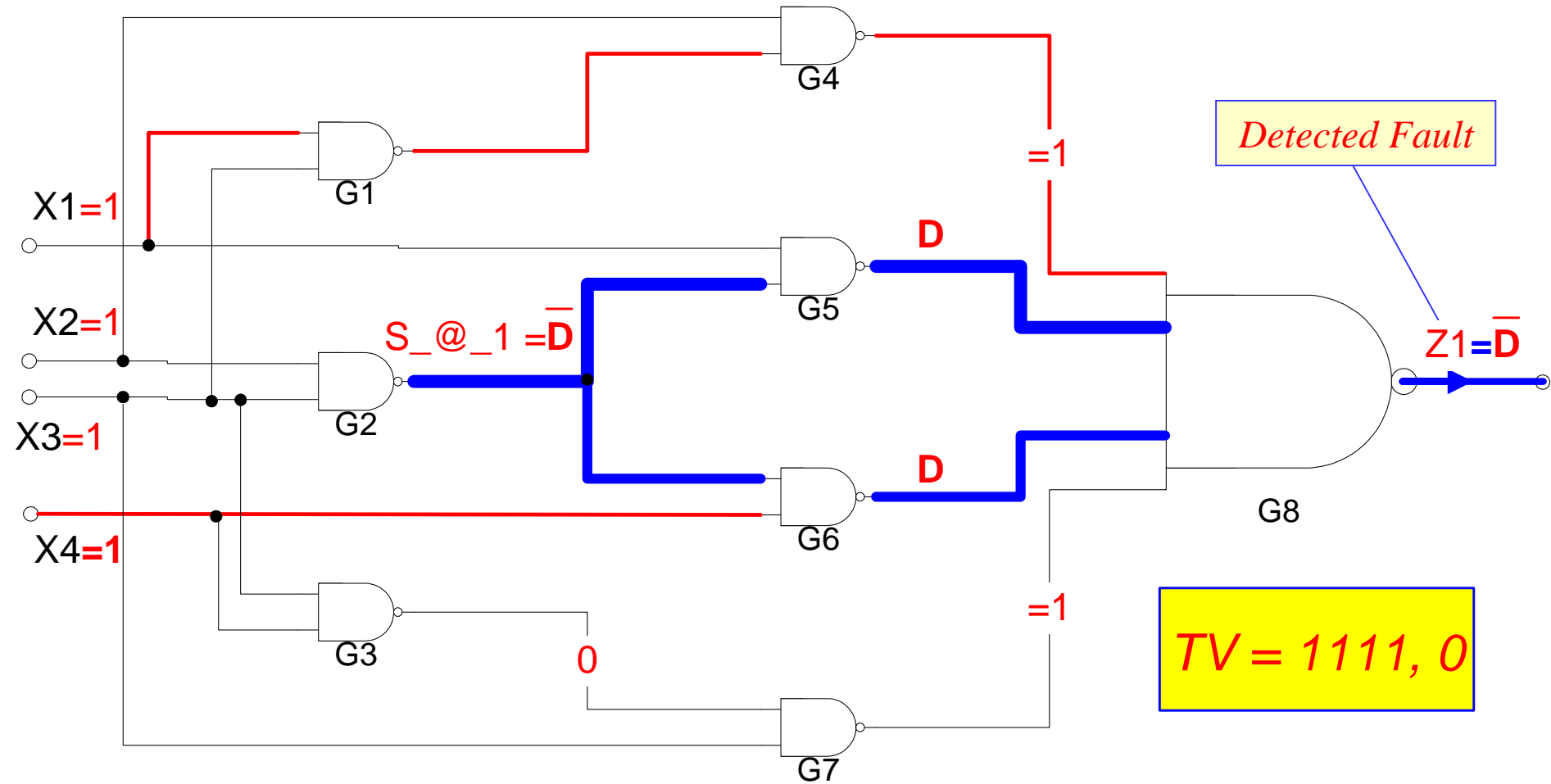

Definitions

1. Singular Covers (SC) of Some Function F

(Primitive Cubes of F) : *Minimal Set of Logic Signal Assignments Showing Essential Prime Implicants*

= Prime Implicants of \underline{F} ($\alpha 1$) &&
 Prime Implicants of \overline{F} ($\alpha 0$)

Examples Singular Covers of 2-Input NAND Gate

A	B	F
0	X	1
X	0	1
1	1	0

Pis of \overline{F}
($\alpha 0$) →
 Pis of F
($\alpha 1$)

Definitions-- Singular Covers (SC) (Primitive Cubes)

Example

A	B	C	F
X	X	1	1
0	0	X	1
X	1	0	0
1	X	0	0

{ PIs of F
 $(\alpha 1)$

{ PIs of \bar{F}
 $(\alpha 0)$

SCs of F

		BC			
		00	01	11	10
A	0	1	1	1	
A	1		1	1	

K-Map of F


Definitions

2. Primitive D-Cubes of a Fault (PDCF)

= Prime Implicants of the *Faulty* Function
which Produce D / \bar{D} Output

*{I/P. Stimuli Required to Activate Faulty Condition at a
Gate/Module Output}*

Examples PDCF of 2-Input NAND Gate

 

A	B	F
D	1	\bar{D}
\bar{D}	1	D
1	D	\bar{D}
1	\bar{D}	D
D	D	\bar{D}
\bar{D}	\bar{D}	D

Definitions -- Primitive D-Cubes of a Fault (PDCF)

Computing PDCF of a General Module (Function)

1. Obtain the SCs of the Fault-Free Function (α_1, α_0)
2. Obtain the SCs of the Faulty Function (β_1, β_0)
3. PDCF for this module Result from Intersecting α_1 with β_0 and α_0 with β_1 .

Thus

$$\text{PDCF} = \{ \alpha_1 \cap \beta_0, \alpha_0 \cap \beta_1 \}$$

Definitions-- -- Primitive D-Cubes of a Fault (PDCF) -- Example

Example

A	B	C	F
X	X	1	1
0	0	X	1
X	1	0	0
1	X	0	0

PIs of F
($\alpha 1$)

PIs of \bar{F}
($\alpha 0$)

A	B	C	F
X	X	1	1
0	1	X	1
X	0	0	0
1	X	0	0

PIs of F
($\beta 1$)

PIs of \bar{F}
($\beta 0$)

PDCF

$\alpha 0 \cap \beta 1$

A	B	C	F
0	0	0	D
0	1	0	D

$\alpha 1 \cap \beta 0$

Definitions

3. Propagation D-Cube of a Gate/Module (PDC)


= Prime Implicants of the Function which Allow a D/\bar{D} Values on Inputs to Propagate to the Output

- Let $\{ \alpha_0 , \alpha_1 \}$ be the Singular Covers of the Function F , Where;
 - α_1 = Be the Prime Implicants of F
 - α_0 = Be the Prime Implicants of \bar{F}

$$\text{PDC} = \{ \alpha_1 \cap \alpha_0 \}$$

Definitions-- Propagation D-Cube (PDC)

Example PDCF of 2-Input NAND Gate

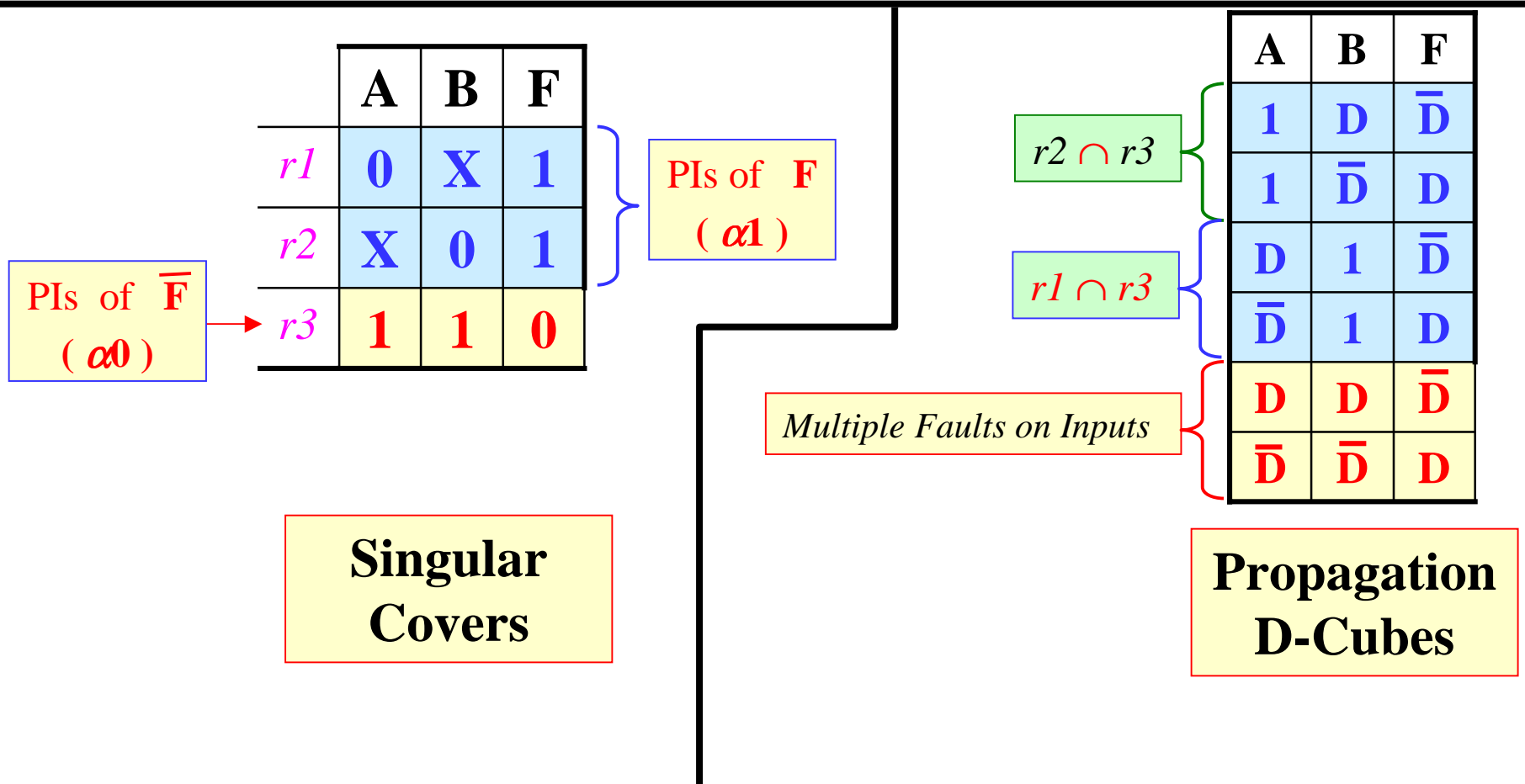


Intersection of D-Cubes

- Let $A = (a_1, a_2, a_3, \dots, a_n)$, and
- Let $B = (b_1, b_2, b_3, \dots, b_n)$ be 2 D-Cubes, where
 $a_i, b_i \in \{0, 1, x, D, \overline{D}\}$
- **The *D*-intersection:** of A and B , denoted $A \cap B$ is given by $\{a_i \cap b_i / a_i \in A, b_i \in B\}$, where :
 1. $x \cap a_i = a_i$
 2. If $(a_i \neq x \text{ and } b_i \neq x)$ Then
$$a_i \cap b_i = \begin{cases} a_i & \text{IF } a_i = b_i \\ \Phi & \text{IF } a_i \neq b_i \end{cases}$$
 3. $A \cap B = \Phi$ “Empty Cube” IF $a_i \cap b_i = \Phi$ For Any i

D- Intersection

- D-Intersection is Used to Generate Sensitized Paths (**D-Drive**)

Example PDC of 2-Input NAND Gate →

 

A	B	F
1	D	\bar{D}
1	\bar{D}	D
D	1	\bar{D}
\bar{D}	1	D
D	D	\bar{D}
\bar{D}	\bar{D}	D

$$\begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline D & 1 & x & \bar{D} & x \\ \hline \end{array} \cap \begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline x & x & 1 & \bar{D} & D \\ \hline \end{array} = \begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline D & 1 & 1 & \bar{D} & D \\ \hline \end{array}$$


D- Algorithm

1. Initialize Test Cube to all x 's ($x, x, x, \dots x$)
2. Fault Provoking \rightarrow Select a Primitive D-Cube of the Fault (PDCF) \rightarrow Usually a *Choice Step*
3. Path Sensitization From the Faulty Line To a **PO**
 - Successive X-ion of Test Cube with the Propagation D-Cubes of Successor Gates (*D-Frontier*) Till a **PO** Gets a **D** / $\bar{\mathbf{D}}$ Value (*Choice Step*) \rightarrow This Step is known as *D-Drive*
 - This Step Requires 2 Major Procedures
 - a. Implication (Forward and Backward), and
 - b. Line Justification (*Consistency Checks*) \rightarrow May Lead to *Backtracks* if Inconsistencies are Detected.

Implication

- Assignments Made Due to Choices, e.g. a Propagation D-Cube, Usually Uniquely Imply Other Signal Values {Forward & Backward}

Example

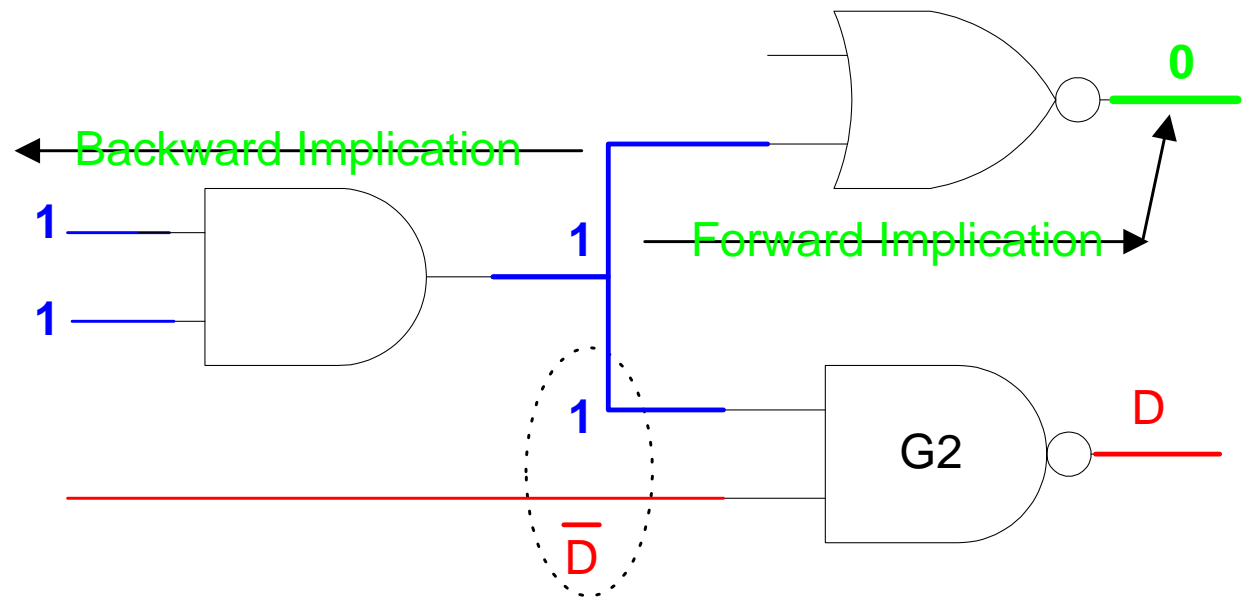

Chosen Propagation
Cube

D-Frontier

- The **D-Frontier** Consists of **ALL** Gates whose Current O/P Value is “**x**” but have one or more **D/ \bar{D}** on their inputs
- One of the **D-Frontier** Gates is Usually Chosen to Propagate The Fault → “**D-Drive**”

Line Justification

Is a Backward *Implication Step* Where The Gate I/P Values are Selected To Justify the Specified Gate Output. This Step is Repeated Till the Relevant **PIs** are Defined.


- *Line Justification* is Performed after **D/ \bar{D}** Appear at Some **PO**.

Line Justification-Example

- An Unjustified Line is a Defined Gate Output which is not Implied By The Gate Inputs

J-Frontier

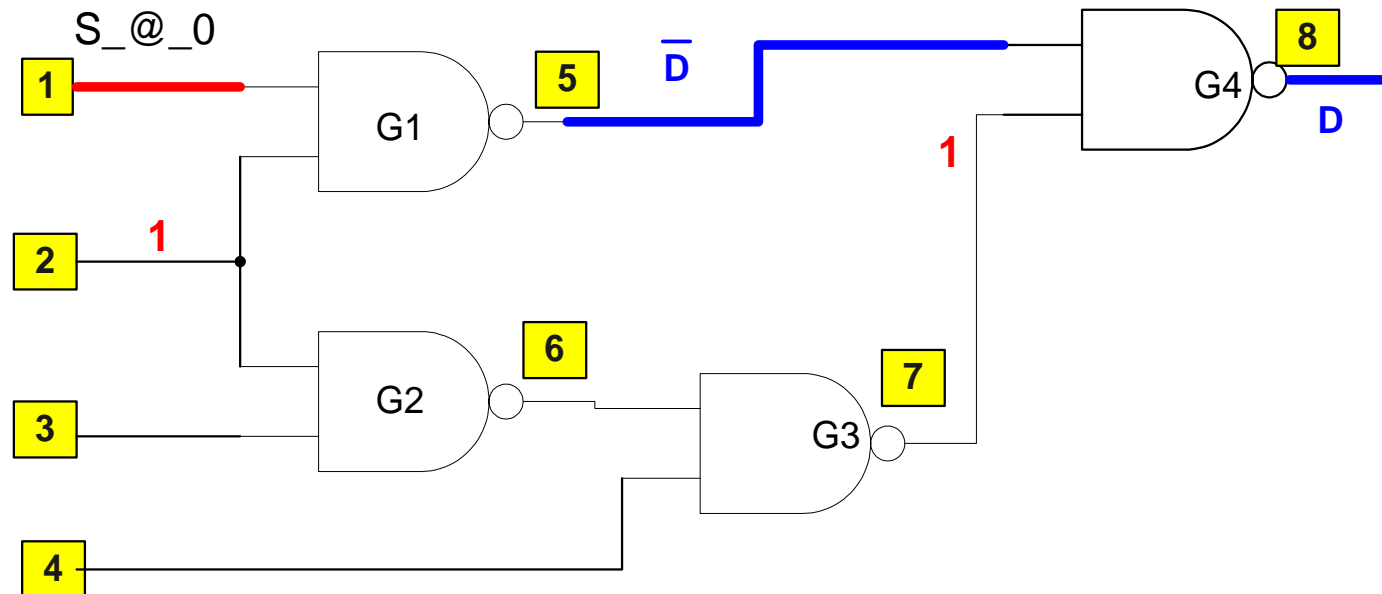
Is the Set of ALL Gates whose Output Lines are Unjustified



Line Justification

Example (*Line Justification*) → Line 1 S_@_0

$t^0 = \text{PDFC}^1$

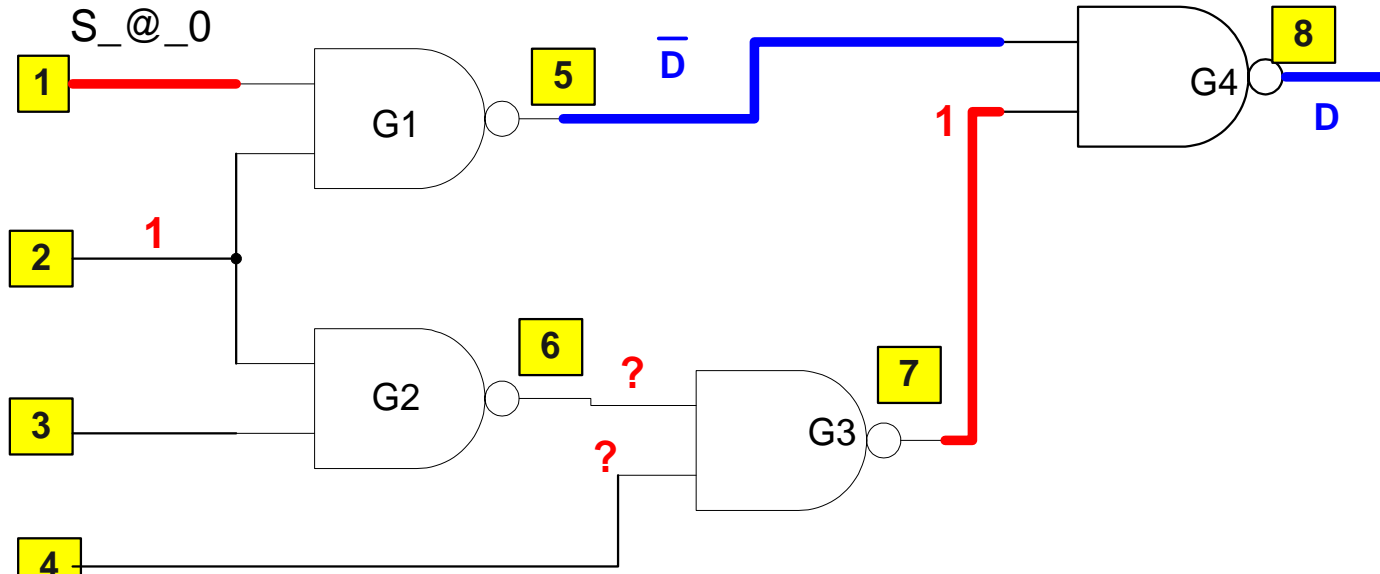

1	2	3	4	5	6	7	8
D	1			\bar{D}			
D	1			\bar{D}		1	D

J-Frontier = {G3} “*Line 7 Unjustified*”

Either Line 4 = 0, OR

Line 6=0

1	2	3	4	5	6	7	8
D	1	x	x	\bar{D}	0	1	D
D	1	1	x	\bar{D}	0	1	D

$t^2 = t^1 \cap Sc^3$ J_F = {G₂}

$t^3 = t^2 \cap Sc^2$ J_F = {Φ}

D-Drive

NOTES on D-ALGORITHM

1. Exhaustive Search of All Possible Choices
2. Guaranteed to Find a Solution (TV) *IF One Exists*.
3. Stops As Soon As A Solution Is Found
4. Being Exhaustive, the Worst Case Complexity is Exponential in the # of Gates
5. The Best Case Behavior Occurs When a Solution IS Generated ***WITHOUT ANY BACKTRACKING***:
 - Always Correct Decisions Are Made
 - Solution Is Obtained Only Through Forward & Backward Implication.

NOTES on D-ALGORITHM

6. THUS, the # of Backtracks Determines the Complexity of the Algorithm (Should be Minimized).
7. An Upper Limit is Placed on the # of Backtracks Beyond Which a Fault Is Declared UNTESTABLE!
8. To Minimize the # of Backtracks, It is Advisable to Discover Inconsistencies as Early as Possible Through *Forward & Backward Implications for Each Change in the Test Cube*

Outline of D-Algorithm

1. Model Fault with appropriate *Primitive D-cube of Fault* (PDF)
2. Select *Propagation D-cubes* to Propagate fault effect to a circuit output (*D-drive* procedure)
3. Select *singular cover* cubes to justify internal circuit signals (*Line Justification / Consistency* procedure)
 - Put Signal Assignments in *Test Cube*
 - Regrettably, Cubes Are Selected Very *Arbitrarily* by D-ALG