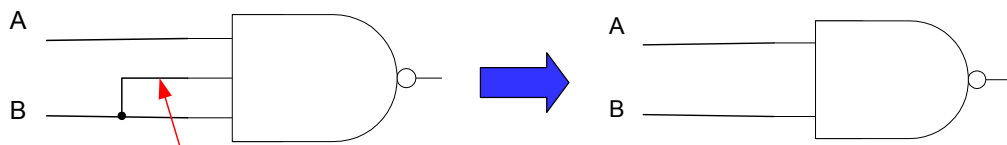


Combinational Circuit Testing

Basic Definitions

- Let fault f change output $Z(X)$ of a circuit C to $Z_f(X)$.
- A TV t detects f if $Z(t) \neq Z_f(t) \rightarrow Z(t) \oplus Z_f(t) = 1$
- Fault f is Undetectable or Redundant if $Z(t) = Z_f(t) \forall t$.
- If the fault line x s-a-d is undetectable, then x and circuits feeding x can be removed from the circuit.



COE - KFUPM


S_@_1

Dr. Alaaeldin Amin (COE 545)

Slide Number 2

Combinational Circuit Testing

Another Example

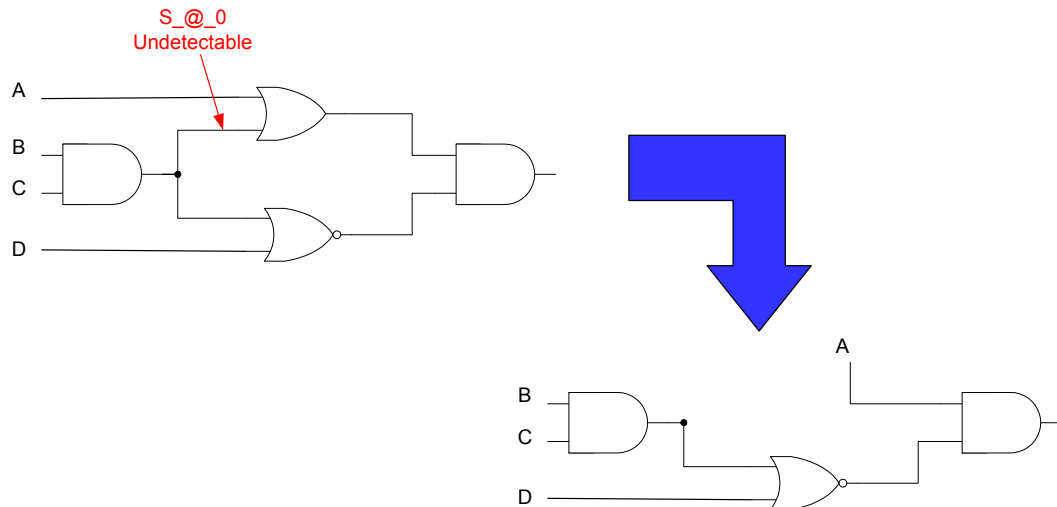


COE - KFUPM

Dr. Alaaeldin Amin (COE 545)


Slide Number 3

Redundancy

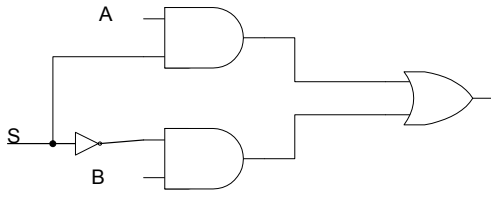

Hazardous Circuit

(a)

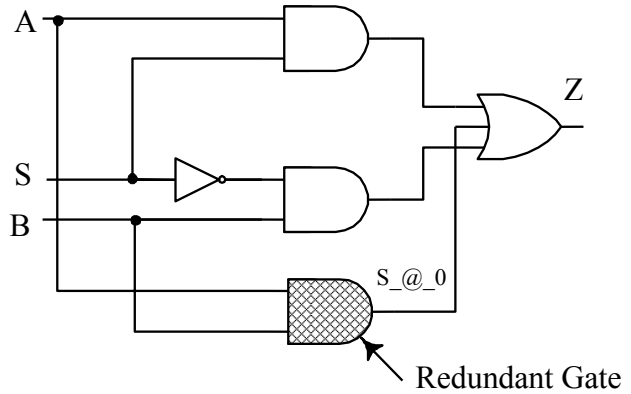

Hazard-Free Circuit

(b)

Combinational Circuit Testing

Basic Definitions (cont'd)

- A set of tests $T = \{t_1, t_2, \dots, t_k\}$ is **complete** if it detects (covers) all detectable SSL faults in the circuit
- We can represent any test set $\{t_1, t_2, \dots, t_k\}$ by the Boolean function whose minterms are $\{t_1, t_2, \dots, t_k\}$.
- **Example**, the function $Z(a,b,c,d) = a'bd' + abcd$ denotes the 3-member test set $\{0100, 0110, 1111\}$.

- The set of all TVs for fault f is expressed by the Boolean function $(Z(x) \oplus Z_f(x))$

Example

- Fault-Free Fun = $F(a,b,c) = (a + b)(b + c)$
- **Fault** = $b/0$
- *Faulty Fun* = $F_{\alpha} = ac$
- TVs Detecting this Fault Should Satisfy: $(F \oplus F_{\alpha}) = 1$
- Thus, $(a + b)(b + c) \oplus ac = B(A' + C')$
- This represents 2 possible Tests
- TV set for $a/1 = \{01x, x10\} \rightarrow \{010, 011, 110\}$

Boolean Difference Method

- Fault-Free Fun = $F(x_1, x_2, \dots, x_n)$
- Assuming a SSL Fault $x_i/1$
- $F_{\alpha} = F(x_i=1) = F(x_1, x_2, \dots, 1, \dots, x_n) = F_i(1)$
- Assuming a SSL Fault $x_i/0$
- $F_{\alpha} = F(x_i=0) = F(x_1, x_2, \dots, 0, \dots, x_n) = F_i(0)$
- According to Shannon's Expansion Theorem:
$$F(x_1, x_2, \dots, x_n) = x_i F_i(1) + \bar{x}_i F_i(0)$$
- Thus, the Test Set to Detect $x_i/0$ corresponds to :

$$T_0 = x_i (F_i(1) \oplus F_i(0)) , \text{ Likewise}$$

- The Test Set to Detect $x_i/1$ corresponds to :

$$T_1 = \bar{x}_i (F_i(1) \oplus F_i(0))$$

Boolean Difference Method

- The Expression $(F_i(1) \oplus F_i(0))$ is Termed the Boolean Difference of F wrt x_i , or (dF/dx_i)
- Thus, the Test Set to Detect $x_i/0$ corresponds to :

$$T_0 = x_i \cdot (dF/dx_i)$$

The Test Set to Detect $x_i/1$ corresponds to :

$$T_1 = \bar{x}_i \cdot (dF/dx_i)$$

Notes:

- The x_i 's are Primary Inputs
- A Fault on some PI (x_i) is Undetectable iff

$$F_i(1) = F_i(0)$$

OR

$$dF/dx_i = 0$$


Which Means that **F is INDEPENDENT OF x_i**

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 8

Example

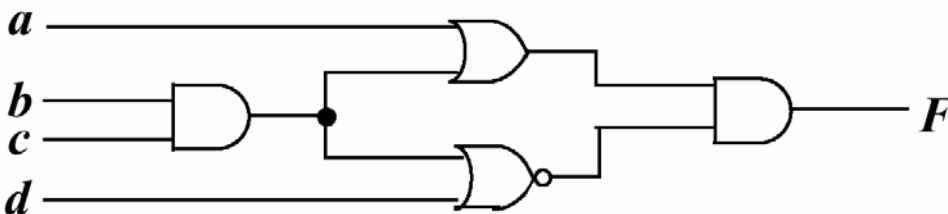

- Fault = $a/1$
- Fault-Free Fun= $F(a,b,c,d) = (a + bc)(b' + c')d'$
- $T(a/1) = a' \cdot dF/da$
- $dF/da = [1(b' + c')d' \oplus bc(b' + c')d'] = b'd' + c'd'$
- So $T(a/1) = a'b'd' + a'c'd'$
- Test set for $a/1 = \{00x0, 0x00\} = \{0000, 0010, 0100\}$

Boolean Difference Method

- Boolean Difference (BD) has the following Properties:

$$1. \frac{d\bar{F}}{dx_i} = \frac{dF}{dx_i}$$


$$2. \frac{d}{dx_i} \left[\frac{dF}{dx_j} \right] = \frac{d}{dx_j} \left[\frac{dF}{dx_i} \right]$$

$$3. \frac{d[F(X) \oplus G(X)]}{dx_i} = \frac{dF}{dx_i} \oplus \frac{dG}{dx_i}$$

$$4. \frac{d[F(X).G(X)]}{dx_i} = F.\frac{dG(X)}{dx_i} \oplus G.\frac{dF(X)}{dx_i} \oplus \frac{dF(X)}{dx_i}.\frac{dG(X)}{dx_i}$$

$$5. \frac{d[F(X) + G(X)]}{dx_i} = \bar{F}.\frac{dG}{dx_i} \oplus \bar{G}.\frac{dF}{dx_i} \oplus (\frac{dF}{dx_i}).(\frac{dG}{dx_i})$$

Example

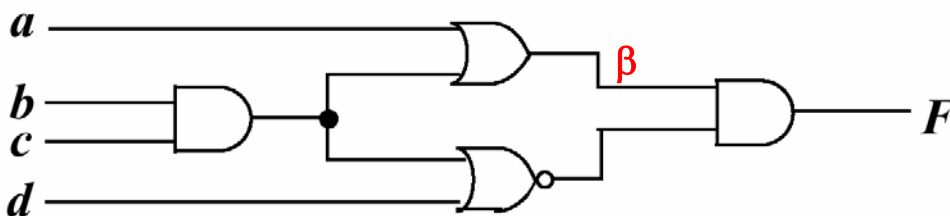

- Fault = $\beta/0$
- $T(\beta/0) = \beta(X).\frac{dF(x, \beta)}{d\beta}$
 - $\beta(X) = a + bc$ $F(x, \beta) = (b' + c')d' \beta$
- $\frac{dF}{d\beta} = (b' + c')d'$
- So $T(\beta/0) = ab'd' + ac'd'$
- Test set for $\beta/0 = \{1000, 1010, 1100\}$

Test Generation Schemes

- BD method is more Theoretical → Too Complex to Use for Practical Circuits
- Need a More Practical Approach
- **Deterministic Test Generation**
 - Fault- Oriented ATG
 - Fault Independent ATG
- **Random Test Generation**
 - Combined Deterministic and Random Test Generation
- **ATG Systems**
- **Conclusions**

Classification & Problems


Testing

- Off- Line
- Edge- Pin
- Stored- Pattern
- Full Comparison of the Output Results

General Problems for TG:


- Cost of Generating the Test
- Quality of the Generated Test
- Cost of Applying the Test

Deterministic Test Generation

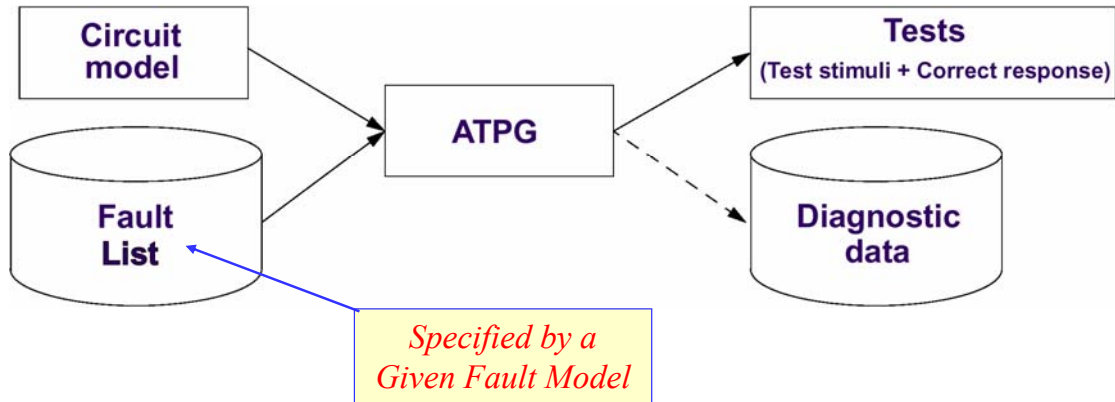

- **Manual / Automatic**
 - **Automatic Test Pattern Generation (ATPG)**
- **Deterministic ATPG Can Be Fault- Oriented / Fault-Independent**

Fault-Oriented ATPG

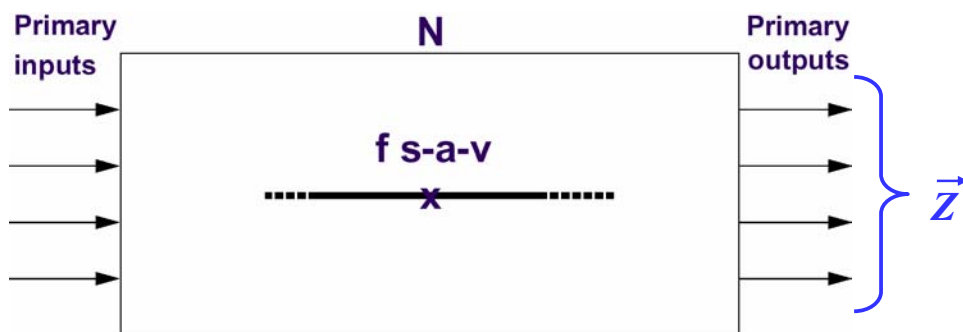

- Targets a Particular Fault $f \in \{ \text{Fault List} \}$
 - Finds a TV t which Detects f
 - ❑ t Detects $f \iff Z(t) \neq Z_f(t) \iff Z(t) \oplus Z_f(t) = 1$

TV Generation

- **Two** Steps Are Necessary to Generate TV t which Detects Fault f :
 - Fault Activation/excitation/provoking: Effecting a Different Value \bar{v} at the Faulty Line x When x Is Stuck at v .
 - Fault Propagation: Propagating Error to an Observable PO


Definitions

- A **Line** whose Value under TV t Changes in the Presence of Fault f is Said to Be Sensitized to the Fault f by the Test t
- A Path Composed of Sensitized Lines Is Called a Sensitized Path

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Single Path Sensitization

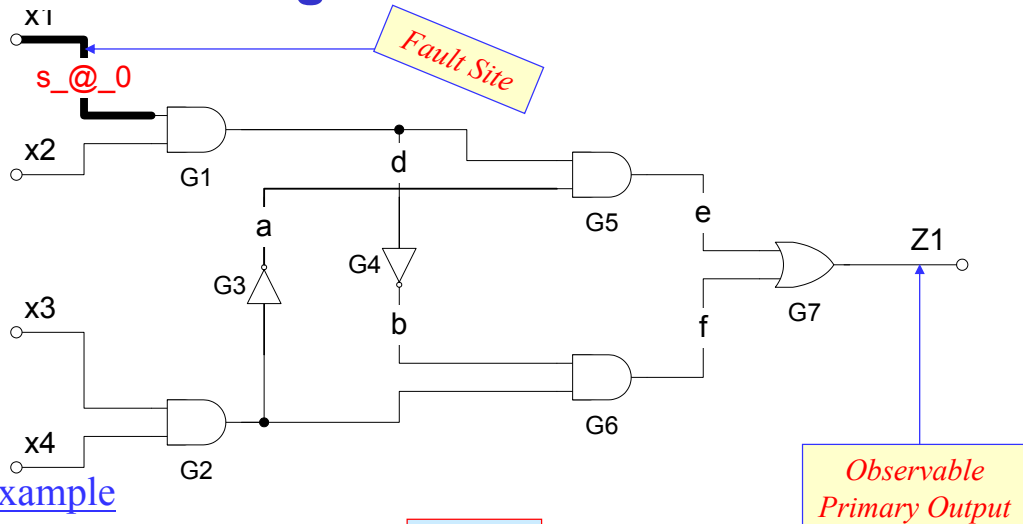

Example


1. Fault Activation \rightarrow **X1=1**
2. Fault Propagation \rightarrow 2 Possible Options (Paths)
 - Option 1: $G_1 - G_5 - G_7$
 - Option 2: $G_1 - G_4 - G_6 - G_7$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 17


Single Path Sensitization *Option 1*

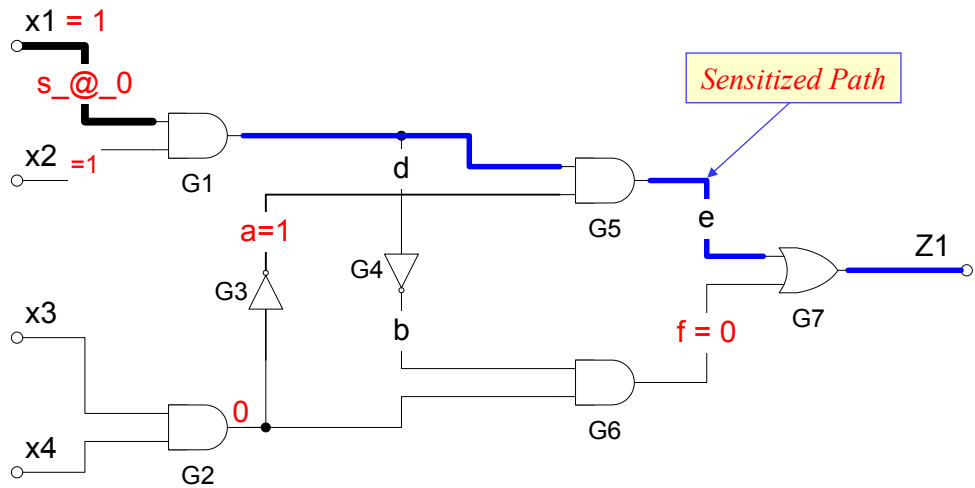

Example

1. Fault Activation $\rightarrow X1=1$
2. Fault Propagation : $G1 - G5 - G7 \rightarrow$ *Two Possible TVs*
 - $T1 = 110X, 1$
 - $T2 = 11X0, 1$

Single Path Sensitization *Option 2*

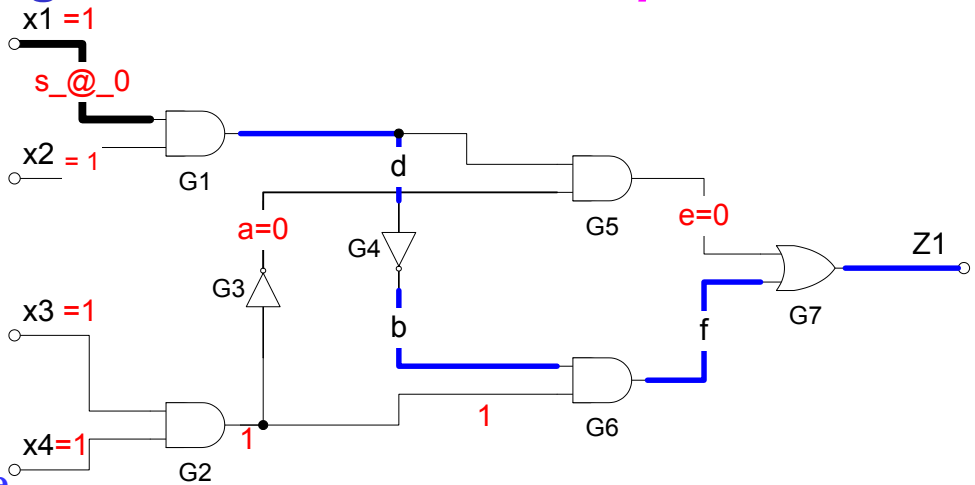


Example

1. Fault Activation $\rightarrow X1=1$
2. Fault Propagation : $G1 - G4 - G6 - G7$
 \rightarrow *One Possible TV* $\rightarrow T = 1111, 0$

Multiple Path Sensitization

Major *Problem* with Single Path Sensitization

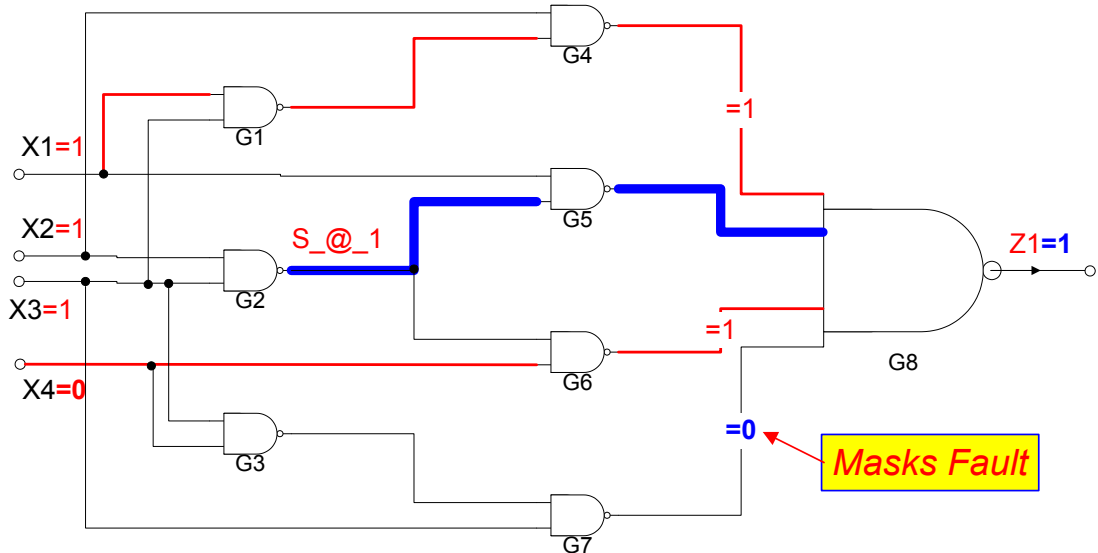- A TV May not be Possible to Generate for Some *Testable* Faults if Only One Path is Sensitized at a Time




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 20

Multiple Path Sensitization

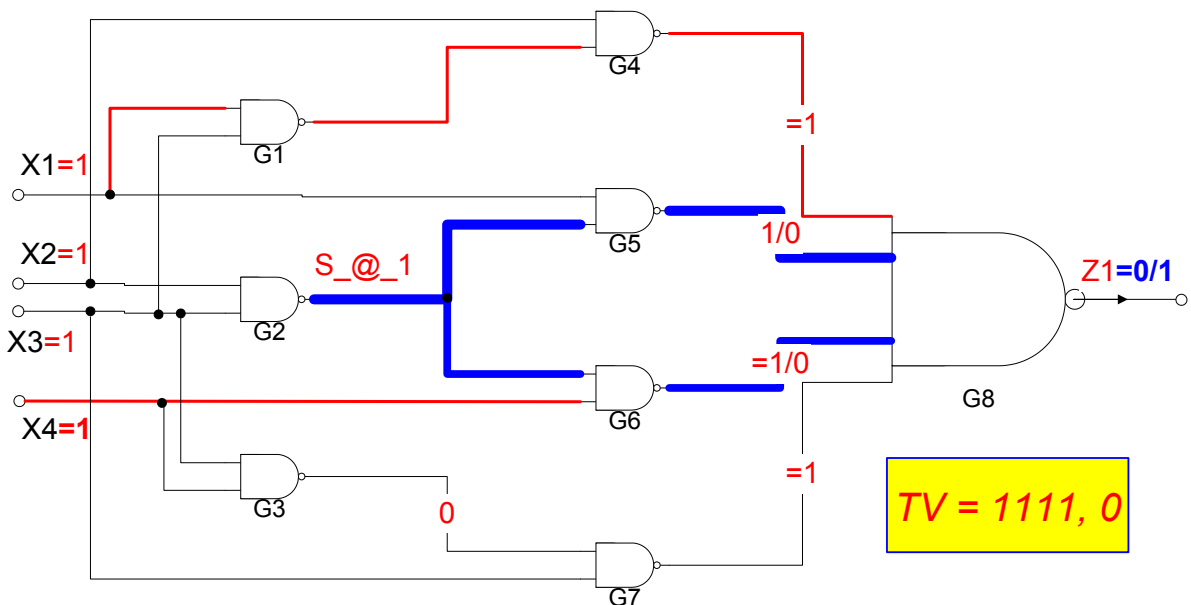

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 21

The D-Algorithm

- An Algorithmic Approach which Generates a TV for a Given Fault if One Exists
- Multiple Path Sensitization
- 5-Valued Logic $\{0, 1, X, D, \bar{D}\}$
- **D**: A Line is Assigned a **D** value if it has a value **1** in the **Fault-Free** Circuit but has a **0** Value in the **Faulty** Circuit.
($D \approx S_@_0$)
- \bar{D} : A Line is Assigned a \bar{D} value if it has a value **0** in the **Fault-Free** Circuit but has a **1** Value in the **Faulty** Circuit.
($\bar{D} \approx S_@_1$)
- D / \bar{D} Follow Rules of Boolean Algebra


The D-Algorithm

$D + D = D$	$\bar{D} + \bar{D} = \bar{D}$
$D \cdot D = D$	$\bar{D} \cdot \bar{D} = \bar{D}$
$\bar{D} + D = 1$	$D \cdot \bar{D} = 0$
$D \cdot 1 = D$	$\bar{D} \cdot 1 = \bar{D}$
$D \cdot 0 = 0$	$\bar{D} \cdot 0 = 0$
$D + 1 = 1$	$\bar{D} + 1 = 1$
$D + 0 = D$	$\bar{D} + 0 = \bar{D}$


•	0	1	D	\bar{D}	x
0	0	0	0	0	0
1	0	1	D	\bar{D}	x
D	0	D	D	0	x
\bar{D}	0	\bar{D}	0	\bar{D}	x
x	0	X	x	x	x

AND Operation of the 5-Valued D-Calculus

Example - Single Path Sensitization

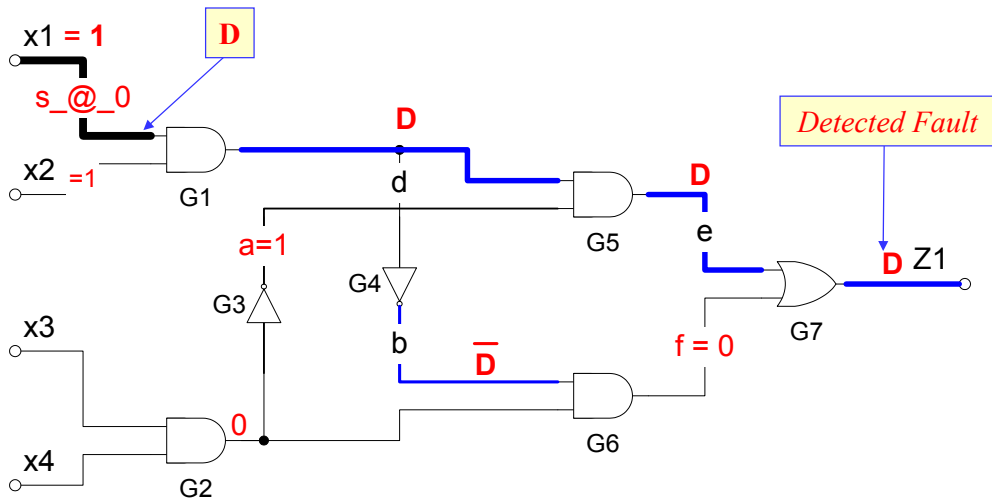

Example - Multiple Path Sensitization

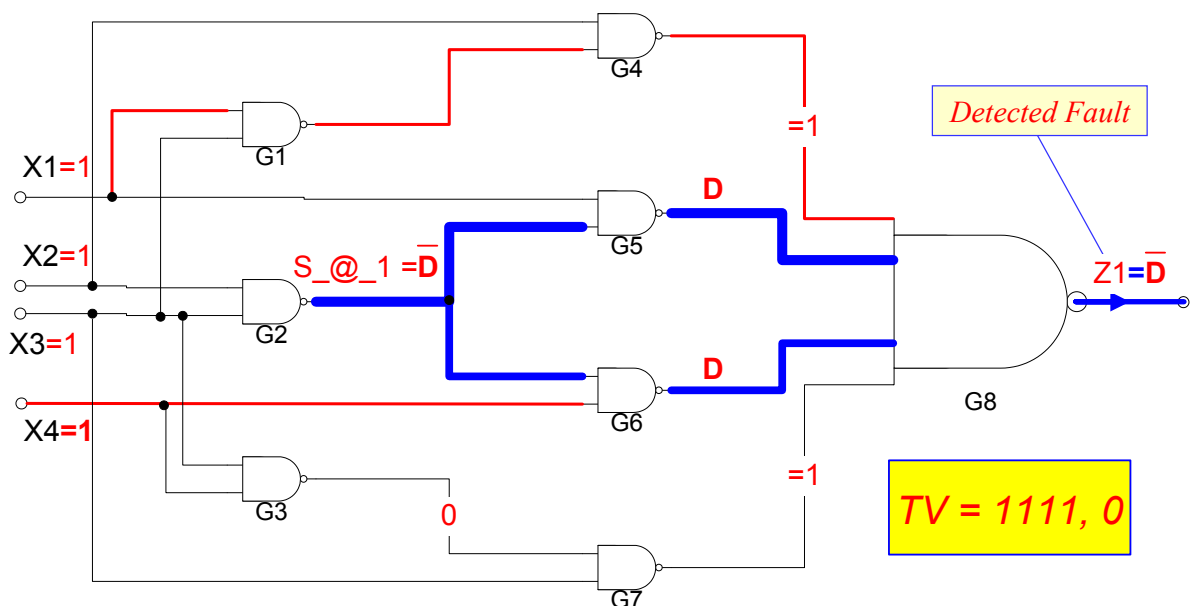

Definitions

1. Singular Covers (SC) of Some Function F

(Primitive Cubes of F) : Minimal Set of Logic Signal Assignments Showing Essential Prime Implicants

= Prime Implicants of \underline{F} ($\alpha 1$) &&
Prime Implicants of \overline{F} ($\alpha 0$)

Examples Singular Covers of 2-Input NAND Gate

A	B	F
0	X	1
X	0	1
1	1	0

Pis of \overline{F}
($\alpha 0$)

Pis of F
($\alpha 1$)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 26

Definitions-- Singular Covers (SC)

(Primitive Cubes)

Example

A	B	C	F
X	X	1	1
0	0	X	1
X	1	0	0
1	X	0	0

Pis of F
($\alpha 1$)

Pis of \overline{F}
($\alpha 0$)

SCs of F

		BC			
		00	01	11	10
A	0	1	1	1	
A	1		1	1	

K-Map of F


Definitions

2. Primitive D-Cubes of a Fault (PDCF)

= Prime Implicants of the *Faulty* Function which Produce D / \bar{D} Output

{I/P. Stimuli Required to Activate Faulty Condition at a Gate/Module Output}

Examples PDCF of 2-Input NAND Gate

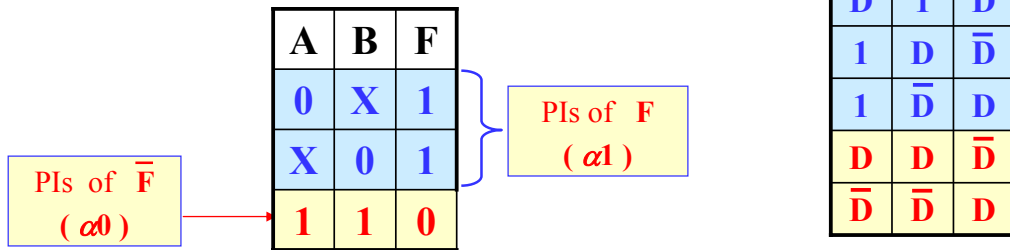

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 28

Definitions -- Primitive D-Cubes of a Fault (PDCF)

Computing PDCF of a General Module (Function)

1. Obtain the SCs of the Fault-Free Function ($\alpha 1, \alpha 0$)
2. Obtain the SCs of the Faulty Function ($\beta 1, \beta 0$)
3. PDCF for this module Result from Intersecting $\alpha 1$ with $\beta 0$ and $\alpha 0$ with $\beta 1$.

Thus

$$\text{PDCF} = \{ \alpha 1 \cap \beta 0, \alpha 0 \cap \beta 1 \}$$

Definitions-- -- Primitive D-Cubes of a Fault (PDCF) -- Example

Example

A	B	C	F
X	X	1	1
0	0	X	1
X	1	0	0
1	X	0	0

PIs of F
($\alpha 1$)

PIs of \bar{F}
($\alpha 0$)

A	B	C	F
X	X	1	1
0	1	X	1
X	0	0	0
1	X	0	0

PIs of F
($\beta 1$)

PIs of \bar{F}
($\beta 0$)

PDCF

A	B	C	F
0	0	0	D
0	1	0	D

$\alpha 0 \cap \beta 1$

$\alpha 1 \cap \beta 0$

Definitions

3. Propagation D-Cube of a Gate/Module (PDC)


= Prime Implicants of the Function which Allow a D/\bar{D} Values on Inputs to Propagate to the Output

- Let $\{ \alpha 0, \alpha 1 \}$ be the Singular Covers of the Function F , Where;
 - $\alpha 1$ = Be the Prime Implicants of F
 - $\alpha 0$ = Be the Prime Implicants of \bar{F}

$$PDC = \{ \alpha 1 \cap \alpha 0 \}$$

Definitions-- Propagation D-Cube (PDC)

Example PDCF of 2-Input NAND Gate

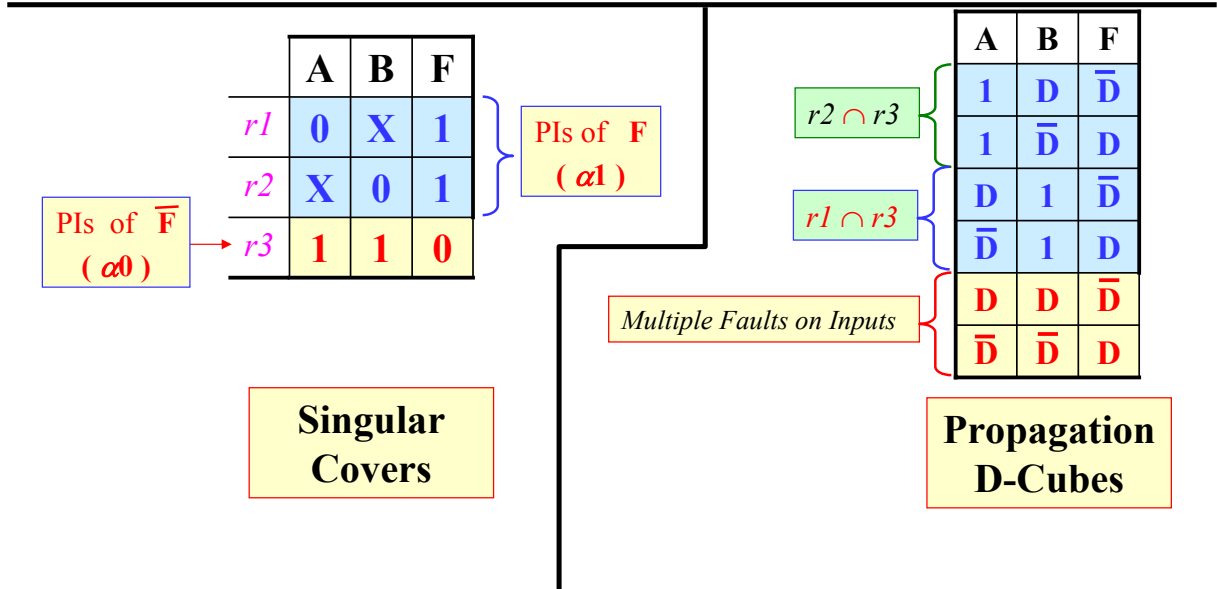

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 32

Intersection of D-Cubes

- Let $A = (a_1, a_2, a_3, \dots, a_n)$, and
 - Let $B = (b_1, b_2, b_3, \dots, b_n)$ be 2 D-Cubes, where
- $$a_i, b_i \in \{0, 1, x, D, \bar{D}\}$$
- The D -intersection:** of A and B , denoted $A \cap B$ is given by $\{a_i \cap b_i \mid a_i \in A, b_i \in B\}$, where :

1. $x \cap a_i = a_i$

2. If $(a_i \neq x$ and $b_i \neq x)$ Then

$$a_i \cap b_i = \begin{cases} a_i & \text{IF } a_i = b_i \\ \Phi & \text{IF } a_i \neq b_i \end{cases}$$

3. $A \cap B = \Phi$ “Empty Cube” IF $a_i \cap b_i = \Phi$ For Any i

COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 33

D- Intersection

- D-Intersection is Used to Generate Sensitized Paths (**D-Drive**)

Example PDC of 2-Input NAND Gate →

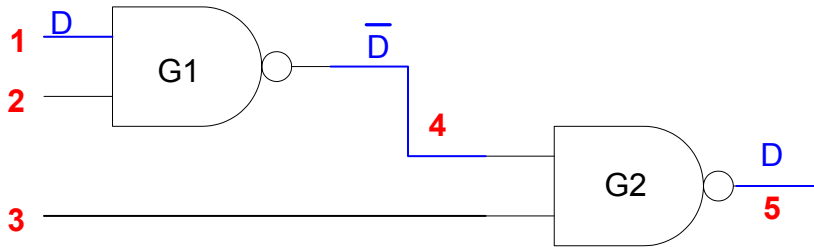

A	B	F
1	D	D-bar
1	D-bar	D
D	1	D-bar
D-bar	1	D
D	D	D-bar
D-bar	D-bar	D

$$\begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline D & 1 & x & \bar{D} & x \\ \hline \end{array} \cap \begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline x & x & 1 & \bar{D} & D \\ \hline \end{array} = \begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline D & 1 & 1 & \bar{D} & D \\ \hline \end{array}$$


D- Algorithm

- Initialize Test Cube to all x 's ($x, x, x, \dots x$)
- Fault Provoking → Select a Primitive D-Cube of the Fault (PDCF) → Usually a *Choice Step*
- Path Sensitization From the Faulty Line To a PO
 - Successive X-ion of Test Cube with the Propagation D-Cubes of Successor Gates (*D-Frontier*) Till a PO Gets a **D** / **D-bar** Value (*Choice Step*) → This Step is known as *D-Drive*
 - This Step Requires 2 Major Procedures
 - Implication (Forward and Backward), and
 - Line Justification (*Consistency Checks*) → May Lead to *Backtracks* if Inconsistencies are Detected.

Implication

- Assignments Made Due to Choices, e.g.a Propagation D-Cube, Usually Uniquely Imply Other Signal Values {Forward & Backward}

Example

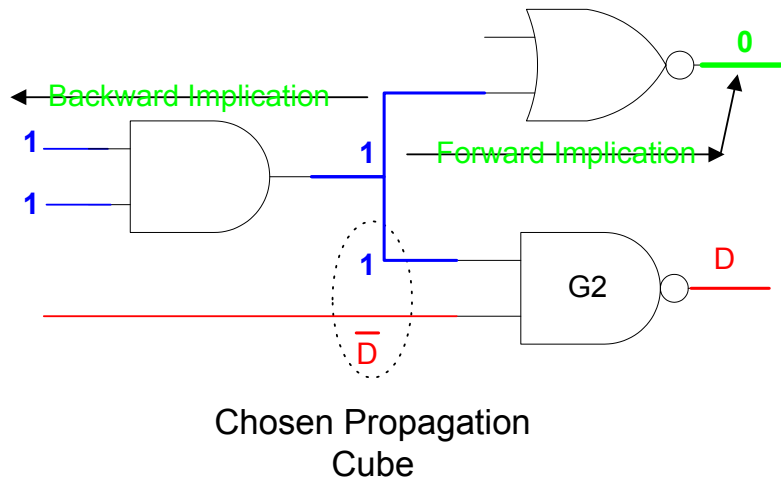

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 36

D-Frontier

- The **D-Frontier** Consists of **ALL** Gates whose Current O/P Value is “**x**” but have one or more **D/D̄** on their inputs
- One of the **D-Frontier** Gates is Usually Chosen to Propagate The Fault → “**D-Drive**”

Line Justification

Is a Backward *Implication Step* Where The Gate I/P Values are Selected *To Justify* the Specified Gate Output. This Step is Repeated Till the Relevant **PIs** are Defined.

- *Line Justification* is Performed after **D/D̄** Appear at Some **PO**.

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)


Slide Number 37

Line Justification-Example

- An Unjustified Line is a Defined Gate Output which is not Implied By The Gate Inputs

J-Frontier

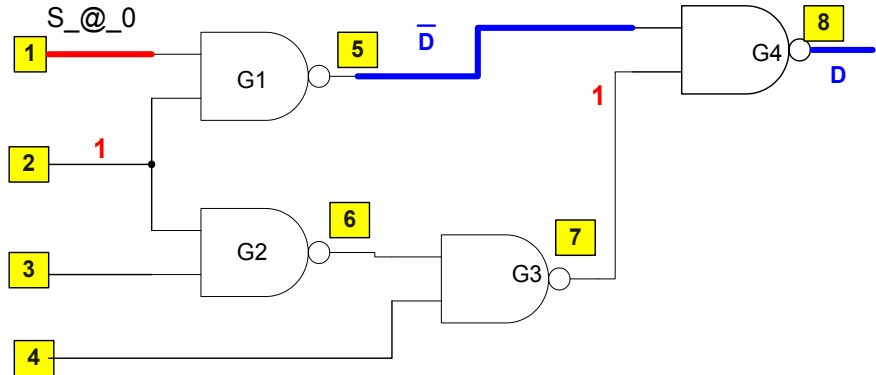Is the Set of ALL Gates whose Output Lines are Unjustified



COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 38

Line Justification

Example (Line Justification) → Line 1 S_@_0

$t^0 = \text{PDFC}^1$

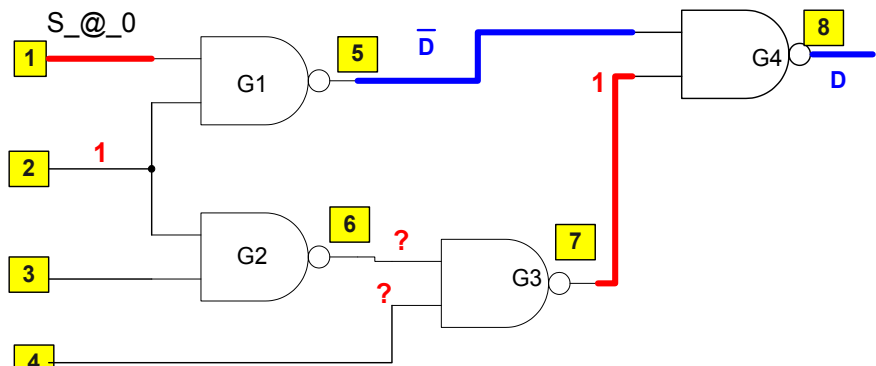

1	2	3	4	5	6	7	8
D	1			\bar{D}			
D	1			\bar{D}		1	D

D-Drive

J-Frontier = {G3} “Line 7 Unjustified”

Either Line 4 = 0, OR

Line 6=0

1	2	3	4	5	6	7	8
D	1	x	x	\bar{D}	0	1	D
D	1	1	x	\bar{D}	0	1	D

$t^2 = t^1 \cap Sc^3$

J_F={G₂}

$t^3 = t^2 \cap Sc^2$

J_F={Φ}

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 39

NOTES on D-ALGORITHM

1. Exhaustive Search of All Possible Choices
2. Guaranteed to Find a Solution (TV) *IF One Exists*.
3. Stops As Soon As A Solution Is Found
4. Being Exhaustive, the Worst Case Complexity is Exponential in the # of Gates
5. The Best Case Behavior Occurs When a Solution IS Generated ***WITHOUT ANY BACKTRACKING***:
 - Always Correct Decisions Are Made
 - Solution Is Obtained Only Through Forward & Backward Implication.

NOTES on D-ALGORITHM

6. THUS, the # of Backtracks Determines the Complexity of the Algorithm (Should be Minimized).
7. An Upper Limit is Placed on the # of Backtracks Beyond Which a Fault Is Declared *UNTESTABLE!*
8. To Minimize the # of Backtracks, It is Advisable to Discover Inconsistencies as Early as Possible Through *Forward & Backward Implications for Each Change in the Test Cube*

OutLine of D-Algorithm

1. Model Fault with appropriate *Primitive D-cube of Fault* (PDF)
2. Select *Propagation D-cubes* to Propagate fault effect to a circuit output (*D-drive* procedure)
3. Select *singular cover* cubes to justify internal circuit signals (*Line Justification / Consistency* procedure)
 - Put Signal Assignments in *Test Cube*
 - Regrettably, Cubes Are Selected Very *Arbitrarily* by D-ALG