

## DIGITAL SYSTEM TESTING COE -545

### Lecture – 08

### Testability Measures

### Objective

- Regrettably, Decisions in the D-ALG are *Arbitrary*
- **PODEM** Uses the Testability of Nodes to help Choose among alternative Choices.
- *Derive* an *Approximate Measure* Of How Easy/Hard it is to Test a Given CUT
- **Usage:**
  - Analyze the Difficulty of Testing a given CUT → *Redesign or Add Special Test Hardware*
  - Guidance for Algorithms Computing Test Patterns → *Make Better Informed Decisions in the D-Drive and Line-Justification Steps*
  - Estimation of Fault Coverage
  - Estimation of Test Vector Length

## Testability Measures

- Generally 2 Measures are Used:
  1. Controllability (CY), and
  2. Observability (OY),
- No Agreed-Upon Standard for measuring CY or OY {SCOAP, CAMELOT, VICTOR, etc.}

### Controllability (CY):

*Defined for Both Logic 1 & 0; as a measure for the Ability to Control the State of a Given Line (node) from PIs → Thus, Every Line Has a 1-Controllability and a 0-Controllability*

### Observability (OY):

*A measure of the Ease/Difficulty with which the State of a given Line can be Observed at one or more PO*

- CY & OY May be Normalized Between 0 & 1.

## Testability Analysis

- Involves Circuit *Topological analysis*, but no test vectors and *no search* algorithm
  - *Static analysis*
- **Linear** computational complexity
  - Otherwise, is pointless – might as well use automatic test-pattern generation and calculate:
    - Exact fault coverage
    - Exact test vectors

## SCOAP – Sandia Controllability and Observability Analysis Program

- Computes Combinational & Sequential CY & OY
- Combinational measures:
  - *CC0* – Difficulty of setting circuit line to logic 0
  - *CC1* – Difficulty of setting circuit line to logic 1
  - *CO* – Difficulty of observing a circuit line
- Sequential measures – analogous:
  - *SC0*
  - *SC1*
  - *SO*

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 5

## Range of SCOAP Measures


- Each Line is Assigned Controllability & Observability *Numeric* Values
- **Controllability** – **1** (easiest to control) to **infinity** (**hardest**)
- **Observability** – **0** (easiest to observe) to **infinity** (**hardest**)
- Combinational measures:
  - Roughly Proportional to # Circuit Lines that must be Set to Control or Observe the Given Line
  - Line Controllabilities are Computed **Starting** at the **PIs** moving *Forward* to **POs**
  - Line Observabilities are Computed **Starting** at the **POs** moving *Backwards* to **PIs**
- Sequential measures:
  - Roughly proportional to # times a flip-flop must be clocked to control or observe given line

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 6

## Controllability Examples

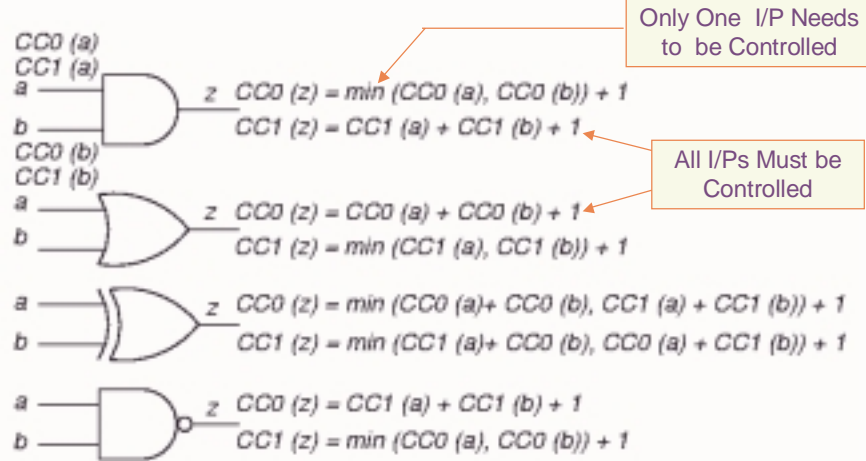


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 7

## Controllability Examples (Contd)

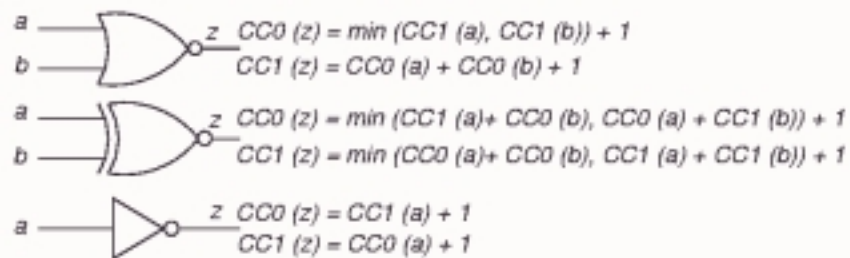

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 8

## Observability Examples

To observe a gate input: *Observe output and make other input values non-controlling*

$$CO(a) = CO(z) + CC1(b) + 1$$

$$CO(b) = CO(z) + CC1(a) + 1$$

$$CO(a) = CO(z) + CC0(b) + 1$$


$$CO(b) = CO(z) + CC0(a) + 1$$

$$CO(a) = CO(z) + \min(CC0(b), CC1(b)) + 1$$

$$CO(b) = CO(z) + \min(CC0(a), CC1(a)) + 1$$

$$CO(a) = CO(z) + CC1(b) + 1$$

$$CO(b) = CO(z) + CC1(a) + 1$$

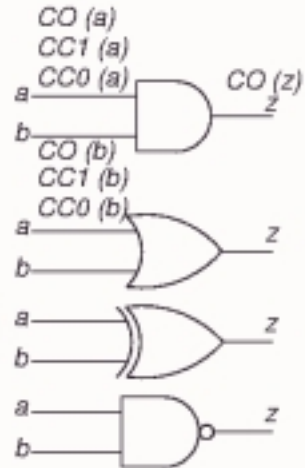

COE - KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 9

## More Observability Examples

To observe a *fanout stems*:

*Observe it through branch with best observability*

$$CO(a) = CO(z) + CC0(b) + 1$$


$$CO(b) = CO(z) + CC0(a) + 1$$

$$CO(a) = CO(z) + \min(CC0(b), CC1(b)) + 1$$

$$CO(b) = CO(z) + \min(CC0(a), CC1(a)) + 1$$

$$CO(a) = CO(z) + 1$$
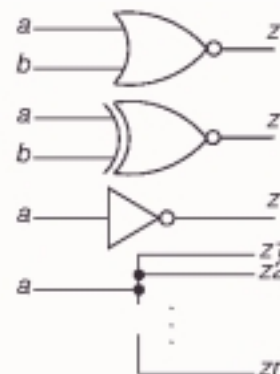
$$CO(a) = \min(CO(z1), CO(z2), \dots, CO(zn))$$



Min → Independent Branches  
Max → Dependent Branches

COE - KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 10

## Goldstein's SCOAP Measures

- **AND gate 0-Controllability:**  

$$\text{Output\_Controllability} = \text{Min} (\text{Input\_Controllability}) + 1$$
- **AND gate 1-Controllability:**  

$$\text{Output\_Controllability} = \Sigma (\text{Input\_Controllability}) + 1$$

---

- **XOR gate O/P Controllability**  

$$\text{Output\_Controllability} = \text{min} (\text{controllabilities of each input set}) + 1$$

---

- **Fanout Stem Observability:**  

$$\Sigma \text{ or min (some or all fanout branch observabilities)}$$


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 11
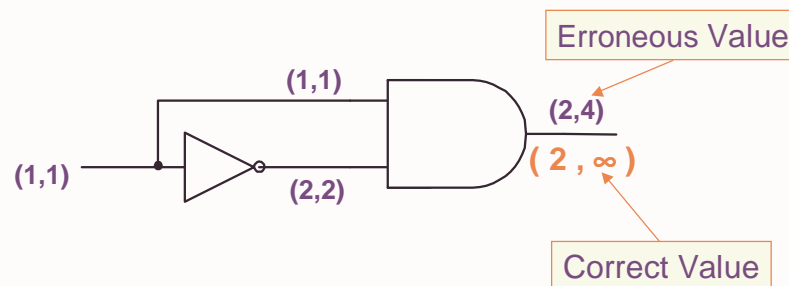
## Error Due to Stems & Reconverging Fanouts

SCOAP measures Incorrectly Computes Controllabilities  
 Assuming that Fanout Branches to Be Independent →  
 Untrue for Reconvergent Branches



COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 12
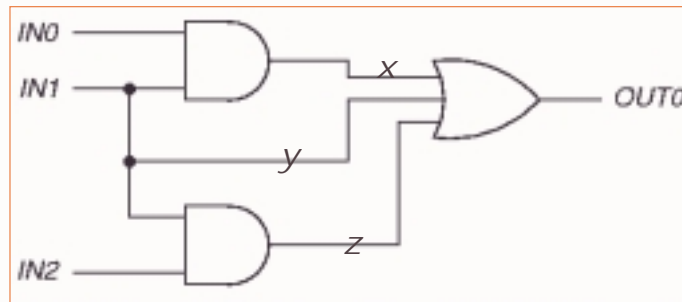
## Error Due to Stems & Reconverging Fanouts

SCOAP measures Incorrectly assume that controlling or observing  $x, y, z$  are *independent* events

- $CC0(x), CC0(y), CC0(z)$  correlate
- $CC1(x), CC1(y), CC1(z)$  correlate
- $CO(x), CO(y), CO(z)$  correlate




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 13
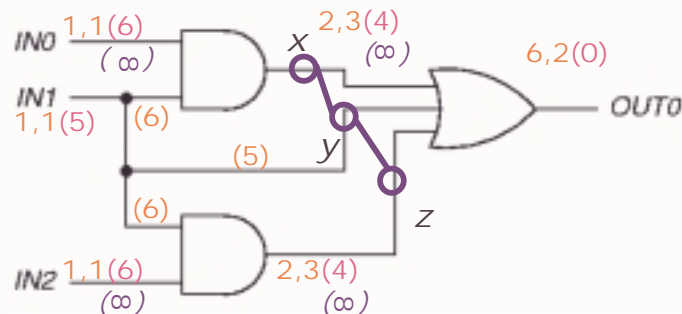
## Correlation Error Example

- **Exact** computation of measures is NP-Complete and impractical
- SCOAP measures are in red or bold  $CC0, CC1 (CO)$  -- Italicized (Blue) measures show correct values



COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 14
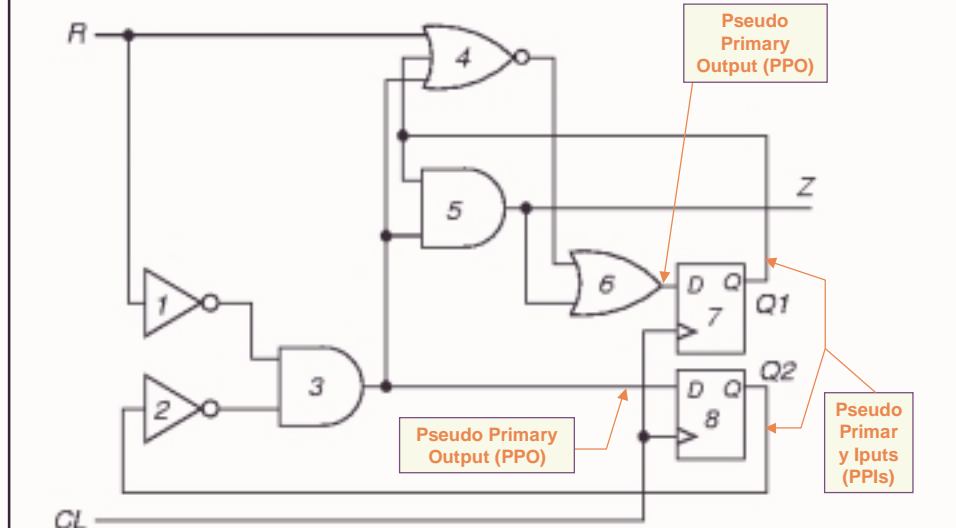
## Sequential Example

**Assumption:** Fully Controllable (Scannable) FFs→

- FF Inputs → Pseudo POs of Combinational Logic
- FF Outputs → Pseudo PIs for Combinational Logic



## Levelization Algorithm 6.1


- **Label** each gate with max # of logic levels from primary inputs or with max # of logic levels from primary output
- **Assign** level # 0 to all *primary inputs* (PIs)
- **For each PI fanout:**
  - Label that line with the PI level number, &
  - Queue logic gate driven by that fanout
- **While queue is not empty:**
  - Dequeue the next logic gate
  - **IF** all gate inputs have level #'s,
    - label the gate with the highest of them + 1;
    - Label O/P Line & its Fanout Lines with the same level number, &
    - Queue logic gates driven by the fanout lines
  - **Else**, requeue the gate

number 16


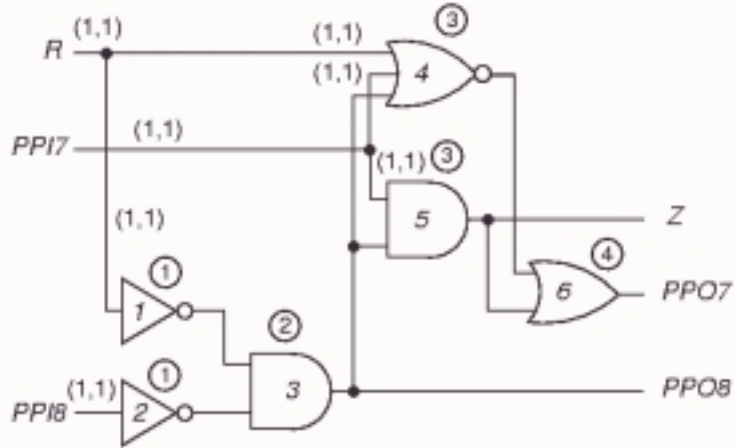
## Controllability Through Level 0

Circled numbers → level number.  
Parenthesized Numbers → (CC0, CC1)




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 17

## Controllability Through Level 2

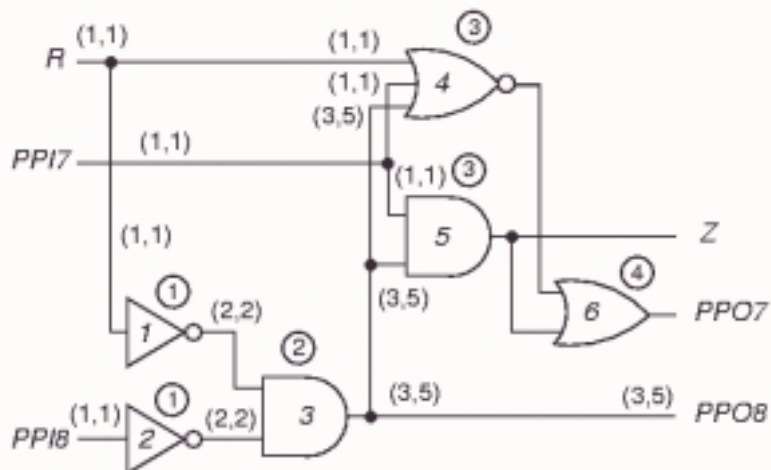


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 18

### Final Combinational Controllability

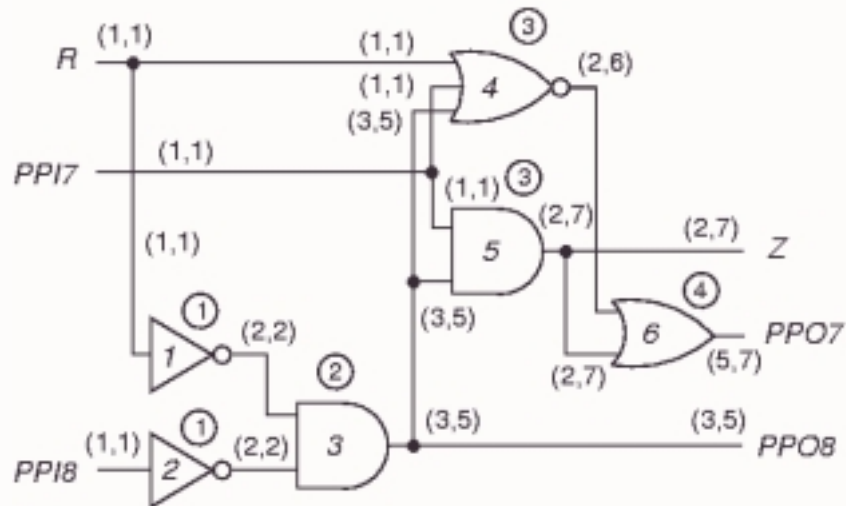


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 19
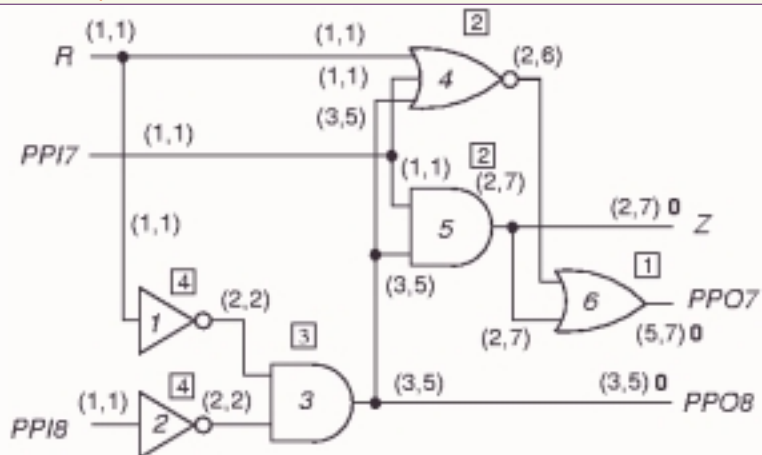
### Combinational Observability for Level 1

Number in square box → level from *primary outputs* (POs).  
(CC0, CC1) CO




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 20
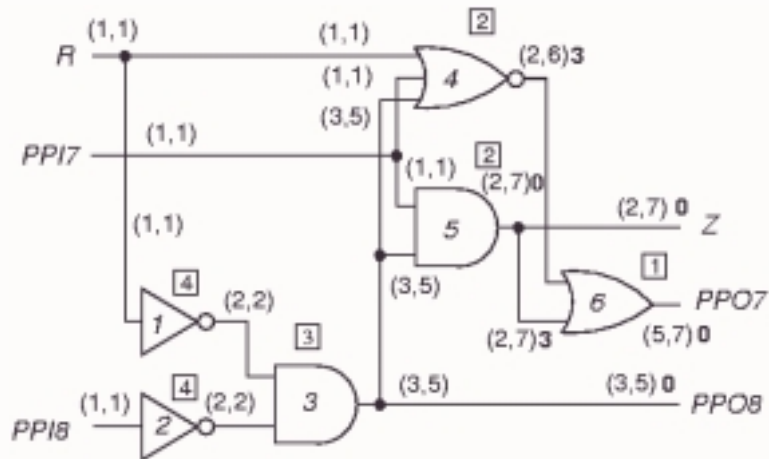
## Combinational Observabilities for Level 2




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 21

## Final Combinational Observabilities

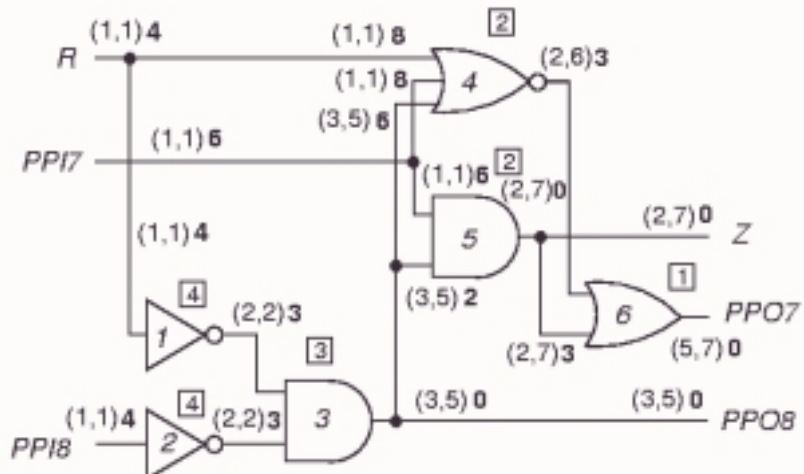

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 22

## Sequential Measure Differences

- **Combinational**
  - **Increment**  $CC0$ ,  $CC1$ ,  $CO$  when **passing through a Gate**, either forwards (Controllability) or backwards (Observability)
  - $CCi$ ,  $CO$  *are not incremented when passing through FFs*, ( $CC0(Q)$ ,  $CC1(Q)$ ,  $CO(D)$ ) either forwards or backwards
- **Sequential**
  - **Increment**  $SCi$ ,  $SO$  only when **Passing through a FF**, either forwards or backwards, to  $Q$ ,  $\bar{Q}$ ,  $D$ ,  $C$ ,  $SET$ , or  $RESET$
  - $SCi$  &  $SO$  *are not incremented when passing through Combinational Gates*, either forwards or backwards.
- **Both**
  - Must iterate on feedback loops until controllabilities stabilize


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 23
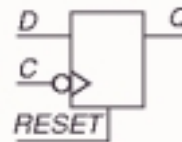
## D Flip-Flop Equations

- **Assume a Synchronous RESET line.**
- $CC1(Q) = CC1(D) + CC1(C) + CC0(C) + CC0(RESET)$
- $SC1(Q) = SC1(D) + SC1(C) + SC0(C) + SC0(RESET) + 1$
- $CC0(Q) = \min \{ CC1(RESET) + CC1(C) + CC0(C), CC0(D) + CC1(C) + CC0(C) \}$
- $SC0(Q) = \min \{ SC1(RESET) + SC1(C) + SC0(C), SC0(D) + SC1(C) + SC0(C) \} + 1$
- $CO(D) = CO(Q) + CC1(C) + CC0(C) + CC0(RESET)$
- $SO(D) = SO(Q) + SC1(C) + SC0(C) + SC0(RESET) + 1$



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

..... Number 24

## D Flip-Flop Clock and Reset

- $CO(RESET) = CO(Q) + CCI(Q) + CCI(RESET) + CCI(C) + CC0(C)$
- $SO(RESET) = SO(Q) + SCI(Q) + SCI(RESET) + SCI(C) + SC0(C) + 1$
- **Three ways to observe the clock line:**
  1. Set  $Q$  to 1 and clock in a 0 from  $D$
  2. Set the flip-flop and then reset it
  3. Reset the flip-flop and clock in a 1 from  $D$
- $CO(C) = \min \{ CO(Q) + CCI(Q) + CC0(D) + CCI(C) + CC0(C), CO(Q) + CCI(Q) + CCI(RESET) + CCI(C) + CC0(C), CO(Q) + CC0(Q) + CC0(RESET) + CCI(D) + CCI(C) + CC0(C) \}$
- $SO(C) = \text{Similar to } CO(C) + 1$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 25

## Algorithm: Testability Computation


1. For all **PIs**,  $CC0 = CCI = 1$  and  $SC0 = SCI = 0$
2. Initialize all other nodes,  $CC0 = CCI = SC0 = SCI = \infty$
3. Go from **PIs** to **POs**, using  $CC$  and  $SC$  equations to get controllabilities -- *Iterate* on loops *until SC stabilizes* → Convergence Guaranteed {Monotonically Decreasing Values, (initially  $\infty$ )} → 2-3 Iterations are Typical.
4. For all **POs**, set  $CO = SO = 0$ , For **Other Nodes**  $CO=SO=\infty$
5. Work from **POs** to **PIs**, Use  $CO$ ,  $SO$ , and *Precomputed controllabilities* to map O/P Node Observabilities of Gates & FFS into I/P observabilities
6. Fanout stem  $(CO, SO) = \min \{ \text{branch } (CO, SO) \}$
7. If a  $CC$  or  $SC$  ( $CO$  or  $SO$ ) is  $\infty$ , that node is uncontrollable or unobservable.

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 26

### Sequential Example Initialization

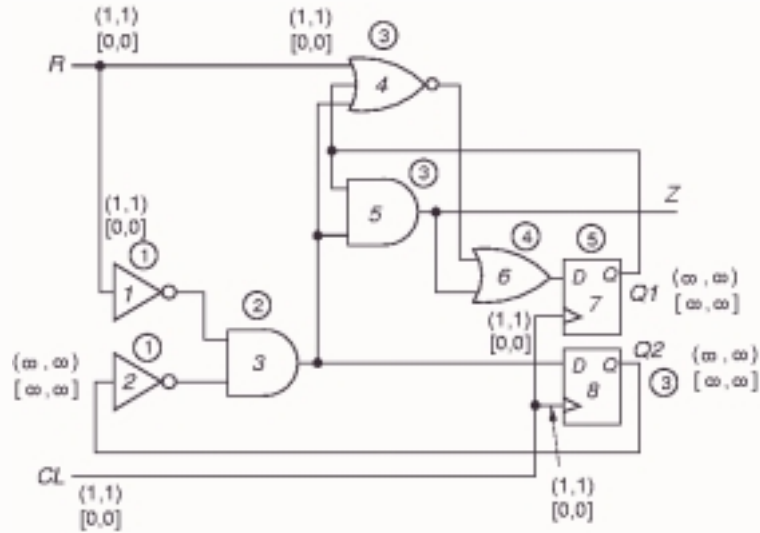


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 27



### After 1 Iteration

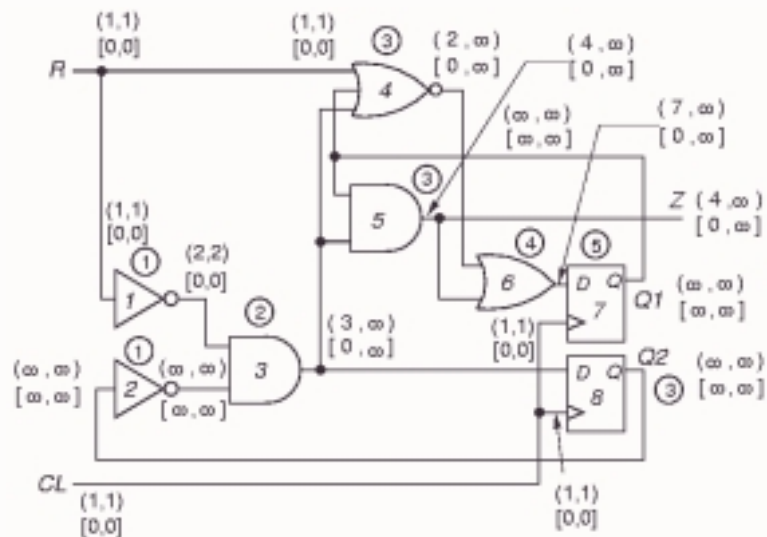


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 28

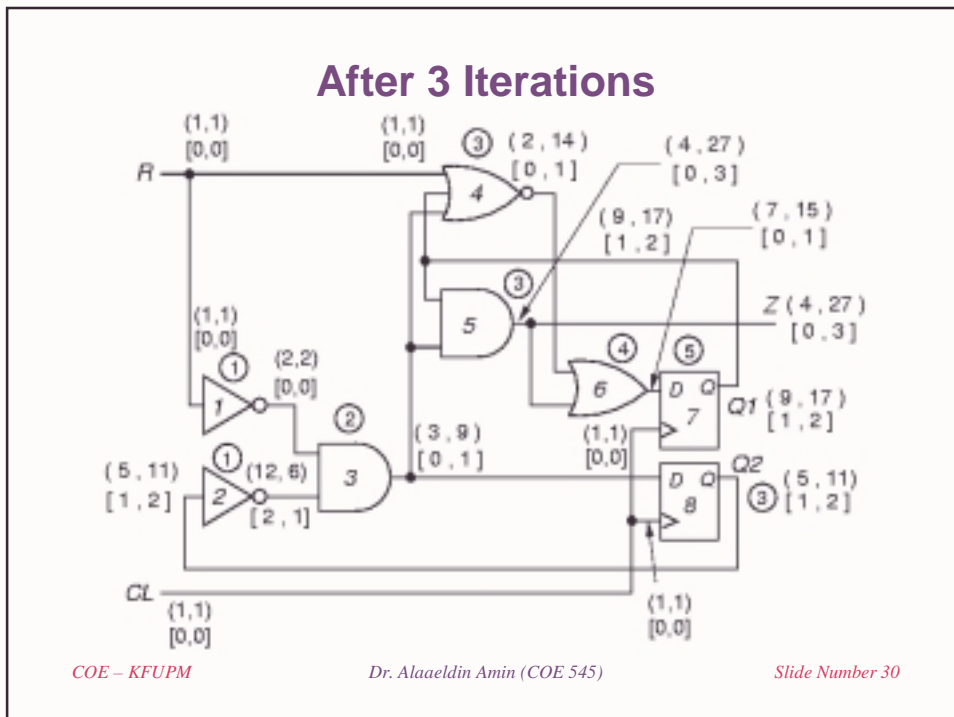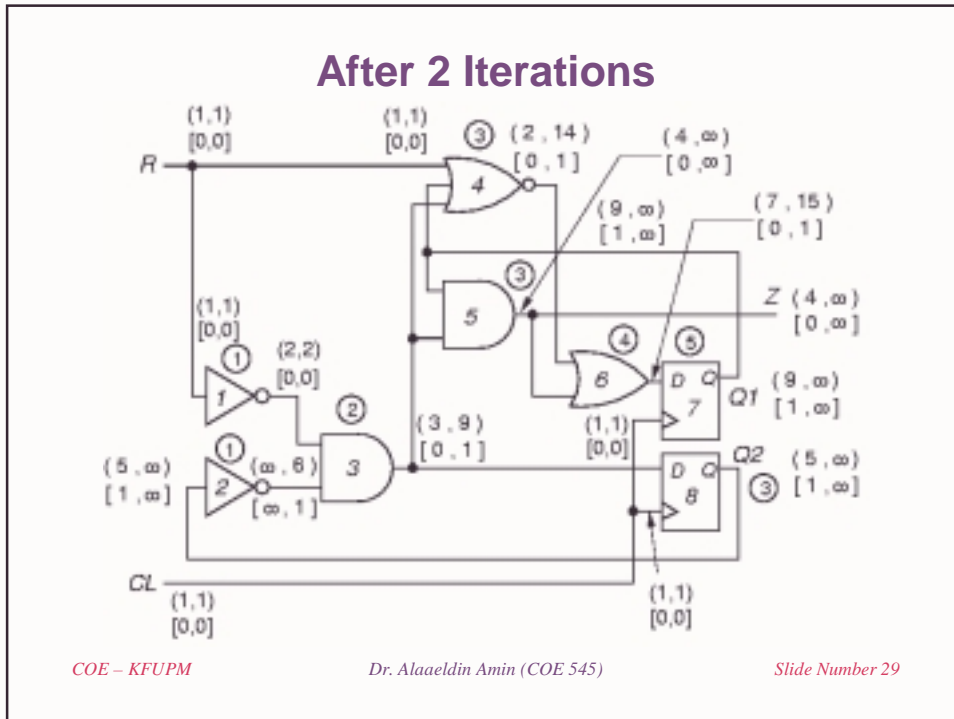

### Stable Sequential Measures

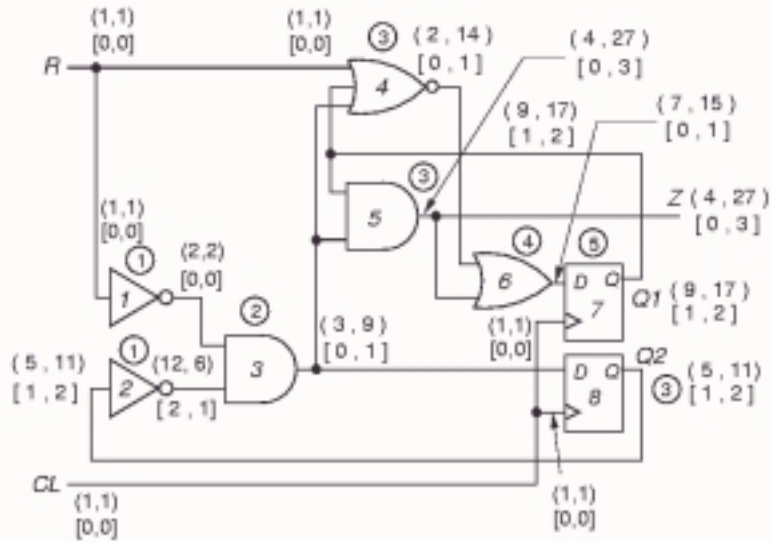


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 31

### Final Sequential Observabilities

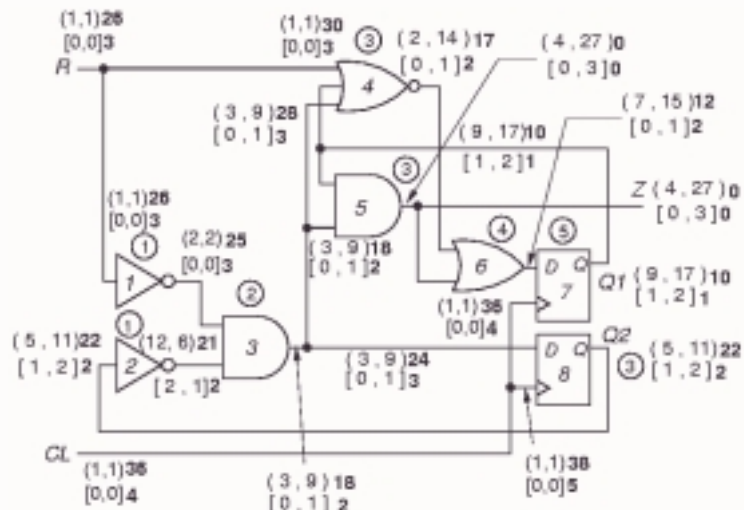

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 32



## Test Vector Length Prediction


- **Testability for node  $x$  stuck-at faults**
  - $T(x_{sa_0}) = CCI(x) + CO(x)$
  - $T(x_{sa_1}) = CC0(x) + CO(x)$
- **Compute testabilities for all stuck-at faults  $T(f_i)$**
- **Define the Testability Index of a Circuit as Follows**
  - $Testability\ index = \text{Log} \sum_{\forall f_i} T(f_i)$
- **An Almost Linear Relation was found to Exist between The Testability Index of a Circuit and the Number of TVs for 90% Fault Coverage**

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 33
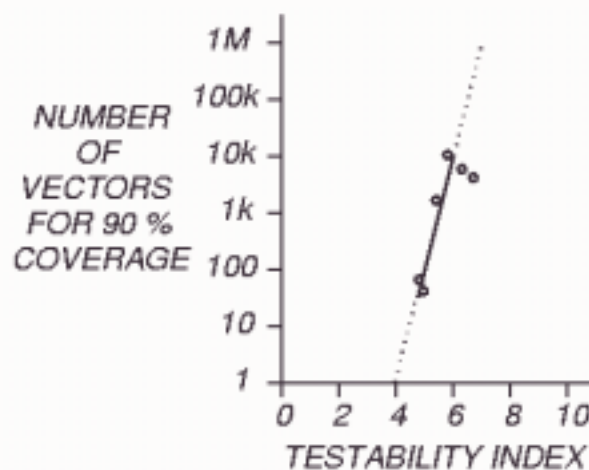
## Number Test Vectors vs. Testability Index



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 34

## High Level Testability


- Build *data path control graph (DPCG)* for circuit
- Compute *sequential depth* -- # arcs along path between PIs, registers, and POs
- Improve Register Transfer Level Testability with redesign

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 35

## Improved RTL Design

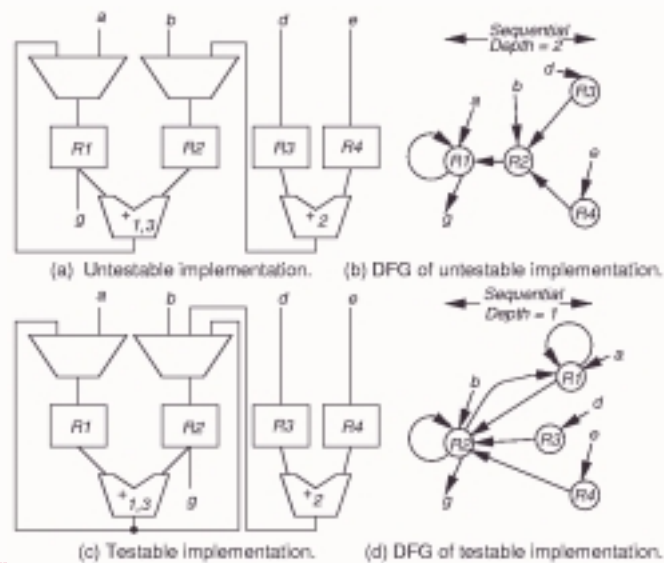

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 36

## Summary

- **Testability approximately measures:**
  - Difficulty of setting circuit lines to 0 or 1
  - Difficulty of observing internal circuit lines
- **Uses:**
  - Analysis of difficulty of testing internal circuit parts
    - Redesign circuit hardware or add special test hardware where measures show bad controllability or observability
  - Guidance for algorithms computing test patterns – avoid using hard-to-control lines
  - Estimation of fault coverage – 3-5 % error
  - Estimation of test vector length


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 37
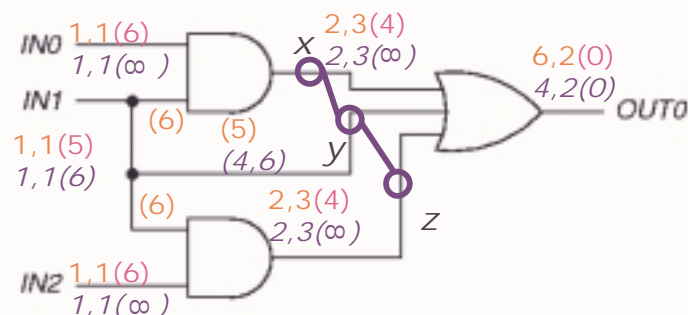
## Correlation Error Example

- **Exact** computation of measures is NP-Complete and impractical
- **SCOAP** measures are in red or bold **CC0,CC1 (CO)** -- **Italicized (Blue)** measures show correct values



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 38

## **Lecture 8 Testability Measures**

- **Controllability and observability**
- **SCOAP measures**
  - Sources of correlation error
  - Combinational circuit example
  - Sequential circuit example
- **Test vector length prediction**
- **High-Level testability measures**
- **Summary**