

Fault Models

- **Transistor Stuck ON (S_ON)**
 - Transistor Source-to-Drain Shorted independent of the state of the Gate Signal
 - Usually Fault is Considered as a Short Circuit ($R=0$), but more practically it has a finite resistance $R>0$
- **Transistor Stuck OPEN (S_OP)**
 - Transistor Always OFF independent of the state of the Gate Signal → Open Circuit between Source & Drain
 - Usually Considered an ideal Open Circuit ($R= \infty$), but more practically it has a finite LARGE resistance R

Advantages:

- More Accurate Fault Model Compared to the SSL FM
- Generated TVs, generally Cover Gate-Level SSL Faults

Disadvantages:

- More Complex Test Generation Algorithms
- SOP Faults Converts the Circuit into a Sequential one

COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 2

Stuck-ON (S_ON) Faults

 Example

- Consider **M2 S_ON**
- **Fault is Provoked (Activated) by Choosing a TV which Should Turn M2 OFF in the FF CUT → $x2=0$**
- **Fault is Propagated by Applying $x1=0$**
- **IF $x1 = 1$ Fault Effect is Masked**



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 3

Stuck-ON (S_ON) Faults

- Let R_p = ON-Resistance of the PMOS Tr.
- Let R_n = Fault Resistance of the NMOS Tr.
- Faulty O/P Voltage is Given By

$$V_F = \frac{R_n}{R_n + 2R_p} V_{DD}$$

- What is the Fault Effect ?
- How would A & B be Interpreted ? (Logic 0/1)

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 4

Stuck-ON (S_ON) Faults

- IF Voltage Levels are Used to Test for PO Validity, M2 S_ON Fault May, or May NOT be Detected Depending on the Relative Strength of the PMOS ON-Resistance and the NMOS S_ON Fault Resistance

$$V_F = \frac{1}{1 + 2\frac{R_p}{R_n}} V_{DD}$$

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 5


Stuck-ON (S_ON) Faults

Conclusion

- **S_ON Faults** May NOT be **Detectable** if Only the Node Logic Levels are Monitored

Solution

 - Instead of Monitoring Node Voltage Levels, the Static (DC) Current Can Be Monitored → **I_{DDQ} Tests**



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 6

I_{DDQ} Tests

- I_{DDQ} = Quiescent (DC/ Steady State /Static) Current Drawn From the V_{DD} Power Supply
- I_{DDQ} = Current Flowing in CMOS CKT when All Nodes are Quiescent (Static)
- $I_{DDQ} = 0$ (except for leakage) for Fault-Free CMOS Logic
- I_{DDQ} Testing: Refers to Test Techniques which Monitor the Static (DC)Current Drawn by the CUT
- **Typical Normal I_{DDQ} values ~ Nano Amps**
- **Abnormal I_{DDQ} values ~ Micro Amps**
- I_{DDQ} Tests Can be Either **External** or **Built-In**

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 7

I_{DDQ} Tests

Advantages

1. Inexpensive Test Generation
2. Detects a Variety of Fault Types that are not Detectable by Voltage monitoring

Disadvantages

1. Longer Application Time / TV
2. Some Faults escape Detection
3. Either Area & Performance Overhead (Built-In I_{DDQ} Test) Or Large Current Resolution (External I_{DDQ} Test)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 8


External I_{DDQ} Tests

Disadvantages

- Large Current Resolution (Low Sensitivity)
- Slow Testing Speed

Advantages

 - Can be Coupled with Boundary Scan to Test all ICs on a PCB



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 9

Built-in I_{DDQ} Tests

- Uses Built-In Current Sensor (BICS) Circuitry
- Each Monitored Circuit Module is Augmented with a BICS

Advantages

- Fine Current Resolution (*High Sensitivity*)
- Higher Test Speed

Disadvantages

- Performance & Area Overhead (BICS & test logic)

Statistical Data


- 5000 SRAM Chips were Tested
 1. 443 Chips Failed Functional Test
 2. 697 Failed I_{DDQ} Test → Failing Parts Included The above 443 Parts + 254 other Bad Parts that were not caught by the Functional Tests (see “ I_{DDQ} Benefits” by Steven D. McEuen in “Bridging Faults and I_{DDQ} Tests” by Y.K. Malaiya, et.al.)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 10

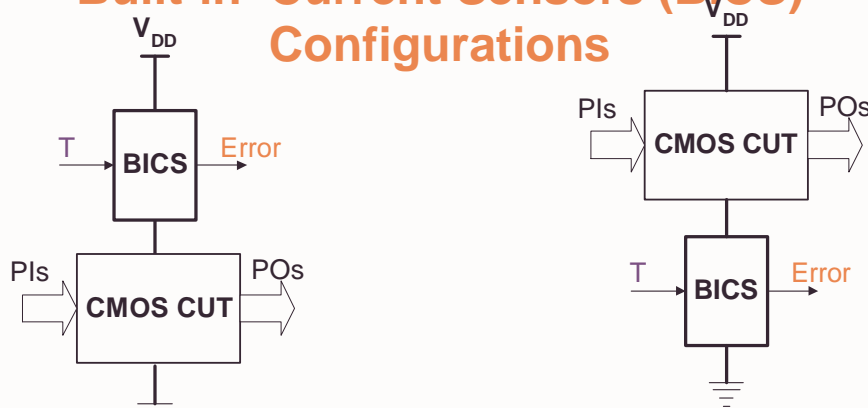Built-in Current Sensors (BICS) Configurations



- T is a Mode Control Signal
 - $T=1$ → Test Mode
 - $T=0$ → Normal Operating Mode
- BICS equivalent Resistance Should be Minimized So as not to Severly Degrade CUT Performance

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 11

Faults Detectable by I_{DDQ} Tests


- Stuck-on faults & Bridging
- Break faults
 - Line break
 - Gate break
 - Drain break
 - Source break
- Transistor Stuck-Open faults
- Other faults

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 12

Bridging Faults

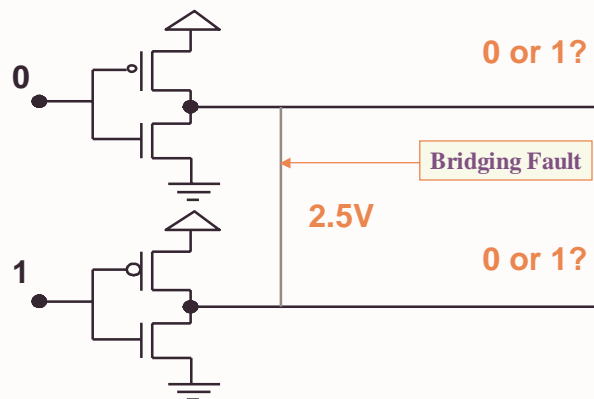


➔ Logic monitoring is inadequate !

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Line Break Faults

 


A floating node may drift to 1.5V~3.5V
and hence may turn on both PMOS
and NMOS transistors

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

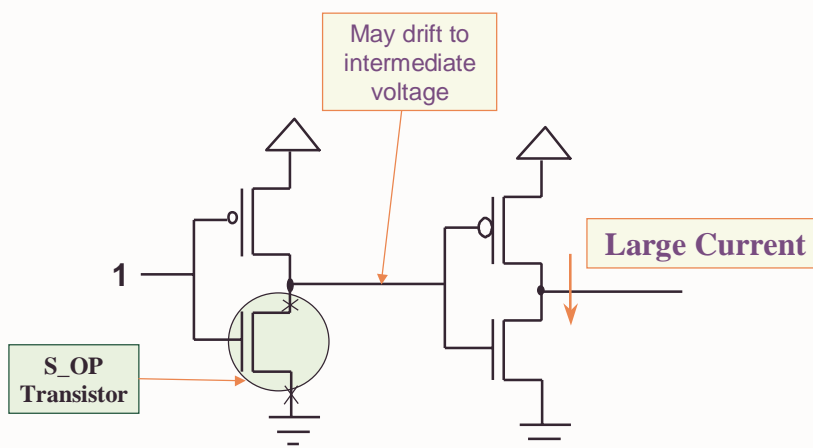Source or Drain Break or Transistor Stuck-Open Faults



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Other Faults That Can Be Detected

- Gate-oxide short (Hawkins ITC85, D&T 86)
- Most stuck-at faults (Fritzmeyer ITC-90)
- Latch-up
- Delay faults
- Any other fault due to extra conductor, missing isolating layer, excess well/substrate leakage, etc.

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Circuit Constraints


To ensure IDDQ detectability, two conditions must be satisfied:

1. Normal IDDQ must be small
2. Faults must result in large IDDQ (**BICS Sensible**)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

A BF That Cannot Be Detected By IDDQ

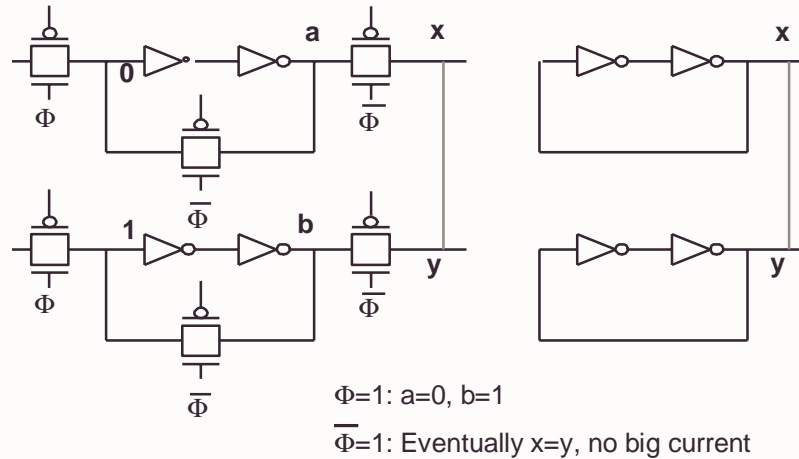

Problem due to feedback loop


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Stuck-OPEN (S_OP) Faults

Consider the Fault **M2 S_OP**

 - **For Fault Activation** Choose a TV which Turns M2 ON in the FF CUT $\rightarrow x_2=1$
- Fault is Sensitized by $x_1 = 0$
- F (Fault-Free) = 0
- F (Faulty) = Hi-Z = $F(t-1)$
- F Must Be Initialized to A Value Opposite to the Fault-Free Value
- A **Sequence of Two TVs** is Needed to Detect S_OP Faults
 1. Initialization TV : $x_1x_2=00$
 2. Detection TV : $x_1x_2=01$




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 19

Test Generation for Static CMOS Logic Gate-Level Test Generation (Jain-Agrawal)

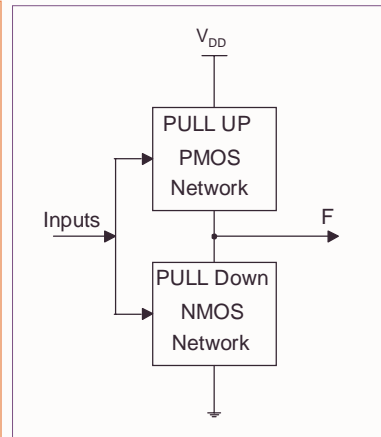- Use Gate Level Model for both Pullup & Pull down Networks
- Use AND, OR & NOT in addition to the “B-Block”
 - Series Connection → AND
 - Parallel Connection → OR
 - I/Ps of PMOS Trs → Complemented
Since PMOS is ON iff I/P=0
 - O/P of NMOS Gate NW = S0
(Implements the 0's of the Function)
 - O/P of PMOS Gate NW = S1
(Implements the 1's of the Function)
 - S0 & S1 are I/Ps of the “B-Block”



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 20

Test Generation for Static CMOS Logic Gate-Level Test Generation (Jain-Agrawal)

S1	S0	O/P of B-Block (Y)
0	0	M (Memory State)
0	1	0
1	0	1
1	1	0 (Contention → PDN assumed Stronger)

- S1 = 1 IFF one or more Paths is enabled in the Pull-Up PMOS NW
- S0 = 1 IFF one or more Paths is enabled in the Pull-Down NMOS NW
- IFF S1S0=11 → Contention State, where the O/P depends on the resistance ratio of the pullup to pull down paths.
→ BICS Can Detect Condition
- In Case of Contention, we assumed a stronger Pulldown

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 21

Test Generation for Static CMOS Logic Gate-Level Test Generation (Jain-Agrawal)

- **S_ON, S_OP in CMOS are Translated into SSL Faults in Gate-Level Model**

Dr. Alaaeldin Amin (COE 545) Slide Number 22

Example

Tr. Fault	Equiv SSL Fault	
M1 S_ON (S_OP)	5/1	(5/0)
M2 S_ON (S_OP)	6/1	(6/0)
M3 S_ON (S_OP)	3/0	(3/1)
M4 S_ON (S_OP)	4/0	(4/1)
$x_1/1$	$(x_1/0)$	1/1 (1/0)
$x_2/1$	$(x_2/0)$	2/1 (2/0)
F/1	(F/0)	9/1 (9/0)

Since only SSL Faults need be Considered
→ D-Alg, PODEM, FAN may be Used to Derive Tests for these Faults

↓

Need The Singular Covers & Propagation D-Cubes of the B-Block

eldin Amin (COE 545) Slide Number 23