

### B-Block Cubes

|                | S <sub>1</sub> | S <sub>0</sub> | O/P |
|----------------|----------------|----------------|-----|
| r <sub>1</sub> | x              | 1              | 0   |
| r <sub>2</sub> | 1              | 0              | 1   |
| r <sub>3</sub> | 0              | 0              | M   |

$r_{11}: 0\ 1\ /0$   
 $r_{12}: 1\ 1\ /0$

Assumes Tri-State Capability

|                                  | S <sub>1</sub> | S <sub>0</sub> | O/P           |
|----------------------------------|----------------|----------------|---------------|
| r <sub>12</sub> ∩ r <sub>2</sub> | 1              | D              | $\bar{D}$     |
| r <sub>12</sub> ∩ r <sub>1</sub> | 1              | $\bar{D}$      | D             |
| r <sub>11</sub> ∩ r <sub>2</sub> | $\bar{D}$      | D              | $\bar{D}$     |
| r <sub>11</sub> ∩ r <sub>1</sub> | D              | $\bar{D}$      | D             |
| r <sub>11</sub> ∩ r <sub>3</sub> | 0              | D              | $\bar{D}$ (1) |
| r <sub>11</sub> ∩ r <sub>3</sub> | 0              | $\bar{D}$      | D (1)         |
| r <sub>12</sub> ∩ r <sub>3</sub> | D              | D              | $\bar{D}$ (1) |
| r <sub>12</sub> ∩ r <sub>3</sub> | $\bar{D}$      | $\bar{D}$      | D (1)         |
| r <sub>2</sub> ∩ r <sub>3</sub>  | D              | 0              | D (0)         |
| r <sub>2</sub> ∩ r <sub>3</sub>  | $\bar{D}$      | 0              | $\bar{D}$ (0) |

- For **S\_OP** Faults, the CUT must be first **Initialized**
- **Initialization** is achieved by *Line Justification* (D-Alg) or by proper *Initial Objective* in PODEM
- The fault Should not Cause False Initialization → If a Line is Stuck at 0 (1), a 1 (0) Should not be Applied to it During Initialization

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 24

Fault Activation: PDFF Line 1 = 0

Implication: Line 3 = DB, Line 5 = 0 = Line 8,

D-Frontier: {G1} → t2 = t1 ∩ PDC(G1)

t2 = (0, x, DB, x, 0, x, x, 0, x) ∩ (x2=1)

= (0, 1, DB, 1, 0, 1, D, 0, x) → = **D Provided F**  
 Initialized at **0**

Initialization: Faulty & Fault-Free CUT Must Give the Same Result, i.e. Fault **Must not MASK the Initialization Value**

Initialization: Since t2 = (0, 1, DB, 1, 0, 1, D, 0, D)

Line Justify: (x, x, 1, x, x, x, x, x, 0)  
 Prevents Fault Masking →

Line Justify: (x, x, 1, x, x, x, 0, 1, 0)

This Yields: (1, 1, 1, 1, 1, 1, 0, 1, 0)

The Test Sequence becomes: (11/0) (01/1)


### Example

**Fault M3 S\_OP ≡ 3/1**

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 25
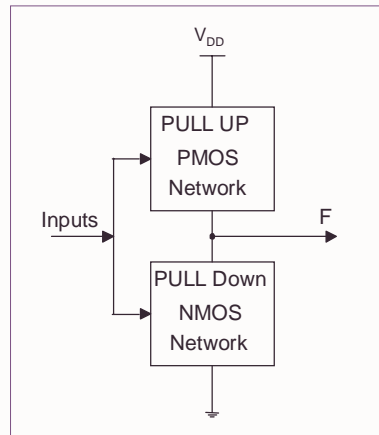
## Test Generation for Transistor-Level Faults of Static CMOS Logic Connection Graph Method (Chiang-Vransic)

- A Connection Graph is Drawn for both the Pullup and Pull Down Networks
- The Connection Graph Models the Transmission Function between the Source and the Sink Node
- The Transmission Function Expresses the Conditions under which Paths are Enabled between the Source and Sink Nodes




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)


Slide Number 26

## Test Generation for Static CMOS Logic Connection Graph Method (Chiang-Vransic)

Example

 


Source F

 

Connection Graph  
for NMOS NW

$$F_n = x_1x_2 + x_3x_4 = \bar{F}_p$$

Source V<sub>DD</sub>

 

Connection Graph  
for PMOS NW

$$F_p = (\bar{x}_1 + \bar{x}_2)(\bar{x}_3 + \bar{x}_4)$$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 27

### Test Generation for Static CMOS Logic Connection Graph Method (Chiang-Vransic)

**Source  $V_{DD}$**

**Sink F**

**Connection Graph for PMOS NW**

$F_p = (\bar{x}_1 + \bar{x}_2)(\bar{x}_3 + \bar{x}_4)$

- The Set of TVs that **Enable** a **SINGLE** Path in the Pull up PMOS Network is :
- $TV(1) = \{0101, 0110, 1001, 1010\}$

COE - KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 28

### Test Generation for Static CMOS Logic Connection Graph Method (Chiang-Vransic)

**Source F**

**Sink  $V_{SS}$**


**Connection Graph for NMOS NW**

$F_n = x_1 x_2 + x_3 x_4 = \bar{F}_p$

- The Set of TVs that **Enable** a **SINGLE** Path in the Pull down NMOS Network is :
- $TV(0) = \{1100, 0011\}$

COE - KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 29
 
### Test Generation for Static CMOS Logic Connection Graph Method (Chiang-Vransic)




- $TV(1) = \{0101, 0110, 1001, 1010\}$
- $TV(0) = \{1100, 0011\}$
- Choose the smallest Subset of TVs which Covers Paths between Source & Sink that Go Through All Transistors
  - $T(1) = \{0101, 1010\}$
  - $T(0) = \{1100, 0011\}$
- Choose a test Sequence that Alternates TVs from T(1) and T(0) → Enables all Conduction Paths between F and  $V_{DD}$  or  $V_{SS}$  alternately.
- Test Sequence =  $T = \{ \underline{0101}, 1100, 1010, 0011, \underline{0101} \}$

Dr. Alaaeldin Amin (COE 545)

Slide Number 30
 
### Test Generation for Static CMOS Logic Connection Graph Method (Chiang-Vransic)



- $T = \{ \underline{0101}, 1100, 1010, 0011, \underline{0101} \}$
- $F = \{ \underline{1}, 0, \underline{1}, 0, \underline{1} \}$
- The First TV Serves as Initialization, thus it is Repeated again at the end of the sequence.
- T Detects ALL Single S\_OP Faults in either the Pull up or the Pull Down Networks.
- A TV Detecting Given S\_OP Faults, ALSO Detects S\_ON Fault of the Corresponding Transistors in the Dual Network
- **Thus:** 1100 Detects S\_OP Faults of M5 & M6
- With a BICS in place, the same TV (1100) Also Detects S\_ON Faults of M1 & M2

## CMOS Test Invalidation (Test Robustness)

- 2 Mechanisms May Prevent a TV Sequence from Detecting the S\_OP Faults it is Designed to Detect:
  1. Circuit Delays, and
  2. Charge Sharing (Only Dynamic Logic)
- Tests that **Can be** Invalidated are called **non-Robust** Tests
- Tests that **Cannot be** Invalidated are called **Robust** Tests

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 32

## CMOS Test Invalidation (Test Robustness)

- 2 Mechanisms May Prevent a TV Sequence from Detecting the S\_OP Faults it is Designed to Detect:
  1. Circuit Delays, and
  2. Charge Sharing (Only Dynamic Logic)
- Tests that **Can be** Invalidated are called **non-Robust** Tests
- Tests that **Cannot be** Invalidated are called **Robust** Tests

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 33

### Test Robustness - Example

$$F = \bar{x}_1 x_2 + x_1 \bar{x}_2 + \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 x_3$$

**Fault**  $f = M19 S\_OP$

$T(0) = \{ 0001, 1101, 1110 \}$   
 $T(1) = \{ 0010 \}$

- Only 3 Test Sequences are Possible to Detect  $f$ .

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 34

### Test Robustness - Example

$$F = \bar{x}_1 x_2 + x_1 \bar{x}_2 + \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 x_3$$

**Fault**  $f = M19 S\_OP$

$T(0) = \{ 0001, 1101, 1110 \}$   
 $T(1) = \{ 0010 \}$

- Only 3 Test Sequences are Possible to Detect  $f$ .
- Transient TVs always Pass by either 0000 or 0011
- For this Fault, There is No Robust 2-Pattern Test Sequence → This CUT is not Robustly Testable

- For a Robust test Sequence, Alternating TVs in the Sequence Must have a Hamming Distance of 1

COE 545 Slide Number 35