 


DIGITAL SYSTEM TESTING COE -545


Lecture – 14 Test Generation for Sequential Circuit

Test Generation for Sequential Circuit



Mealy Machine

$$Z = F(x, y)$$
$$Y = Y(x, y)$$

 

Moore Machine

$$Z = F(y)$$
$$Y = Y(x, y)$$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 2

Introduction

- Test Generation Problem is More Complicated for Seq. Circuits, where output is function of past history
→ Temporal Dimension

Characteristics of Sequential Testing

- Much harder to test than combinational circuits
- Tests are *Sequences* of input vectors
- Two circuit types: asynchronous and synchronous (Only Synchronous is Considered here)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 3

Introduction

Basic Approaches

- State table analysis
- Machine identification (checking sequence) method
- *Time-Frame Expansion*: combinational ATPG methods such as PODEM) are applied to an *iterative logic array (ILA)* model of the target sequential circuit
- Simulation-based methods

Key Assumptions

- Unknown initial state
- Known Initial State

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 4

State Table Method

		x	
y1y2		0	1
0	0	A,0	B,0
0	1	B,0	C,0
1	1	C,0	D,1
1	0	D,1	A,0

Fault-free
state table

		x	
y1y2		0	1
0	0	A,0	B,0
0	1	B,0	C,0
1	1	B,0	D,1
1	0	A,0	A,0

State table
with fault a/1

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 5

State Table Method (Diagnostic/Decision Tree)

		x	
A		0	1
A	A,0	B,0	
B	B,0	C,0	
C	C,0	D,1	
D	D,1	A,0	

Fault-free
machine M_0

		x	
A		0	1
A	A,0	B,0	
B	B,0	C,0	
C	B,0	D,1	
D	A,0	A,0	

Faulty
machine M_1

Initial state A known

Circuits produce
different outputs

Minimum length test for a/1 with
initial state A: $x(t) = 1\ 1\ 0\ 1$

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 6

State Table Method (Diagnostic/Decision Tree)

	0	1
A	A,0	B,0
B	B,0	C,0
C	C,0	D,1
D	D,1	A,0

Fault-free machine M_0

	0	1
A	A,0	B,0
B	B,0	C,0
C	B,0	D,1
D	A,0	A,0

Faulty machine M_1

Initial state unknown

Minimal test for a/1 with unknown initial state: $x(t) = 0\ 1\ 1\ 0\ 1$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 7

Useful Sequences

Homing Sequence

- **Definition:** An input sequence S that takes M to a final state that is uniquely determined by the output response to S
- Every reduced M has a homing sequence [length $< n(n-1)/2$]

Synchronizing Sequence

- **Definition:** An input sequence S that takes M to a unique final state, independent of the initial state
- Not every machine has a synchronizing sequence

Distinguishing Sequence

- **Definition:** An input sequence S that yields a unique output response for every possible initial state
- Not every M has a distinguishing sequence, but every M has a complete set of partial distinguishing sequences called characterizing sequences

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 8


Homing Sequence

Example

- Build Successor Tree, Terminate When
 - New Uncertainty Vector Identical to a Previous Level Uncertainty Vector
 - Uncertainty Vector Resolved (No 2 Different States in the same Subcomponent)
- Shortest Homing Sequence is **010**

Initial State	Response to 010	Final State
A	000	A
B	001	D
C	101	D
D	101	D

PS	NS, Z	
	x=0	x=1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

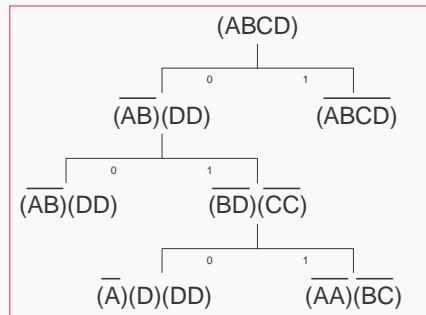

COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 9

Synchronizing Sequence

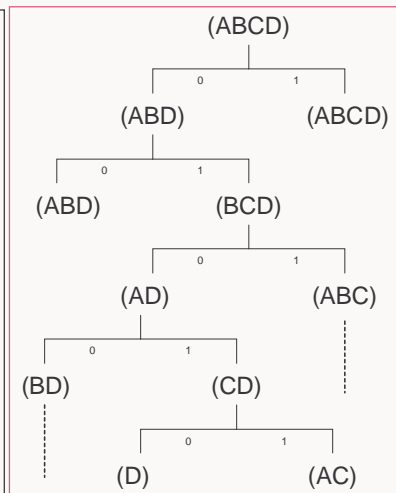Example

- Build Successor Tree, Terminate When
 - New Uncertainty Vector Identical to a Previous Level One
 - A Node is Associated with an Uncertainty of Just One State
- Shortest Synchronizing Sequence is **01010**



PS	NS, Z	
	x=0	x=1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)


Slide Number 10

Distinguishing Sequence

Example

- Build Successor Tree, Terminate When
 - New Uncertainty Vector whose non-individual components appear at a preceding level
 - One or more component of the Uncertainty Vector has repeated state occurrence
 - Node has components of individual States
- Shortest Synchronizing Sequence is 01010

PS	NS, Z	
	x=0	x=1
A	C, 0	D, 1
B	C, 0	A, 1
C	A, 1	B, 0
D	B, 0	C, 1

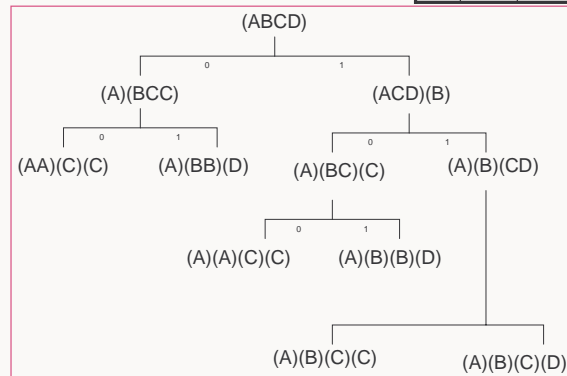

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 11

Machine Identification

Problem

- Given an n -state sequential machine M described by a state table T (or equivalent), construct a test called a *checking sequence* that will determine whether any given (potentially faulty) machine M^* has the same state table as M .

Assumptions

- M is Completely Specified
- M is reduced
- M is strongly connected (every state reachable from every other state)
- *In general*, the initial state before testing begins is unknown

Fault Model

- Any behavioral change that does not increase the number of states n

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 12

Fault Detection Experiments

Two Parts

1. *Initialization*: Transfer the Ckt., into a Prespecified State .
2. *Transition Tests*: Take the CUT through all possible transitions
 - Verify Current State, e.g. Using a Distinguishing Sequence
 - Perform actual transition by applying a Transfer sequence from the current to the desired state .

M has a distinguishing sequence (DS)

- Let the States of M be S_1, S_2, \dots, S_n
- Let X_0 be a DS of M
- Let $T(S_p, S_j)$ be a transfer Sequence that takes M from state S_i to state S_j
- $X_k S_i$, is the final state reached when the sequence X_k is applied to State S_i

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 13

Fault Detection Experiments

- Let $Q_i (= X_0 S_i)$ denote the State M reaches when the Sequence X_0 is applied to M while in state S_i

First Part

- Apply a Homing/Synchronizing Sequence to reach some known initial state, Say S_1
- Applying the Sequence:
 $X_0 T(Q_1, S_2) X_0 T(Q_2, S_3) X_0 T(Q_3, S_4) \dots X_0 T(Q_n, S_1) X_0$
 Takes M through each of its states \rightarrow Experiment Leaves M in state Q_1
- Verify Each State Transition, e.g. to Verify the 0-Transition out of State S_i when M is in Q_j , use the Sequence $X_0 T(Q_j, S_{i-1}) X_0 T(Q_{i-1}, S_i) X_0$


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 14


Time Frame Expansion

 - Turn the Temporal Relationship between Machine (CUT) States into a Spatial one →
- Convert the Seq CUT into a 1-Dimensional Iterative Array of Identical Combinational CUT →
- Each CUT Copy Represents a Time Frame which is Fed information about its State from the Previous Stage (Copy).




Time Frame Expansion

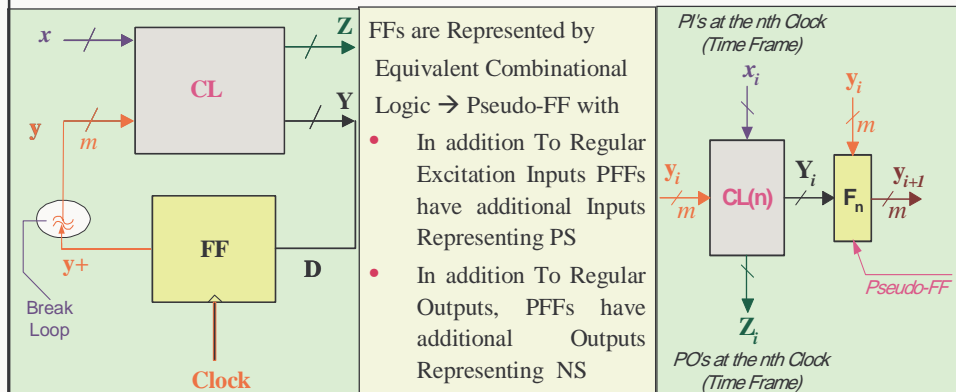- Turn the Temporal Relationship between Machine (CUT) States into a Spatial one →
- Convert the Seq CUT into a 1-Dimensional Iterative Array of Identical Combinational CUT →
- Each CUT Copy Represents a Time Frame which is Fed information about its State from the Previous Stage (Copy).



Time Frame Expansion

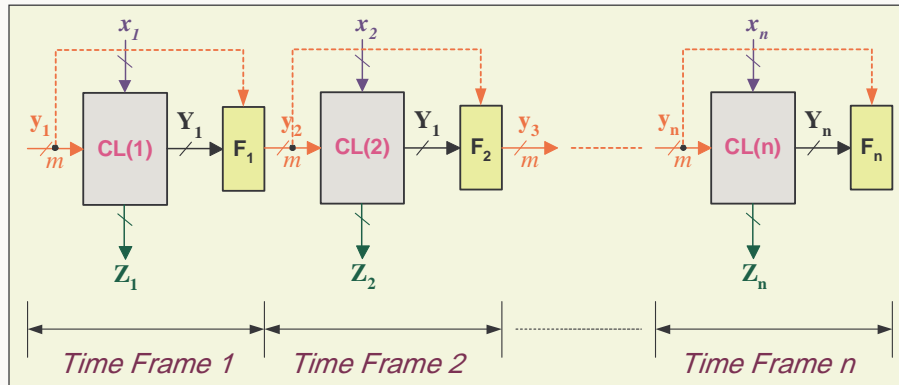- The Pseudo-FF is Purely Combinational CKT with
 - No Clock Input
 - Extra Input Representing the Present State
 - Extra Output Representing the Next State




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 17


Example

- JK - FF
 - $y^+ = J y' + K' y$

 

Pseudo JK-FF

- D-FF
 - $y^+ = D$

 


Pseudo D-FF

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 18

Iterative Array Model for D-FFs

 


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 19

Time Frame Expansion

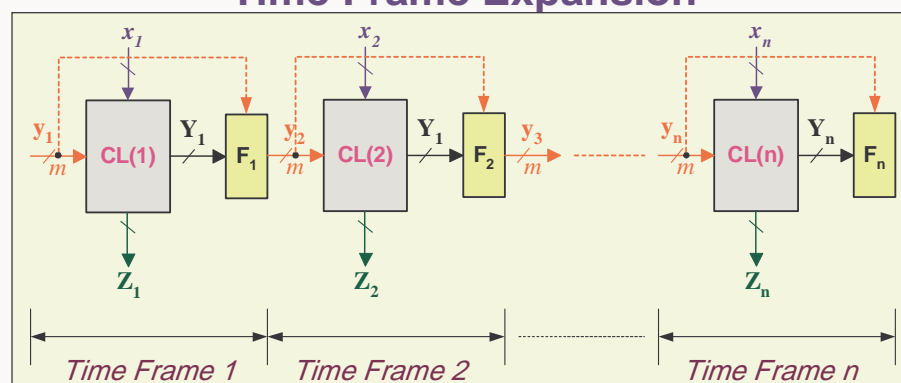

- FFs and Clock Line are Fault-Free
- Same Clock Signal Gating all FFs
- Fault doesn't Increase the Number of States
- Resulting Iterative Model is Purely Combinational \rightarrow D-Alg, PODEM FAN May be Used.

- All Time Frames Have Identical Ckts
 - \triangleright A Single Stuck Fault is Mapped into n Multiple Faults
 - \triangleright TG Algorithm need not Construct n -Copies of the Same Ckt \rightarrow One is Enough.
 - \triangleright Signal Values in Different Time Frames Must be Maintained

Time Frame Expansion

- Attempt is first made to propagate the fault (**D or DB**) to a PO → If Successful a TV is generated
- If not Successful, attempts are made to Propagate the Fault to the Next State Variables which Requires another Time Frame.
- A Signal Value Assigned to **y+** Must be **Propagated** into the Next Time-Frame
- A Signal Value Assigned to **y** Must be **Justified** Backwards into the Previous Time-Frame
- Number of Time Frames is Unknown → Complexity
- If Initial States of the Fault-Free and the Faulty Circuits are not known → Added Complexity.
- Even if Initial State is Known, it May not be Activatable in the first Frame → A Sequence may be Required to Activate the Fault

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 21

Time Frame Expansion

- With Multiple Faults in the Multiple Time-Frames, Propagating Signal Values $\in \{0, 1, D, DB\}$ onto a Faulty Line Follows the Shown Table

Propagated Value	Line Fault	Resulting Line Value
0	S_a_0	0
1	S_a_0	D
0	S_a_1	DB
1	S_a_1	1
D	S_a_0	D
DB	S_a_0	0
D	S_a_1	1
DB	S_a_1	DB

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 22

Sequential ATPG

- **Initial state is assumed to be known**

```
While  $r < f_{max}$  do
begin
  Build model with  $r$  time frames;
  Ignore primary outputs in first  $r - 1$  time frames;
  Ignore secondary (Y) outputs in last time frame;
  Set initial state to  $Y(0)$ ;
  if (test is found) return(SUCCESS);
  /* No solution exists with  $r$  time frames */
   $r = r + 1$ 
end
return(FAILURE);
```

Where: f_{max} : maximum number of frames,

Test Generation Procedure

- 1. In time-frame model of the CUT set $t = 0$ and the flip-flops to an initial state $Y(0)$ by**
 - Resetting to a known state, or else
 - Setting state values to unknown X
- 2. Apply combinational ATPG to frame corresponding to current t . Try to drive D/D' to primary output Z . If successful, exit.**
- 3. Otherwise, try to drive D/D' to secondary output Y . If unsuccessful exit with no test and go to step 2.**
- 4. Perform justification. If successful and D/D' is at Z , exit with a test. Otherwise, increment t to $t + 1$ and go to step 2.**

Example

- Line a: s-a-1 fault. Known state (0, 0).

Time frame 1: Fault activation: $(y_1, y_2) = (0, 0) \rightarrow y_2 = \text{DB}$


- Fault propagation $I(1) = 1 \rightarrow y_2^+ = \text{DB}$, $Z = 1$

Time frame 2: **Depending on the Chosen D-Frontier Gate**

Either $I(2) = 1 \rightarrow (y_2^+, y_1^+) = (\text{DB}, \text{DB}) \rightarrow y_2(2) = \text{DB} \ \& \ y_1(2) = \text{D}$


OR $I(2) = 0 \rightarrow (y_2^+, y_1^+) = (\text{D}, 0) \rightarrow y_2(2) = \text{D} \ \& \ y_1(2) = 0$

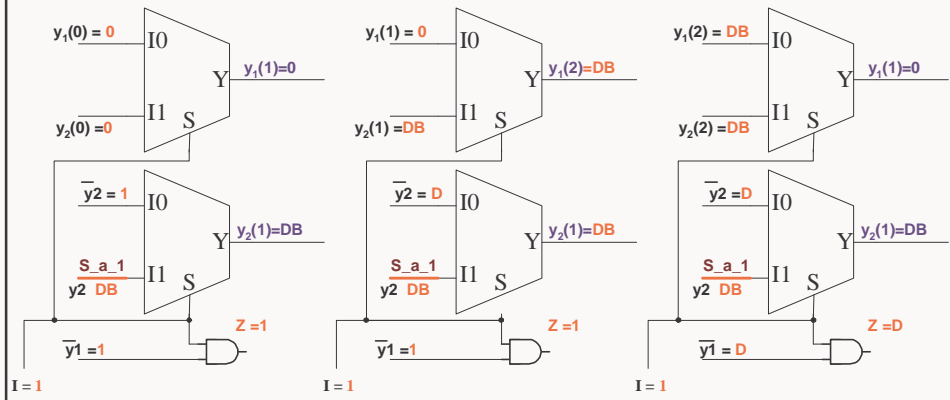Time frame 3: First Choice $(y_2^+, y_1^+) = (\text{DB}, \text{DB})$ Puts Z on the D-Frontier
 $\rightarrow I(3) = 1 \rightarrow Z = \text{DB}$



Sequential ATPG

- Initial state is Unknown**
- Initial State = $xx \dots xx$
- Three main components of sequential circuit test generation (not in order):
 - Excite the fault in one Time Frame (Labeled 1 Say)
 - Propagate the fault effects Forwards (in Time) to a PO if possible or to a State (Secondary) Variable \rightarrow Requires $r \geq 1$ Frames
 - Justify the state with **backward** propagation Using p Frames (Frames 0, -1, -2, ...-(p-1))
 - Stop when All State Variables are all x's

 

Sequential ATPG

- **Initial state is Unknown**

```

r = 1
p = 0
repeat
  begin
    Build model with  $p+r$  time frames
    Ignore the POs in the first  $p+r-1$  frames
    Ignore the  $q+$  outputs in the last frame
    If (test generation success) and every  $q$  input in the first
    frame has value  $xthen return SUCCESS
    Increment  $r$  or  $p$ 
  end
until ( $r + p = fmax$ )
return FAILURE$ 
```


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 27

 Example

- Consider the Fault
Z/0
- Use Pseudo JK-FF
(PJKFF)
- Singular Covers of
the PJKFF and
Propagation D-
Cubes need to be
Derived



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 28


Example

- Pseudo JK-FF Implements the Function

$y^+ = J y' + K' y$

Time Frame 1

 - Only Test to Detect Fault is: $(I, y_1) = 10$
- Only one Frame ($r = 1$) is Thus Needed to Propagate the Fault to the PO (Z)
- Need to Justify $y_1 = 0 \rightarrow (p > 0)$



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 29



Example

- Pseudo JK-FF Implements the Function

$y^+ = J y' + K' y$

Time Frame 0

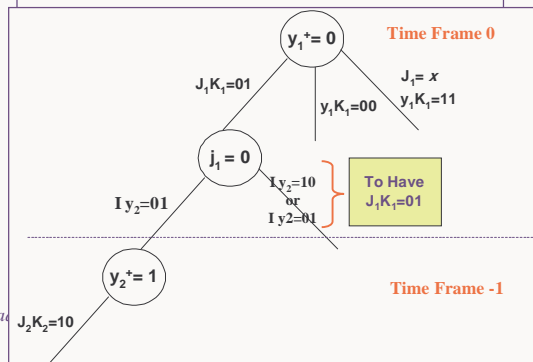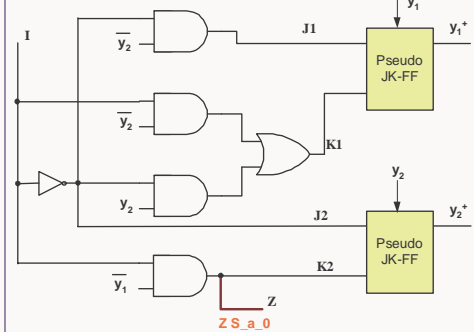- To Justify $y_1^+ = 0 \rightarrow (J_1 K_1 = 01)$ is Thus Needed to Propagate the Fault to the PO (Z)
- Need to Justify $y_1 = 0 \rightarrow (p > 0)$
- For All options to set $(J_1 K_1 = 01)$, y_2 Must be Assigned a Value \rightarrow Needs to be Justified in YET ANOTHER Time Frame $\rightarrow (p > 1)$




COE – KFUPM

Dr. Alaaeldin Amin

 Example

Time Frame -1

- Justify $y_2^+=1 \rightarrow$
($J_2K_2=10$) \rightarrow Both
Satisfied by $I=0$
- This Represents a
Self-Initializing Test
Sequence Since
 - $\triangleright y_2y_1=xx$
 - \triangleright All Lines are Justified
- The Test Sequence
Becomes:
 $I=001$




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 31

Example: A Serial Adder

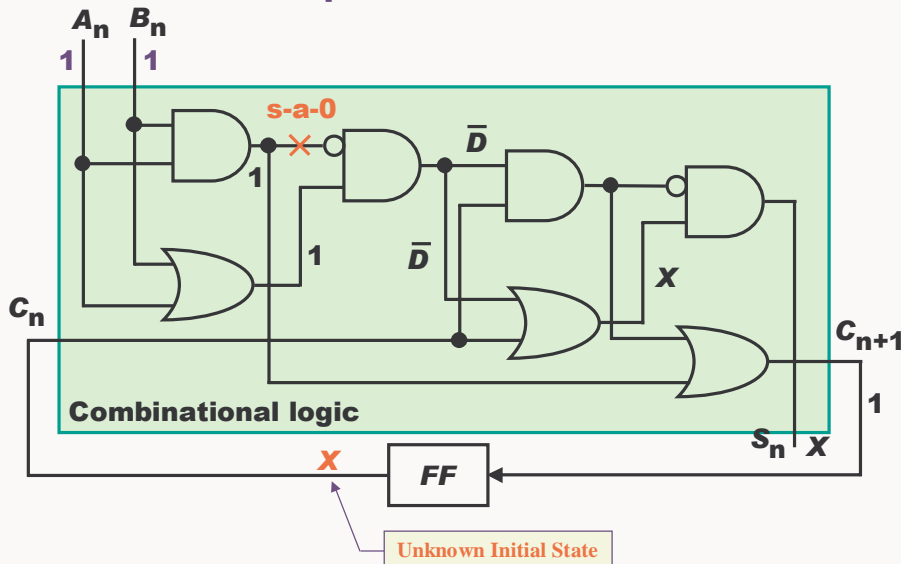

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 32

