

## DIGITAL SYSTEM TESTING COE -545


### Lecture – 05

#### Test Generation (Boolean Difference)

### Combinational Circuit Testing

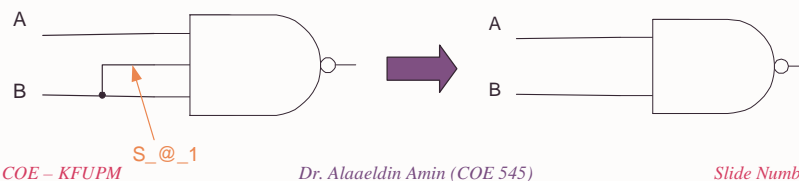
#### Basic Definitions

- Let fault  $f$  change output  $Z(X)$  of a circuit  $C$  to  $Z_f(X)$ .
- A TV  $t$  detects  $f$  if  $Z(t) \neq Z_f(t) \rightarrow Z(t) \oplus Z_f(t) = 1$
- Fault  $f$  is Undetectable or Redundant if  $Z(t) = Z_f(t) \forall t$ .
- If the fault line  $x$  s-a-d is undetectable, then  $x$  and circuits feeding  $x$  can be removed from the circuit.



## Combinational Circuit Testing

### Another Example

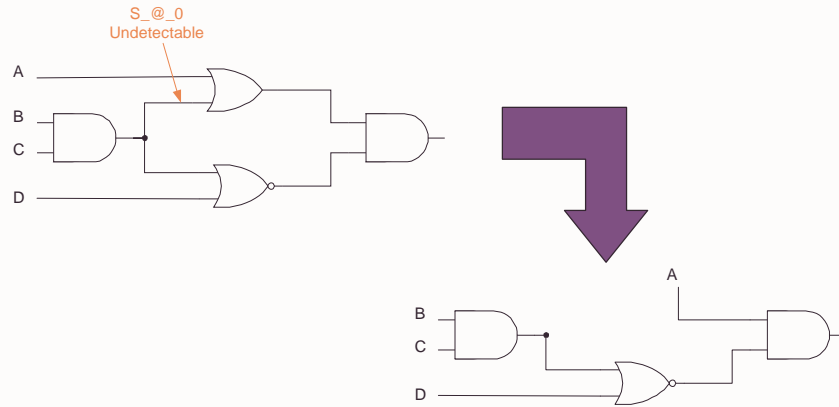


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)


Slide Number 3

## Redundancy

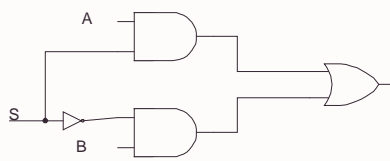

**Hazardous Circuit**

(a)

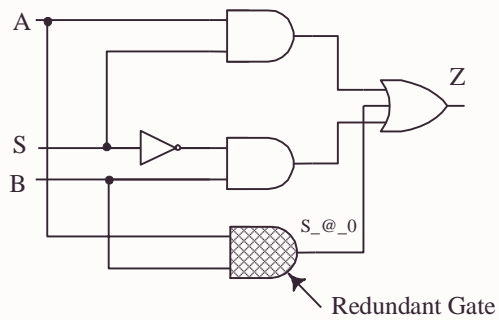

**Hazard-Free Circuit**

(b)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 4

## Combinational Circuit Testing

### Basic Definitions (cont'd)

- A set of tests  $T = \{t_1, t_2, \dots, t_k\}$  is **complete** if it detects (covers) all detectable SSL faults in the circuit
- We can represent any test set  $\{t_1, t_2, \dots, t_k\}$  by the Boolean function whose minterms are  $\{t_1, t_2, \dots, t_k\}$ .
- **Example**, the function  $Z(a,b,c,d) = a'bd' + abcd$  denotes the 3-member test set **{0100, 0110, 1111}**.

- The set of all TVs for fault  $f$  is expressed by the Boolean function  $(Z(x) \oplus Z_f(x))$

## Example

- Fault-Free Fun =  $F(a,b,c) = (a + b)(b + c)$
- **Fault = b/0**
- **Faulty Fun =  $F_\alpha = ac$**
- TVs Detecting this Fault Should Satisfy:  $(F \oplus F_\alpha) = 1$
- Thus,  $(a + b)(b + c) \oplus ac = B(A' + C')$
- This represents 2 possible Tests
- TV set for a/1 =  $\{01x, x10\} \rightarrow \{010, 011, 110\}$

## Boolean Difference Method

- Fault-Free Fun=  $F(x_1, x_2, \dots, x_n)$
- Assuming a SSL Fault  $x_i/1$
- $F_\alpha = F(x_i=1) = F(x_1, x_2, \dots, 1, \dots, x_n) = F_i(1)$
- Assuming a SSL Fault  $x_i/0$
- $F_\alpha = F(x_i=0) = F(x_1, x_2, \dots, 0, \dots, x_n) = F_i(0)$
- According to Shannon's Expansion Theorem:  
 $F(x_1, x_2, \dots, x_n) = x_i F_i(1) + \bar{x}_i F_i(0)$
- Thus, the Test Set to Detect  $x_i/0$  corresponds to :

$$T_0 = x_i (F_i(1) \oplus F_i(0)) \quad , \text{ Likewise}$$

- The Test Set to Detect  $x_i/1$  corresponds to :

$$T_1 = \bar{x}_i (F_i(1) \oplus F_i(0))$$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 7

## Boolean Difference Method

- The Expression  $(F_i(1) \oplus F_i(0))$  is Termed the Boolean Difference of F wrt  $x_i$ , or  $(dF/dx_i)$
- Thus, the Test Set to Detect  $x_i/0$  corresponds to :

$$T_0 = x_i \cdot (dF/dx_i)$$

The Test Set to Detect  $x_i/1$  corresponds to :

$$T_1 = \bar{x}_i \cdot (dF/dx_i)$$

### Notes:

- The  $x_i$ 's are Primary Inputs
- A Fault on some PI ( $x_i$ ) is Undetectable iff

$$F_i(1) = F_i(0) \quad \text{OR} \quad dF/dx_i = 0$$


Which Means that **F is INDEPENDENT OF  $x_i$**

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 8

### Example

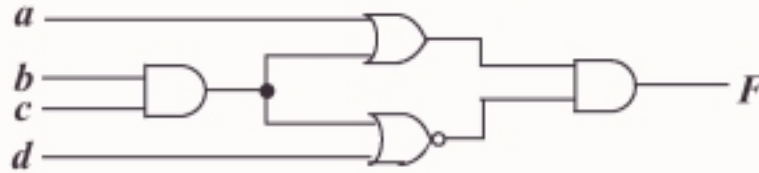

- Fault = a/1
- Fault-Free Fun=  $F(a,b,c,d) = (a + bc)(b' + c')d'$
- $T(a/1) = a'.dF/da$
- $dF/da = [1(b' + c')d' \oplus bc(b' + c')d'] = b'd' + c'd'$
- So  $T(a/1) = a'b'd' + a'c'd'$
- Test set for a/1 = {00x0, 0x00} = {0000, 0010, 0100}

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 9

### Boolean Difference Method


- Boolean Difference (BD) has the following Properties:
  1.  $d\bar{F}/dx_i = dF/dx_i$
  2.  $d/dx_i[dF/dx_j] = d/dx_j[dF/dx_i]$
  3.  $d[F(X) \oplus G(X)]/dx_i = dF/dx_i \oplus dG/dx_i$
  4.  $d[F(X).G(X)]/dx_i = F.dG(X)/dx_i \oplus G.dF(X)/dx_i \oplus dF(X)/dx_i .dG(X)/dx_i$
  5.  $d[F(X) + G(X)]/dx_i = \bar{F}.dG/dx_i \oplus \bar{G}.dF/dx_i \oplus (dF/dx_i).(dG/dx_i)$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 10

### Example

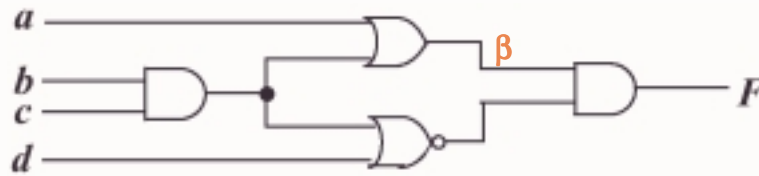

- Fault =  $\beta/0$
- $T(\beta/0) = \beta(X) \cdot dF(x, \beta)/d\beta$ 
  - $\beta(X) = a + bc$        $F(x, \beta) = (b' + c')d' \beta$
- $dF/d\beta = (b' + c')d'$
- So  $T(\beta/0) = ab'd' + ac'd'$
- Test set for  $\beta/0 = \{1000, 1010, 1100\}$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 11

## Test Generation Schemes

- BD method is more Theoretical → Too Complex to Use for Practical Circuits
- Need a More Practical Approach
- **Deterministic Test Generation**
  - **Fault- Oriented ATG**
  - **Fault Independent ATG**
- **Random Test Generation**
  - **Combined Deterministic and Random Test Generation**
- **ATG Systems**
- **Conclusions**

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 12

## Classification & Problems

### Testing

- Off- Line
- Edge- Pin
- Stored- Pattern
- Full Comparison of the Output Results

### General Problems for TG:


- Cost of Generating the Test
- Quality of the Generated Test
- Cost of Applying the Test

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 13

## Deterministic Test Generation

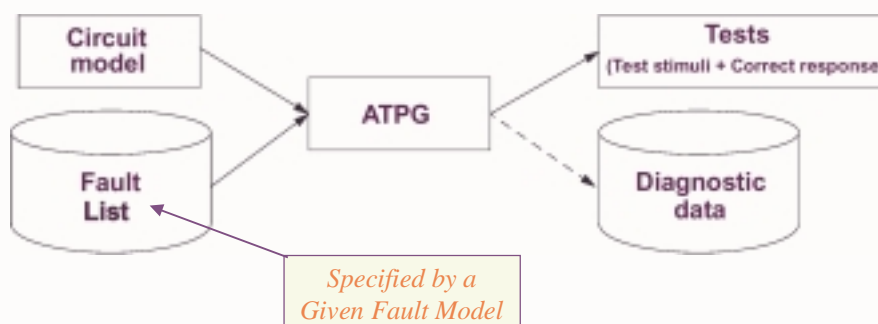

- Manual / Automatic
  - Automatic Test Pattern Generation (ATPG)
- Deterministic ATPG Can Be Fault- Oriented / **Fault-Independent**

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 14

### Fault-Oriented ATPG

The diagram shows a circuit block labeled 'N'. On the left, there are four arrows pointing into the block labeled 'Primary inputs'. On the right, there are four arrows pointing out of the block labeled 'Primary outputs'. A bracket groups these four outputs and points to a label 'Z'. Inside the block 'N', there is a horizontal line representing a signal path. Above this line is the text 'f s-a-v' and below it is a small 'x' with a vertical line through it, indicating a stuck-at fault on a line 'x'.

- Targets a Particular Fault  $f \in \{ \text{Fault List} \}$ 
  - Finds a TV  $t$  which Detects  $f$ 
    - $t$  Detects  $f \Leftrightarrow Z(t) \neq Z_f(t) \Leftrightarrow Z(t) \oplus Z_f(t) = 1$

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 15

### TV Generation

- **Two** Steps Are Necessary to Generate TV  $t$  which Detects Fault  $f$ :
  - Fault Activation/excitation/provoking: Effecting a Different Value  $\bar{v}$  at the Faulty Line  $x$  When  $x$  Is Stuck at  $v$ .
  - Fault Propagation: Propagating Error to an Observable PO

**Definitions**

- A **Line** whose Value under TV  $t$  Changes in the Presence of Fault  $f$  is Said to Be Sensitized to the Fault  $f$  by the Test  $t$
- A Path Composed of Sensitized Lines Is Called a Sensitized Path

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)



### Single Path Sensitization

**Example**

1. Fault Activation → **X1=1**
2. Fault Propagation → 2 Possible Options (Paths)
  - Option 1: G1 – G5 – G7
  - Option 2: G1 – G4 – G6 – G7

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 17


### Single Path Sensitization *Option 1*

**Example**

1. Fault Activation → X1=1
2. Fault Propagation : G1 – G5 – G7 → *Two Possible TVs*
  - T1 = 110X , 1
  - T2 = 11X0 , 1

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 18

## Single Path Sensitization *Option 2*

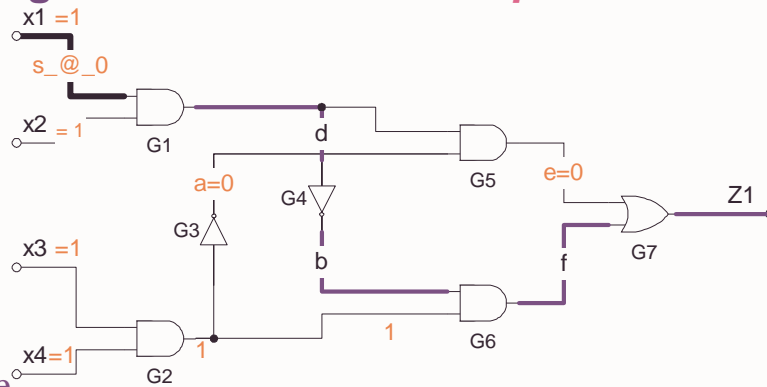

### Example

1. Fault Activation  $\rightarrow X1=1$
2. Fault Propagation : G1 – G4 – G6 - G7  
 $\rightarrow$  *One Possible TV*  $\rightarrow T = 1111, 0$

COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 19

## Multiple Path Sensitization
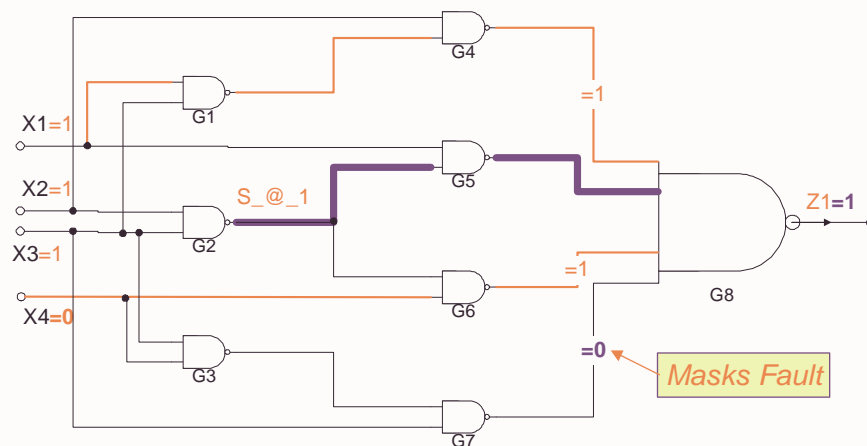
### Major *Problem* with Single Path Sensitization


- A TV May not be Possible to Generate for Some *Testable* Faults if Only One Path is Sensitized at a Time



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 20

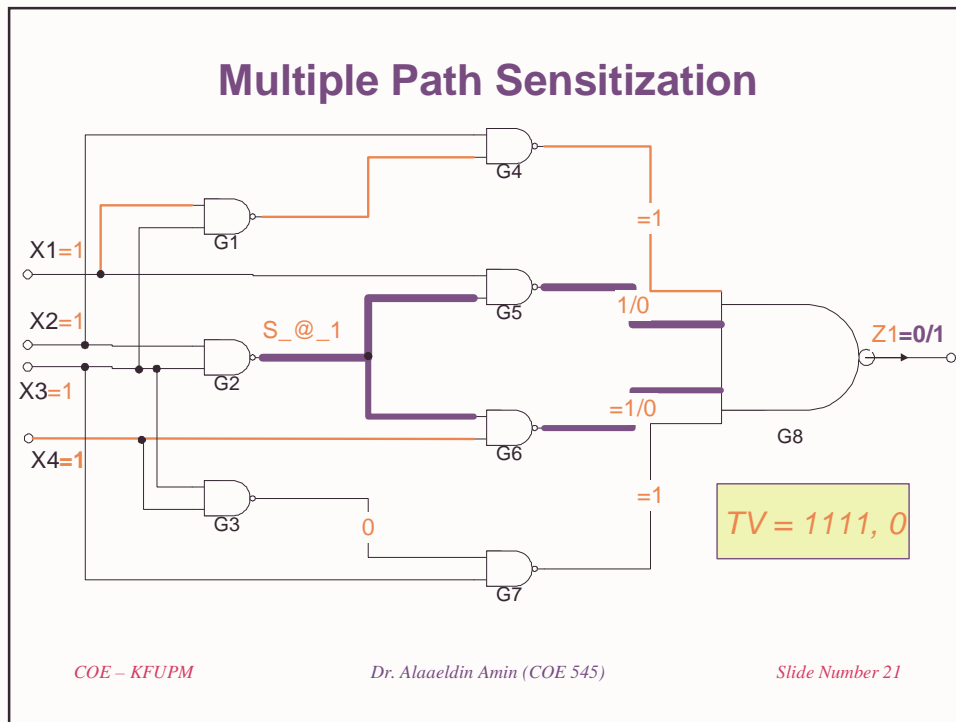

### The D-Algorithm

- An Algorithmic Approach which Generates a TV for a Given Fault if One Exists
- Multiple Path Sensitization
- 5-Valued Logic { 0, 1, X, D,  $\bar{D}$  }
- **D**: A Line is Assigned a **D** value if it has a value **1** in the **Fault-Free** Circuit but has a **0** Value in the **Faulty** Circuit.  
( $D \approx S_{@_0}$ )
- $\bar{D}$ : A Line is Assigned a  $\bar{D}$  value if it has a value **0** in the **Fault-Free** Circuit but has a **1** Value in the **Faulty** Circuit.  
( $\bar{D} \approx S_{@_1}$ )
- D /  $\bar{D}$  Follow Rules of Boolean Algebra

COE – KFUPM      Dr. Alaaeldin Amin (COE 545)      Slide Number 22

## The D-Algorithm

$D + D = D$	$\bar{D} + \bar{D} = \bar{D}$
$D \cdot D = D$	$\bar{D} \cdot \bar{D} = \bar{D}$
$\bar{D} + D = 1$	$D \cdot \bar{D} = 0$
$D \cdot 1 = D$	$\bar{D} \cdot 1 = \bar{D}$
$D \cdot 0 = 0$	$\bar{D} \cdot 0 = 0$
$D + 1 = 1$	$\bar{D} + 1 = 1$
$D + 0 = D$	$\bar{D} + 0 = \bar{D}$

•	0	1	D	$\bar{D}$	x
0	0	0	0	0	0
1	0	1	D	$\bar{D}$	x
D	0	D	D	0	x
$\bar{D}$	0	$\bar{D}$	0	$\bar{D}$	x
x	0	X	x	x	x


AND Operation of the  
5-Valued D-Calculus

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 23


## Example - Single Path Sensitization

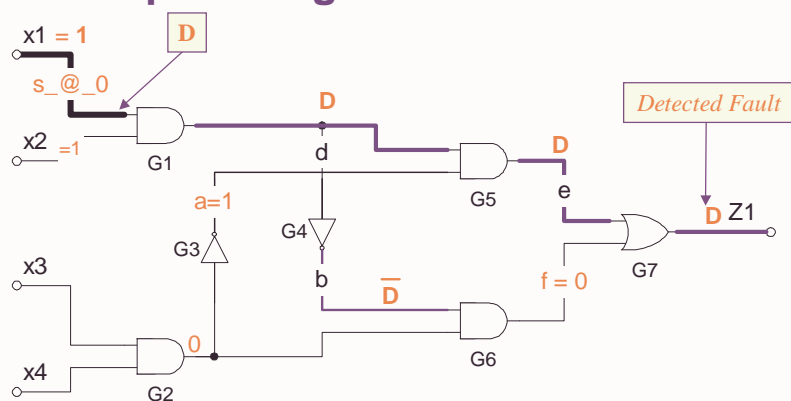

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 24

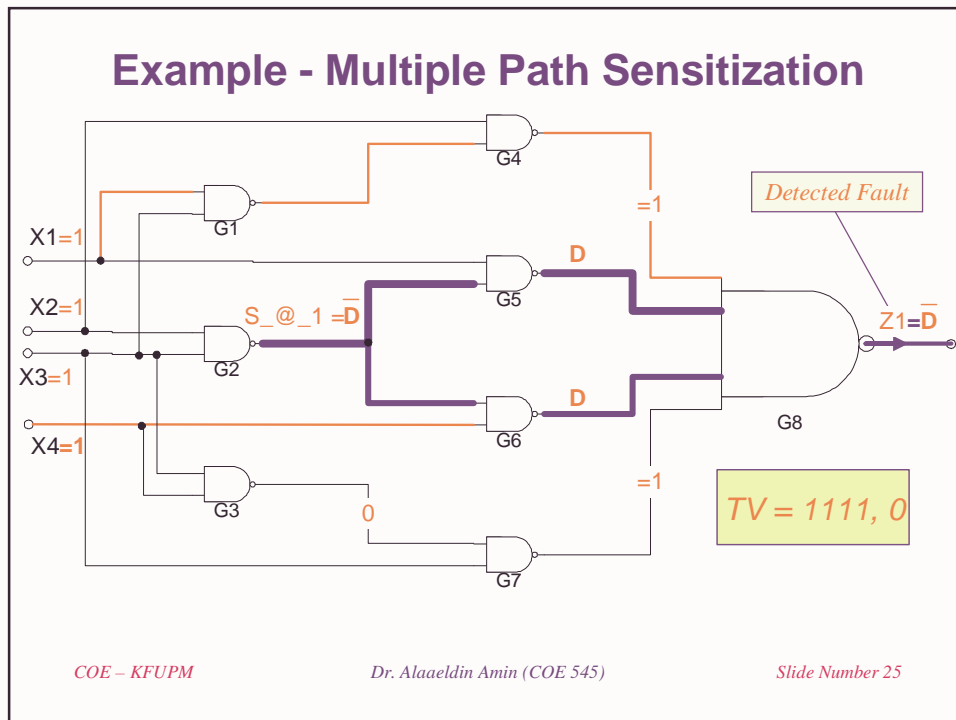

## Definitions

1. Singular Covers (SC) of Some Function F  
(Primitive Cubes of F) : *Minimal Set of Logic Signal Assignments Showing Essential Prime Implicants*

= Prime Implicants of  $F$  ( $\alpha 1$ ) &&  
 Prime Implicants of  $\bar{F}$  ( $\alpha 0$ )

Examples Singular Covers of 2-Input NAND Gate

A	B	F
0	X	1
X	0	1
1	1	0

Pis of  $\bar{F}$   
( $\alpha 0$ )

Pis of  $F$   
( $\alpha 1$ )

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 26