

DIGITAL SYSTEM TESTING COE -545

Lecture - 02

Feasibility of Exhaustive Testing

Example

- Consider a *Small-Size IC* of 20 PT's and 100 FFs. Assuming a testing frequency of 1GHz, Estimate the time required to Exhaustively Test this device.
- The Minimum # of Test Patterns = $2^{(20+100)} = 2^{120}$
- Time taken by Each Test Pattern = $1/10^9 = 1$ Nano-Second
- Lower Bound on the Required Test Time = $10^{-9} \times 2^{120} = 42,120,693,455,298,117,502$ years $\approx 42 \times 10^{18}$ years



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 2

Alternative to Exhaustive Testing

- **Functional Tests:** *Validates, in a Cost-Effective Way, If a Given CKT Performs its intended Function*
 - *Test Stimuli Are Applied at a Relaxed Frequency (Much Slower Than Normal Speed) To Avoid AC Speed Sensitivities.*
- Exhaustive Functional Testing is a *Computationally Intractable* Problem (only feasible for very small CUTs) → Cannot Fully Verify All Circuit States → *Not Cost-Effective*
- **Instead** of Exhaustive Testing for Proper Operation, We *Test for the ABSENCE of Faults* from the circuit.
- The List of Possible Faults (**Fault List**) Must be of a *Manageable Finite Size*

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 3

Physical Faults (Defects)

- The Number of ALL Possible *Physical Faults (Defects)* in any Product is **HUGE**
- Huge Fault List Based on *Physical Faults (Defects)* → *Computationally Intractable*
- Physical Faults (Defects) Can Be Introduced During Any Fabrication Step.

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 4

Physical Faults (Defects)

Example for a VLSI Chip:


- Material Defects →
 - Bulk defects (cracks, crystal imperfections)
 - Surface impurities (ion migration)
 - Passivation pits and cracks
 - Gate oxide Defects → breakdown
 - Pinholes or thin spots in oxide
 - Electrical over-stress
 - Surface potential instability → Threshold Voltage Instability
- Photolithographic & Fabrication Errors →
 - Missing Contact Windows
 - Signal Shorts (Metal Bridging, Pinholes),
 - Signal Open (Defects, Metal Step Coverage)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 5

Defect Photo Example

 

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 6

Defect Photo Example


- Packaging Defects
 - Contact Defect (Wire Bonding Failure)
 - Improper Die-Attach
 - Improper Sealing
- Wear out Defects
 - Electromigration
 - Oxide Charges & VT Shifts (Hot Carrier Effects)
 - Dielectric Breakdown
- Environmental Effects
 - Radiation Effects, ALPHA Particles, Temperature, etc.

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 7

Failure Rate Vs Product Lifetime

 


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 8

VLSI Defects (contd.)

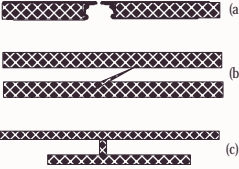

(a) Open in a line
(b) Short between two lines (whisker)
(c) Short between lines on different layers (hillock)

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 9

Observed PCB Defects

| Defect classes | Occurrence frequency (%) |
|-----------------------|--------------------------|
| Shorts | 51 |
| Opens | 1 |
| Missing components | 6 |
| Wrong components | 13 |
| Reversed components | 6 |
| Bent leads | 8 |
| Analog specifications | 5 |
| Digital logic | 5 |
| Performance (timing) | 5 |

Ref.: J. Bateson, *In-Circuit Testing*, Van Nostrand Reinhold, 1985.

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 10

Conclusions?

- Exhaustive Functional Testing is a *Computationally Intractable* For Most Systems.
- Testing for the **ABSENCE** of Faults Requires a **Fault List** of Manageable Size
- **Physical Faults** (Defects) too Numerous and Often not Easily Analyzable to form a Useful Fault List.
- Instead, a **Logical Fault Model** Needs To Be Adopted.

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 11

Why Fault Models?

- Models are often easier to work with, e.g. one logical fault can cover many physical ones (defects).
- Models are portable
- Models can be used for simulation, thus avoiding expensive hardware/actual circuit implementation
- Nearly all engineering systems are studied using models
- All the above apply for logic as well as for fault modeling

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 12

Fault Model Requirements


1. **Accuracy.**
 - The Logical Model Should Represent the Circuit Behavior Under Realistic Physical Fault Condition.
2. **Tractability (Cost-Effectiveness).**
 - The Logical Fault Model Should Have a Manageable Complexity, both for Test Generation and Test Application.

- Engineering Tradeoff is Involved in the Choice of a Fault Model. The more Accurate the Model IS the More Complex (and Less Tractable) it will be.


COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 13

Fault Models at Different Levels

- Fault Models May Describe Faults at Various Levels of Abstraction
 - At the Geometrical (Mask) Level
 - At the Switch (Transistor) Level
 - At the Logical (Gate) Level
 - At the Functional (Behavioral) Level



Higher Accuracy



Lower Complexity

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 14

Types of Logical Fault Models

1. **Structural Fault Models.**
 - Defined in Conjunction with a Circuit Structure
 - Their Effect is to Modify Interconnection between Components while Components themselves are Assumed to Be Fault Free (e.g. Stuck_at, Bridging, and Transistor-Level Fault Models)
 - Not Possible if Detailed Structural Description is Not Available
 - More Structural Details Increases the Complexity of Test Generation
2. **Functional Fault Models.**
 - Defined in Conjunction with a Functional Model, independent of a Specific Implementation
 - Their Effect is to Change the Function of Components Without Worrying about their Interconnection
 - Examples Include Changes in a Truth Table of a Component Cross Point Faults in PLAs, Pattern-Sensitive Faults in RAMs, etc.
 - Useful when Detailed Structural Description is Not Available

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 15

W.R.T. Time , Physical Faults Can Be Classified As:-

1. **Transient Faults**
 - Temporary, Non-Recurring Faults, e.g. Due to Power Supply Fluctuations and Alpha-Particle Induced Faults
2. **Intermittent Faults**
 - Recurring Faults that Appear Under a Given Set of Circumstances Due to Some Unstable Physical Condition
 - Generally May Result From
 - Poor Design
 - Partially Defective Elements
 - Loose Interconnects
 - Ambient Conditions

Too Difficult To Model

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 16

W.R.T. Time , Physical Faults Can Be Classified As:-

3. Permanent Faults

- This is the Category of Faults that We Will Consider.

W.R.T. # of Faults , Fault Models Are Classified As:

1. Single Fault Model

- Only One Fault Exists at a Time. More Commonly Used Since It is
 - ❑ Less Complex
 - ❑ Covers (Detects) Most Multiple Faults

2. Multiple Fault Model

- More Than one Fault May Exist at a Time

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 17

Fault Effects

- On the electrical level
 - Most physical defects results into
 - ❑ Opens
 - ❑ Shorts
- Effect of open:
 - technology dependent (e.g. TTL I/P → Logic 1, Transistor Open → Sequential Behavior)
 - not strictly high-Z behavior (e.g. TTL I/P)
- Effect of a Short:
 - Solid Short (0 Resistance) Usually Assumed
 - Realistically Finite Resistance

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 18

Common Fault Models

| Fault Model | Description |
|------------------------------|---|
| Single Stuck-at Faults (SSA) | One line (Signal) gets Stuck at a constant value either a 0 or 1. |
| Multiple Stuck-at Faults | Two or more lines have fixed values, not necessarily the same. |
| Bridging Faults | Two or more lines that are normally independent get shorted together. |

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 19

More Fault Types

| Fault Model | Description |
|--------------------------|--|
| Stuck-Open Faults (SOP) | A failure in a pull-up or pull-down transistor in a CMOS logic causes it to behave as a memory element |
| Stuck-On Faults (SON) | A transistor is always conducting. |
| Delay Faults | A fault is caused by delays in one or more Gate/path in the circuit. |
| Pattern Sensitive Faults | Fault Model for Memory Arrays where data stored in some Cell(s) are affected by the stored Data Pattern in Neighboring Cells |

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 20

Single Stuck-at Fault (SSF) Model

- Three properties Characterize a Single-Stuck-at Fault (SSF)
 - Only one line is faulty
 - Faulty line has a Fixed 0 or 1 Value Independent of Other Signal Values
 - The fault can be at an input or output of a gate
- It is Technology-Independent.
- Experience shows that tests covering SSFs are Highly Likely to Detect Many Other Types of Non-Classical Faults.
- Many (But not All) Physical Faults (Defects Can be Represented by this Model.
- If Signal x is Stuck at value i , we Write x / I
- Every Line L Has 2 Possible Faults ($L / 0$), and ($L / 1$)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 21

Single Stuck-at Fault (SSF) Model Example



| Inputs AB | Fault-Free Response | Faulty Response | | | | | |
|--------------|------------------------|-----------------|-----|-----|-----|-----|-----|
| | | A/0 | B/0 | Z/0 | A/1 | B/1 | Z/1 |
| 00 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 01 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 10 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 11 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 22

Single Stuck-at Fault (SSF) Model Example –2

 - Example: XOR circuit has 12 fault sites (●) and 24 single stuck-at faults




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 23

SA Faults Example –3

 

| Input SAB | Response | | | | | | |
|--------------|----------|-----|-----|-----|-----|-----|-----|
| | FF | S/0 | S/1 | C/0 | C/1 | D/0 | D/1 |
| 000 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 001 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| 010 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 011 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 100 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 101 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 110 | 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 111 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 24

Mapping Physical Defect into Faults 1

● **Physical Defect**

● **Electrical**

● **Logical**

Physical Defect: Shorts O/P Node To GND Bus
Failure mode: Output Shorted To Ground (Z / 0)

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 25

Mapping Physical Defect into Faults 2

- **Physical defect:** A missing Poly Leg
 - Missing NMOS Transistor
- **Failure mode:** Output Shorted To Ground (Z / 0)

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 26

Mapping Physical Defect into Faults 1

- Both the defective resistances in bipolar and a the oxide breakdown in oxide between the source and drain of the NMOS transistor form a short failure mode
- Both cases Can Be Mapped into a stuck-at fault

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 27

Mapping Physical Defect into Faults 3

(a)

(b)

Stuck-at 1
V_{dd}

Stuck-at 0
GND

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 28

Multiple Stuck-at Faults

- A Multiple Stuck-at fault → any set of lines is stuck-at some combination of (0,1) values.

For a Circuit Having L lines, The Number of Possible Faults is

- > $2L$ Single-Stuck Faults
- > ${}^L C_2$ Double-Stuck Faults $\approx L^2/2$
- In General, the total number of single and multiple stuck-at faults in a circuit with k single fault sites is $3^k - 1$.
- Statistically, single fault tests cover a very large number of multiple faults.
- With Multiple Faults, a Test for some fault can fail to detect the target fault due to the presence of another → Masking


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 29

Multiple Stuck-at Faults & Fault Masking

 Example Fault $C \underline{S} _ @ _ 0$ ($C/0$) is Detectable By $TV=011$
The Same TV Cannot Detect the Multiple Faults $\{C/0, A/1\}$



Definition: Let T_g be the Set of All TVs that Detect Some Fault g . Another Fault f is said To *Mask* g iff the multiple fault $\{f, g\}$ is not detected by any TV in T_g

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 30

Bridging Fault Model

- This Model Deals with Shorts Bet 2 Lines
- Behavior of the Shorted Lines is Technology Dependent (Wired-OR & Wired-AND)
- Bridging Faults May Cause an Indeterminate Logic Value at the Faulty Lines (Midway Voltage Level)
- Bridging Faults can cause Feedback Loops Thus Converting a Combinational Circuit into a Sequential One



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 31