

DIGITAL SYSTEM TESTING COE -545

Lecture – 06-07

Test Generation (D-Algorithm)

The D-Algorithm

- An Algorithmic Approach which Generates a TV for a Given Fault if One Exists
- Multiple Path Sensitization
- 5-Valued Logic { 0, 1, X, D, \bar{D} }
- **D**: A Line is Assigned a **D** value if it has a value **1** in the **Fault-Free** Circuit but has a 0 Value in the **Faulty** Circuit.
($D \approx S_{@_0}$)
- **\bar{D}** : A Line is Assigned a **\bar{D}** value if it has a value **0** in the **Fault-Free** Circuit but has a 1 Value in the **Faulty** Circuit.
($\bar{D} \approx S_{@_1}$)
- D / \bar{D} Follow Rules of Boolean Algebra

The D-Algorithm

$D + D = D$	$\bar{D} + \bar{D} = \bar{D}$
$D \cdot D = D$	$\bar{D} \cdot \bar{D} = \bar{D}$
$\bar{D} + D = 1$	$D \cdot \bar{D} = 0$
$D \cdot 1 = D$	$\bar{D} \cdot 1 = \bar{D}$
$D \cdot 0 = 0$	$\bar{D} \cdot 0 = 0$
$D + 1 = 1$	$\bar{D} + 1 = 1$
$D + 0 = D$	$\bar{D} + 0 = \bar{D}$

•	0	1	D	\bar{D}	x
0	0	0	0	0	0
1	0	1	D	\bar{D}	x
D	0	D	D	0	x
\bar{D}	0	\bar{D}	0	\bar{D}	x
x	0	X	x	x	x


AND Operation of the
5-Valued D-Calculus

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 3


Example - Single Path Sensitization

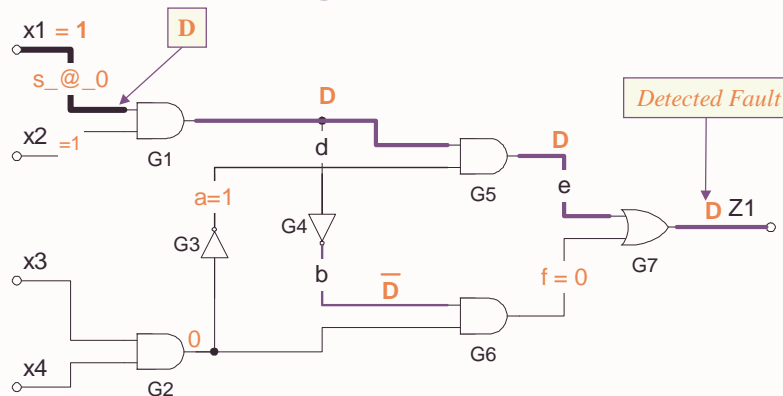

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 4

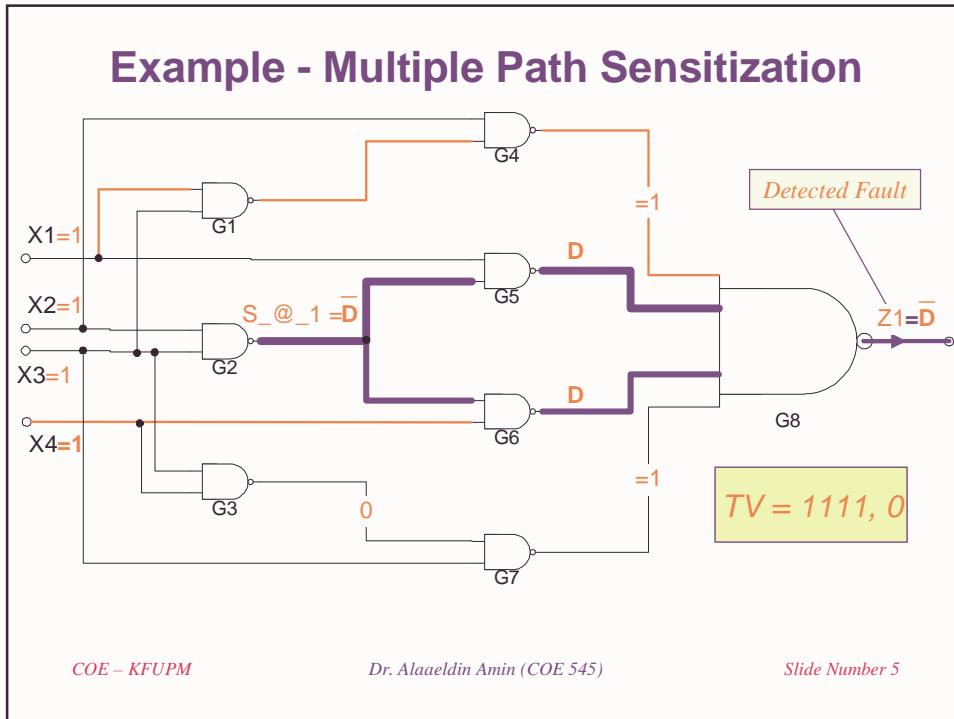

Definitions

1. Singular Covers (SC) of Some Function F
(Primitive Cubes of F) : Minimal Set of Logic Signal Assignments Showing Essential Prime Implicants
 = Prime Implicants of \overline{F} ($\alpha 1$) &&
 Prime Implicants of F ($\alpha 0$)

Examples Singular Covers of 2-Input NAND Gate


A	B	F
0	X	1
X	0	1
1	1	0

Pis of \overline{F} ($\alpha 0$)
 Pis of F ($\alpha 1$)

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 6

Definitions-- Singular Covers (SC) (Primitive Cubes)

Example

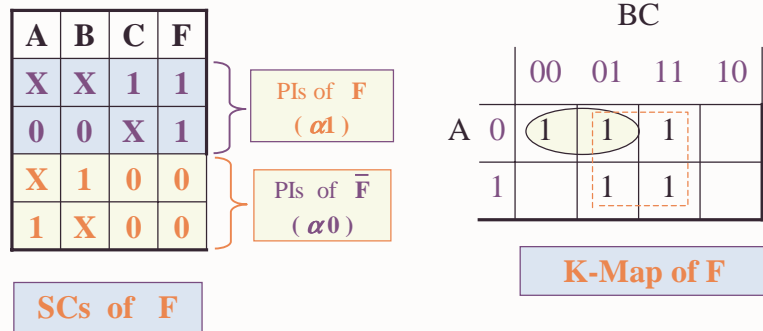

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 7



Definitions

2. Primitive D-Cubes of a Fault (PDCF)

= Prime Implicants of the *Faulty* Function
which Produce D / \bar{D} Output

{I/P. Stimuli Required to Activate Faulty Condition at a
Gate/Module Output}

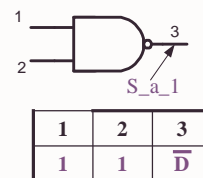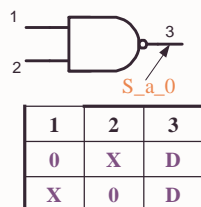Examples PDCF of 2-Input NAND Gate S_{a_0} & S_{a_1}



COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 8

Definitions -- Primitive D-Cubes of a Fault (PDCF)

Computing PDCF of a General Module (Function)

1. Obtain the SCs of the Fault-Free Function (α_1, α_0)
2. Obtain the SCs of the Faulty Function (β_1, β_0)
3. PDCF for this module Result from Intersecting α_1 with β_0 and α_0 with β_1 .

Thus

$$\text{PDCF} = \{ \alpha_1 \cap \beta_0, \alpha_0 \cap \beta_1 \}$$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 9

Definitions-- -- Primitive D-Cubes of a Fault (PDCF) -- Example

Example

A	B	C	F
X	X	1	1
0	0	X	1
X	1	0	0
1	X	0	0

Pls of F (α_1)

Pls of \bar{F} (α_0)

A	B	C	F
X	X	1	1
0	1	X	1
X	0	0	0
1	X	0	0

Pls of F_α (β_1)

Pls of \bar{F}_α (β_0)

PDCF

$\alpha_0 \cap \beta_1$

A	B	C	F
0	0	0	D
0	1	0	\bar{D}

$\alpha_1 \cap \beta_0$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 10

Definitions

3. Propagation D-Cube of a Gate/Module (PDC)


= Prime Implicants of the Function which Allow a D/\bar{D} Values on Inputs to Propagate to the Output

- Let $\{ \alpha_0, \alpha_1 \}$ be the Singular Covers of the Function F, Where;
 - α_1 = the Prime Implicants of F
 - α_0 = the Prime Implicants of \bar{F}

$$\text{PDC} = \{ \alpha_1 \cap \alpha_0 \}$$

Definitions-- Propagation D-Cube (PDC)

Example PDCF of 2-Input NAND Gate

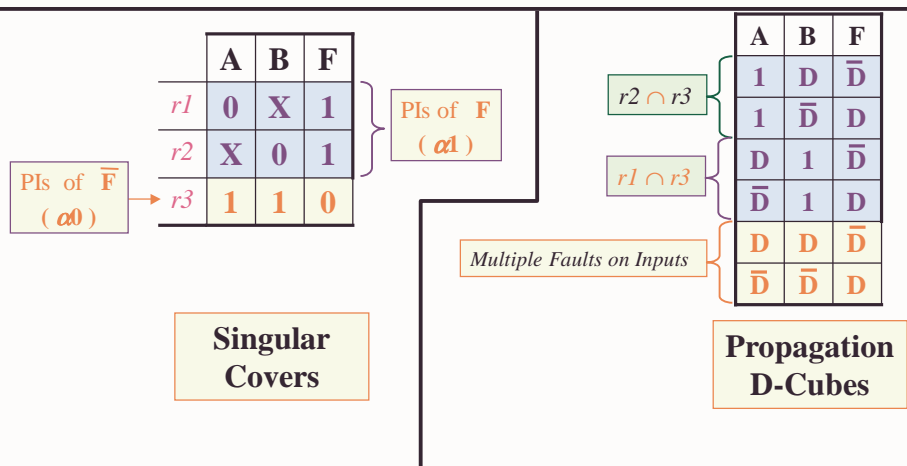

Intersection of D-Cubes

- Let $A = (a_1, a_2, a_3, \dots, a_n)$, and
- Let $B = (b_1, b_2, b_3, \dots, b_n)$ be 2 D-Cubes, where
 $a_i, b_i \in \{0, 1, x, D, \bar{D}\}$
- The D-intersection:** of A and B , denoted $A \cap B$ is given by $(a_i \cap b_i \mid a_i \in A, b_i \in B)$, where :
 - $x \cap a_i = a_i$
 - If $(a_i \neq x$ and $b_i \neq x)$ Then

$$a_i \cap b_i = \begin{cases} a_i & \text{IF } a_i = b_i \\ \Phi & \text{IF } a_i \neq b_i \end{cases}$$
 - $A \cap B = \Phi$ "Empty Cube" IF $a_i \cap b_i = \Phi$ For Any i

COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 13

D- Intersection

- D-Intersection is Used to Generate Sensitized Paths (**D-Drive**)

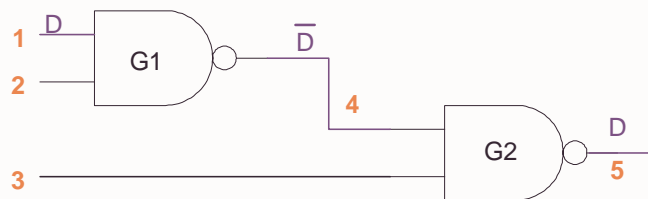Example PDC of 2-Input NAND Gate \rightarrow



A	B	F
1	D	\bar{D}
1	\bar{D}	D
D	1	\bar{D}
\bar{D}	1	D
D	D	\bar{D}
\bar{D}	\bar{D}	D

$$\begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline D & 1 & x & \bar{D} & x \\ \hline \end{array} \cap \begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline x & x & 1 & \bar{D} & D \\ \hline \end{array} = \begin{array}{|c|c|c|c|c|} \hline 1 & 2 & 3 & 4 & 5 \\ \hline D & 1 & 1 & \bar{D} & D \\ \hline \end{array}$$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 14

D- Algorithm

1. Initialize Test Cube to all x 's ($x, x, x, \dots x$)
2. Fault Provoking \rightarrow Select a Primitive D-Cube of the Fault (PDCF) \rightarrow Usually a *Choice Step*
3. Path Sensitization From the Faulty Line To a **PO**
 - \triangleright Successive X-ion of Test Cube with the Propagation D-Cubes of Successor Gates (*D-Frontier*) Till a **PO** Gets a **D** / $\bar{\mathbf{D}}$ Value (*Choice Step*) \rightarrow This Step is known as *D-Drive*
 - \triangleright This Step Requires 2 Major Procedures
 - a. Implication (Forward and Backward), and
 - b. Line Justification (*Consistency Checks*) \rightarrow May Lead to *Backtracks* if Inconsistencies are Detected.

COE – KFUPM


Dr. Alaaeldin Amin (COE 545)

Slide Number 15

Implication

- Assignments Made Due to Choices, e.g.a Propagation D-Cube, Usually Uniquely Imply Other Signal Values {Forward & Backward}

Example

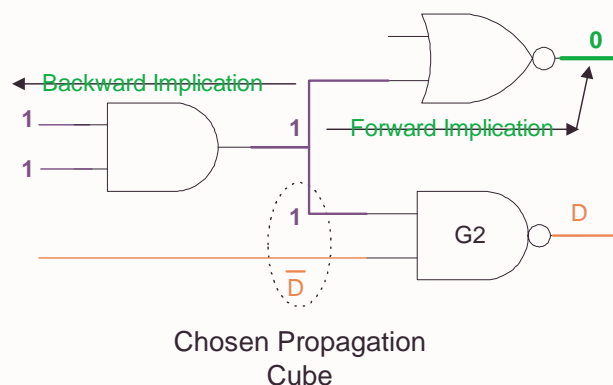

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 16

D-Frontier

- The **D-Frontier** Consists of **ALL** Gates whose Current O/P Value is “x” but have one or more **D/ \bar{D}** on their inputs
- One of the **D-Frontier** Gates is Usually Chosen to Propagate The Fault → “**D-Drive**”

Line Justification

Is a Backward *Implication Step* Where The Gate I/P Values are Selected *To Justify* the Specified Gate Output. This Step is Repeated Till the Relevant **PIs** are Defined.


- *Line Justification* is Performed after **D/ \bar{D}** Appear at Some **PO**.

Line Justification-Example

- An Unjustified Line is a Defined Gate Output which is not Implied By The Gate Inputs

J-Frontier

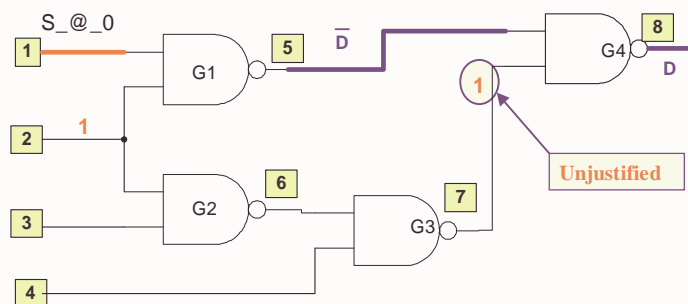Is the Set of **ALL** Gates whose Output Lines are *Unjustified*



Line Justification

Example (Line Justification) → Line 1 S_@_0

$t^0 = \text{PDFC}^1$

1	2	3	4	5	6	7	8
D	1			\bar{D}			
D	1			\bar{D}		1	D

J-Frontier = {G3} “Line 7 Unjustified”

Either Line 4 = 0, OR

Line 6=0

$t^2=t^1 \cap S c^3$	1	2	3	4	5	6	7	8	J_F={G ₂ }
	D	1	x	x	\bar{D}	0	1	D	
$t^3=t^2 \cap S c^2$	1	2	3	4	5	6	7	8	J_F={Φ}
	D	1	1	x	\bar{D}	0	1	D	

D-Drive

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 19

NOTES on D-ALGORITHM

1. Exhaustive Search of All Possible Choices
2. Guaranteed to Find a Solution (TV) *IF One Exists.*
3. Stops As Soon As A Solution Is Found
4. Being Exhaustive, the Worst Case Complexity is Exponential in the # of Gates
5. The Best Case Behavior Occurs When a Solution IS Generated **WITHOUT ANY BACKTRACKING:**
 - Always Correct Decisions Are Made
 - Solution Is Obtained Only Through Forward & Backward Implication.

NOTES on D-ALGORITHM

6. THUS, the # of Backtracks Determines the Complexity of the Algorithm (Should be Minimized).
7. An Upper Limit is Placed on the # of Backtracks Beyond Which a Fault Is Declared UNTESTABLE!
8. To Minimize the # of Backtracks, It is Advisable to Discover Inconsistencies as Early as Possible Through *Forward & Backward Implications for Each Change in the Test Cube*

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 21



Outline of D-Algorithm

1. Model Fault with appropriate *Primitive D-cube of Fault* (PDCF)
2. Select *Propagation D-cubes* to Propagate fault effect to a circuit output (*D-drive* procedure)
3. Select *singular cover* cubes to justify internal circuit signals (*Line Justification / Consistency* procedure)
 - Put Signal Assignments in *Test Cube*
 - Regrettably, Cubes Are Selected Very Arbitrarily by D-ALG

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 22

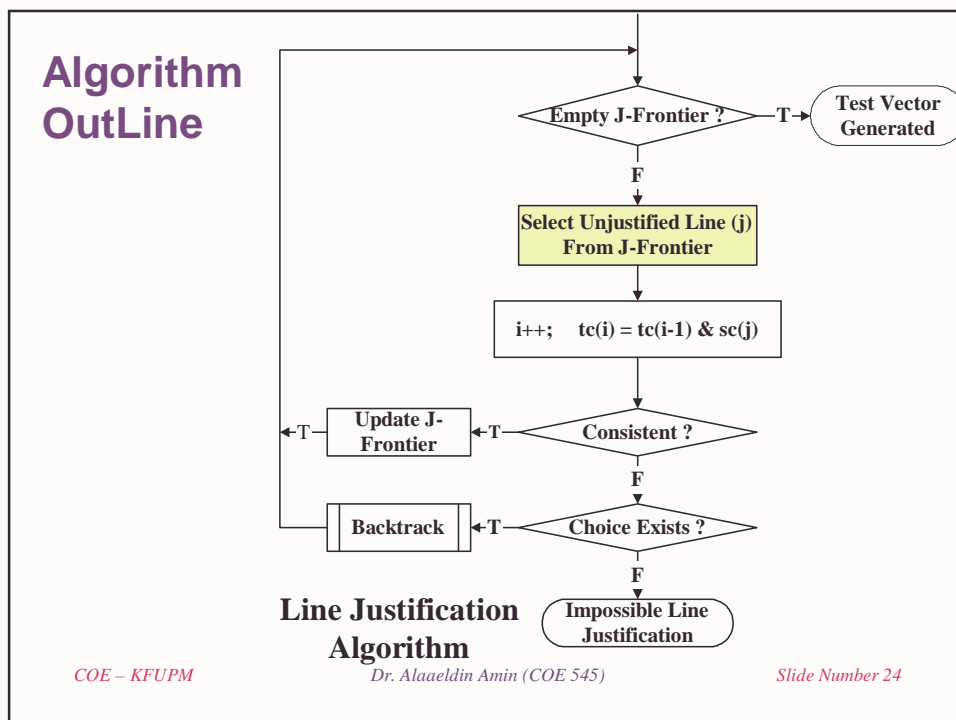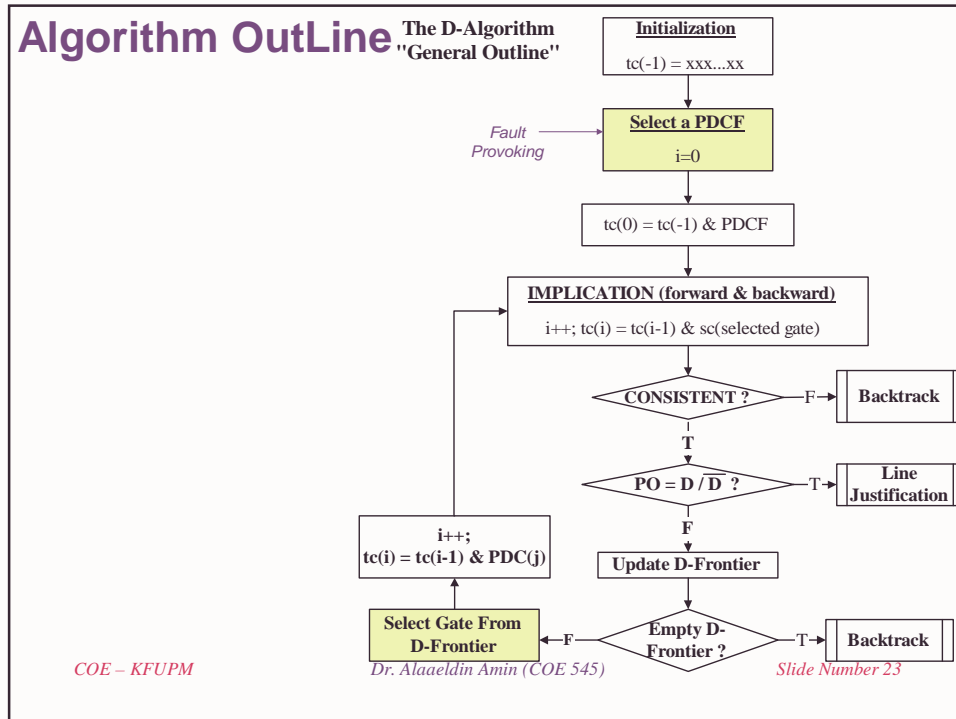


D-Algorithm – Top Level

1. Levelize the Circuit (Gates are Defined in Levels)
 - Primary Inputs Are Assigned a Zero Level
 - Level of a Gate = Max(Levels of Gate Input Signals) + 1
2. Number All Circuit Lines in Increasing Level Order From PIs to POs;
3. Initialize the **Test Cube** (t^{-1}) to All x 's;
4. Select a Primitive D-cube of the Fault (**PDCF**) and Generate the new **Test Cube** (t^0); -- **Choice**
 - Construct the initial *D-Frontier*;
5. **D-drive** (); -- *Generate a Chain of PDC from Fault to a PO*
6. **Consistency** (); -- *Justify Unjustified Gate Outputs*
7. **Return** ();

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 25

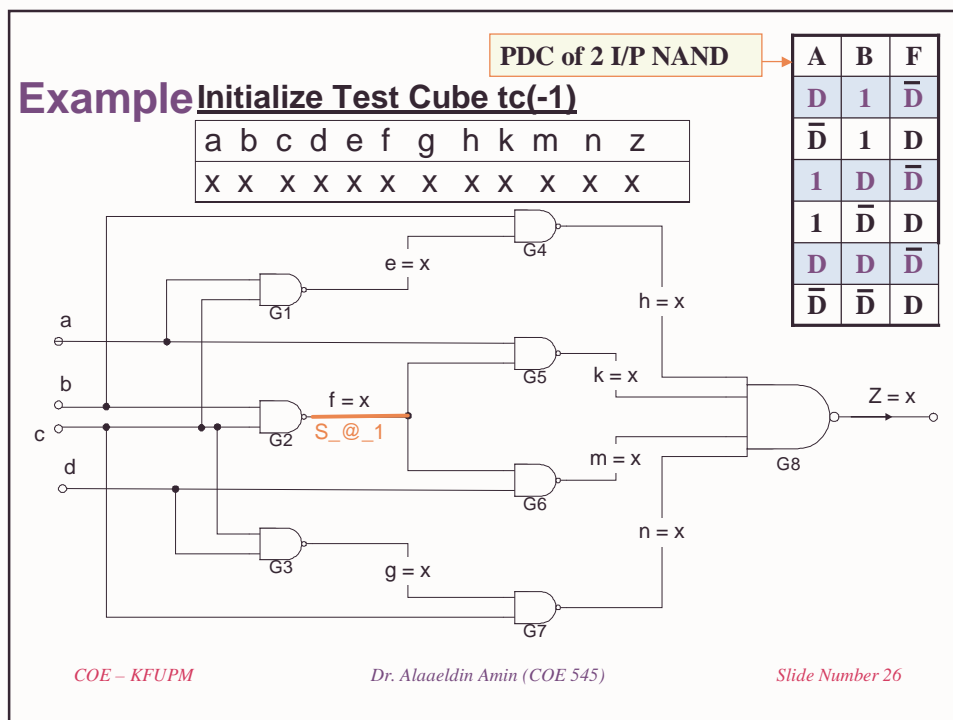

Example

Excite (Provoke) the Fault
(Select a PDCF)

	a	b	c	d	e	f	g	h	k	m	n	z
tc(-1)	x	x	x	x	x	x	x	x	x	x	x	x
PDCF(G2)		1	1			DB						
tc(0) = tc(-1) & PDCF	x	1	1	x	x	DB	x	x	x	x	x	x
D - Frontier	{G5, G6}											
J - Frontier	{}											

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 27

Example

D-Drive

	a	b	c	d	e	f	g	h	k	m	n	z
tc(0)	x	1	1	x	x	DB	x	x	x	x	x	x
PDC(G5)		1				DB			D			
tc(1) = tc(0) & PDC(G5)	1	1	1	x	x	DB	x	x	D	x	x	x
D - Frontier	{G8, G6}											
J - Frontier	{}											

Propagate Fault (D-Drive)
(Select D-Frontier Gate $\{G5, G6\}$)
"CHOICE"

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 28

Example

	a	b	c	d	e	f	g	h	k	m	n	z
IMPLICATION (Forward) (Through G1)	1	1	1	x	x	DB	x	x	D	x	x	x
SC(G1)	1	1	1	0	0							
tc(2) = tc(1) & SC(G1)	1	1	1	x	0	DB	x	x	D	x	x	x
D - Frontier	{G8, G6}											
J - Frontier	{}											

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 29

Example

	a	b	c	d	e	f	g	h	k	m	n	z
IMPLICATION (Forward) (Through G4)	1	1	1	x	0	DB	x	x	D	x	x	x
SC(G4)	1	1	1	0	0			1				
tc(3) = tc(2) & SC(G4)	1	1	1	x	0	DB	x	1	D	x	x	x
D - Frontier	{G8, G6}											
J - Frontier	{}											

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 30

Example

	a	b	c	d	e	f	g	h	k	m	n	z	
tc(3)	1	1	1	x	0	DB	x	1	D	x	x	x	
PDC(G8)									1	D	1	1	DB
tc(4) = tc(3) & PDC(8)	1	1	1	x	0	DB	x	1	D	1	1	DB	
D - Frontier	{ }												
J - Frontier	{ G6 , G7 }												

Propagate Fault (D-Drive)
(Select D-Frontier Gate "CHOICE")

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 31

Example


	a	b	c	d	e	f	g	h	k	m	n	z
tc(4)	1	1	1	x	0	DB	x	1	D	1	1	DB
SC(G7)			1				0				1	
tc(5) = tc(4) & SC(G7)	1	1	1	x	0	DB	0	1	D	1	1	DB
D - Frontier	{ }											
J - Frontier	{ G6 , G3 }											

Line Justification
(Select J-Frontier Gate "CHOICE")

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 32


Example

	a	b	c	d	e	f	g	h	k	m	n	z
tc(5)	1	1	1	x	0	DB	0	1	D	1	1	DB
SC(G6)				0	x					1		
tc(6) = tc(5) & SC(G6)	1	1	1	0	0	DB	0	1	D	1	1	DB
D - Frontier	{ }											
J - Frontier	{G3}											

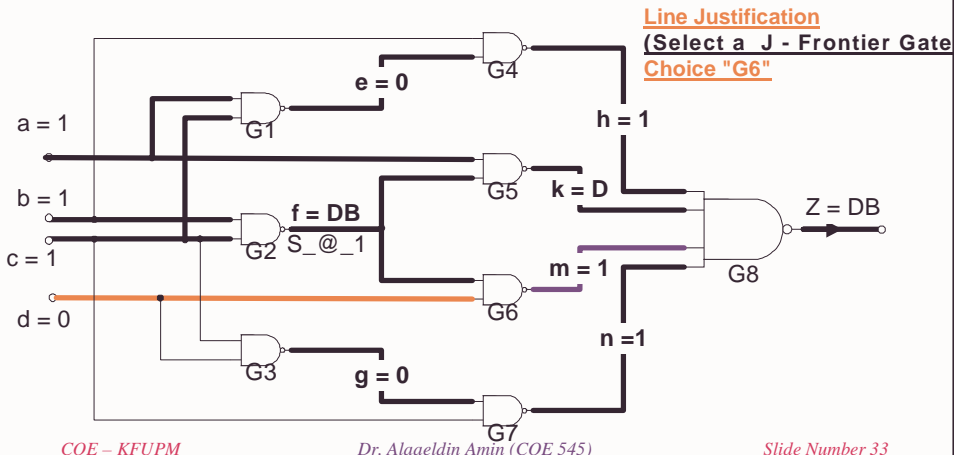

Example

	a	b	c	d	e	f	g	h	k	m	n	z
tc(6)	1	1	1	0	0	DB	0	1	D	1	1	DB
SC(G3)			1	0			1					
tc(7) = tc(6) & SC(G3)	INCONSISTENCY											
D - Frontier	{ }											
J - Frontier	{G3}											

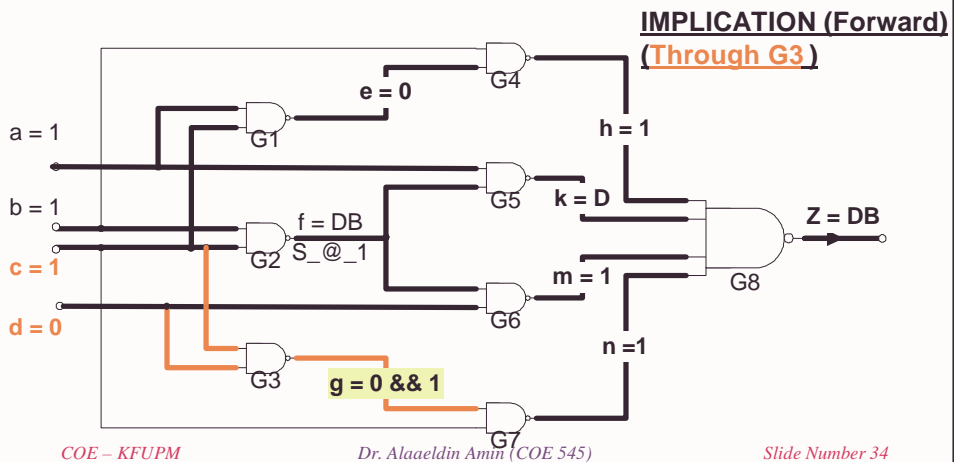

Example

1. **Inconsistency** → **Backtrack** to the Last Choice Step
 - Line Justification Choice of G6 or G3 → Choice was G6
 - Backtrack and Choose G3 instead for Line Justification
2. Another **Inconsistency** Develops → **Backtrack** to the Last Choice Step
 - Line Justification Choice of G6 or G7 → Choice was G7
 - Backtrack and Choose G6 instead for Line Justification
3. Another **Inconsistency** Develops → **Backtrack** to the Last Choice Step
 - D-Drive Choice of G6 or G8 → Choice was G8
 - Backtrack to D-Drive Step and Choose G6 instead


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 35

Example

	a	b	c	d	e	f	g	h	k	m	n	z
tc(3)	1	1	1	x	0	DB	x	1	D	x	x	x
PDC(G6)				1		DB				D		
tc(4)= tc(3) & PDC(G6)	1	1	1	1	0	DB	x	1	D	D	x	x
D - Frontier	{G8 }											
J - Frontier	{ }											

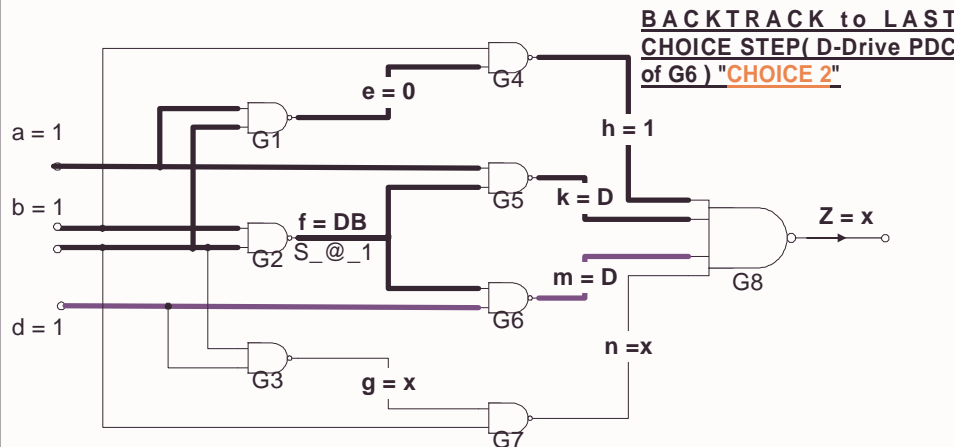


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 36


Example

	a	b	c	d	e	f	g	h	k	m	n	z
tc(4)	1	1	1	1	0	DB	x	1	D	D	x	x
SC(G3)			1	1			0					
tc(5) = tc(4) & SC(G3)	1	1	1	1	0	DB	0	1	D	D	x	x
D - Frontier	{G8}											
J - Frontier	{}											

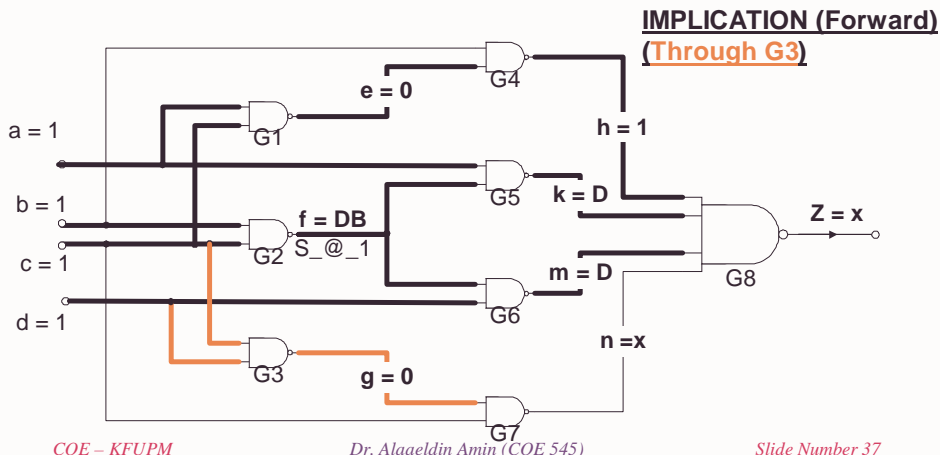

Example

	a	b	c	d	e	f	g	h	k	m	n	z
tc(5)	1	1	1	1	0	DB	0	1	D	D	x	x
SC(G7)			1				0				1	
tc(6) = tc(5) & SC(G7)	1	1	1	1	0	DB	0	1	D	D	1	x
D - Frontier	{G8}											
J - Frontier	{}											

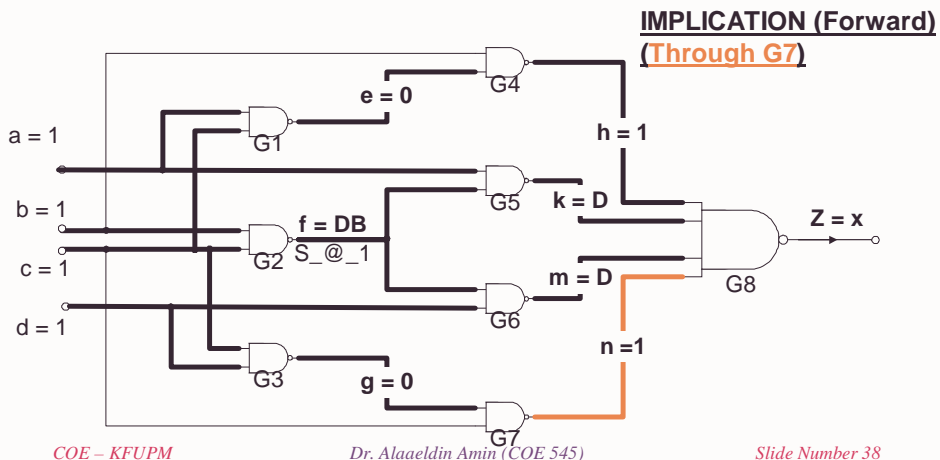

Example

	a	b	c	d	e	f	g	h	k	m	n	z
tc(6)	1	1	1	1	0	DB	x	1	D	D	x	x
PDC(G8)								1	D	D	1	DB
tc(7)= tc(6) & PDC(G8)	1	1	1	1	0	DB	0	1	D	D	1	DB
D - Frontier	{ }											
J - Frontier	{ }											

Propagate Fault (D-Drive Through G8)

Line Justification (Consistency Check)

All Lines are Consistent



COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 39

Implication Stack

- **Push-down stack. Records:**
 - Each signal set in circuit by ATPG
 - Whether alternate signal value already tried
 - Portion of binary search tree already searched

Signal	Value	Alternative tried
A	1	NO
C	1	NO
E	1	NO
B	0	YES

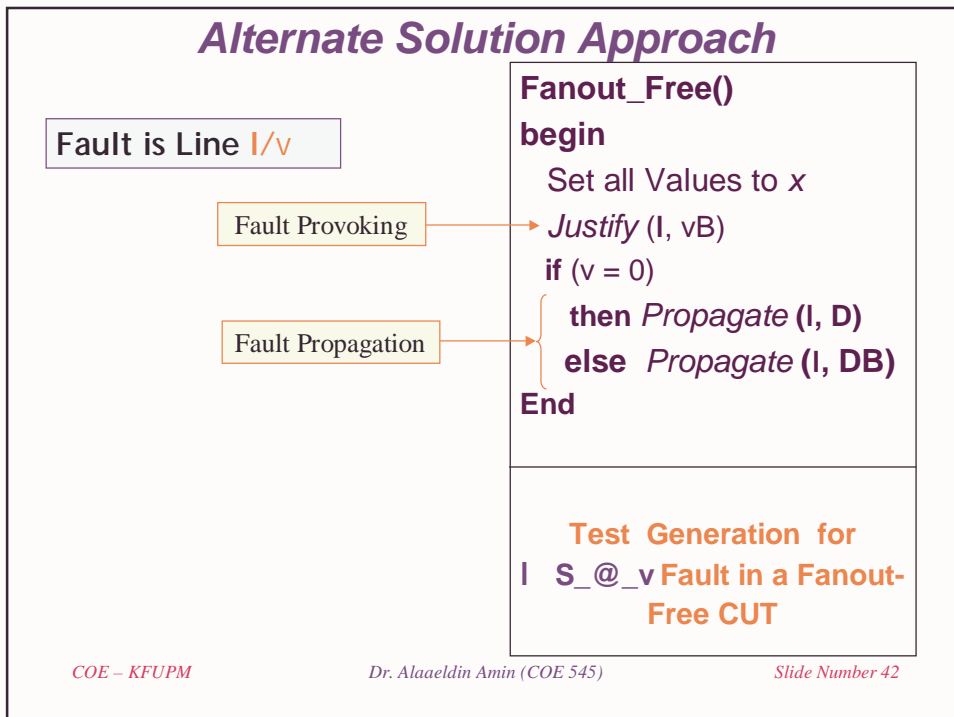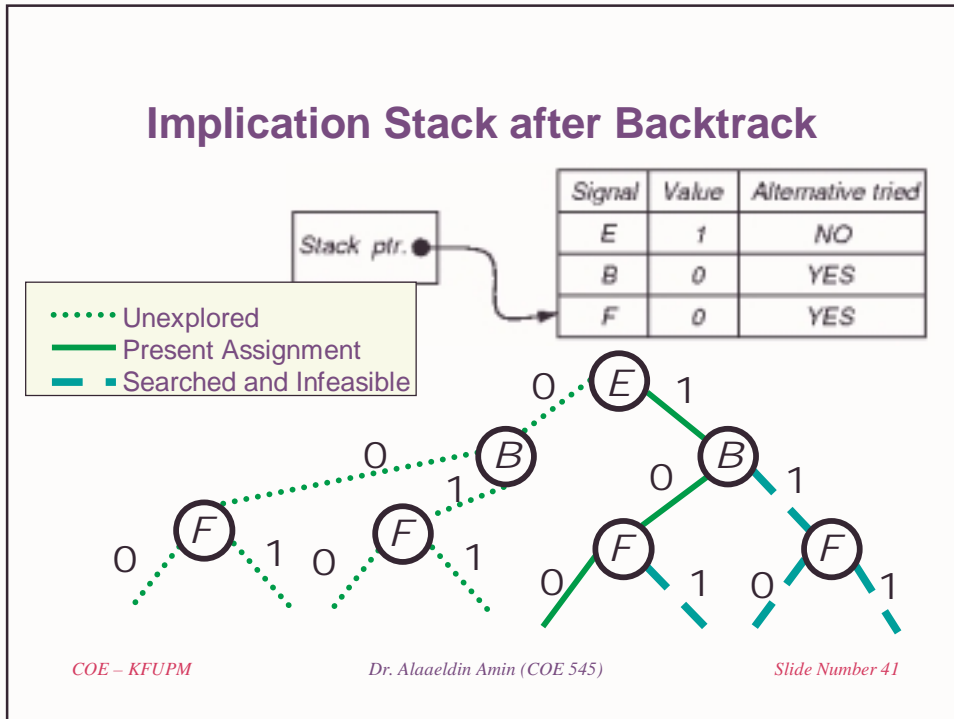COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 40



Alternate Solution Approach

• Justify is a Recursive Procedure

C	i	Gate
0	0	AND
0	1	NAND
1	0	OR
1	1	NOR

Justify(I, val) -- For Fanout-Free CUTs

Begin

I = val

If (I is PI) **then return**

/ (I is a Gate Output */*

C = Control Value of I

i = inversion of I

$inval = val \oplus i$

if (inval = not(c))

then for Every I/P j of I

Justify(j, inval)

else

begin

Select *One* I/P j of I

Justify(j, inval)

end

end

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 43

Alternate Solution Approach

Fault Propagation Problem
Converted into a Line-Justification Problem

Propagate(I, err)

-- For Fanout-Free CUTs

/ err is D or DB */*

Begin

I = err

If (I is PO) **then return**

k = Fanout Gate of I

C = Control Value of k

i = inversion of k

For Every I/P j of k **Other Than I**

▶ Justify(j, not(C))

Propagate(k, $err \oplus i$)

end

Reduces Fault Propagation to a set of line-justification problems

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 44

```
D-alg()
begin
if ( Imply_and_check() = FAILURE ) then return FAILURE
if (error not at PO) then begin
  if (D-frontier = void) then return FAILURE
  repeat
    begin
      select an untried gate(G) from D-frontier
      c = controlling value of G
      assign c to every input of G with value x
      if (D-alg() = SUCCESS) then return SUCCESS
    end
  until all gates from D-frontier have been tried
  return FAILURE
end
if (J-frontier = void) then return SUCCESS -- Fault Appeared at PO
select a gate (G) from J-frontier
c = controlling value of G
repeat
  begin
    select an input (j) of G with value x, assign c to j
    if (Solve() = SUCCESS) then return SUCCESS
    assign  $\bar{C}$  to j -- Reverse Decision
  end
until all inputs of G are specified
return FAILURE
end
```

Alternate Solution Approach

```
Solve()
begin
if (Imply_and_check() = FAILURE) then return FAILURE
if (error at PO and all lines are justified)
  then return SUCCESS
if (error can't be propagated to a PO)
  then return FAILURE
Select an unsolved problem
repeat
  begin
    select one untried way to solve it
    if (Solve() = SUCCESS) then return SUCCESS
  end
until all ways to solve it have been tried
return FAILURE
end
```

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 46