

**DIGITAL SYSTEM TESTING
COE -545**


Lecture – 05

Test Generation (Boolean Difference)

Combinational Circuit Testing

Basic Definitions

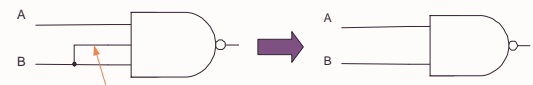- Let fault f change output $Z(X)$ of a circuit C to $Z_f(X)$.
- A TV t detects f if $Z(t) \neq Z_f(t) \rightarrow Z(t) \oplus Z_f(t) = 1$
- Fault f is Undetectable or Redundant if $Z(t) = Z_f(t) \forall t$.
- If the fault line x s-a-d is undetectable, then x and circuits feeding x can be removed from the circuit.




COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 2

Combinational Circuit Testing

Another Example

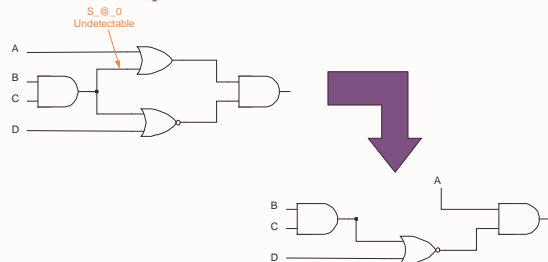


COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 3

Redundancy

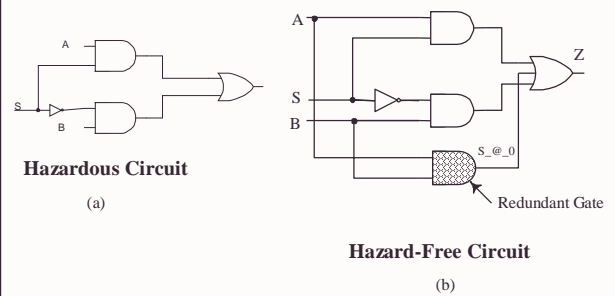

Hazardous Circuit

(a)

Hazard-Free Circuit

(b)

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 4

Combinational Circuit Testing

Basic Definitions (cont'd)

- A set of tests $T = \{t_1, t_2, \dots, t_k\}$ is **complete** if it detects (covers) all detectable SSL faults in the circuit
- We can represent any test set $\{t_1, t_2, \dots, t_k\}$ by the Boolean function whose minterms are $\{t_1, t_2, \dots, t_k\}$.
- **Example**, the function $Z(a,b,c,d) = a'bd' + abcd$ denotes the 3-member test set $\{0100, 0110, 1111\}$.
- The set of all TVs for fault f is expressed by the Boolean function $(Z(x) \oplus Z_f(x))$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 5

Example

- Fault-Free Fun = $F(a,b,c) = (a+b)(b+c)$
- **Fault** = $b/0$
- **Faulty Fun** = $F_\alpha = ac$
- TVs Detecting this Fault Should Satisfy: $(F \oplus F_\alpha) = 1$
- Thus, $(a+b)(b+c) \oplus ac = B(A' + C')$
- This represents 2 possible Tests
- TV set for $a/1 = \{01x, x10\} \rightarrow \{010, 011, 110\}$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 6

Boolean Difference Method

- Fault-Free Fun = $F(x_1, x_2, \dots, x_n)$
- Assuming a SSL Fault $x_i/1$
- $F_\alpha = F(x_i=1) = F(x_1, x_2, \dots, 1, \dots, x_n) = F_i(1)$
- Assuming a SSL Fault $x_i/0$
- $F_\alpha = F(x_i=0) = F(x_1, x_2, \dots, 0, \dots, x_n) = F_i(0)$
- According to Shannon's Expansion Theorem:
 $F(x_1, x_2, \dots, x_n) = x_i F_i(1) + \bar{x}_i F_i(0)$
- Thus, the Test Set to Detect $x_i/0$ corresponds to :
 $T_0 = x_i (F_i(1) \oplus F_i(0))$, Likewise
- The Test Set to Detect $x_i/1$ corresponds to :
 $T_1 = \bar{x}_i (F_i(1) \oplus F_i(0))$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 7

Boolean Difference Method

- The Expression $(F_i(1) \oplus F_i(0))$ is Termed the Boolean Difference of F wrt x_i , or (dF/dx_i)
- Thus, the Test Set to Detect $x_i/0$ corresponds to :

$$T_0 = x_i \cdot (dF/dx_i)$$

The Test Set to Detect $x_i/1$ corresponds to :

$$T_1 = \bar{x}_i \cdot (dF/dx_i)$$

Notes:

- The x_i 's are Primary Inputs
- A Fault on some PI (x_i) is Undetectable iff

$$F_i(1) = F_i(0) \quad \text{OR} \quad dF/dx_i = 0$$

Which Means that **F is INDEPENDENT OF x_i**

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 8

Example

- Fault = a/1
- Fault-Free Fun= $F(a,b,c,d) = (a + bc)(b' + c')d'$
- $T(a/1) = a'.dF/da$
- $dF/da = [1(b' + c')d' \oplus bc(b' + c')d'] = b'd' + c'd'$
- So $T(a/1) = a'b'd' + a'c'd'$
- Test set for a/1 = {00x0, 0x00} = {0000, 0010, 0100}

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 9

Boolean Difference Method

- Boolean Difference (BD) has the following Properties:
 1. $d\bar{F}/dx_i = dF/dx_i$
 2. $d/dx_i[dF/dx_j] = d/dx_j[dF/dx_i]$
 3. $d[F(X) \oplus G(X)]/dx_i = dF/dx_i \oplus dG/dx_i$
 4. $d[F(X).G(X)]/dx_i = F.dG/dx_i \oplus G.dF/dx_i \oplus dF(X)/dx_i .dG(X)/dx_i$
 5. $d[F(X) + G(X)]/dx_i = \bar{F}.dG/dx_i \oplus \bar{G}.dF/dx_i \oplus (dF/dx_i).(dG/dx_i)$

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 10

Example

- Fault = $\beta/0$
- $T(\beta/0) = \beta(X).dF(x, \beta)/d\beta$
 $\beta(X) = a + bc$ $F(x, \beta) = (b' + c')d' \beta$
- $dF/d\beta = (b' + c')d'$
- So $T(\beta/0) = ab'd' + ac'd'$
- Test set for $\beta/0 = \{1000, 1010, 1100\}$

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 11

Test Generation Schemes

- BD method is more Theoretical → Too Complex to Use for Practical Circuits
- Need a More Practical Approach
- **Deterministic Test Generation**
 - Fault- Oriented ATG
 - Fault Independent ATG
- **Random Test Generation**
 - Combined Deterministic and Random Test Generation
- **ATG Systems**
- **Conclusions**

COE – KFUPM
Dr. Alaaeldin Amin (COE 545)
Slide Number 12

Classification & Problems

Testing

- Off- Line
- Edge- Pin
- Stored- Pattern
- Full Comparison of the Output Results

General Problems for TG:


- Cost of Generating the Test
- Quality of the Generated Test
- Cost of Applying the Test

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 13

Deterministic Test Generation

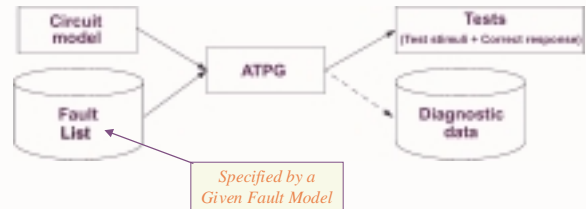


- Manual / Automatic
 - Automatic Test Pattern Generation (ATPG)
- Deterministic ATPG Can Be Fault- Oriented / **Fault-Independent**

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 14

Fault-Oriented ATPG

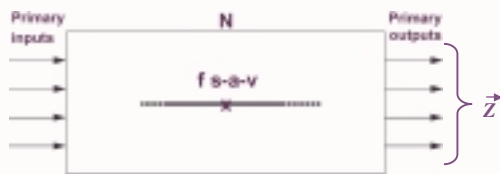

- Targets a Particular Fault $f \in \{ \text{Fault List} \}$
 - Finds a TV t which Detects f
 - t Detects $f \Leftrightarrow Z(t) \neq Z_f(t) \Leftrightarrow Z(t) \oplus Z_f(t) = 1$

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Slide Number 15

TV Generation

- Two Steps Are Necessary to Generate TV t which Detects Fault f :
 - Fault Activation/excitation/provoking: Effecting a Different Value \bar{v} at the Faulty Line x When x Is Stuck at v .
 - Fault Propagation: Propagating Error to an Observable PO

Definitions

- A Line whose Value under TV t Changes in the Presence of Fault f is Said to Be Sensitized to the Fault f by the Test t
- A Path Composed of Sensitized Lines Is Called a Sensitized Path

COE – KFUPM

Dr. Alaaeldin Amin (COE 545)

Single Path Sensitization

Example

- Fault Activation → **X1=1**
- Fault Propagation → 2 Possible Options (Paths)
 - Option 1: G1 – G5 – G7
 - Option 2: G1 – G4 – G6 – G7

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 17

Single Path Sensitization Option 1

Example

- Fault Activation → X1=1
- Fault Propagation : G1 – G5 – G7 → *Two Possible TVs*
 - T1 = 110X , 1
 - T2 = 11X0 , 1

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 18

Single Path Sensitization Option 2

Example

- Fault Activation → X1=1
- Fault Propagation : G1 – G4 – G6 - G7
→ *One Possible TV* → T = 1111 , 0


COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 19

Multiple Path Sensitization

Major Problem with Single Path Sensitization

- A TV May not be Possible to Generate for Some *Testable* Faults if Only One Path is Sensitized at a Time

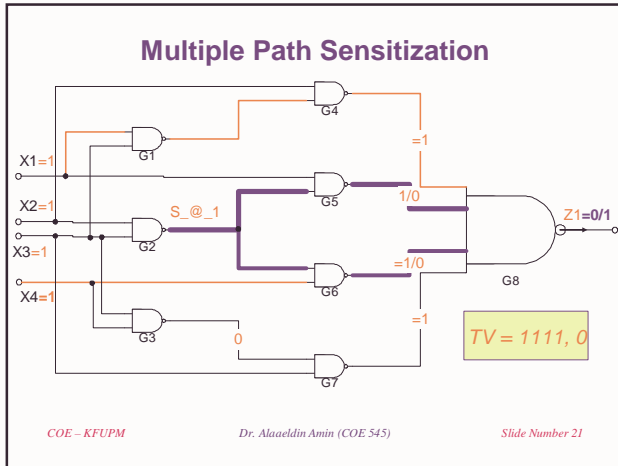COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 20



The D-Algorithm

- An Algorithmic Approach which Generates a TV for a Given Fault if One Exists
- Multiple Path Sensitization
- 5-Valued Logic { 0, 1, X, D, \bar{D} }
- **D**: A Line is Assigned a **D** value if it has a value **1** in the **Fault-Free** Circuit but has a **0** Value in the **Faulty** Circuit. ($\bar{D} \approx S_{_@_0}$)
- **\bar{D}** : A Line is Assigned a **\bar{D}** value if it has a value **0** in the **Fault-Free** Circuit but has a **1** Value in the **Faulty** Circuit. ($\bar{D} \approx S_{_@_1}$)
- D / \bar{D} Follow Rules of Boolean Algebra

COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 22


The D-Algorithm


$D + D = D$	$\bar{D} + \bar{D} = \bar{D}$
$D \cdot D = D$	$\bar{D} \cdot \bar{D} = \bar{D}$
$\bar{D} + D = 1$	$D \cdot \bar{D} = 0$
$D \cdot 1 = D$	$\bar{D} \cdot 1 = \bar{D}$
$D \cdot 0 = 0$	$\bar{D} \cdot 0 = 0$
$D + 1 = 1$	$\bar{D} + 1 = 1$
$D + 0 = D$	$\bar{D} + 0 = \bar{D}$

•	0	1	D	\bar{D}	x
0	0	0	0	0	0
1	0	1	D	\bar{D}	x
D	0	D	D	0	x
\bar{D}	0	\bar{D}	0	\bar{D}	x
x	0	X	x	x	x

AND Operation of the 5-Valued D-Calculus

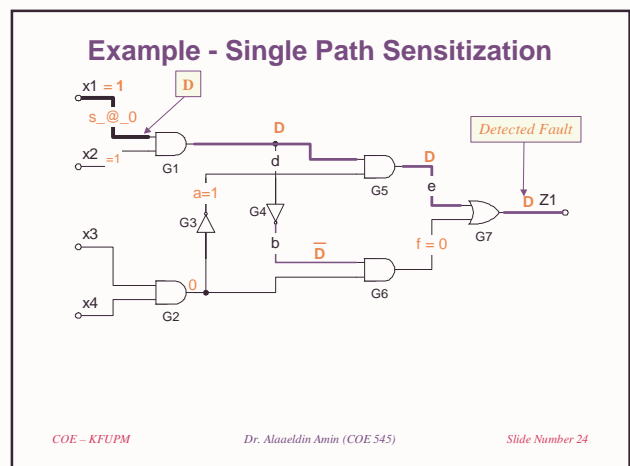COE – KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 23



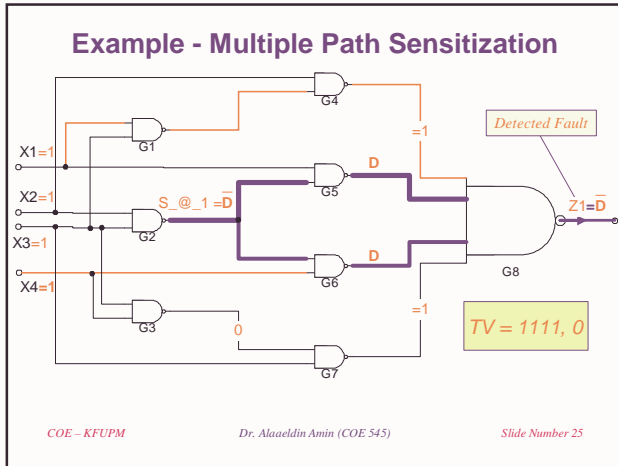

Definitions

1. Singular Covers (SC) of Some Function F
(Primitive Cubes of F) : *Minimal Set of Logic Signal Assignments Showing Essential Prime Implicants*
 = Prime Implicants of \overline{F} ($\alpha 1$) &&
 Prime Implicants of $\overline{\overline{F}}$ ($\alpha 0$)

Examples Singular Covers of 2-Input NAND Gate

A	B	F
0	X	1
X	0	1
1	1	0

Pis of \overline{F}
($\alpha 0$) → Pis of $\overline{\overline{F}}$
($\alpha 1$)

COE - KFUPM Dr. Alaaeldin Amin (COE 545) Slide Number 26