

# King Fahd University of Petroleum & Minerals Computer Engineering Dept

**COE 200 – Fundamentals of Computer  
Engineering**

**Term 021**

**Dr. Ashraf S. Hasan Mahmoud**

**Rm 22-144**

**Ext. 1724**

**Email: ashraf@ccse.kfupm.edu.sa**

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

1

## Flip-Flop Characteristic Tables

Table 4-1

(a) JK Flip-Flop				(b) SR Flip-Flop			
J	K	Q(t+1)	Operation	S	R	Q(t+1)	Operation
0	0	Q(t)	No change	0	0	Q(t)	No change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	Q'(t)	Complement	1	1	?	Undefined
(c) D Flip-Flop			(d) T Flip-Flop				
D	Q(t+1)	Operation	T	Q(t+1)	Operation		
0	0	Reset	0	Q(T)	No change		
1	1	Set	1	Q'(t)	Complement		

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

2

## JK Flip-Flop Characteristic Equation (Refer to Problem 4-10)

- Using table 4-1 (previous slide), one can write:

KQ(t)	00	01	11	10
J				
0	0	1	0	0
1	1	1	0	1

J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q(t+1) = J\overline{Q(t)} + \overline{K}Q(t)$$

## SR Flip-Flop Characteristic Equation (Refer to Problem 4-10)

- Using table 4-1 (previous slide), one can write:

RQ(t)	00	01	11	10
S				
0	0	1	0	0
1	1	1	X	X

S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

$$Q(t+1) = S + \overline{R}Q(t)$$

## **D Flip-Flop Characteristic Equation (Refer to Problem 4-10)**

- Using table 4-1 (previous slide), one can write:

$$Q(t+1) = D$$

D	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1

## **T Flip-Flop Characteristic Equation (Refer to Problem 4-10)**

- Using table 4-1 (previous slide), one can write:

$$Q(t+1) = T \oplus Q(t)$$

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

## Problem 4-10

- **Problem:** Write characteristic equations for each type of flip-flops, using the information in Table 4-1. A characteristic equation gives the function  $Q(t+1)$  in terms of  $Q(t)$  and the input variables to the flip-flop. Use the characteristic equation for the  $JK$  flip-flop to find equations  $A(t+1)$  and  $B(t+1)$  from the flip-flop input equations corresponding to Table 4-4.
- **Solution:**
  - a) Refer to previous slides for the development of characteristic equations

## Problem 4-10

- **Solution (cont'd):**

b)

- The columns  $J_A$ ,  $K_A$  (for flip flop A) and  $J_B$ ,  $K_B$  (for flip flop B) are obtained with the aid of the characteristic table

- From table:  $J_A = B(t)$ ,  $K_A = B(t)X'$ , while  $J_B = X'$ ,  $K_B = A(t)X' + A'(t)X$

- Using the characteristic equation for the A  $JK$  flip-flop:

$$A(t+1) = J_A A(t) + K_A' A(t) \rightarrow$$

$$A(t+1) = B(t)A(t) + (BX')'A(t) \\ = B(t)A(t) + B(t)'A(t) + XA(t)$$

- Same for the B  $JK$  flip-flop:

$$B(t+1) = J_B B(t) + K_B' B(t) \rightarrow$$

$$B(t+1) = X'B(t) + (A(t)X' + A'(t)X)B(t)$$

$$B(t+1) = X'B(t) + A(t)B(t)X + A'(t)B(t)X'$$

**Table 4-4**

Present State		Input X	Next State		Flip-Flop Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

This is input

This is derived from problem specification or state diagram

This is derived from characteristic table of the particular flip-flop

# Flip-Flop Excitation Tables

**Table 4-10**

(a) JK Flip-Flop				(b) SR Flip-Flop			
Q(t)	Q(t+1)	J	K	Q(t)	Q(t+1)	S	R
0	0	0	X	0	0	0	X
0	1	1	X	0	1	1	0
1	0	X	1	1	0	0	1
1	1	X	0	1	1	X	0

(c) D Flip-Flop			(d) T Flip-Flop		
Q(t)	Q(t+1)	D	Q(t)	Q(t+1)	T
0	0	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	1	1	1	1	0

# Sequence Recognizer


- **Problem:** Design a circuit to recognize the occurrence of the bits 1101 on an input line X by making an output signal Z equal to 1; Otherwise Z is equal to 0

- **Solution:**

Sequential circuit with one input X and one output Z

- Examples of operation:

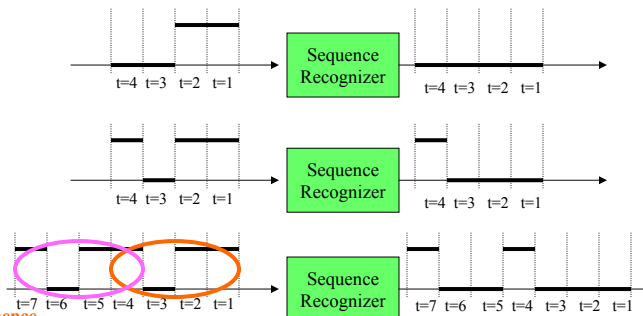1. No sequence – Z remains zero
2. sequence occurs – Z is one
3. Two overlapping sequences – Z is one twice!



## Sequence Recognizer – State Diagram

- Solution (cont'd):**


You always start from an initial state → State  $S_0$

To remember first '1' of sequence → State  $S_1$

To remember two consecutive 1s of sequence → State  $S_2$

To remember '110' sequence → State  $S_3$

 **Note** an arrival of  $S_1$  while in state  $S_3$  should make the output  $Z = 1$ , and move to state  $S_0$  to remember this '1' which could be the first digit of another 1101 sequence





1/6/2003

Dr. Ashraf S. Hasan Mahmoud

11

## Sequence Recognizer – State Table

- Solution (cont'd):**

  

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
$S_0$	$S_0$	$S_1$	0	0
$S_1$	$S_0$	$S_2$	0	0
$S_2$	$S_3$	$S_2$	0	0
$S_3$	$S_0$	$S_1$	0	1

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

12


## Sequence Recognizer – State Table (2)

### • Solution (cont'd):

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0	0
S <sub>1</sub>	S <sub>0</sub>	S <sub>2</sub>	0	0
S <sub>2</sub>	S <sub>3</sub>	S <sub>2</sub>	0	0
S <sub>3</sub>	S <sub>0</sub>	S <sub>1</sub>	0	1
 
### State Code Assignment (Grey Coding):

S<sub>0</sub> → 00  
 S<sub>1</sub> → 01  
 S<sub>2</sub> → 11  
 S<sub>3</sub> → 10



Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	00	11	0	0
11	10	11	0	0
10	00	01	0	1

1/6/2003

Dr. Ashraf S. Hasan Mahmoud


13

## Sequence Recognizer – State Table (3)

### • Solution (cont'd):

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	00	11	0	0
11	10	11	0	0
10	00	01	0	1

 -Another way of writing the state table  
 - Four states → we need two flip-flops A & B  
 (in general if number of states is n, then we require  $\log_2 n$  flip-flops)



Present State		Input X	Next State		Output Z
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	1	0

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

14

# Sequence Recognizer – Design Using D Flip-Flops

• **Solution (cont'd):**

Present State			Next State			Output
A	B	X	A	B	Z	
0	0	0	0	0	0	
0	0	1	0	1	0	
0	1	0	0	0	0	
0	1	1	1	1	0	
1	0	0	0	0	0	
1	0	1	0	1	1	
1	1	0	1	0	0	
1	1	1	1	1	0	

-The characteristic equation for the D flip-flop is  $Q(t+1) = D$   
 → The D input is the same as the desired next state

Present State			Next State			Output	D Flip-Flops Input	
A	B	X	A	B	Z	D <sub>A</sub>	D <sub>B</sub>	
0	0	0	0	0	0	0	0	
0	0	1	0	1	0	0	1	
0	1	0	0	0	0	0	0	
0	1	1	1	1	0	1	1	
1	0	0	0	0	0	0	0	
1	0	1	0	1	1	0	1	
1	1	0	1	0	0	1	0	
1	1	1	1	1	0	1	1	

(c) D Flip-Flop

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1



# Sequence Recognizer – Design Using D Flip-Flops (2)

• **Solution (cont'd):**

Present State			Next State			Output	D Flip-Flops Input	
A	B	X	A	B	Z	D <sub>A</sub>	D <sub>B</sub>	
0	0	0	0	0	0	0	0	
0	0	1	0	1	0	0	1	
0	1	0	0	0	0	0	0	
0	1	1	1	1	0	1	1	
1	0	0	0	0	0	0	0	
1	0	1	0	1	1	0	1	
1	1	0	1	0	0	1	0	
1	1	1	1	1	0	1	1	

-Use K-maps to get D<sub>A</sub> and D<sub>B</sub> in terms of the states A and B and the input X  
 -Use K-map to get Z in terms of states A and B and the input X

BX	00	01	11	10
A				
0	0	0	1	0
1	0	0	1	1

D<sub>A</sub> = AB + BX

BX	00	01	11	10
A				
0	0	1	1	0
1	0	1	1	0

D<sub>B</sub> = X

BX	00	01	11	10
A				
0	0	0	0	0
1	0	1	0	0

Z = AB'X






## Sequence Recognizer – Design Using *D* Flip-Flops (3)

### • Solution (cont'd):

$$D_A = AB + BX$$

$$D_B = X$$

$$Z = AB'X$$

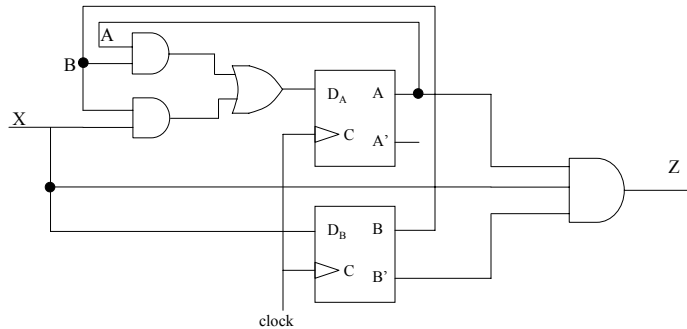

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

17

## Sequence Recognizer – Design Using *JK* Flip-Flops

### • Solution (cont'd):

-Use the excitation table for the *JK* flip-flop  
-To fill the *J/K* entries for each flip-flop

Present State			Input X	Next State		Output Z
A	B	A		B		
0	0	0	0	0	0	
0	0	1	0	1	0	
0	1	0	0	0	0	
0	1	1	1	1	0	
1	0	0	0	0	0	
1	0	1	0	1	1	
1	1	0	1	0	0	
1	1	1	1	1	0	

(a) *JK* Flip-Flop

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



Present State			Input X	Next State		Output Z	<i>JK</i> Flip-Flop Input		<i>JK</i> Flip-Flop Input	
A	B	A		B	J <sub>A</sub>		K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	
0	0	0	0	0	0	0	X	0	X	
0	0	1	0	1	0	0	X	1	X	
0	1	0	0	0	0	0	X	X	1	
0	1	1	1	1	1	0	1	X	0	
1	0	0	0	0	0	X	1	0	X	
1	0	1	0	1	1	X	1	1	X	
1	1	0	1	0	0	X	0	X	1	
1	1	1	1	1	0	X	0	X	0	

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

18



## Serial Two's Complementer – Problem 4-20

- Problem:** A serial two's complementer is to be designed. A binary integer of arbitrary length is presented to the serial two's complementer least significant bit first on input X. When a given bit is presented on input X, the corresponding output bit is to appear during the same clock cycle on output Z. To indicate that a sequence is complete and that the circuit is to be initialized to receive another sequence, input Y becomes 1 for one clock cycle. Otherwise, Y is 0
  - Find the state diagram for the serial two's complementer
  - Find the state table for the serial two's complementer
  - Design the circuit using *D* flip-flops
  - Design the circuit using *JK* flip-flops

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

21

## Serial Two's Complementer – Problem 4-20

- Solution:**


Remember to complement  $A_n A_{n-1} \dots A_1 A_0$ , we scanned the binary digits from LSB to MSB, skipping all zeros and passing the first 1 bit. All subsequent bits are complemented. The result is the two's complement of  $A_n A_{n-1} \dots A_1 A_0$

Example: 2's complement of (10110100) is equal to (01001100)

Example: 2's complement of (0011) is equal to (1101)

Example: 2's complement of (000) is equal to (000)

 Example: 2's complement of (10) is equal to (10)



1/6/2003

Dr. Ashraf S. Hasan Mahmoud

22

## Serial Two's Complementer – Problem 4-20 – State Diagram

- Solution (cont'd):**

Two inputs X: the binary bits in serial

Y: indicator when number is complete


Scanning the binary number, we switch between two modes:

copying binary digits till first 1 is found

inverting subsequent bits

Hence TWO states are needed – need to remember that we passed the one

 Because we have four inputs, each state has FOUR departing arcs



1/6/2003

Dr. Ashraf S. Hasan Mahmoud

23

## Serial Two's Complementer – Problem 4-20 – State Diagram (2)

- Solution (cont'd):**

State  $S_0$ : initial state (copying X to Z without inverting bits)


1. if zero arrives (input patterns 00 or 01) on X it is copied to Z –

2. if one arrives (input pattern 11) on X it is also copied to Z if Y is 1 (i.e last bit of number)

 3. if one arrives and it is not last bit (input pattern 10) then it is copied to Z but circuit moves to the other state – to start complementing bits

State  $S_1$ : (copying X to Z while inverting bits) till Y = 1

when Y = 1, another number is about to start – move to initial state  $S_0$



1/6/2003

Dr. Ashraf S. Hasan Mahmoud


24

## Serial Two's Complementer – Problem 4-20 – State Table

- Solution (cont'd):**

2 States → need one flip-flop

Let  $S_0 = 0$ , while  $S_1 = 1$

 

Present State	Inputs		Next State	Output
	Q(t)	X Y		
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	0	1
1	0	0	1	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

25

## Serial Two's Complementer – Problem 4-20 – Implementation Using D Flip-Flops

- Solution (cont'd):**

Present State	Inputs		Next State	Output	D-Flip-Flop Input
	Q(t)	X Y			
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	1	1
0	1	1	0	1	0
1	0	0	1	1	1
1	0	1	0	1	0
1	1	0	1	0	1
1	1	1	0	0	0

(c) D Flip-Flop

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

XY	00	01	11	10
Q(t)	0	0	0	1
Q(t)	1	1	0	1

$$D_0 = QY' + XY'$$

XY	00	01	11	10
Q(t)	0	0	1	1
Q(t)	1	1	0	0

$$Z = Q'X + QX'$$

1/6/2003

Dr. Ashraf S. Hasan Mahmoud


26

## Serial Two's Complementer – Problem 4-20 – Implementation Using *D* Flip-Flops (2)

• **Solution (cont'd):**

$$D_Q = QY' + XY'$$

$$Z = Q'X + QX'$$

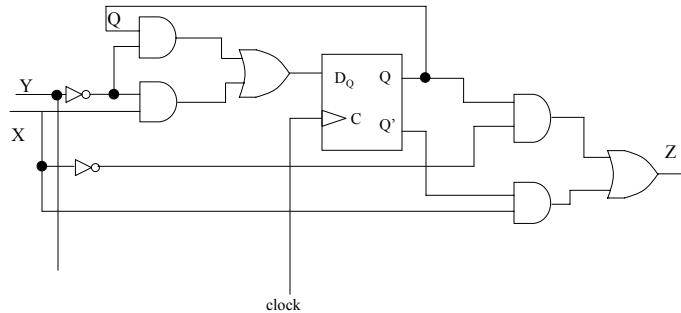

## Serial Two's Complementer – Problem 4-20 – Implementation Using *JK* Flip-Flops

• **Solution (cont'd):**

Present State	Inputs		Next State	Output	<i>JK</i> -Flip-Flop Input	
$Q(t)$	X	Y	$Q(t+1)$	Z	$J_0$	$K_0$
0	0	0	0	0	0	X
0	0	1	0	0	0	X
0	1	0	1	1	1	X
0	1	1	0	1	0	X
1	0	0	1	1	X	0
1	0	1	0	1	X	1
1	1	0	1	0	X	0
1	1	1	0	0	X	1

(a) *JK*-Flip-Flop

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$XY$	00	01	11	10
$Q(t)$	0	0	0	1
1	x	x	x	x

$$J_Q = XY'$$

$XY$	00	01	11	10
$Q(t)$	0	x	x	x
1	0	1	1	0

$$K_Q = Y$$

$XY$	00	01	11	10
$Q(t)$	0	0	1	1
1	1	1	0	0

$$Z = Q'X + QX'$$


## Serial Two's Complementer – Problem 4-20 – Implementation Using JK Flip-Flops (2)

- **Solution (cont'd):**

$$J_Q = XY'$$

$$K_Q = Y$$

$$Z = Q'X + QX'$$

 


## More Examples: Problem 4-19

- **Problem:** Design a sequential circuit with two  $D$  flip-flops A and B and one input X. When  $X = 0$ , the state of the circuit remains the same. When  $X = 1$ , the circuit goes through the state transitions 00 to 10 to 11 to 01, and back to 00, and then repeats.

## Problem 4-19 – State Diagram/Table

• **Solution:**

 

Present State		Input	Next State	
A	B	X	A	B
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1

BX

	00	01	11	10
A				
0	0	1	0	0
1	1	1	0	1

$D_A = AX' + B'X$

BX

	00	01	11	10
A				
0	0	0	0	1
1	0	1	1	1

$D_B = AX + BX'$


Note that the output in this case is the states AB

## Problem 4-19 – Circuit Implementation

• **Solution:**

$D_A = AX' + B'X$

$D_B = AX + BX'$

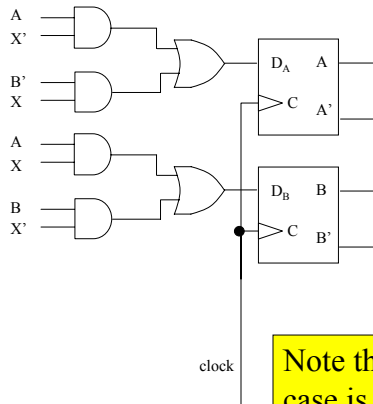

Note that the output in this case is the states AB



## Another Example: Problem 4-11

- Problem:** A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following input equations:


$$D_A = X'Y + XA; D_B = X'B + XA; Z = XB$$

- Draw the logic diagram of the circuit
- Derive the state table
- Derive the state diagram


This is NOT a design problem – should be much easier than the ones presented earlier!

## Problem 4-11:

- Solution:**

 

Present State		Inputs		Next State		Output
A	B	X	Y	A	B	Z
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	0
0	1	0	1	1	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	0
1	0	0	0	0	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 

## Yet Another Example: Problem 4-33

- Problem:** Design a sequential circuit with two *JK* flip-flops A and B and two inputs X and E. If  $E = 0$ , the circuit remains in the same state, regardless of the input X. When  $E = 1$  and  $X = 1$ , the circuit goes through the state transitions from 00 to 01 to 10 to 11, back to 00, and then repeats. When  $E = 1$  and  $X = 0$ , the circuit goes through the state transitions from 00 to 11 to 10 to 01, back to 00 and then repeats.


1/6/2003

Dr. Ashraf S. Hasan Mahmoud

35

## Problem 4-33 – State Diagram/Table

- Solution:**

 

Format: EX

(a) JK Flip-Flop			
Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present State		Inputs		Next State		FF Inputs			
A	B	E	X	A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	0	X	0	X
0	0	0	1	0	0	0	X	0	X
0	0	1	0	1	1	1	X	1	X
0	0	1	1	0	1	0	X	1	X
0	1	0	0	0	1	0	X	X	0
0	1	0	1	0	1	0	X	X	0
0	1	1	0	0	0	0	X	X	1
0	1	1	1	1	0	1	X	X	1
1	0	0	0	1	0	X	0	0	X
1	0	0	1	1	0	X	0	0	X
1	0	1	0	0	1	X	1	1	X
1	0	1	1	1	1	X	0	1	X
1	1	0	0	1	1	X	0	X	0
1	1	0	1	1	1	X	0	X	0
1	1	1	0	1	0	X	0	X	1
1	1	1	1	0	0	X	1	X	1

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

36

## Problem 4-33 – Logic Circuit

### • Solution:

EX AB	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

$$J_A = BEX + B'EX'$$

EX AB	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	0	0	1	0
10	0	0	0	1


$$K_A = BEX + B'EX'$$

EX AB	00	01	11	10
00	0	0	1	1
01	x	x	x	x
11	x	x	x	x
10	0	0	1	1

$$J_B = E$$

EX AB	00	01	11	10
00	x	x	x	x
01	0	0	1	1
11	0	0	1	1
10	x	x	x	X

$$K_B = E$$

 

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

37

## Recommended Set of Problems

- **Problems:** 4-10<sup>s</sup>, 4-11<sup>s</sup>, 4-14, 4-16, 4-18, 4-19<sup>s</sup>, 4-20<sup>s</sup>, 4-24, 4-30, 4-33<sup>s</sup>, 4-34 (a,b), 4-36
- Homework#4: 4-13, 4-17, 4-23, 4-25
- **Due Date:** Wednesday Dec 25<sup>th</sup>, 2002
- Problems with "s" are solved in this slides package

1/6/2003

Dr. Ashraf S. Hasan Mahmoud

38