

King Fahd University of Petroleum & Minerals Computer Engineering Dept

COE 200 – Fundamentals of Computer
Engineering

Term 043

Dr. Ashraf S. Hasan Mahmoud

Rm 22-144

Ext. 1724

Email: ashraf@ccse.kfupm.edu.sa

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

1

Karnaugh Map (K-Map)

- A tabular method to simplify function expressions – an alternative to algebraic manipulation
- Produces 2-level (sum of products or product of sums) implementation

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

2

1-variable K-map

- Consider the function $F(X)$

$$F(X) = 0 \quad \begin{array}{c} x \\ \text{(F is NOT dependent on X)} \end{array} \begin{array}{cc} 0 & 1 \\ \boxed{0} & \boxed{0} \end{array}$$

$$F(X) = 1 \quad \begin{array}{c} x \\ \text{(F is NOT dependent on X)} \end{array} \begin{array}{cc} 0 & 1 \\ \boxed{1} & \boxed{1} \end{array}$$

$$F(X) = X \quad \begin{array}{c} x \end{array} \begin{array}{cc} 0 & 1 \\ \boxed{0} & \boxed{1} \end{array}$$

$$F(X) = X' \quad \begin{array}{c} x \end{array} \begin{array}{cc} 0 & 1 \\ \boxed{1} & \boxed{0} \end{array}$$

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

3

2-variable K-map

- Consider the function $F(X,Y)$
- The general 2-variable K-map is as shown
- The map is formed by putting two 1-variable K-maps side by side

		Y=1	
		0	1
X	0	$X'Y'$ (m_0)	$X'Y$ (m_1)
	1	XY' (m_2)	XY (m_3)

- Examples:

		Y	
		0	1
X	0	0	0
	1	0	1

$$F(X,Y) = XY$$

7/14/2005

		Y	
		0	1
X	0	0	1
	1	1	1

$$F(X,Y) = X'Y + XY' + XY = X + Y$$

4

2-variable K-map - cont'd

- Neighbors sharing one literal:

- $X'Y'$ (or m_0) and $X'Y$ (or m_1) \rightarrow sharing the literal X'
- $X'Y'$ (or m_0) and XY' (or m_2) \rightarrow sharing the literal Y'
- $X'Y$ (or m_1) and XY (or m_3) \rightarrow sharing the literal Y
- XY' (or m_2) and XY (or m_3) \rightarrow sharing the literal X

- If for example

$$F(X,Y) = m_0 + m_1 = X'Y' + X'Y$$

Then once can simplify F as follows:


$$F(X,Y) = X'(Y' + Y)$$

$$= X' \rightarrow \text{the shared literal}$$

	Y	0	1
X	0	1	1
1	0	0	0

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

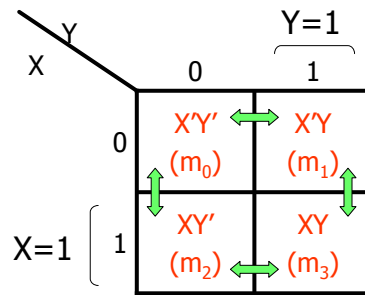


5

2-variable K-map - cont'd

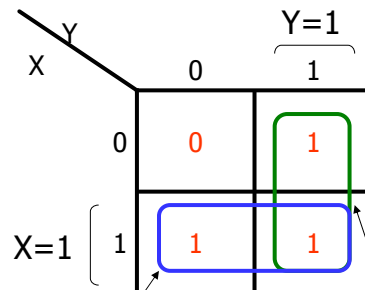- Example2: $F(X,Y) = \Sigma m(1,2,3)$

F can be simplified as in

$$\begin{aligned} F &= X'Y + XY' + XY \\ &= X'Y + XY + XY' + XY \\ &= (X'+X)Y + X(Y'+Y) \\ &= Y + X \end{aligned}$$



X - the common literal for this neighboring group


Y - the common literal for this neighboring group

7/14/2005

Dr. Ashraf S. Has

2-variable K-map – All Possible Squares

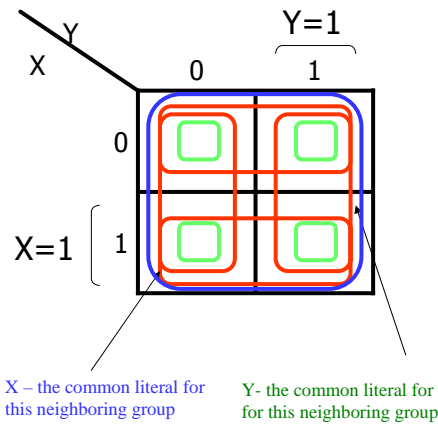- 4 Groups each of one minterm
- 4 groups each of two minterms
- 1 group of 4 minterms




7/14/2005

Dr. Ashraf S. Has

3-variable K-map

- Consider the function $F(X,Y,Z)$
- The general 3-variable K-map is as shown
- The map is formed by putting two 2-variable K-maps side by side
- Note:
 - The minterms are ordered such that any two neighboring minterm differ only in one literal

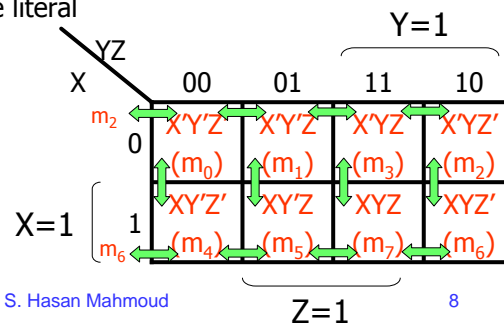- The K-Map (the numbering of the minterms) assumes X is the most significant variable and Z is the least significant variable



7/14/2005

Dr. Ashraf S. Hasan Mahmoud

8

3-variable K-map – cont'd

- Example $F(X,Y,Z) = m_5 + m_7$

Once can simplify as in

$$\begin{aligned} F &= m_5 + m_7 \\ &= XY'Z + XYZ \\ &= XZ(Y'+Y) \\ &= XZ \end{aligned}$$

Or once can use the K-map as shown

The common literals for this group is XZ (they differ in Y)

Therefore: $F(X,Y) = XZ$

		YZ			
		00	01	Y=1 11 10	
X	0				
	X=1 [1		1	1	
		Z=1			

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

9

3-variable K-map – cont'd

- Example $F(X,Y,Z) = \Sigma m(2,3,4,5)$

Once can simplify as in

$$\begin{aligned} F &= m_2 + m_3 + m_4 + m_5 \\ &= X'YZ' + X'YZ + XY'Z' + XY'Z \\ &= X'Y(Z'+Z) + XY'(Z'+Z) \\ &= X'Y + XY' \end{aligned}$$

Or one can use the K-map as shown

The common literals for the 1st group is $X'Y$ (they differ in Z), while the common literals for the 2nd group is XY' (they differ in Z)

Therefore: $F(X,Y) = X'Y + XY'$

		YZ			
		00	01	Y=1 11 10	
X	0			1	1
	X=1 [1	1	1		
		Z=1			

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

10

3-variable K-map - cont'd

- Example $F(X,Y,Z) = \Sigma m(0,2,4,5,6)$


Once can simplify as in

$$\begin{aligned}
 F &= m_0 + m_2 + m_4 + m_5 + m_6 \\
 &= X'Y'Z' + X'YZ' + XY'Z' + XY'Z + XYZ' \\
 &= X'Y'Z' + X'YZ' + XY'Z' + XY'Z + XY'Z \\
 &\quad + XYZ' \\
 &= Y'Z'(X' + X) + YZ'(X' + X) + \\
 &\quad XY'(Z' + Z) \\
 &= Z'(Y' + Y) + XY' \\
 &= Z' + XY'
 \end{aligned}$$

Or one can use the K-map as shown

The common literals for the 1st group is XY' (they differ in Z), while the common literal for the 2nd group is Z' (they differ in XY)

Therefore: $F(X,Y) = Z' + XY'$

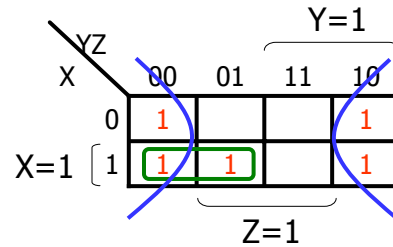



7/14/2005

Dr. Ashraf S. Hasan Mahmoud

11

3-variable K-map - All Possible Groups

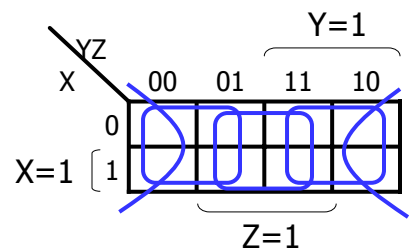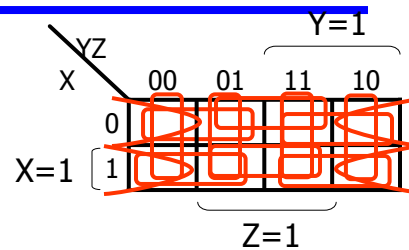- 8 groups each of 1 minterms
- 12 groups each of 2 minterms
- 4 groups each of 4 minterms
- 1 group of 8 minterms



7/14/2005

Dr. Ashraf S. Hasan Mahmoud

12

Rules for Choosing Groups

- The groups SHOULD cover all minterms
- The groups SHOULD have minimum overlap
- The groups SHOULD be maximized in size (to reduce their number or product terms)

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

13

Example

- Consider $F(X,Y,Z) = \Sigma m(1,3,4,5,6)$


Following the groups selection rules:

- there is no group of 8 or 4 that can be selected
- there are only groups of 2 that can be selected
- once can select the groups as shown (minimum no of groups)

Therefore $F(X,Y,Z) = X'Z + Y'Z + XZ'$

OR (See second K-Map)

$F(X,Y,Z) = X'Z + XZ' + XY'$

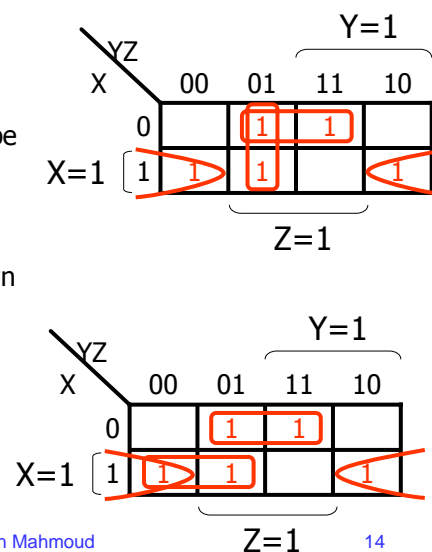

The simplest expression is NOT unique!

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

14

Definitions

- Map manipulation: to minimize number of terms (i.e. simplify function and avoid redundant terms)
- Implicant:
 - A product term
 - Any valid square or group
- Prime Implicant: If you list all implicants, the removal of any literal does not lead to an implicant – the original implicant is a prime implicant
 - i.e. largest possible square
- Essential Prime Implicant: A prime implicant covering a minterm no other prime implicant does

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

15


Example

- Consider $F(X,Y,Z) = \Sigma m(1,3,4,5,6)$

List all implicants, prime implicants and essential prime implicants

- Solution:
- Implicants: $XY'Z'$, XZ' , XY' , $XY'Z$, $X'Y'Z$, $Y'Z$, ...
- P.Is: XY' , XZ' , $Y'Z$, $X'Z$
- EPIs: $X'Z$, XZ'

The simplest expression is NOT unique!

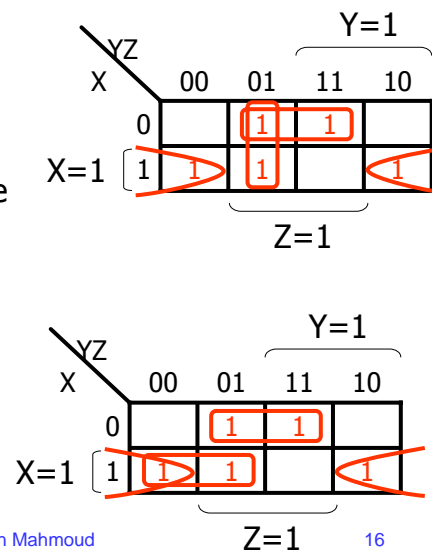

7/14/2005

Dr. Ashraf S. Hasan Mahmoud


16

4-variable K-map

- Consider the function $F(W,X,Y,Z)$
- The general 4-variable K-map is as shown
- The map is formed by putting two 3-variable K-maps on top of each other

- Note:

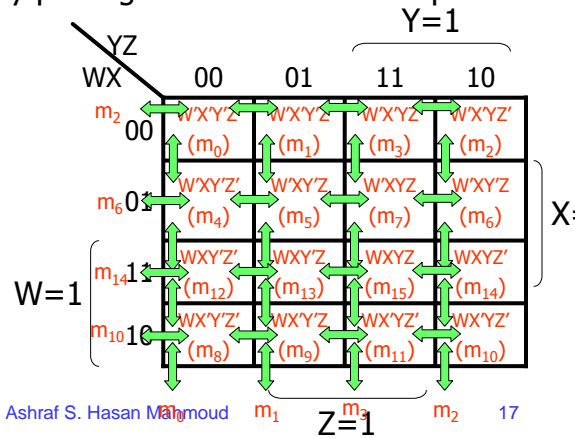- The minterms are ordered such that any two neighboring minterm differ only in one literal
- The K-Map (the numbering of the minterms) assumes W is the most significant variable and Z is the least significant




7/14/2005 variable

Dr. Ashraf S. Hasan Mahmoud

m₁ m₂ 17

4-variable K-map - All Possible Groups

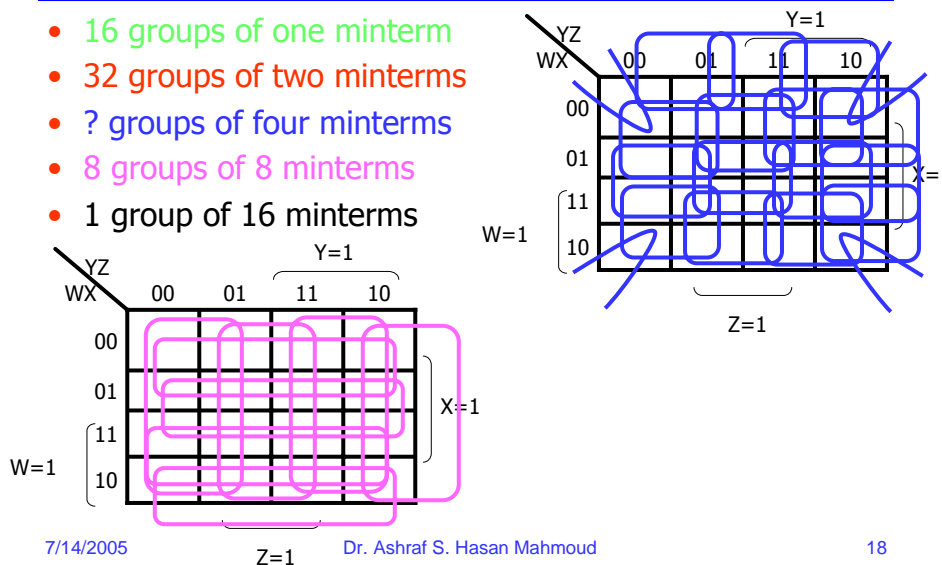- 16 groups of one minterm
- 32 groups of two minterms
- ? groups of four minterms
- 8 groups of 8 minterms
- 1 group of 16 minterms



7/14/2005

Z=1


Dr. Ashraf S. Hasan Mahmoud

18

4-variable K-map - Example

- Consider $F(W,X,Y,Z) = \Sigma m(0,1,2,4,5,6,8,9,12,13,14)$

$$F(W,X,Y,Z) = Y' + W'Z' + XZ'$$

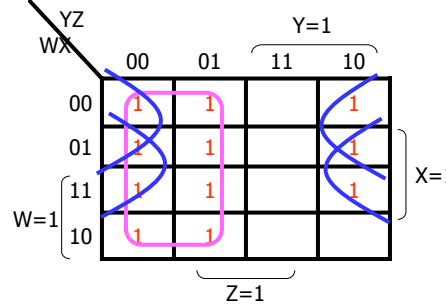

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

19

Example


- Consider $F(A,B,C,D) = \Sigma m(0,1,3,4,5,6,7,12,13,14, 15)$
Find essential prime implicants?

- Solution:

$A'D$ and BD' are EPI

$A'B$ is not an EPI

What is $F(A,B,C,D)$?

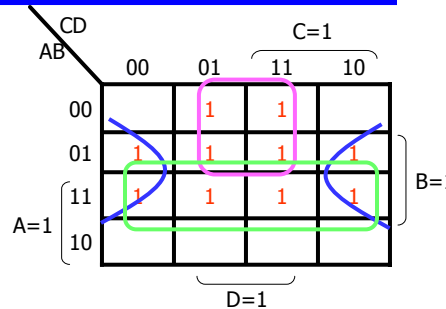

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

20


Example

- Consider $F(W,X,Y,Z) = \Sigma m(0,1,5,10,11,12,13,15)$
Find all essential prime implicants?
Write all possible expressions for F?

- Solution:

$$\text{EPI} = A'B'C'D', BC'D, ABC', AB'C$$
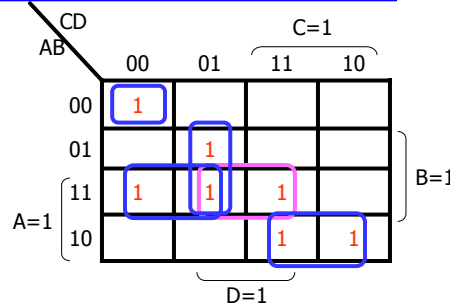
$$F(A,B,C,D) = A'B'C'D' + BC'D + ABC' + AB'C + ACD \text{ (or ABD)}$$



7/14/2005

Dr. Ashraf S. Hasan Mahmoud

21

Problem 2-19(a)

- Consider $F(W,X,Y,Z) = \Sigma m(0,2,5,7,8,10,12,13,14,15)$
Find all implicants, prime implicants, and essential prime implicants? Write all possible expressions for F?


- Solution:

Implicants: $W'X'Y'Z', W'X'Z', WX'Y'Z', WX'YZ', WX'Z', X'Z', \dots$

PIs: $WZ', XZ, X'Z', WX$

EPIs: $X'Z'$ (only PI covering $W'X'Y'Z'$),
 XZ (only PI covering $W'XY'Z'$ or $W'XYZ$)
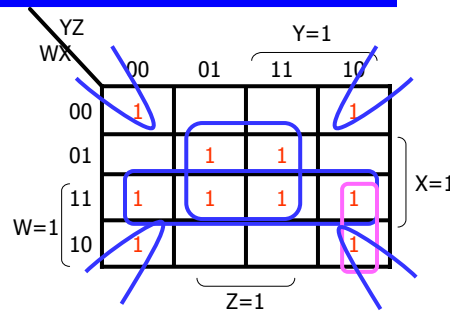
$$F(W,X,Y,Z) = X'Z' + XZ + WX, \text{ OR} \\ = X'Z' + XZ + WZ'$$



7/14/2005

Dr. Ashraf S. Hasan Mahmoud

22

Product of Sums Simplification - Example


- Consider $F(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$
Write F in the simplified product of sums

- Solution:
Follow same rule as before but for the ZEROS

$$F' = AB + CD + BD'$$

Therefore,

$$F'' = F = (A'+B')(C'+D')(B'+D)$$

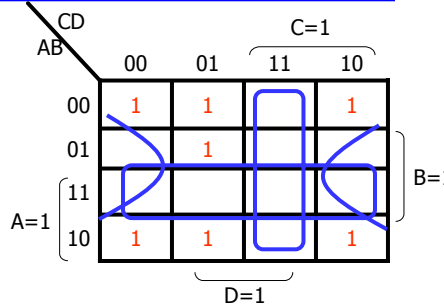

7/14/2005

Dr. Ashraf S. Hasan Mahmoud


23

Don't Care Conditions - Example

- Consider
 $F(A,B,C,D) = \Sigma m(1,3, 11, 15)$
 $d(A,B,C,D) = \Sigma m(0,2,5)$
Simplify F.

- Solution:
 $F = A'B' + CD$

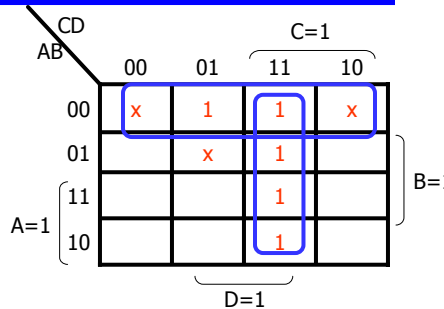Note – for the simplification we assumed $A'B'C'D'$ (m_0) = 1, and $A'B$ (m_2) = 1, while $A'BC'D$ (m_5) = 0




7/14/2005


Dr. Ashraf S. Hasan Mahmoud

24

More Gates: NAND - NOR

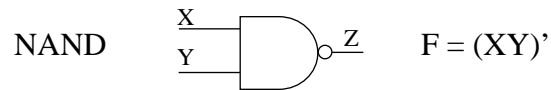

X	Y	Z=(XY)'
0	0	1
0	1	1
1	0	1
1	1	0

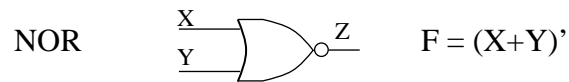

X	Y	Z=(X+Y)'
0	0	1
0	1	0
1	0	0
1	1	0

- Sometimes it is desirable to build circuits using NAND gates only or NOR gates only

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

25

More Gates: XOR - XNOR



X	Y	Z=X⊕Y
0	0	0
0	1	1
1	0	1
1	1	0



X	Y	Z=(X⊕Y)'
0	0	1
0	1	0
1	0	0
1	1	1


7/14/2005

Dr. Ashraf S. Hasan Mahmoud

26

NAND Circuits

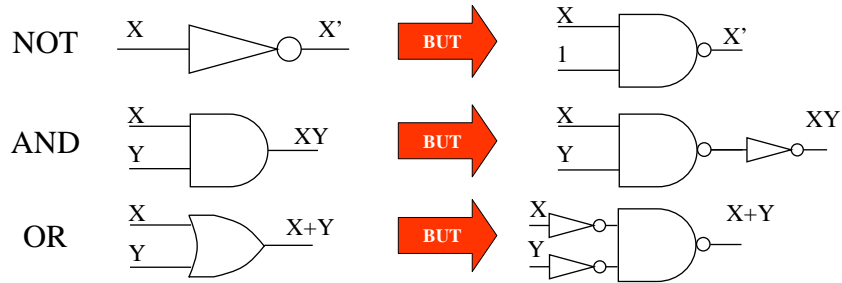We have learned how to build any function using



- Therefore, we can build all functions we learned so far using NAND gates ONLY
- NAND is a UNIVERSAL gate



7/14/2005

Dr. Ashraf S. Hasan Mahmoud

27

Graphic Symbols for NAND Gate

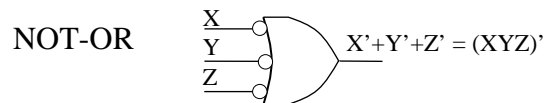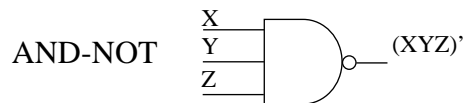- Two equivalent graphic symbols or shapes for the SAME function



7/14/2005

Dr. Ashraf S. Hasan Mahmoud

28

Two Level Implementation

- We use the sum of products form
 - This results from K-map simplification or algebraic manipulation
- The AND gates – 1st level
- The OR gate – 2nd level
- Inverters to inputs of ANDs or output of OR are not counted as levels


7/14/2005

Dr. Ashraf S. Hasan Mahmoud

29

Two Level Implementation – cont'd

- Example: Consider $F = AB + CD$

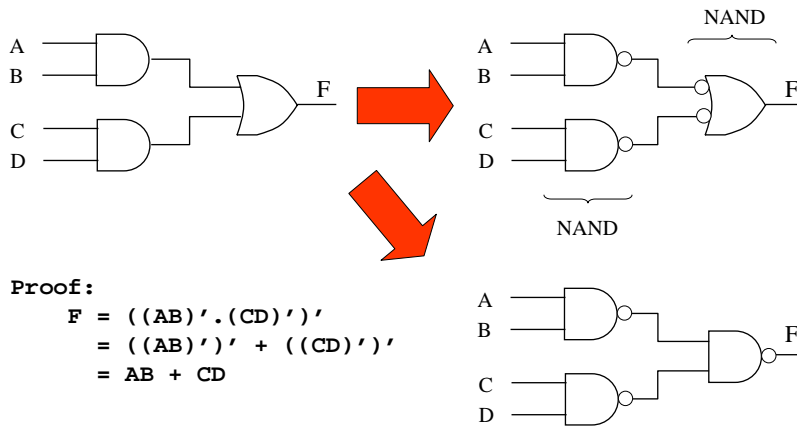

Proof:

$$\begin{aligned}
 F &= ((AB)' \cdot (CD)')' \\
 &= ((AB)')' + ((CD)')' \\
 &= AB + CD
 \end{aligned}$$

7/14/2005

Dr. Ashraf S. Hasan Mahmoud



30

Example

- Consider $F = \sum m(1,2,3,4,5,7)$ – Implement using NAND gates

		Y=1			
	YZ	00	01	11	10
X	0		1	1	1
X=1	1	1	1	1	
		Z=1			

$$F(X,Y) = Z + XY' + X'Y$$

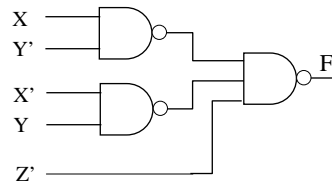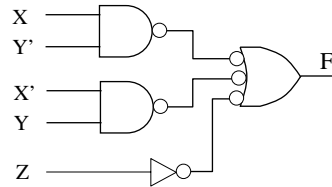

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

31

Rules for 2-Level NAND Implementations

- Simplify the function and express it in sum-of-products form
- Draw a NAND gate for each product term (with 2 literals or more)
- Draw a single NAND gate at the 2nd level (in place of the OR gate)
- A term with single literal requires a NOT

What about multi-level circuits?

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

32

Rules for Multi-Level NAND Implementations

- NOTE: the function is NOT in the standard form – WHY?
- Steps:
 - Draw a NAND gate for each AND gate
 - Draw a NAND gate (using the NOT-OR symbol) for each OR gate
 - Check paths – add inverters to make even number of bubbles


7/14/2005

Dr. Ashraf S. Hasan Mahmoud

33

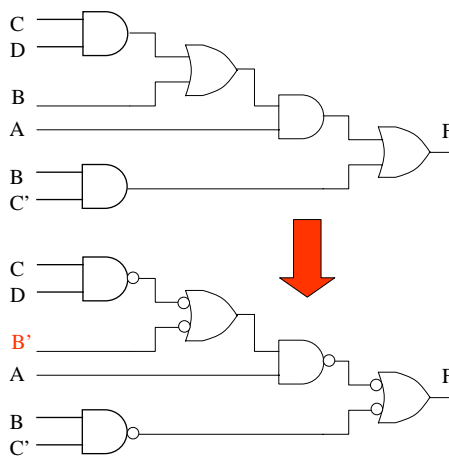Example (1): Rules for Multi-Level NAND Implementations

- Consider the function $F = A(CD+B)+BC'$



Note: an inverter is added to the path for the literal B


7/14/2005

Dr. Ashraf S. Hasan Mahmoud

34

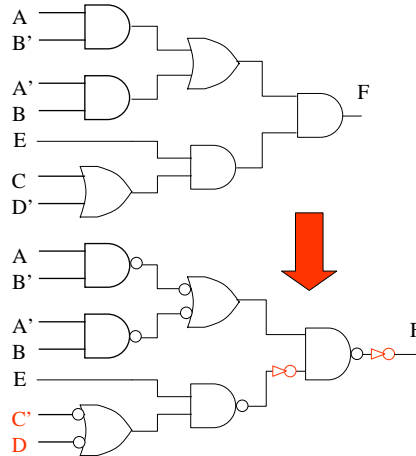Example (2): Rules for Multi-Level NAND Implementations

- Consider the function $F = (AB' + A'B)E(C + D')$



Note: an inverter is added to three paths


7/14/2005

Dr. Ashraf S. Hasan Mahmoud

35

NOR Circuits

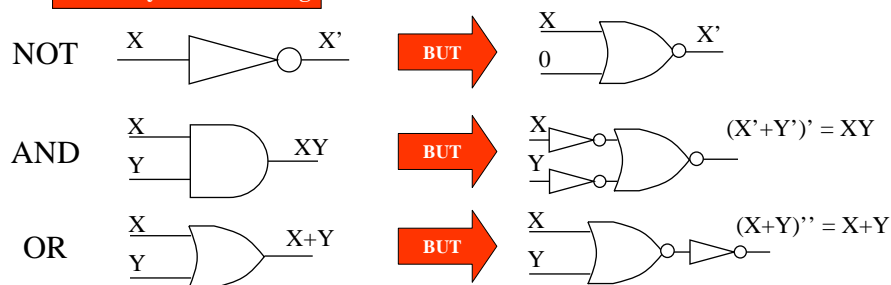We have learned how to build any function using



- Therefore, we can build all functions we learned so far using NOR gates ONLY
- NOR is a UNIVERSAL gate


7/14/2005

Dr. Ashraf S. Hasan Mahmoud

36

Graphic Symbols for NOR Gate

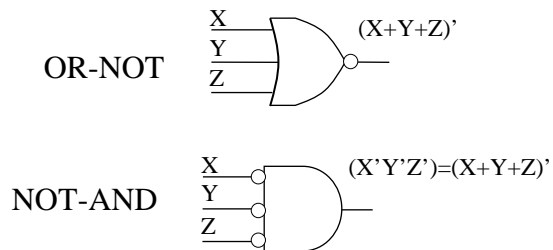- Two equivalent graphic symbols or shapes for the SAME function




7/14/2005

Dr. Ashraf S. Hasan Mahmoud

37

Two Level Implementation - NOR

- Consider $F = (A+B)(C+D)E$

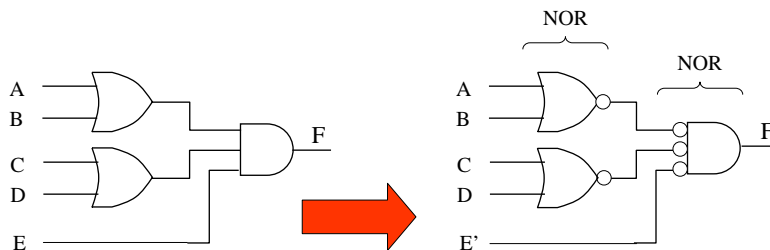

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

38

Two Level Implementation - NOR

- We use the *product of sums* form
 - This results from K-map simplification or algebraic manipulation
 - Note to get product of sums we use the zeros – simplify and then complement the expression
- The OR gates – 1st level
- The AND gate – 2nd level
- Inverters to inputs of ORs or output of AND are not counted as levels

7/14/2005

Dr. Ashraf S. Hasan Mahmoud



39

Example

- Consider $F = \sum m(1,2,3,4,5,7)$ – Implement using NAND gates

		Y=1			
	YZ	00	01	11	10
X	0	0	1	1	1
X=1	1	1	1	1	0
		Z=1			

$$F(X,Y) = Z + XY' + X'Y$$

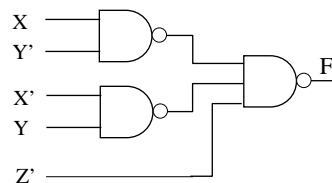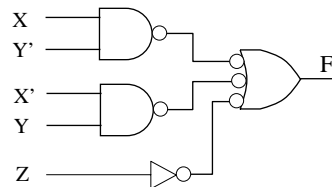

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

40

Rules for 2-Level NOR Implementations

- Simplify the function and express it in product of sums form
- Draw a NOR gate (using OR-NOT symbol) for each sum term (with 2 literals or more)
- Draw a single NOR gate (using NOT-AND symbol) the 2nd level (in place of the AND gate)
- A term with single literal requires a NOT

What about multi-level circuits?

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

41

Rules for Multi-Level NOR Implementations

- NOTE: the function is NOT in the standard form – WHY?
- Steps:
 - Draw a NOR (OR-NOT) gate for each OR gate
 - Draw a NOR (NOT-AND) gate for each AND gate
 - Check paths – add inverters to make even number of bubbles


7/14/2005

Dr. Ashraf S. Hasan Mahmoud

42

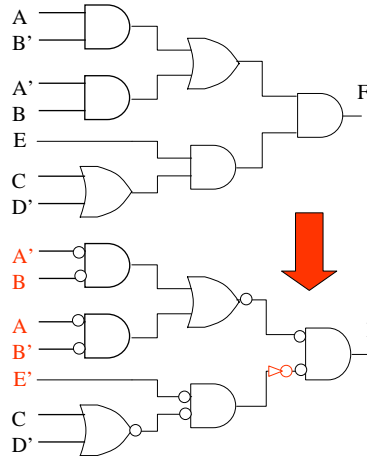Example: Rules for Multi-Level NOR Implementations

- Consider the function $F = (AB' + A'B)E(C + D')$



Note: an inverter is added to six paths


7/14/2005

Dr. Ashraf S. Hasan Mahmoud


43

Example (2): Rules for Multi-Level NOR Implementations

- Consider the function $F = (AB)' + C$

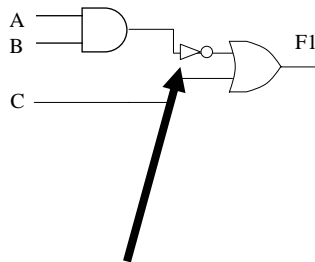

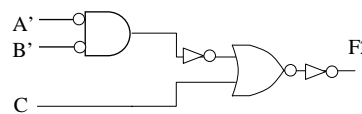• Hence this bubble need not be complemented
• Only the ones added!!



$$\begin{aligned}
 \mathbf{F2} &= ((A' B')' + C)' \\
 &= (AB)' + C \\
 &= \mathbf{F1}
 \end{aligned}$$


7/14/2005

Dr. Ashraf S. Hasan Mahmoud


44

Example (3): Rules for Multi-Level NOR Implementations

- Consider the function $F = (A+B)'C$

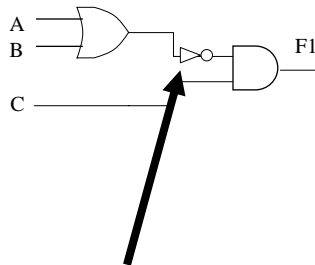

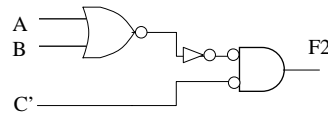•Hence this bubble need not be complemented
•Only the ones added!!



$$\begin{aligned} F2 &= (A+B)''C'' \\ &= (A+B)'C' \\ &= (A+B)'C \\ &= F1 \end{aligned}$$

7/14/2005

Dr. Ashraf S. Hasan Mahmoud

45