

King Fahd University of Petroleum & Minerals Computer Engineering Dept

COE 200 – Fundamentals of Computer
Engineering

Term 043

Dr. Ashraf S. Hasan Mahmoud

Rm 22-148-3

Ext. 1724

Email: ashraf@ccse.kfupm.edu.sa

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

1

Counter

- **Counter:** A register (sequential circuit) that goes through a pre-determined sequence of states upon the application of input (clock or other source) pulses
- **Binary Counter:** The sequence of the states follows the binary number sequence (e.g. 000 → 001 → 010 → 011 → etc.)
 - n-bit binary counter requires n flip-flops – counts from 0 to $2^n - 1$
- Two Types of Counters:
 1. **Ripple counter:**
 - Flip-flop output transition serves as source for triggering the other flip-flops
 2. **Synchronous counter:** the clock input of all flip-flops receive the common clock signal

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

2

Binary Counter

Counting Sequence for Binary Number


No	Upward Counting Sequence				No	Downward Counting Sequence			
	Q3	Q2	Q1	Q0		Q3	Q2	Q1	Q0
0	0	0	0	0	15	1	1	1	1
1	0	0	0	1	14	1	1	1	0
2	0	0	1	0	13	1	1	0	1
3	0	0	1	1	12	1	1	0	0
4	0	1	0	0	11	1	0	1	1
5	0	1	0	1	10	1	0	1	0
6	0	1	1	0	9	1	0	0	1
7	0	1	1	1	8	1	0	0	0
8	1	0	0	0	7	0	1	1	1
9	1	0	0	1	6	0	1	1	0
10	1	0	1	0	5	0	1	0	1
11	1	0	1	1	4	0	1	0	0
12	1	1	0	0	3	0	0	1	1
13	1	1	0	1	2	0	0	1	0
14	1	1	1	0	1	0	0	0	1
15	1	1	1	1	0	0	0	0	0

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

3

4-bit Ripple Counter

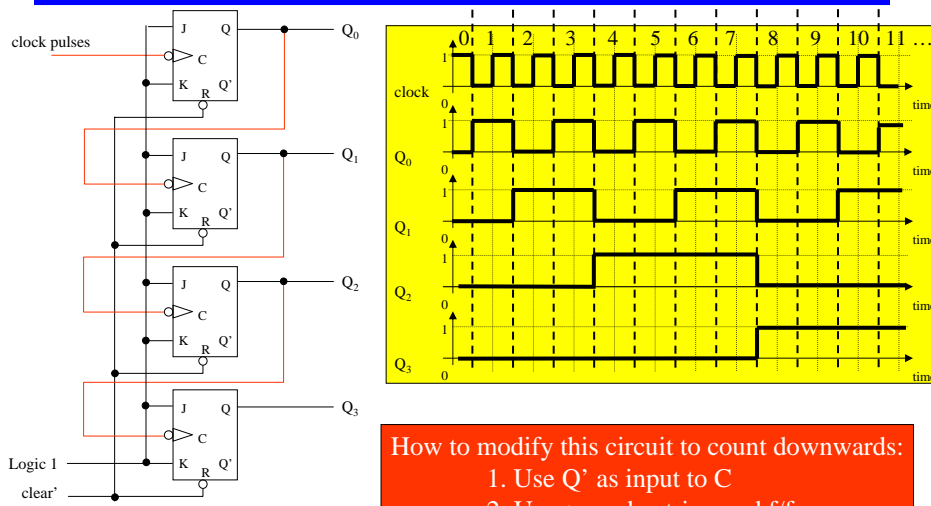

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

4

Ripple Counter

- Advantages:
 - Simple hardware
- Disadvantages:
 - Asynchronous – delay dependent
- Good for low power circuits

Synchronous Binary Counter

- Clock pulses are applied to the inputs of all of the flip-flops.
- Design of binary counters
 - Same as we learned in Chapter 4!

Example: 4-bit Binary Counter

State Table and Flip-Flops Inputs for Binary Counter

Present State				Next State				Flip-flops inputs							
Q ₃	Q ₂	Q ₁	Q ₀	Q ₃	Q ₂	Q ₁	Q ₀	J _{Q3}	K _{Q3}	J _{Q2}	K _{Q1}	J _{Q1}	K _{Q1}	J _{Q0}	K _{Q0}
0	0	0	0	0	0	0	1	0	X	0	X	0	X	0	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	1	0	1	0	X	0	0	X	1	X	X	1
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
1	0	1	1	1	1	0	0	X	0	1	X	X	1	X	1
1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	X
1	1	0	1	1	1	1	0	X	0	X	0	1	X	X	1
1	1	1	0	1	1	1	1	X	0	X	0	X	0	1	X
1	1	1	1	0	0	0	0	X	1	X	1	X	1	X	1

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

7

Example: 4-bit Binary Counter – cont'd

Q ₃ Q ₀	00	01	11	10
Q ₃ Q ₂	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

$$J_{Q3} = Q_0Q_1Q_2$$

Q ₃ Q ₀	00	01	11	10
Q ₃ Q ₂	00	01	11	10
00	0	0	1	0
01	x	x	x	x
11	x	x	x	x
10	0	0	1	0

$$J_{Q2} = Q_0Q_1$$

Q ₃ Q ₀	00	01	11	10
Q ₃ Q ₂	00	01	11	10
00	0	1	x	x
01	0	1	x	x
11	0	1	x	x
10	0	1	x	x

$$J_{Q1} = Q_0$$

Q ₃ Q ₀	00	01	11	10
Q ₃ Q ₂	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	0	0	1	0
10	0	0	0	0

$$K_{Q3} = Q_0Q_1Q_2$$

Q ₃ Q ₀	00	01	11	10
Q ₃ Q ₂	00	01	11	10
00	x	x	x	x
01	0	0	1	0
11	0	0	1	0
10	x	x	x	x

$$K_{Q2} = Q_0Q_1$$

Q ₃ Q ₀	00	01	11	10
Q ₃ Q ₂	00	01	11	10
00	x	x	1	0
01	x	x	1	0
11	x	x	1	0
10	x	x	1	0

$$K_{Q1} = Q_0$$

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

8

Example: 4-bit Binary Counter – Implementation

Q_3, Q_2	Q_1, Q_0	00	01	11	10
00		1	x	x	1
01		1	x	x	1
11		1	x	x	1
10		1	x	x	1

$$J_{Q_0} = 1$$

Q_3, Q_2	Q_1, Q_0	00	01	11	10
00		x	1	1	x
01		x	1	1	x
11		x	1	1	x
10		x	1	1	x

$$K_{Q_0} = 1$$

$$J_{Q_3} = Q_0 Q_1 Q_2$$

$$K_{Q_3} = Q_0 Q_1 Q_2$$

$$J_{Q_2} = Q_0 Q_1$$

$$K_{Q_2} = Q_0 Q_1$$

$$J_{Q_1} = Q_0$$

$$K_{Q_1} = Q_0$$

$$J_{Q_0} = 1$$

$$K_{Q_0} = 1$$

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

9

Example: 4-bit Binary Counter – Implementation - continued

- Sometimes it is desirable to control the counter operation by added a count enable signal: En
 - When En = 1 → counter counts
 - When En = 0 → counter holds state (stops counting)
- Hence the new input equations are:

$$J_{Q_3} = Q_0 Q_1 Q_2 \text{En}, K_{Q_3} = Q_0 Q_1 Q_2 \text{En}$$

$$J_{Q_2} = Q_0 Q_1 \text{En}, K_{Q_2} = Q_0 Q_1 \text{En}$$

$$J_{Q_1} = Q_0 \text{En}, K_{Q_1} = Q_0 \text{En}$$


$$J_{Q_0} = \text{En}, K_{Q_0} = \text{En}$$

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

10

Example: 4-bit Binary Counter – Circuit

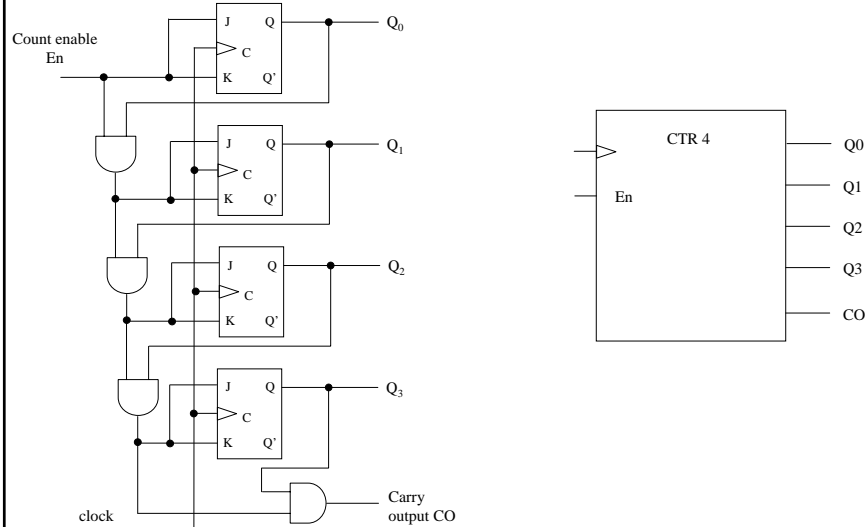

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

11

Notes on Binary Synchronous Counter

- When $En = 0 \rightarrow J = K = 0 \rightarrow$ flip-flop holds state
- For general n -bit binary synchronous counter the input equation for the i th JK flip-flop is:

$$J_{Q_i} = K_{Q_i} = Q_0 Q_1 Q_2 \dots Q_{i-1} Q_i En$$

- The CO output can be used to extend the counter to more stages (How?)

If we use a –ve edge triggered clock, will this circuit count downwards?

Draw the state diagram for this counter?

- Binary synchronous counters are MOST efficiently constructed with complementing T or JK flip-flops – but can be designed with D flip-flops

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

12

Problem 5-17: 4-bit Binary Counter with D flip-flops

Problem: Design a 4-bit binary synchronous counter with counter enable (En) signal

Solution:

State Table and Flip-Flop inputs for Binary Counter

Present State				Next State				Flip-flops inputs			
Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0	D_{03}	D_{02}	D_{01}	D_{00}
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	0
0	0	1	0	0	0	1	1	0	0	1	1
0	0	1	1	0	1	0	0	0	1	0	0
0	1	0	0	0	1	0	1	0	1	0	1
0	1	0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	0	1	1	1
0	1	1	1	1	0	0	0	1	0	0	0
1	0	0	0	1	0	0	1	1	0	0	1
1	0	0	1	1	0	1	0	1	0	1	0
1	0	1	0	1	0	1	1	1	0	1	1
1	0	1	1	1	1	0	0	1	1	0	0
1	1	0	0	1	1	0	1	1	1	0	1
1	1	0	1	1	1	1	0	1	1	1	0
1	1	1	0	1	1	1	1	1	1	1	1
1	1	1	1	0	0	0	0	0	0	0	0

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

13

Problem 5-17: 4-bit Binary Counter with D flip-flops – cont'd

- The flip-flops input equations are given by:

Q_1Q_0	00	01	11	10
Q_3Q_2	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

$$D_{Q0} = Q_0' = Q_0 \oplus 1$$

Q_1Q_0	00	01	11	10
Q_3Q_2	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$D_{Q1} = Q_0Q_1' + Q_0'Q_1 = Q_1 \oplus Q_0$$

Q_1Q_0	00	01	11	10
Q_3Q_2	00	01	11	10
00	0	0	1	0
01	1	1	0	1
11	1	1	0	1
10	0	0	1	0

$$D_{Q2} = Q_0Q_1Q_2' + Q_1'Q_2 + Q_0'Q_2 = Q_2 \oplus (Q_0Q_1)$$

Q_1Q_0	00	01	11	10
Q_3Q_2	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	1	1	0	1
10	1	1	1	1

$$D_{Q3} = Q_0Q_1Q_2Q_3' + Q_2'Q_3 + Q_1'Q_3 + Q_0'Q_3 = Q_3 \oplus (Q_2Q_1Q_0)$$

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

14

Problem 5-17: 4-bit Binary Counter with D flip-flops – cont'd


- Rewriting the input equations and using the count enable signal En :

$$D_{Q_0} = Q_0' = Q_0 \oplus 1$$

$$D_{Q_1} = Q_0 Q_1' + Q_0' Q_1 = Q_1 \oplus Q_0$$

$$D_{Q_2} = Q_0 Q_1 Q_2' + Q_1' Q_2 + Q_0' Q_2 = Q_2 \oplus (Q_0 Q_1)$$
 
$$D_{Q_3} = Q_0 Q_1 Q_2 Q_3' + Q_2' Q_3 + Q_1' Q_3 + Q_0' Q_3 = Q_3 \oplus (Q_2 Q_1 Q_0)$$



Note: when $En = 0$, the Q_i is input to $D_{Q_i} \rightarrow$ i.e. flip-flop holds state

$$D_{Q_0} = Q_0 \oplus En = Q_0' \text{ if } En = 1 \\ = Q_0 \text{ if } En = 0$$

$$D_{Q_1} = Q_1 \oplus (Q_0 En) = Q_0 Q_1' + Q_0' Q_1 \text{ if } En = 1 \\ = Q_1 \text{ if } En = 0$$

$$D_{Q_2} = Q_2 \oplus (Q_0 Q_1 En) = Q_0 Q_1 Q_2' + Q_1' Q_2 + Q_0' Q_2 \text{ if } En = 1 \\ = Q_2 \text{ if } En = 0$$

$$D_{Q_3} = Q_3 \oplus (Q_2 Q_1 Q_0 En) = Q_0 Q_1 Q_2 Q_3' + Q_2' Q_3 + Q_1' Q_3 + Q_0' Q_3 \text{ if } En = 1 \\ = Q_3 \text{ if } En = 0$$

8/8/2005

Dr. Ashraf S. Hasan Mahmoud


15

Problem 5-17: 4-bit Binary Counter with D flip-flops – Circuit Diagram

- Notes:

- For a general n -bit counter, the i^{th} D flip-flop input equation is given by:
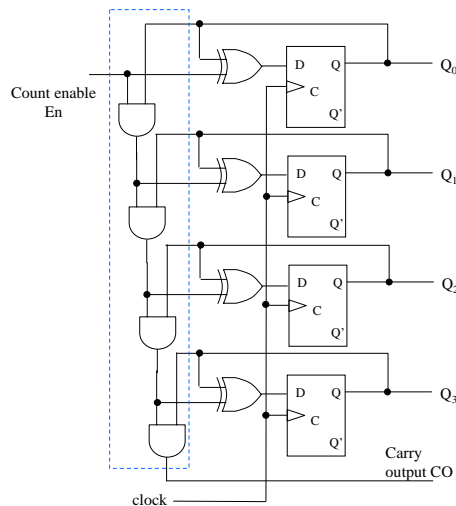
$$D_{Q_i} = Q_i \oplus (Q_0 Q_1 \dots Q_{i-1} En)$$



8/8/2005

Dr. Ashraf S. Hasan Mahmoud


16

Exercise: 4-bit Binary Counter with T flip-flops



- **Problem:** Verify that the circuit shown in Figure is a 4-bit synchronous binary counter

(Hint: Draw the timing diagram)

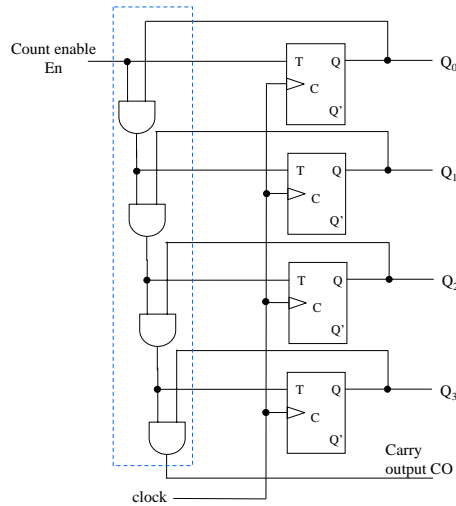


8/8/2005

Dr. Ashraf S. Hasan Mahmoud

17

What is the Use of the CO signal? Design of 8-bit Binary Counter

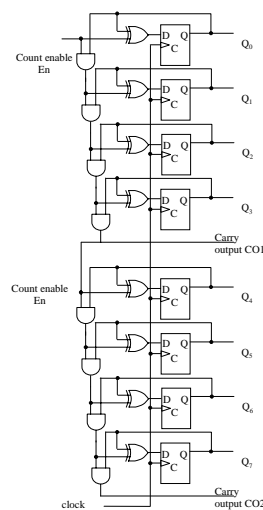- Using 4-bit counters with carry out signal one can construct larger counters by using the carry out signal from one stage as the enable signal of the next
- Figure shows 2 4-bit binary counters connected in series to form an 8-bit binary counter
- **Exercise:** Draw the timing diagram showing clock, Q0, Q1, Q2, Q3, CO1, Q4, Q5, Q6, Q7, and CO2



8/8/2005


Dr. Ashraf S. Hasan Mahmoud

18

Serial and Parallel Counters

- **When counter changes state from 1111 to 0000, how many AND gate delays there will be before CO is generated?**

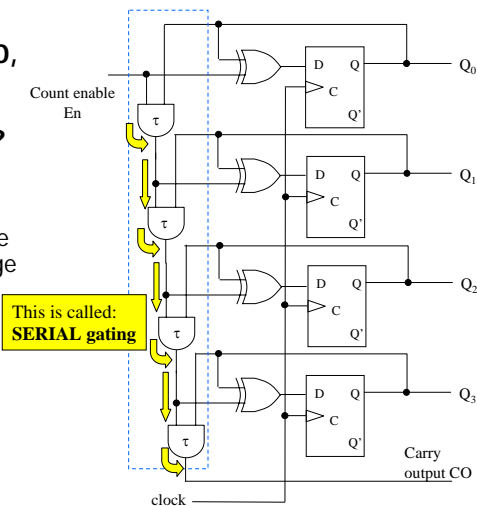- **Answer:** FOUR. Because stage 1 requires one AND gate delay to know the state change in Q_0 ; stage 2 requires one additional AND gate delay to know the state change in Q_1 ; stage 3 requires on additional AND gate delay to know the state change in Q_2 ; and to generate CO, one more AND gate delay is required.




8/8/2005

Dr. Ashraf S. Hasan Mahmoud


SERIAL counter

19

Timing Diagram for Serial Gating

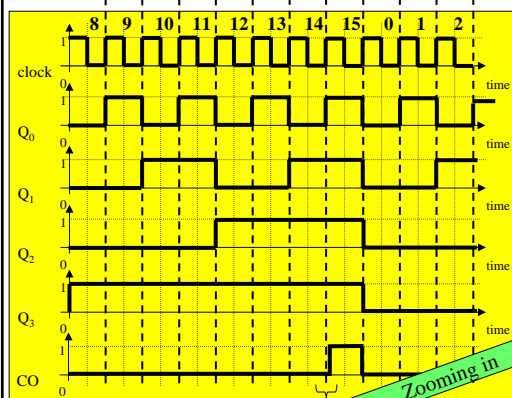

 CO has to be zeros after +ve edge border since $Q_{0,3}=0$



What happens if 4τ is greater than T ?

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

20

Why Serial Gating is Bad?

- Delay taken when CO signal is generated – if this CO signal is used to drive another counter (refer to 8-bit counter construction) → cumulative delay may exceed clock pulse (or cumulative delay limits speed of counting – clock frequency)
- Not good for design of fast counters
- **Solution:** Use parallel gating!

This problem is similar to the delay problem we faced with the ripple carry adder. The parallel gating is analogous to the carry lookahead adder idea where the required signals are generated without propagating the f/f status from Q0 to Q1 to Q2 to Q3


8/8/2005

Dr. Ashraf S. Hasan Mahmoud

21

Parallel Gating

 - For the D flip-flop synchronous binary counter, the equations for parallel gating can be taken directly from the AND terms in the flip-flop input equations on slide 15



parallel counter: ONE AND gate delay (τ) is required to generate CO


8/8/2005

Dr. Ashraf S. Hasan Mahmoud

22

Serial-Parallel Counter

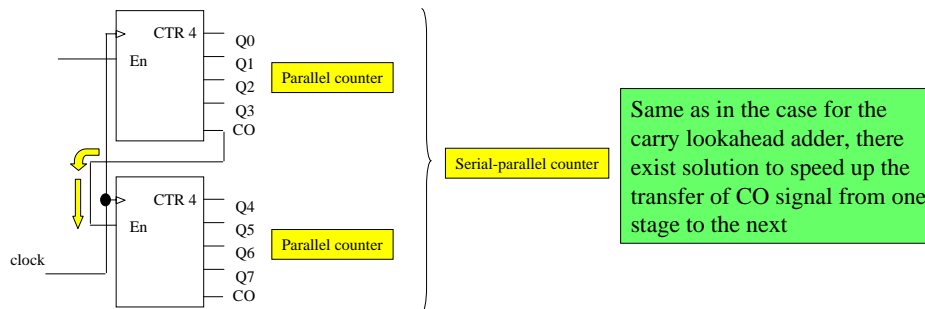- Each stage (4-bit counter) is constructed using parallel gating
- Stages are connected in series by using the CO output of one stage as the counter enable input of the next state



8/8/2005

Dr. Ashraf S. Hasan Mahmoud

23

Problem 5-20: Parallel Counter Design – Maximum Frequency

Problem: A 64-bit synchronous parallel counter is to be designed


- (a) Draw the logic diagram of a 64-bit parallel counter using 8-bit parallel counter blocks and two levels of parallel gating connections between the blocks. In these blocks CO is not driven by En

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

24

Problem 5-20: Solution

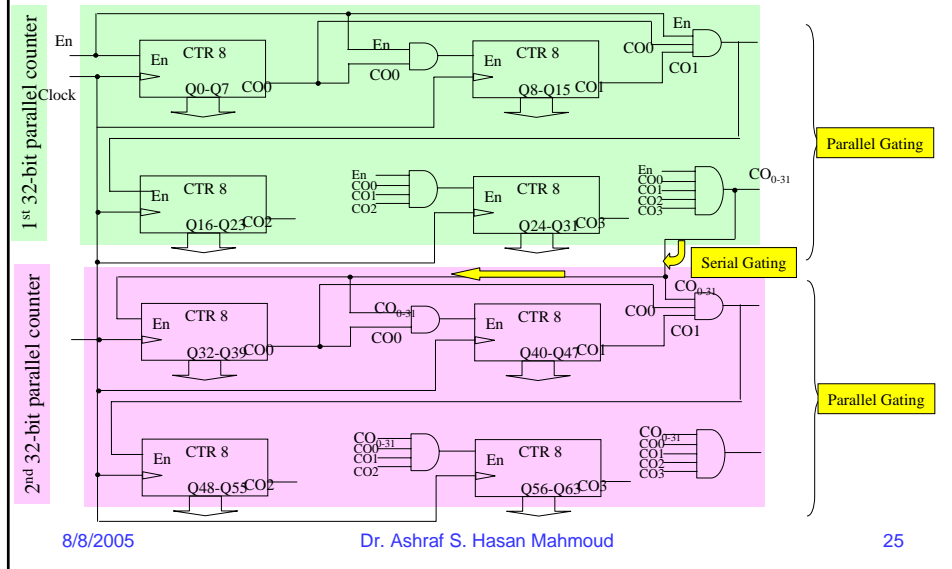

Problem 5-20: Solution – cont'd

- Notes:
 - Each of the CTR 8 blocks is a parallel counter (i.e. it uses parallel gating)
 - The 32-bit counter resulting from connecting the first (or second) 4 8-bit block counters is also a parallel counter since it uses parallel gating to generate the CO signals
 - The 2 32-bit counters are serially connected to form the required 64-bit counter



• Would it be possible to use only parallel gating to obtain the 64-bit counter? What would be the maximum fan in for the used AND gates in this case?

Synchronous Binary Down-Counter

- **Problem:** Design a 4-bit synchronous T flip-flop down-counter.
- **Solution:** (show that the previous circuits work as a down-counter if we use Q' instead of Q in the input equations; i.e. the as input to the AND gates – This applies to the JK flip-flop counter on slide 11, the D flip-flop counter on slide 16 and the T flip-flop counter on slide 17)

8/8/2005

Dr. Ashraf S. Hasan Mahmoud


27

Refer to problem 4-33 solved in the previous package – same problem but using JK F/Fs

Up-Down Binary Counter

- **Problem:** Design a synchronous up-down T flip-flop 2-bit binary counter with a select input line S and a count enable En input. When $S = 0$, the counter counts down; and when $S = 1$, the counter counts up. When $En = 1$, the counter is in normal up- or down- counting; and $En = 0$ for disabling both counts.
- **Solution:** Required mode of operation:

Functional Table:

 


Inputs		Operation
En	S	
0	x	Hold status
1	0	Count Down
1	1	Count Up

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

28

 State Diagram/Table for 2-bit Up-Down Binary Counter



Arc Label: EnS

T Flip-Flop		
Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

Present State			Inputs		Next State			T flip-flops	
No	Q1	Q0	En	S	No	Q1	Q0	T ₀₁	T ₀₀
0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	0
0	0	0	1	0	3	1	1	1	1
0	0	0	1	1	1	0	1	0	1
1	0	1	0	0	1	0	1	0	0
1	0	1	0	1	1	0	1	0	0
1	0	1	1	0	0	0	0	0	1
1	0	1	1	1	2	1	0	1	1
2	1	0	0	0	2	1	0	0	0
2	1	0	0	1	2	1	0	0	0
2	1	0	1	0	1	0	1	1	1
2	1	0	1	1	3	1	1	0	1
3	1	1	0	0	3	1	1	0	0
3	1	1	0	1	3	1	1	0	0
3	1	1	1	0	2	1	0	0	1
3	1	1	1	1	0	0	0	1	1

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

29

Input Equations for 2-bit Up-Down Binary Counter

EnS	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	0	0	1	0
10	0	0	0	1

$$T_{Q1} = Q_0 \text{EnS} + Q_0' \text{EnS}'$$

EnS	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

$$T_{Q0} = \text{En}$$

- The carry out signals:

- CO_{up} and CO_{down}

$\text{CO}_{\text{up}} = Q_0 Q_1 \text{EnS} \rightarrow$ counter reached 11 and it is counting up

$\text{CO}_{\text{down}} = Q_0' Q_1' \text{EnS}' \rightarrow$ counter reached 00 and it is counting down

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

30


Circuit for 2-bit Up-Down Binary Counter

$$T_{Q1} = Q_0EnS + Q_0'EnS'$$

$$T_{Q0} = En$$

$$CO_{up} = Q_0Q_1EnS$$

$$CO_{down} = Q_0'Q_1'EnS'$$

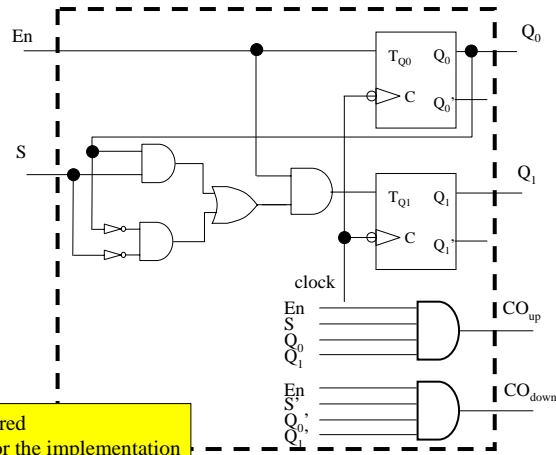

The F/Fs can be +ve or -ve edge triggered
 This would NOT affect the equations or the implementation
 It would, however, effect when the F/Fs can change state
 – see the timing diagram on next slide


8/8/2005

Dr. Ashraf S. Hasan Mahmoud

31

Circuit for 2-bit Up-Down Binary Counter –Timing Diagrams

Assume En = 1
 -ve edge trig F/Fs

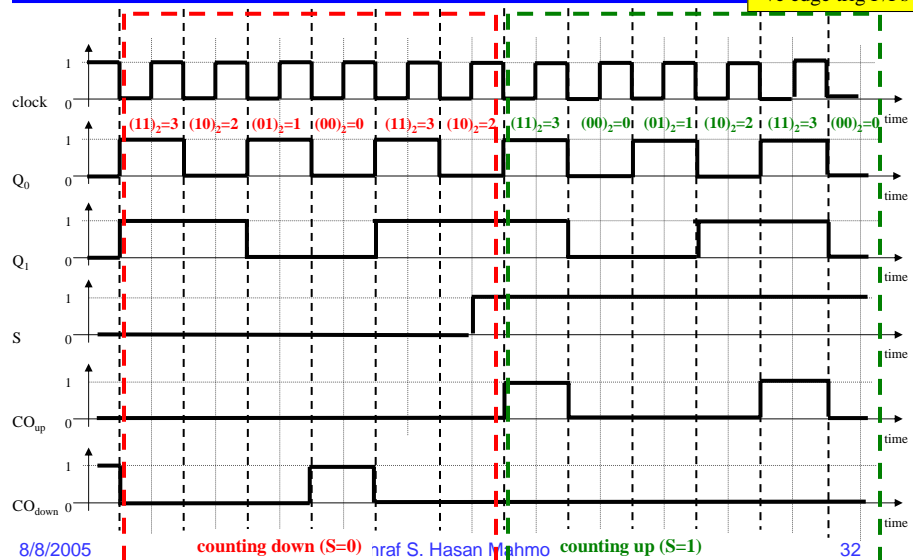

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

32

4-bit Up-Down Binary Counter

- You can show that input equations for 4-bit up-down binary counter are given by (compare to 2-bit case):

$$TQ0 = E_n$$

$$TQ1 = Q0.S.E_n + Q0'.S'.E_n$$

$$TQ2 = Q1.Q0.S.E_n + Q1'.Q0'.S'.E_n$$

$$TQ3 = Q2.Q1.Q0.S.E_n + Q2'.Q1'.Q0'.S'.E_n$$


$$CO_{up} = Q0.Q1.Q2.Q3.S.E_n$$

$$CO_{down} = Q0'.Q1'.Q2'.Q3'.S'.E_n$$

Binary Counter with Parallel Load

- **Counter with parallel load:** capability for transferring an initial binary number into the counter prior to the count operation

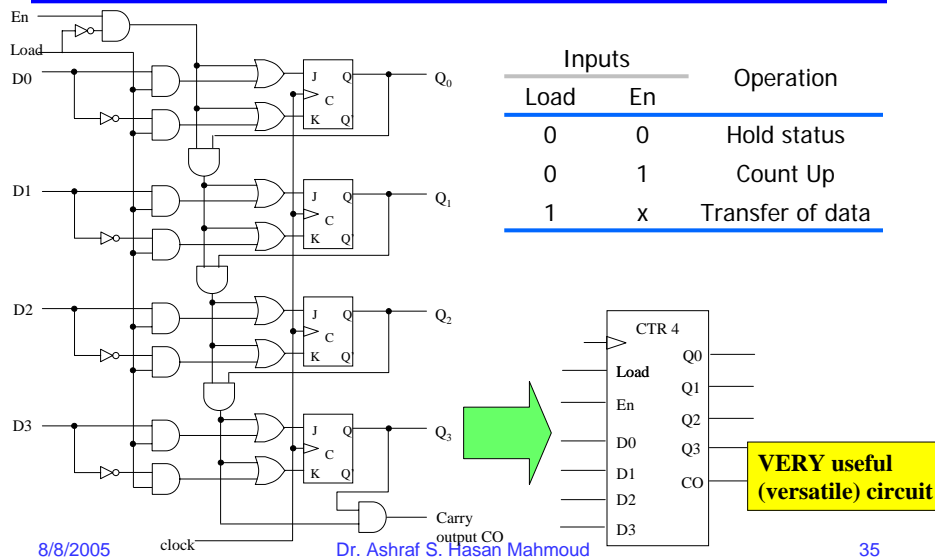Binary Counter with Parallel Load - Circuit




**VERY useful
(versatile) circuit**

BCD Counter

- **BCD Counter:**
0000 → 0001 → 0010 → ... → 1000 → 1001 → 0000 → 0010 → ...
- We can use the use binary counter with load (previous slide) as follows:

 Note: When $Q_3Q_2Q_1Q_0 = 1001$, the load signal is equal to 1 and the counter loads 0000 and starts counting again



Other Counters

- **Divide-by-N counter OR Modulo-N counter**: A counter that goes through a repeated sequence of N state
- This is the general definition of the counter
- The 4-bit Binary counter → divide-by-16 counter or modulo-16 counter (because we have 16 states)

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

37

BCD Counter - Revisited

- **Problem**: Design a BCD counter (without En) using T flip-flops with an output signal that can be used to extend the counter
- **Solution**:
 - Let's design one state (4-bit BCD which counts 0000→0001→ ... →1000→1001→0000→ ...)
 - Use the output 1001 to generate the carry out signal

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

38

BCD Counter – State Table

7 Flip-Flop			Present State				Next State				Output	Flip-flops inputs			
Q(t)	Q(t+1)	T	Q ₈	Q ₄	Q ₂	Q ₁	Q ₈	Q ₄	Q ₂	Q ₁	Y	T _{O8}	T _{O4}	T _{O2}	T _{O1}
0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	1	1	0	0	0	1	0	0	1	0	0	0	0	1	1
1	0	1	0	0	1	0	0	0	1	1	0	0	0	0	1
1	1	0	0	1	0	0	0	1	0	0	0	0	1	1	1
0	0	0	0	1	0	0	0	1	0	0	0	0	0	0	1
0	1	0	0	0	0	1	0	1	0	1	0	0	0	0	1
0	1	1	0	0	1	0	1	1	0	0	0	0	0	1	1
0	1	1	1	0	0	0	1	0	0	0	0	1	1	1	1
1	0	0	0	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	0	1	1	0	0	1

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

39

BCD Counter – Input Equation

Q ₂ Q ₁	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	x	x	x
10	1	1	x	x

$T_{Q1} = 1$

Q ₂ Q ₁	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	x	x	x	x
10	0	0	x	x

$T_{Q2} = Q_1 Q_8'$

Q ₂ Q ₁	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	x	x	x	x
10	0	0	x	x

$T_{Q4} = Q_1 Q_2$

Q ₂ Q ₁	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	x	x	x	x
10	0	1	x	x

$T_{Q8} = Q_1 Q_8 + Q_1 Q_2 Q_4$

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

40

BCD Counter – Input Equation


$$T_{Q1} = 1$$

$$T_{Q2} = Q_1 Q_8'$$

$$T_{Q4} = Q_1 Q_2$$

$$T_{Q8} = Q_1 Q_8 + Q_1 Q_2 Q_4$$

$$Y = Q_8 Q_1$$

 

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

41

Decimal Numbers Counters

- Synchronous BCD counters (same as the one built in previous slide) can be cascaded to form counters for decimal numbers of any length



- **Exercise 1:** Using the logic diagram of previous slide, design a counter which counts from 0 till 99 and then repeats



- **Exercise 2:** Given synchronous BCD counter with parallel load blocks (on slide 31) and perhaps using other logic gates design a stop watch that times up to one minute
 - What should be the frequency of the driving clock signal?

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

42

Arbitrary Count Sequence

- **Problem:** Design a counter that has a repeated sequence of 6 states, as listed in table. In this sequence, flip-flops B and C repeat the binary count 00, 01, 10, while flip-flop A alternates between 0 and 1 every three counts.
- **Solution:**

Present State			Next State		
A	B	C	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	0	0	0

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

43

Arbitrary Count Sequence – State Table

- Assuming *JK* flip-flops


Present State			Next State			Flip-flop Inputs					
A	B	C	A	B	C	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	x	1	0	x

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

44

 Arbitrary Count Sequence – Input Equations





8/8/2005

Dr. Ashraf S. Hasan Mahmoud

45

 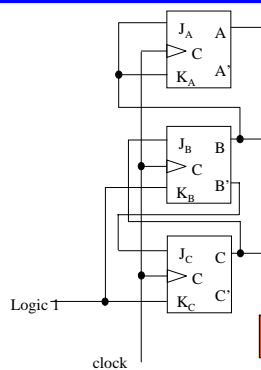Arbitrary Count Sequence – Circuit and Unused States



1) What if the counter “finds itself” in state 111 or state 011? Will the counter be able to proceed (count) normally afterward? How?

2) Is this circuit safe or reliable?


8/8/2005

Dr. Ashraf S. Hasan Mahmoud

46

Problem 5-23:

 - **Problem:** Using the two binary counters shown in figure and logic gates, construct a *binary* counter that counts from 9 through *binary* 69. Add an additional input to the counter that initializes it synchronously to 9 when the INIT is 1



8/8/2005

Dr. Ashraf S. Hasan Mahmoud

47

Problem 5-23: Solution

- **Solution:**

The key word in the problem statement is "*BINARY*"
Hence the designed counter should count in binary from binary 9 through binary 69 and then back to binary 9 and so on

Binary 9 → 0000 1001

Binary 69 → 0100 0101

Hence it is obvious that the two counters providing 8 Qs are enough to represent 69

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

48

Problem 5-23: Solution-cont'd

- **Solution:**
- The counting sequence is as shown in table
- Note that:
 - The we can assign first bit counter to count $Q_3Q_2Q_1Q_0$ while the second is assigned $Q_7Q_6Q_5Q_4$
 - Note that second counter increments count only if $Q_3Q_2Q_1Q_0$ is equal to 1111; i.e the CO signal first counter is 1
 - During count – first counter counts normally from 01001 all the way to 1111 and back to 0000, 0001, etc except when binary 69 is reached – 1001 is reloaded again
 - During count – second counter counts normally from 0000 all the way to 0100 and then it restarts from 0000 again.


No	Binary
	$Q_7Q_6Q_5Q_4$ $Q_3Q_2Q_1Q_0$
9	0000 1001
10	0000 1010
11	0000 1011
12	0000 1100
.	.
15	0000 1111
16	0001 0000
17	0001 0001
18	0001 0010
19	0001 0011
20	0001 0100
21	0001 0101
.	.
68	0100 0100
69	0100 0101
9	0000 1001
10	0000 1010
.	.

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

49

Problem 5-23: Solution-cont'd

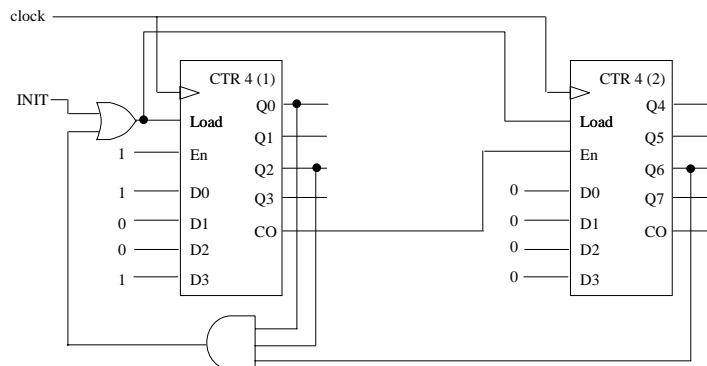


8/8/2005

Dr. Ashraf S. Hasan Mahmoud

50

Exercise: BCD Counter

 - **Problem:** Using the two binary counters shown in figure and logic gates, construct a *BCD* counter that counts from 9 through *BCD* 69. Add an additional input to the counter that initializes it synchronously to 9 when the INIT is 1



8/8/2005

Dr. Ashraf S. Hasan Mahmoud

51

Exercise: BCD Counter – cont'd

Solution:

- The key word in the problem statement is "*BCD*"
- The counting sequence is as shown in table:
 - Counter 1 ($Q_3Q_2Q_1Q_0$) counts 9, 0, 1, 2, ..., 9, 0 and so on
 - Counter 1 increments every clock cycle
 - Counter 2 ($Q_7Q_6Q_5Q_4$) counts 0, 1, 2, 3, 4, 5, 6, 0, 1, and so on
 - Counter 2 increments every time counter 1 reaches 1001
 - Counter 1 loads
 - 0000 when 9 is reached; OR
 - 1001 if INIT is 1 or 69 is reached
 - Counter 2 loads 0000 when 69 is reached or when INIT is 1


No	Binary			
	Q_7	Q_6	Q_5	Q_4
9	0000	1001		
10	0001	0000		
11	0001	0001		
12	0001	0010		
13	0001	0011		
14	0001	0100		
15	0001	0101		
16	0001	0110		
17	0001	0111		
18	0001	1000		
19	0001	1001		
20	0010	0000		
21	0010	0001		
22	0010	0010		
23	0010	0011		
24	0010	0100		
25	0010	0101		
26	0010	0110		
27	0010	0111		
28	0011	0000		
29	0011	0001		
30	0011	0010		
31	0011	0011		
32	0011	0100		
33	0011	0101		
34	0011	0110		
35	0011	0111		
36	0100	0000		
37	0100	0001		
38	0100	0010		
39	0100	0011		
40	0100	0100		
41	0100	0101		
42	0100	0110		
43	0100	0111		
44	0101	0000		
45	0101	0001		
46	0101	0010		
47	0101	0011		
48	0101	0100		
49	0101	0101		
50	0101	0110		
51	0101	0111		
52	0110	0000		
53	0110	0001		
54	0110	0010		
55	0110	0011		
56	0110	0100		
57	0110	0101		
58	0110	0110		
59	0110	0111		
60	0111	0000		
61	0111	0001		
62	0111	0010		
63	0111	0011		
64	0111	0100		
65	0111	0101		
66	0111	0110		
67	0111	0111		
68	1000	0000		
69	1000	0001		
70	1000	0010		
71	1000	0011		
72	1000	0100		
73	1000	0101		
74	1000	0110		
75	1000	0111		
76	1001	0000		
77	1001	0001		
78	1001	0010		
79	1001	0011		

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

52

Exercise: BCD Counter – cont'd

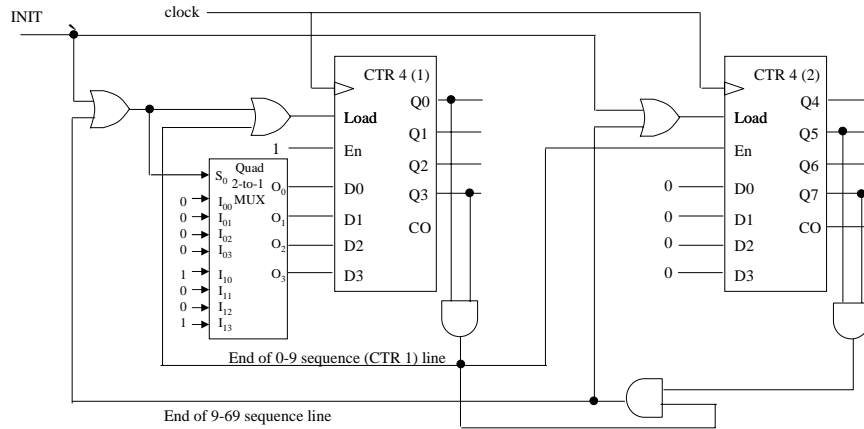


The circuit can be built without using the MUX as shown in next slide

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

53

Exercise: BCD Counter – cont'd

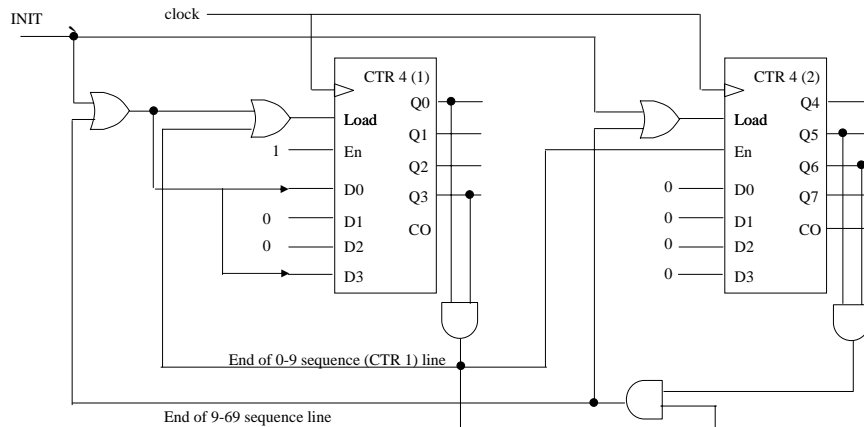

8/8/2005

Dr. Ashraf S. Hasan Mahmoud

54

Problems of Interest:

- Problems (registers): 5-3, 5-4, 5-6, 5-7, 5-8, 5-9, 5-10, 5-11, 5-12,
- Problems (counters) : 5-16, 5-17^s, 5-18, 5-19, 5-20 (a) ^s