

COMPUTER ENGINEERING DEPARTMENT

COE-202 – Fundamentals of Computer Engineering (section 02)

Student Name:


Student Number:

Q1. (20 points) Given the function $F(A,B,C,D) = AB'C' + AC + A'CD'$


- Plot the K-Map for $F(A,B,C,D)$
- Determine the Prime Implicants and the Essential Prime Implicants for function $F(A,B,C,D)$.
- Simplify the function $F(A,B,C,D)$ in the form of sum of products
- Simplify the function $F(A,B,C,D)$ in the form of product of sums
- Implement the circuit in part (d) with NOR gates.

Solution:

a) The K-Map is as shown in figure:

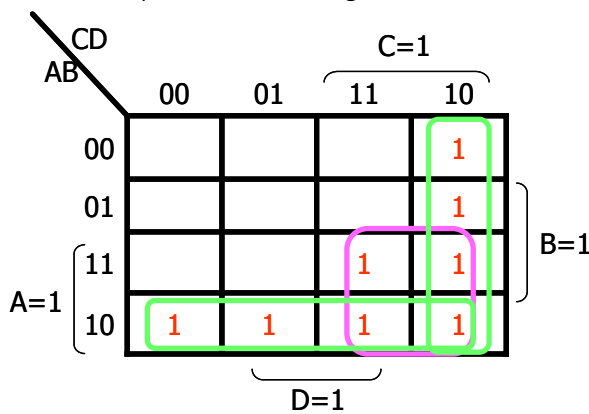

K-map for $F(A,B,C,D)$

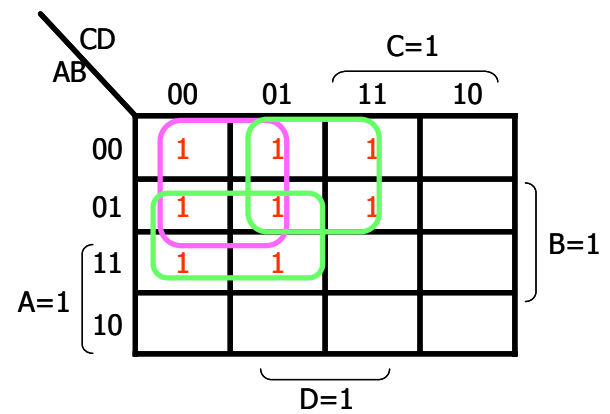

K-map for $F'(A,B,C,D)$ {NOT REQUIRED}

- The Prime Implicants are: AB', CD', AC
The Essential Prime Implicants are: AB', CD', AC
- $F(A,B,C,D) = AB' + AC + CD'$
- $F'(A,B,C,D) = BC' + A'C' + A'D$, →
therefore, $F(A,B,C,D) = (B'+C)(A+C)(A+D')$
- The implementation for part (d) is as shown:

