

COMPUTER ENGINEERING DEPARTMENT**COE-202 – Fundamentals of Computer Engineering (section 02)
POP QUIZ****Student Name:****Student Number:****Q1. (20 points)** Consider the T-Latch shown in figure.

- Write the functional table.
- Write the characteristic table for the latch.
- Derive the characteristic equation for the latch.
- Write the excitation table for the latch.

