

***KFUPM - ELECTRICAL ENGINEERING DEPARTMENT***

**EE-200 – Digital Logic Circuit Design (section 05) – Quiz03**

**Student Name:**

**Student Number:**

---

---

**Problem:**

Design a combinational circuit that produces a 1 if the 4-bit input ABCD represents an invalid BCD digit. Implement the circuit using NAND only gates.