

EE 200: Digital Logic Circuit Design

Dr Radwan E Abdel-Aal, COE

Unit 4 Sequential Circuits

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)


Unit 4: Sequential Circuits (Finite State Machines FSM)

1. Sequential Circuit Definitions, Types of Latches: SR, Clocked SR, and D Latches
 2. Flip-Flops: SR, D, JK, and T Flip-Flops
 3. Flip-Flop Timing Parameters: Setup, hold, propagation, clocking
 4. Flip-Flops: Characteristic Tables and Excitation Tables
 5. Analysis of Sequential Circuits with various types of flip-flops: Deriving the input equations, state table, and state diagram. Timing.
 6. Design of Sequential Circuits with various types of flip-flops: Determining the state diagrams and tables, State assignment, Combinational Logic
-
- Introduce
New needed
Components
(memory
elements)
- Analysis
- Design

 part 1 2

Introduction to Sequential Circuits


Outputs are functions of inputs and **some previous (state) outputs**



■ A Sequential Circuit (SC) consists of:

- **Data Storage (memory) elements: (Latches / Flip-Flops)** The storage (memory) elements isolate the next state from the present state, So changes occur only when desired
- **+ Combinatorial Logic:** Implements a multiple-output function
 - **External Inputs** are signals **from** outside
 - **External Outputs** are signals **to** outside
 - **State inputs (Internal to SC) = Present State** at o/p of storage elements
 - **State outputs, Next State** at i/p of storage elements

Introduction to Sequential Circuits (SC)

 


■ Combinational Circuit outputs:

- **Next state:**
Next State = $f(\text{Inputs}, \text{State})$
- **External Output:- Two Possibilities:**
 - **Mealy Circuits**
Outputs = $g(\text{Inputs}, \text{State})$
 - **Moore Circuits**
Outputs = $h(\text{State only})$


Timing of Sequential Circuits

Two Approaches

- Behavior depends on the times at which the storage elements 'sense' their inputs and 'change' their outputs ("next state" becomes "present state")
- Asynchronous (No clock)**
 - Behavior defined from knowledge of inputs **at any instant of time** and the order in which inputs change in **continuous time**
- Synchronous (More common)**
 - Behavior is determined by the signals at **discrete** times (**clock pulses**)
 - Storage elements sense their inputs / change state **only** according to a **timing and synchronizing signal** (a **clock**)
- Will use mainly the **synchronous** approach here

 


Data Storage Logic Structures for SCs

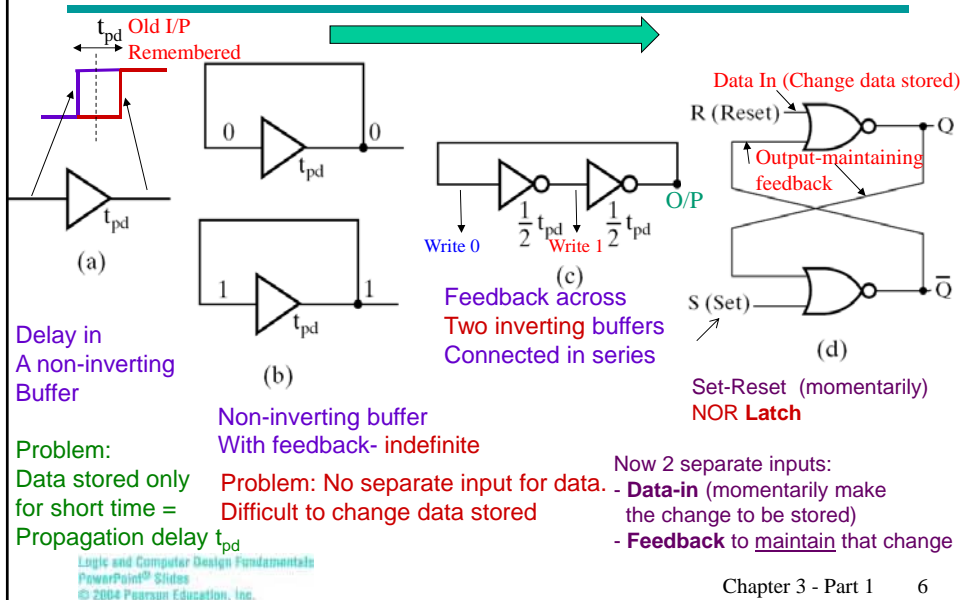

Basic NOR Set-Reset (SR) Latch

Set: Make Q = 1, Reset: Make Q = 0

 - **Cross-coupling** two NOR gates gives the Set - Reset Latch:




- Which has the time sequence behavior:

00 = Normal input condition
No input change (show last stored I/P)
Input R S stored (written) in Q Q-bar (remains at O/P after input is removed)

Time	R	S	Q	Q-bar	Comment
	0	0	Q	Q-bar	Show the last stored data
	0	1	1	0	"Set" Q to 1 (Write 1)
	0	0	1	0	Q "remembers" written 1 after I/P disappeared
	1	0	0	1	"Reset" Q to 0 (Write 0)
	0	0	0	1	Q "remembers" written 0 after I/P disappeared
	1	1	0	0	Both Q and Q-bar = 0 (Avoid)
	0	0	?	?	Undefined! (Q = 1 or 0)


S = 1, R = 1 simultaneously is a forbidden input pattern

Basic NOR Set-Reset (SR) Latch

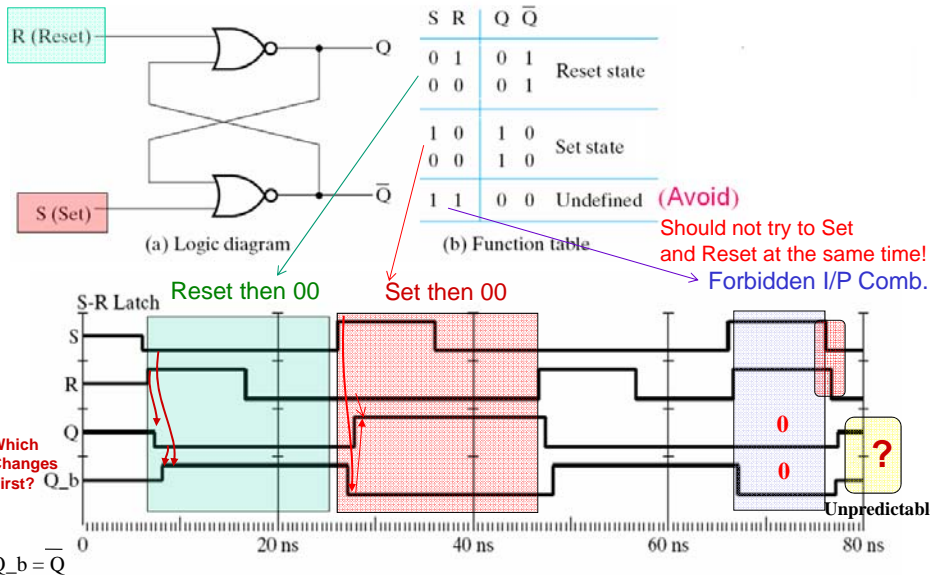

Basic NAND \overline{S} - \overline{R} Latch

 - Cross-coupling two NAND gates gives the \overline{S} - \overline{R} Latch:




- Which has the time sequence behavior:

Time	\overline{S}	\overline{R}	Q	\overline{Q}	Comment
	1	1	Q	\overline{Q}	Show the last stored data
	0	1	1	0	"Set" Q to 1 (Write 1)
	1	1	1	0	Q "remembers" written 1 after I/P disappeared
	1	0	0	1	"Reset" Q to 0 (Write 0)
	1	1	0	1	Q "remembers" written 0 after I/P disappeared
	0	0	1	1	Both Q and \overline{Q} go high (Avoid)
	1	1	?	?	Undefined! (Q could be 0 or 1)

S = 0, R = 0 simultaneously is a forbidden input pattern

Clocked (or Controlled) S-R NAND Latch

 - Adding two NAND gates to the basic \overline{S} - \overline{R} NAND latch gives the **clocked** S - R latch:



Clock is a "gate" for S, R

This latch is **Transparent**: i.e. O/P follows the I/P **directly** when C = 1

- C = normally 0 \rightarrow \overline{S} \overline{R} inputs to the latch = normally 1 1 (No output change)

So this **prevents** the forbidden conditions \overline{S} \overline{R} = 0 0 **with** C = 0

- C = 1 **Opens** the two input NANDs for the S R, inverting them.

This gives normal S R (not \overline{S} \overline{R})

latch operation \rightarrow Allow changes in latch state

But here both S R = 1 1 with C = 1 is still a problem

- C means "control" or "clock". Changes in SR **affect the latch only** during the clock pulse

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

Freeze (Read)

The Clocked D Latch-

Totally avoids the SR = 11 Problem!

- Adding this inverter to the S-R Latch, makes it a D Latch
- We got rid of the unwanted condition (SR = 11 with C = 1)
- But also lost SR = 00 (no change)!


When C = 1, this latch

is **transparent**:

The D I/P is


effectively 'connected'

to output Q, i.e. Q follows D

 

With C = 0:

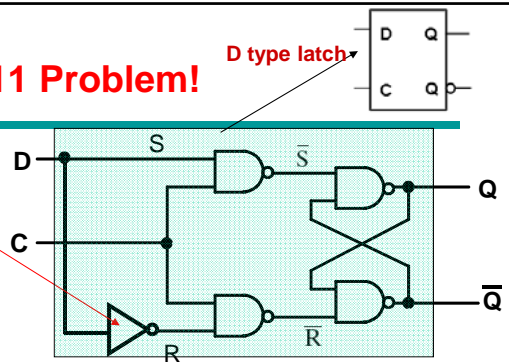Freeze Output at last value written when C was 1, (can change only when C becomes 1 again)



To get 'no change':

Must block the clock pulses!

C	D	Next state of Q
0	X	No change (Q = last Q before C went from 1 to 0)
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

Function Table

Chapter 3 - Part 1


11

From Latches to Flip-Flops

- The **transparent** latch timing problem
- Solution: Flip-Flop
 - Master-slave **flip-flop**
 - Edge-triggered **flip-flop**
- Standard symbols for storage elements
- **Direct inputs** to flip-flops
- Flip-flop timing
- Types of flip-flops: D, JK, T

The Transparent Latch as a Storage Element: Timing Problem

- Consider this sequential circuit:

 


- Suppose that initially $Y = 0$.
- As long as $C = 1$, the value of Y keeps changing!
- Changes occur based on the delay in the Y-to-Y loop
- If $t_{y,y} \ll t_{cw}$ this causes **several unwanted state changes** to occur during the same clock pulse- **unacceptable!**
- Desired behavior:** Y should change **only once** per clock pulse, in order to get **only one** state transition per clock pulse!

Solving the Latch Timing Problem Flip flops instead of latches

- Two approaches:
 - Break the path within the storage element into **two** successive (mutually exclusive) steps in time:
 - Step - 1. Register the change in input D (then stop)
 - Step - 2. Apply that change to the output Y (then stop)
 This uses a **master-slave** (Pulse Triggered) flip-flop
 - OR
 - Use an **edge-triggered** flip-flop:
 - Change in D is sensed and applied to the Q output in **one go at the edge** of the clock pulse (+ ive or - ive edge) i.e. Effectively as if we have a Zero-width clock pulse, which obviously solves the problem (see previous slide)

S-R Master-Slave (Pulse-Triggered) Flip-Flop

 - Consists of two clocked S-R latches in series, with the clock to the second latch **inverted**



- C = 1: - Master is open

1st half Of clock Pulse · Slave is blocked

Only “input is sensed” by master for this pulse duration (→ **pulse-triggered**) while output is unchanged by slave



- C = 0: - Master is Blocked

2nd half Of clock Pulse · Slave is open → “output is changed”

- The path from input to output is thus **broken** by the different 2 clock levels for the two latches (C = 1 and C = 0)
- Sensing I/P then changing O/P are now **two separate steps** - **not** one **transparent** step as the case with the transparent latch


S-R Master-Slave Flip-Flop: Simulation

 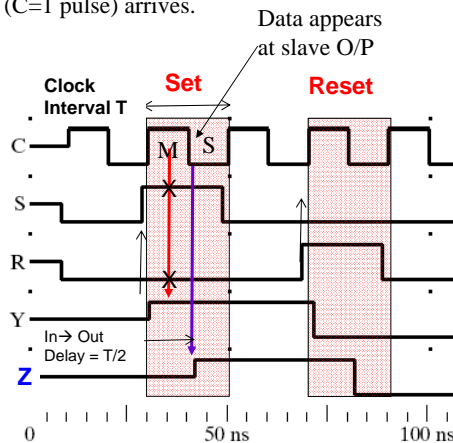Ideally, changes in S, R inputs from combinational circuit should **arrive to master before** the next clock interval (C=1 pulse) arrives.



Edge-Triggered D-type Flip-Flop

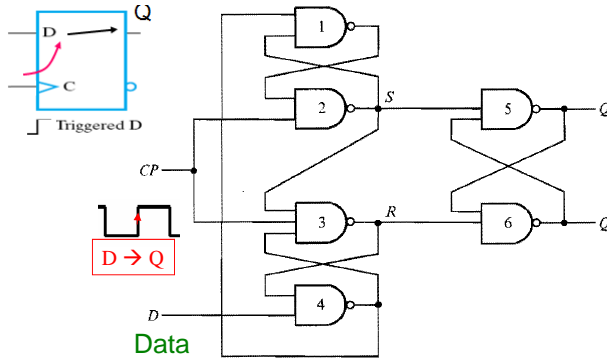- This is a **Positive Edge-triggered D-type flip-flop**



- Is currently the **most preferred FF** for building sequential circuits

- The D data input is transferred to the Q output **only** at the rising edge of the clock, subject to **timing constraints on the D input relative to effective clock edge**: **Setup time before** edge and **Hold time after** edge
- Negative edge triggered D FF is also available

17


Flip-Flop Timing Parameters: - ive Edge Triggered FF (Section 6.3)

Requirements:

- t_w - clock pulse width (for both low & high)
- t_s : setup time
- t_h : hold time (usually 0 ns)

Outcomes:

- t_p : propagation delay

 


Consider a **Negative Edge-Triggered D Flip Flop**

D input can still change up to here!
Better utilization of time
→ faster sequential cct designs compared to Master-Slave FF


Standard Symbols for Storage Elements

Unlocked
clocked


1. Latches (Transparent)

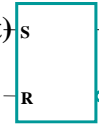


SR

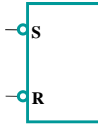

$\overline{S}\overline{R}$

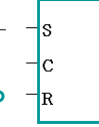

SR, Active high Clk




D, Active high Clk

Transparent Latches,
Provide No I-O isolation

2. Flip Flops

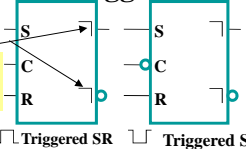a. Master-Slave (M-S) Pulse-Triggered:

O/P determined during clock pulse width and changed at its end




Triggered SR Triggered SR

(b) Master-Slave Flip-Flops

In a sequential that uses different Types of FFs, Ensure that all FFs circuit change their outputs at the **same clock edge**. Invert clock signal to some FFs if needed

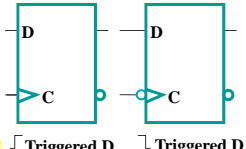b. Edge-Triggered:

O/P determined & changed on the indicated clock edge




Triggered D Triggered D

(c) Edge-Triggered Flip-Flops

One problem with D type FF is that no D inputs produce "no change" at the output
Solution:
- Block the clock pulses
- Feed back the Q to the D input when **no change** is required (See Unit 5)

FF Direct Inputs

- When power is turned ON, the state of a sequential circuit FFs could be **anything!**
- We usually need to **initialize** the circuit to a **known state** before operation starts
- This initialization is often done **directly** outside the clocked behavior of the circuit, i.e., **asynchronously**
- Direct S and/or R inputs that control the state of the latches within the flip-flops are added to FFs for this purpose
- For the example the flip-flop shown
 - 0 applied to \overline{R} directly ($\overline{S}=1$): resets the flip-flop to the 0 state **regardless of the clock**
 - 0 applied to \overline{S} directly ($\overline{R}=1$): sets the flip-flop to the 1 state **regardless of the clock**

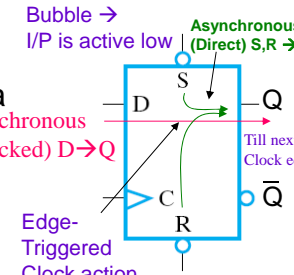

Bubble → I/P is active low
Asynchronous (Direct) S,R → Q
Synchronous (clocked) D → Q
Edge-Triggered Clock action
Till next Clock edge

S	R	C	D	Q	\overline{Q}
0	1	X	X	1	0
1	0	X	X	0	1
0	0	X	X	Undefined	

Active Low

Asynchronous Action- **Regardless** of the clock

Synchronous (clocked) action

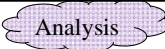

(b) Function table

Chapter 3 - Part 1 20



Other Types of Flip-Flops


- We know about the master-slave S-R and D flip-flops
- We will briefly introduce the J-K and T flip-flops
 - Implementation
 - Behavior
 - **Characteristic** Table/Equation: For use in **SC Analysis**
 - **Excitation** Table/Equation: For use in **SC Design**

© 2004 Pearson Education, Inc.

Analysis  **Characteristic** 


Basic Flip-Flop Descriptors

Excitation  

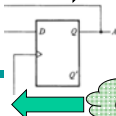

- In **analysis**: Given a Circuit:
 Present state, I/Ps → CL → FF Inputs → ? FF O/P (Next state) ?
 FF: FF Inputs & Present output → Next FF output?
 - **Characteristic table** - defines the next output of the flip-flop given its **present output and its inputs**
 - **Or Characteristic equation** - defines the next output of the flip-flop as a Boolean function of its present output and its inputs
- In **design**: Given a **state transition** behavior → ? CL ?
 FF: Present output & Next output → ? FF inputs? (that give such behavior)
 - **Excitation table** - defines the flip-flop inputs that give a **required present-to-next output behavior**

D Flip-Flop

 

Analysis

Characteristic Table

Input-Driven	Analysis		Operation	Does not depend on the present O/P Next O/P = Present I/P
	D(t)	Q(t+1)		
0	0	0	Reset	
1	1	1	Set	

Characteristic Equation

$$Q(t+1) = D(t)$$

Limitation of D FF:
No built-in "No Change" Condition while clock is connected

Design

Excitation Table

Output-Driven	Design		Operation	Present I/P = Desired Next O/P
	Q(t+1)	D(t)		
0	0	0	Reset	
1	1	1	Set	

Hence simplicity of using D FF

S-R Flip-Flop

Pulse or Edge -Triggered?



Characteristic Table

Input-Driven	Analysis		Operation	Given the present FF I/Ps, O/P → Next FF O/P = ? ← Improvement on D !
	S	R		
0 0	0	0	$Q(t)$ No change	
0 1	0	1	Reset	
1 0	1	0	Set	
1 1	1	1	? Undefined	Limitation: SR=11: "Undesirable" Condition

Characteristic Equation

$$Q(t+1) = S + \bar{R} Q(t)$$

Excitation Table

Output behavior-Driven	Design		S	R	Operation	Given Present, next O/P s → FF Inputs = ? Get from above
	Q(t)	Q(t+1)				
0	0	0	0	X	No change , Or Reset	
0	1	1	1	0	Set	
1	0	0	0	1	Reset	
1	1	1	X	0	No change , Or Set	

J-K Flip-Flop- Improvements on SR and D types
 → on SR: Avoids the “SR = 11”, JK = 11 → Toggle, i.e. $Q(t+1) = \bar{Q}(t)$
 → on D type: Allows a ‘No Change’ condition

▪ **Characteristic Table**


S	R	Q(t+1)	Operation	J	K	Q(t+1)	Operation
0	0	Q(t)	No change	0	0	Q(t)	No change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	?	Undefined	1	1	$\bar{Q}(t)$	Complement (Toggle)

▪ **Characteristic Equation**

$$Q(t+1) = J\bar{Q}(t) + \bar{K}Q(t)$$

▪ **Excitation Table**

Q(t)	Q(t+1)	J	K	Operation
0	0	0	X	No change , Or Reset
0	1	1	X	Set , Or Toggle
1	0	X	1	Reset , Or Toggle
1	1	X	0	No Change , Or Set

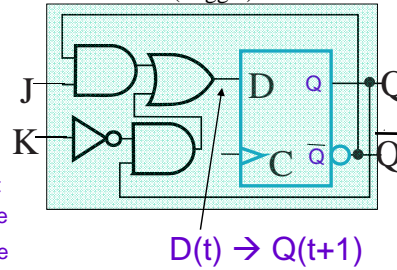

T (Toggle) Flip-Flop
 D FF with only “No change” & “toggle” capabilities

▪ **Characteristic Table**


T	Q(t+1)	Operation
0	Q(t)	No change
1	$\bar{Q}(t)$	Complement (Toggle)

▪ **Characteristic Equation**

$$Q(t+1) = D(t) = T \oplus Q(t)$$


▪ **Excitation Table**

Q(t+1)	T	Operation
Q(t)	0	No change
$\bar{Q}(t)$	1	Complement (Toggle)

 

Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

Sequential Circuit Analysis & Design

 

Analysis:

Given a circuit. → Describe how it behaves, in terms of: Present State, Inputs → Next State? Outputs?,

Design:


Given how a circuit behaves, in terms of: Present State, Inputs → Next State, Outputs, → Determine the circuit

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Sequential Circuit Analysis: With D-type FFs

General Model

 - Present State (state) at time (t) are the O/Ps of an array of flip-flops
- Next State at (t+1) are O(t) combinational fns of {State & Inputs}
- (External) Outputs at time (t) are a combinational function of State (t) only (Moore) and also Inputs (t) (Mealy)



Max # of states for a circuit with 4 FFs?

How many FFs needed for a circuit with 6 states?

... the next clock pulse comes:
→ t becomes t+1,
→ O(t) is moved to FF output, thus becoming State (t+1), i.e. next state

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Sequential Circuit Analysis

- Given a sequential Circuit
- Objective: Obtain outputs & state behavior (**External outputs and next state**) from (**External inputs and present state**) for **all combinations** of I/Ps & present state
- Two equivalent approaches to represent the results of the analysis:
 - State table: A **truth table-like** approach
 - State diagram: A **graphical, more intuitive** way to represent the state table and express sequential circuit operation


Analysis Example using D FF:

Given a Sequential Circuit → Determine how it behaves

- External Inputs: $x(t)$
- External Outputs: $y(t)$
- State Outputs: $A(t), B(t)$

In **Analysis** we determine:

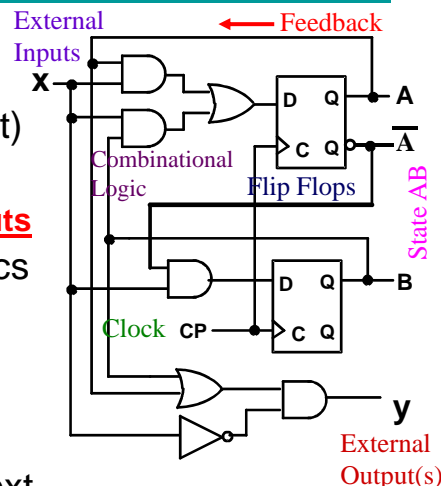
- Comb. Equations for the **FF inputs**
→ then use FF characteristics to get the next state given a present state and inputs
- Comb. Equations for the **External Outputs**
→ and use them to get the ext outputs given a present state and inputs



→ Synchronous or asynchronous?
→ Mealy or Moore?

Analysis Example 1: **A Mealy Circuit**, Ext. Output = F(state, inputs)
 Deriving flip flop input equations

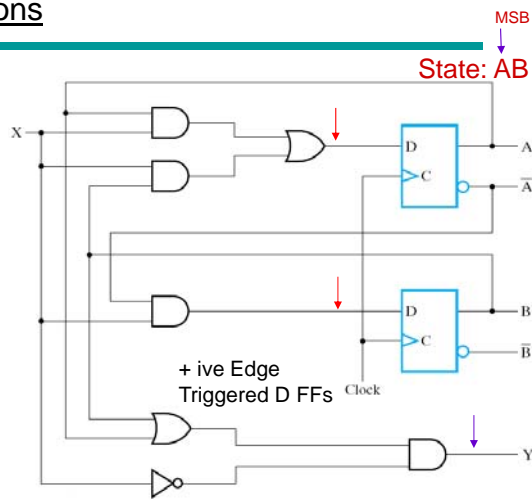- Right at the outset, there are things we can do:
 We can derive Boolean equations for *all outputs* of the combinational logic (CL) circuits
- Two types of CL outputs:
 - **Flip flop inputs**
 (Will determine the next state based on FF characteristics)
 $D_A = AX + BX$
 $D_B = \overline{A}X$
 - **External Outputs:**
 $Y = (A+B) \overline{X}$



Note: Flip flop inputs needed to determine next state depend on the type of flip flop used, e.g. D, SR, etc.

State Table Characteristics

- State table** – a multi variable table with the following four “vertical” components: **CL = Combinational Logic**
 - **CL Inputs:** FF = Flip Flop
 - Present State (MSBs) – Values of the state variables (FF outputs) for each allowed state
 - External Inputs
 - **Outputs:**
 - Next-state – Value of the state (FF outputs) at time (t+1). Determined by:
 - FF inputs (outputs of CL)
 - the FF characteristics: Simplest for D-type FF: $D \rightarrow Q$
 - CL External Outputs – the value of the outputs as a function of the present state only (Moore) or present state & external inputs (Mealy)

State Table for Circuit of Figure 6-17

Present State			Input	Next State		Output
A	B	X		(D _A)	(D _B)	Y
0	0	0		0	0	0
0	0	1		0	1	0
0	1	0		0	0	1
0	1	1		1	1	0
1	0	0		0	0	1
1	0	1		1	0	0
1	1	0		0	0	1
1	1	1		1	0	0

One-Dimensional State Table

FF Input Equations:

$$D_A = AX + BX$$

$$D_B = \overline{AX}$$

of rows in Table = $2^{(\# \text{ of FFs} + \# \text{ of external inputs})}$

In general, Get from:
 - Equations for FF input (CL)
 - Then FF Characteristic table or equation
 For D-type FF: Simply $D_i \rightarrow Q_i$ Purely Combinational

Two State Variables:
 A, B: \rightarrow 4 states

State Table for Circuit of Figure 6-17

Present State			Input	Next State		Output
A	B	X		A ⁺ (DA)	B ⁺ (DB)	Y
0	0	0	Inputs Vary	0	0	0
0	0	1		0	1	0
0	1	0		0	0	1
0	1	1		1	1	0
1	0	0		0	0	1
1	0	1		1	0	0
1	1	0		0	0	1
1	1	1		0	0	0

4 states, 1 ext input

Logic and Computer Design Fundamentals
 PowerPoint® Slides
 © 2004 Pearson Education, Inc.

The Two-Dimensional State Table a step closer to the State Diagram

$D_A = AX + BX$
 $D_B = \overline{AX}$

of rows in Table = $2^{(\# \text{ of FFs})}$
 and O/Ps are given separately for each I/P combination

Two State Variables A, B
 \rightarrow 4 states

(If Moor?)

of bays = # of input combinations

Present state Only		Next state (Mealy) Output			
		X = 0		X = 1	
A	B	A	B	Y	Y
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	0	1	0
1	1	0	0	1	0



of rows = # of states

Next State = $f(\text{State, I/P})$

Output (Mealy) = $f(\text{State, I/P})$

Chapter 3 - Part 1 34

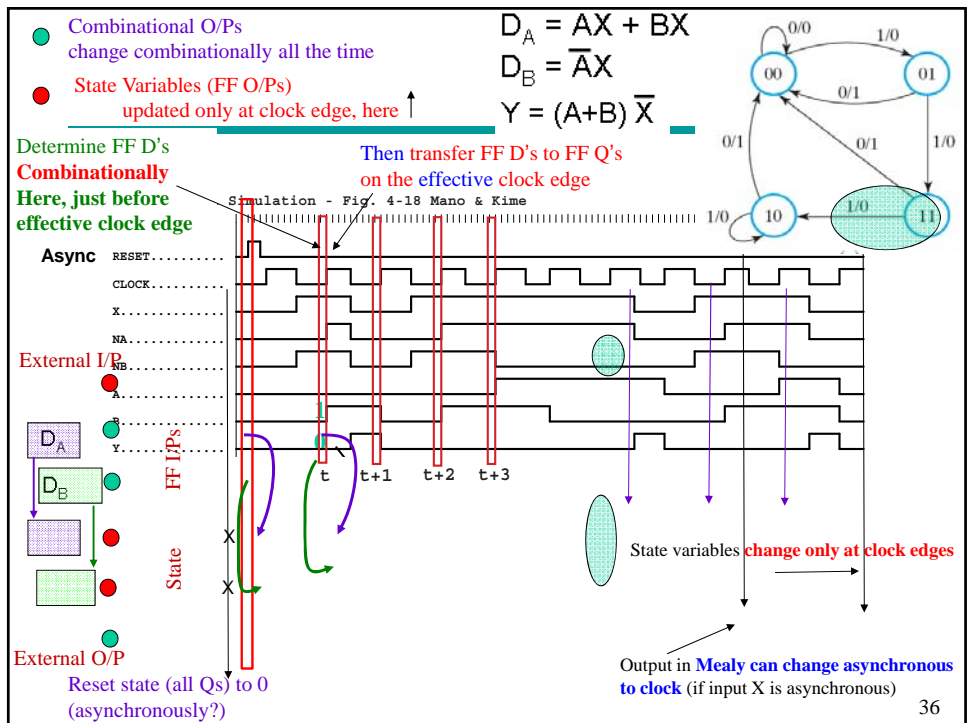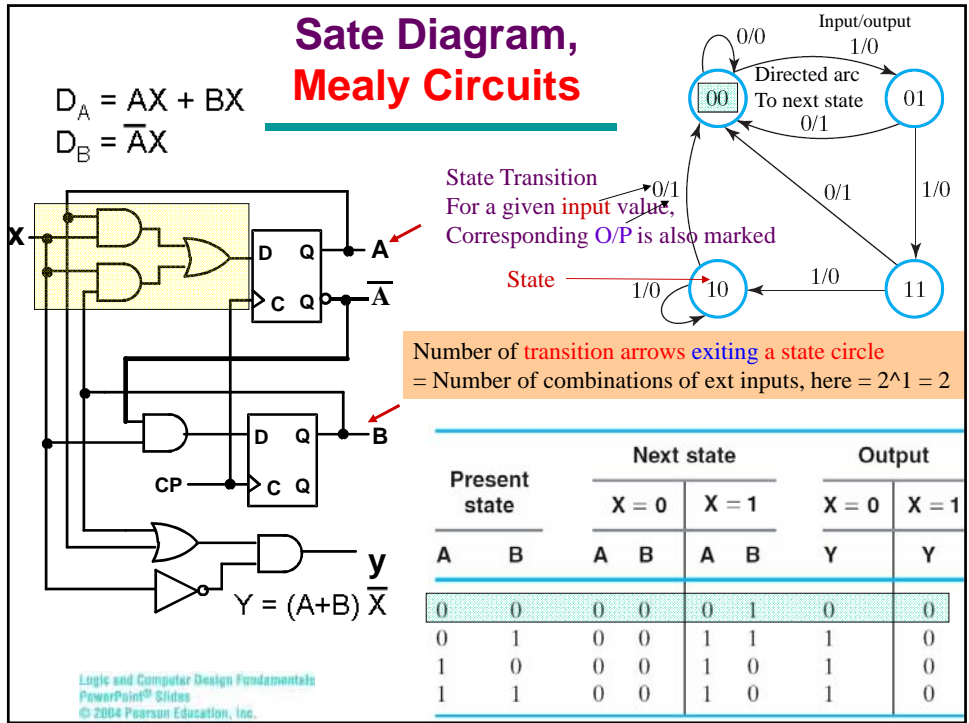Logic and Computer Design Fundamentals
 PowerPoint® Slides
 © 2004 Pearson Education, Inc.



Moore and Mealy Models

- Sequential Circuits are also called **Finite State Machines (FSMs)**. Two formal models exist- according to dependencies of **External Outputs**

- Moore Model**

- Named after E.F. Moore.
- External Outputs (O/Ps) are functions of the state **ONLY**

- Mealy Model**

- Named after G. Mealy
- External Outputs are functions of the state **AND** external inputs

In State Diagram

- O/Ps are shown next to the state value (inside the state node)

In Timing Waveforms

- O/Ps change **only** with the state → with the clock → Sync. to clk

- O/Ps are shown on the state transition arcs- next to the I/P

- O/Ps can change with I/Ps → possibly asynchronous to clock

- In contemporary designs, FSM are sometimes **mixed**: Some O/Ps are Moore and some are Mealy

Analysis Example 2: A Moore Circuit

Output = F (States only)

- Right at the outset, there are things we can do:

Derive Boolean expressions for all outputs of the combinational logic (CL) circuits

- These CL outputs are:


→ Inputs to the flip flops

$$D_A = X \oplus Y \oplus A \text{ (the odd fn)}$$

→ Output to the outside world

$$Z = A$$

 Depends only on state – not on inputs, → Moore



Present state	Inputs		Next state	Output
	A	X Y	Next A = D _A	Z = Present A
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

One +ive Edge Triggered D FF, → 2¹ = 2 states


Ext. O/P Determined only by the present state (not the I/Ps) → Moore

Output is determined only by the State (→ so in the circle) State, Output

I/P combinations

Affect state transitions only 01, 10 Not the O/Ps 00, 11

 How many arcs emanate From each circle? As many as the I/P combinations



Sequential Circuit Analysis: Using other types of Flip Flops: JK, T

- D type FF was easy to use, as the Dinput from CL is the same as the Next state bit (e.g. $DA(t) = A(t+1)$)
- For other types of FFs, this is not so, and you will have to go through either:
 - The Characteristic Table
 - Or the Characteristic Equation

Sequential Circuit Analysis Example: Using JK Flip Flops

CL Equations of FF Inputs

$$J_A = B, K_A = Bx'$$

$$J_B = x', K_B = A \oplus x$$

JK Characteristic Eqn.
 $Q(t+1) = J\bar{Q} + \bar{K}Q$

- Substituting for FF A: To simplify the derivation of state table, get as SOP

$$A(t+1) = BA' + (Bx')A$$


$$= A'B + AB' + Ax \quad \leftarrow \text{Gives A Next State}$$

- Substituting for FF B:

$$B(t+1) = x'B' + (A \oplus x)B$$

$$= B'x' + (Ax + A'x')B$$
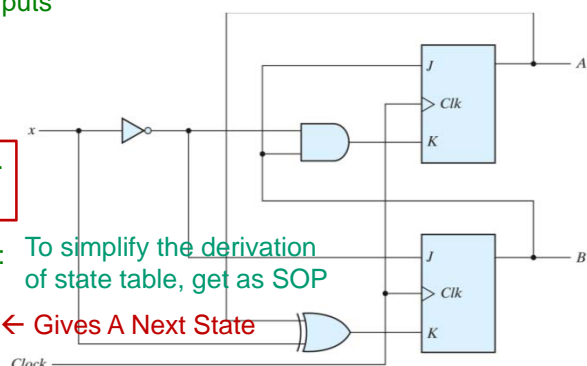
$$= B'x' + ABx + A'Bx' \quad \leftarrow \text{Gives B Next State}$$



No external O/Ps!

Sequential Circuit Analysis Example: Using JK Flip Flops

CL Equations of FF Inputs

$$J_A = B, K_A = Bx'$$

$$J_B = x', K_B = A \oplus x$$

All RHS is at t

JK Characteristic Eqn.
 $Q(t+1) = J\bar{Q} + \bar{K}Q$

- Substituting for FF A:
 $A+ = A(t+1) = BA' + (Bx')'A$
 $= A'B + AB' + Ax$ ← Gives A Next State
 SOP to simplify plotting in state table

- Substituting for FF B:
 $B+ = B(t+1) = x'B' + (A \oplus x)'B$
 $= B'x' + (Ax + A'x')B$
 $= B'x' + ABx + A'Bx'$ ← Gives B Next State

Standard I/P Listing ABx

Present State			Input	Next State	
A	B	x	A+	B+	
0	0	0	0	1	
0	0	1	0	0	
0	1	0	1	1	
0	1	1	1	0	
1	0	0	1	1	
1	0	1	1	0	
1	1	0	0	0	
1	1	1	1	1	

Needed only if you use The characteristic table

Flip-Flop Inputs			
J _A	K _A	J _B	K _B
0	0	1	0
0	0	0	1
1	1	1	0
1	0	0	1
0	0	0	1
0	0	0	0
1	1	1	1
1	0	0	0


J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	$\bar{Q}(t)$	Toggle

Logic and Computer Design Fundamentals
 PowerPoint® Slides
 © 2004 Pearson Education, Inc.

Chapter 3 - Part 1 41

Sequential Circuit Analysis Example: Using JK Flip Flops

State Diagram

 

Present State			Input	Next State	
A	B	x	A	B	
0	0	0	0	1	
0	0	1	0	0	
0	1	0	1	1	
0	1	1	1	0	
1	0	0	1	1	
1	0	1	1	0	
1	1	0	0	0	
1	1	1	1	1	

If FSM is at state S2 and x fixed at 0:
 When do we return next to S2?

Sequential Circuit Analysis Example: Using T Flip Flop

CL Equations for FF Inputs & Ext O/P

$$\begin{aligned} T_A &= Bx \\ T_B &= x \\ y &= AB \end{aligned}$$

T-FF Characteristic Eqn.


$$Q(t+1) = T \oplus Q(t)$$

- Substituting for FF A:

$$\begin{aligned} A(t+1) &= Bx \oplus A = BxA' + A(BX)' = A'Bx + A(B'+x') \\ &= A'Bx + AB' + Ax' \quad \leftarrow \text{A Next State} \end{aligned}$$

- Substituting for FF B:
 
$$B(t+1) = x \oplus B \quad \leftarrow \text{B Next State}$$



One external O/P
Mealy or Moore?

Sequential Circuit Analysis Example: Using T Flip Flop

CL Equations for FF Inputs & Ext O/P

$$\begin{aligned} T_A &= Bx \\ T_B &= x \\ y &= AB \end{aligned}$$

T FF Characteristic Eqn.

$$Q(t+1) = T \oplus Q(t)$$

- Substituting for FF A:


$$\begin{aligned} A(t+1) &= Bx \oplus A \\ &= BxA' + A(BX)' \\ &= A'Bx + A(B'+x') \\ &= A'Bx + AB' + Ax' \quad \leftarrow \text{Gives A Next State} \end{aligned}$$

- Substituting for FF B:

$$B(t+1) = x \oplus B \quad \leftarrow \text{Gives B Next State}$$

Present State		Input x	Next State		Output y
A	B		A ⁺	B ⁺	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

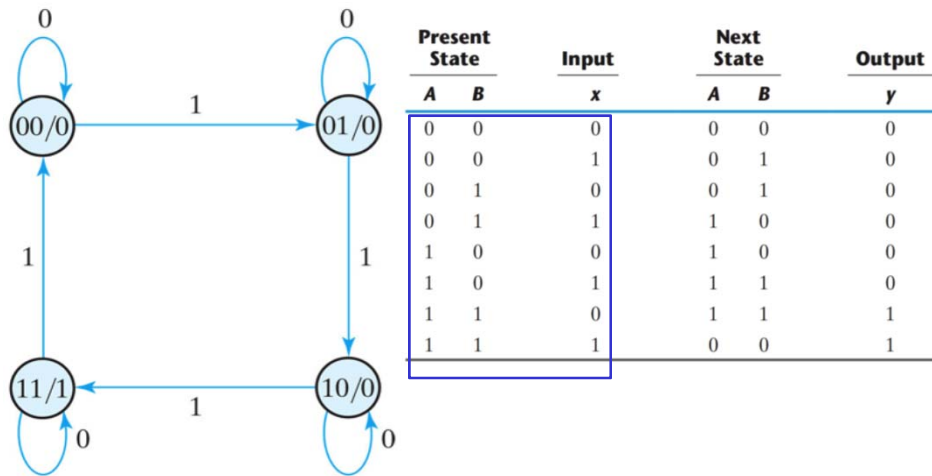Sequential Circuit Analysis Example: Using T Flip Flop



Note how O/P y is represented
in the state diagram

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 45

Sequential Circuit Design: The Design Procedure

Steps in green
are similar to
CL Desing



1. Specification (Word Description) → State Diagram (Can be **symbolic** at this “thinking” stage)
2. State **Reduction**: Try to reduce the number of states (Will cover later)
 - This may reduce the number of FFs required 10 → 8?
3. State **Assignment** - Assign **binary** codes to the symbolic states
4. Obtain a **Binary** state table.
5. For the selected type of Flip Flops: Use the excitation table to obtain the binary **FF inputs**
6. Derive **Optimized** logic expressions for **each of** the:
 - FF Inputs
 - External Outputs
7. Generate the logic diagram for the **complete sequential cct.**

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 46

Sequential Circuits

Analysis Versus Design

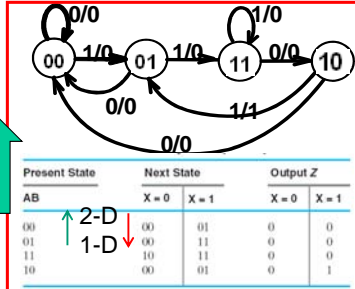 


- Analysis of a given circuit:**

Given a circuit → behavior [state table (state diagram)]:
 {Circuit, Present state, inputs} → Next state?, Outputs?

Flip Flop Consideration: (inputs → outputs?)

 → FF: Use input-driven Characteristic tables/equations



- Design to achieve a specified circuit performance**

Given desired behavior [(state diagram (State table))] → get circuit
 (behavior: Present to next changes → Needed FF Inputs? → CL circuit?)


Flip Flop Considerations: (behavior at O/P → inputs that give behavior?)

→ FF: Use output-driven Excitation tables/Equations

Complete Design Procedure

 
Example: "3 or more successive 1s" detector

Specification (word description) → Symbolic State Diagram




Detect three or more consecutive 1's at the circuit input

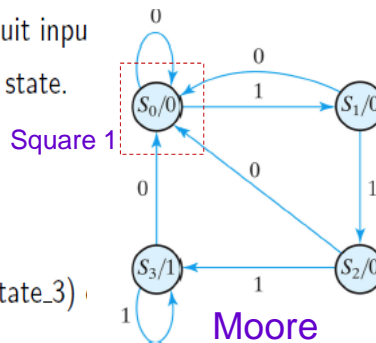- If input = 0, stay/go at/to a state_0/reset state.
- If input = 1 after 0, go to state_1.
- If input = 1 after 01, go to state_2.
- If input = 1 after 11, go to state_3.
- We have 4 states (reset, state_1, state_2, state_3) (S₀, S₁, S₂, S₃) respectively.



3 1s Detector Example: with D-type FFs

 

Present State	Input	Next State	Tied to State Output
S ₀	0	S ₀	0
S ₀	1	S ₁	0
S ₁	0	S ₀	0
S ₁	1	S ₂	0
S ₂	0	S ₀	0
S ₂	1	S ₃	0
S ₃	0	S ₀	1
S ₃	1	S ₃	1

Circuit Details:

- Two D flip-flops (A, B) to represent the four states.
- One input (x).
- One output (y).
- $Q_{(t+1)} = DQ$ (D-FF)

State Assignment

Present State	Input		x	Next State		Output
	A	B		A	B	
S ₀	0	0	0	0	0	0
	0	0	1	0	1	0
	0	1	0	0	0	0
	0	1	1	1	0	0
	1	0	0	0	0	0
	1	0	1	1	1	0
	1	1	0	0	0	1
	1	1	1	1	1	1

PowerPoint Slides
© 2004 Pearson Education, Inc.


3 1s Detector Example

Present State		Input	Next State		Output
A	B		D _A	D _B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Combinational Logic Design

- $D_A(A, B, x) = \sum(3, 5, 7)$.
- $D_B(A, B, x) = \sum(1, 5, 7)$.
- $y(A, B, x) = \sum(6, 7)$.

 
Optimized implementation
Obtained from 3 K-maps



Logic and Computer Design Fundamentals
PowerPoint Slides
© 2004 Pearson Education, Inc.

3 1s Detector Example

The Circuit

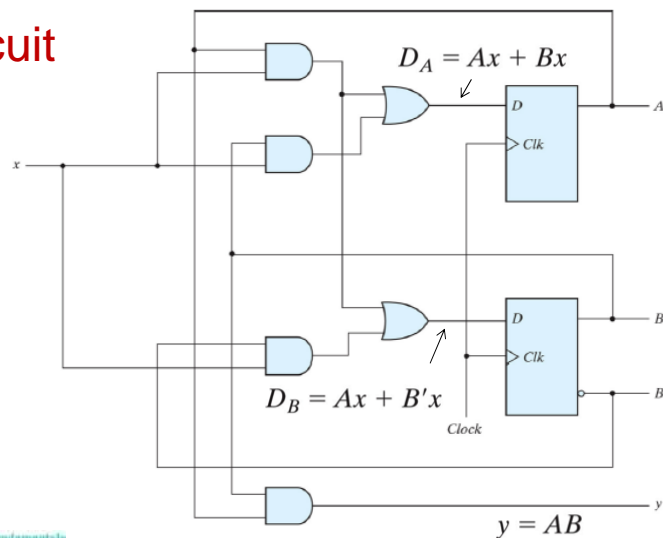


Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 51


3 1s Detector Example Design with JK Flip Flops

Specified Cct Behavior: Need to derive the FF Inputs

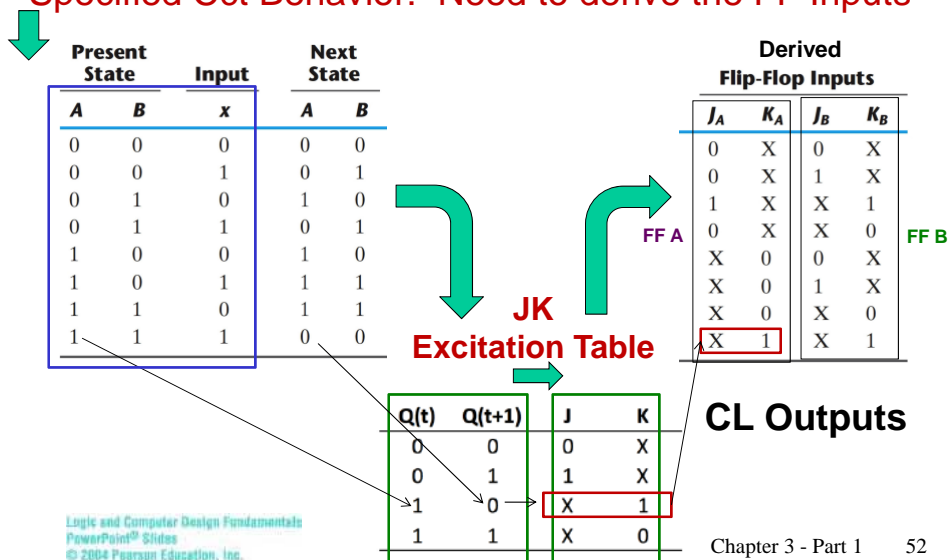

Chapter 3 - Part 1 52

 
3 1s Detector Example Design with JK Flip Flops



 Example: A 3-bit binary up counter Design with T Flip Flops

Design an n -bit up counter that counts from 0 to $2^n - 1$
Assume $n=3$

- A 3-bit counter counts from 0 to 7.
- Has no inputs.



Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

T FF
Simplifies
Designing
Counter

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0


Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

State Table
Desired Performance

Required FF Inputs

Design with T Flip Flops

Example: A 3-bit binary counter

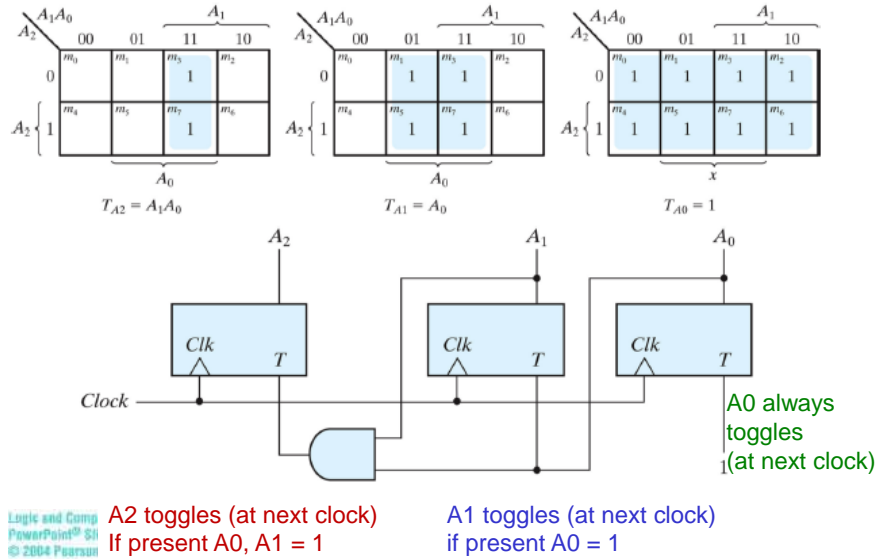

State Reduction

When we are interested only in the input-output sequence and not in the state values themselves (in counters)

- Reducing the number of states may result in reduction in the number of flip-flops needed. (without affecting the in-out sequence)
- Sometimes, reduction in flip-flops result in a bigger combinational circuit to realize the next state and the outputs.

Input Sequence

Consider the '01010110100' as your input

State	a	b	c	d	e	f	f	g	f	g	a
Input	0	1	0	1	0	1	1	0	1	0	0
Output	0	0	0	0	0	1	1	0	1	0	0

7-State FSM

States e, g are equivalent, Same:
-Next state - O/P
for all input combinations (Important)

56

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

State Reduction

When we are interested only in the input-output sequences and not in state values (With counters we ARE interested in the states)

- Try to reduce the number of states without altering the input-output relationship.
- It is easier to work on state tables.
- Two states are equal/equivalent if, for each input combination, they give the same outputs and send the circuit to the same (or equivalent state).
- If we have two equivalent states, one of them should be removed :
 - Remove its row from the truth table
 - Replace its symbol everywhere in the truth table with that of its equivalent state

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

State Reduction

When we are interested only in the input-output sequences and not in state values (With counters we are interested in the states)

Present State	Next State		Output		# of States (originally 7)	# of FFs	# of Unused States
	x = 0	x = 1	x = 0	x = 1			
a	a	b	0	0	7	3	1
b	c	d	0	0			
c	a	d	0	0			
d	e	f	0	1			
e	a	f	0	1			
f	g	f	0	1			
g	a	f	0	1			

Remove Row $e = g \rightarrow$ Remove g row and replace gs with es

Present State	Next State		Output		# of States	# of FFs	# of Unused States
	x = 0	x = 1	x = 0	x = 1			
a	a	b	0	0	6	3	2
b	c	d	0	0			
c	a	d	0	0			
d	e	f	0	1			
e	a	f	0	1			
f	d	f	0	1			


Remove Row $d = f \rightarrow$ Remove f row and replace fs with ds

Present State	Next State		Output		# of States	# of FFs	# of Unused States
	x = 0	x = 1	x = 0	x = 1			
a	a	b	0	0	5	3	3
b	c	d	0	0			
c	a	d	0	0			
d	e	d	0	1			
e	a	d	0	1			

Any Advantage? (More Don't Cares)

After State Reduction- Now using 5 states only

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

 

Reduced 5-State FSM

- Consider the '01010110100' as your input


State	a	a	b	c	d	e	f	f	g	f	g	a
Input	0	1	0	1	0	1	1	0	1	0	0	
Output	0	0	0	0	0	1	1	0	1	0	0	

Maintains same input-output sequence as the original 8-state circuit
On slide 56

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

State Assignment: Symbols → Binary

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

 

- Input-output sequence is not affected by the binary assignment
- But generally: **it affects CL circuit cost**
- 3 Possible state coding schemes:

3 FFs

5 FFs (1 FF/State)

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
a	000	000	00001
b	001	001	00010
c	010	011	00100
d	011	010	01000
e	100	110	10000

but simpler
CL circuit
for the
FF inputs

Logic and Com
PowerPoint®
© 2004 Pearson