

# EE 200: Digital Logic Circuit Design

Dr Radwan E Abdel-Aal, COE

---

## Unit 5 Registers and Counters

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

### Unit 5: Registers and Counters

#### Useful MSI blocks made of Flip-Flops


#### Chapter 6: Registers and Counters

1. Registers with parallel load
2. **Shift** Registers
  
3. Counters
  - Asynchronous (Ripple)
  - Synchronous

# Registers

- Register – a set of binary storage elements
- Used to perform simple operations on data such as **storage, movement, and processing**  
Examples: **load, shift, rotate, increment, etc.**
- A processor processes data by performing operations on **registers**, e.g. **ADD A, B** where A and B are say **32-bit registers**
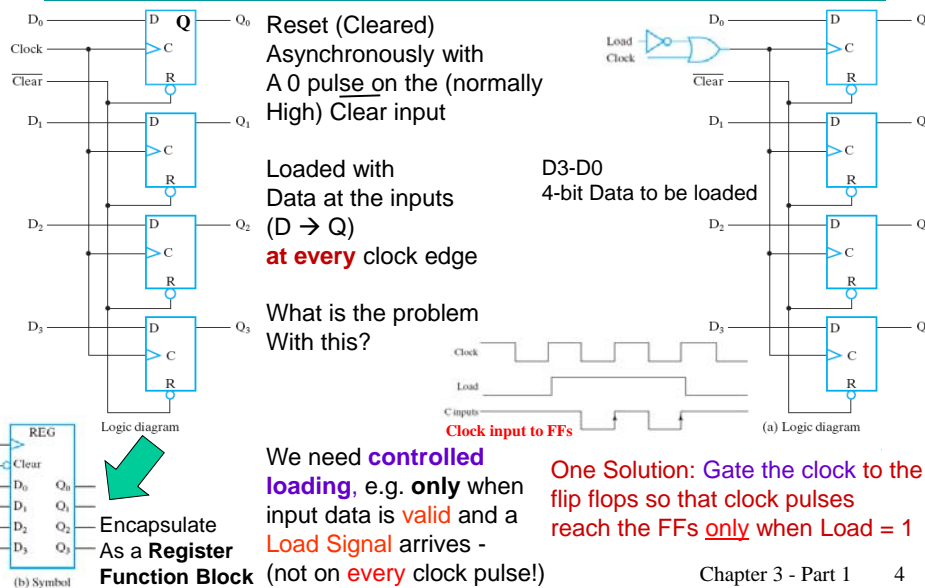
## Examples: - 4-bit Register, with Clear - Selective **Parallel Load** by **gating the clock**



## Better Approach

### Avoid clock gating. Apply Load control at D input

Register with Parallel Load & no clock skew

Avoid clock gating if you can! Why?

It causes clock skew – clock pulses may arrive to various registers in the system at different times

So such flip flops will change state at different times


No good- could lead to erroneous state transitions or data transfers!

Load now does not gate the clock, But controls what goes into the D input

Load = 1 → EN = 1, D = Ext. input data will be loaded on the next clock edge  
Load = 0 → EN = 0, D = present Q, so no change on the next clock edge

EN = 1 for Load  
EN = 0 for no change


External Data to be loaded

 

But we now control what Clock pulses do using The EN control on D

Clock pulses go all the time Unobstructed To all FFs


I3-I0 Data to be loaded

 
 
## Shift Registers

Shift Register → Serial Loading

- A Shift Register moves data **laterally** ( $\leftrightarrow$ ) within the register FFs toward the MSB or LSB position
- In its simplest form, the shift register is a **set of D flip-flops having a common clock & connected in a row** like this:




- Data input, In, is the **serial input** (the **shift right input**).
- Data output, Out, is the **serial output** (=D).
- The vector (ABCD) is called the **parallel output** of the register.

# Shift Registers: Serial Loading

- Behavior of the 4-stage serial shift register

Initial register state just before the first clock pulse arrives

 - Assume Register was cleared to 0000 initially, e.g. by S-R
- T1: State after the first pulse and before the second
- Complete the last two rows of the table



CP	In	A	B	C	D: Serial Out
	0	0	0	0	0
T1	1	0	0	0	0
T2	1	1	0	0	0
T3	0	1	1	0	0
T4	1	0	1	1	0
T5	1				1
T6	1				1
T7					0


Applications: Delay, Serial to Parallel conversion

1. 4-bit Serial I/P  
Appears in parallel  
In register after 4 clock pulses  
(serial loading of the register)


2. Serial I/P  
Starts to appear  
Serially at O/P  
(after 4T delay)
 
## Some Applications of n-stage Shift Register

- Delay:
  - Serial input sequence starts to appear at output after n-clock cycles (i.e. is delayed by  $nT$  ns)




 - Parallel to Serial and Serial to Parallel conversion:



- Arithmetic:
  - Shifting 1 place to the right (feeding in 0s) = dividing by ?
  - Shifting 1 place to the left (feeding in 0s) = multiplying by ?

# Shift Registers with Feedback

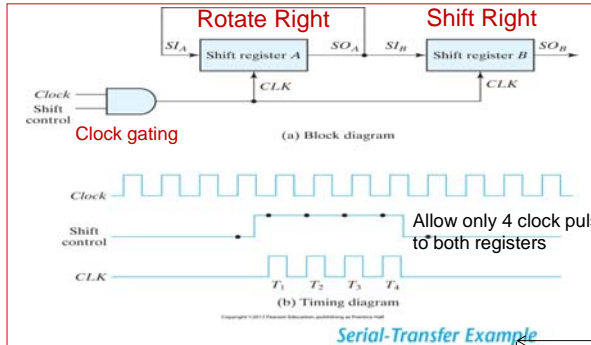

Each of A, B is a 4-bit Right-Shift register

Clock gating is not a good practice

As it leads to Clock skew

Regardless of initial Contents in B (flushed out)


Timing Pulse	Shift Register A	Shift Register B
Initial value	1 0 1 1	X X X X
After $T_1$	1 1 0 1	0 0 1 0
After $T_2$	1 1 1 0	1 1 0 0
After $T_3$	0 1 1 1	0 1 1 0
After $T_4$	1 0 1 1	1 0 1 1

After 4 clock pulses:

Initial 4-bit value restored in A and serially loaded into B


Logic and Computer Design Fundamentals  
PowerPoint Slides  
© 2004 Pearson Education, Inc.
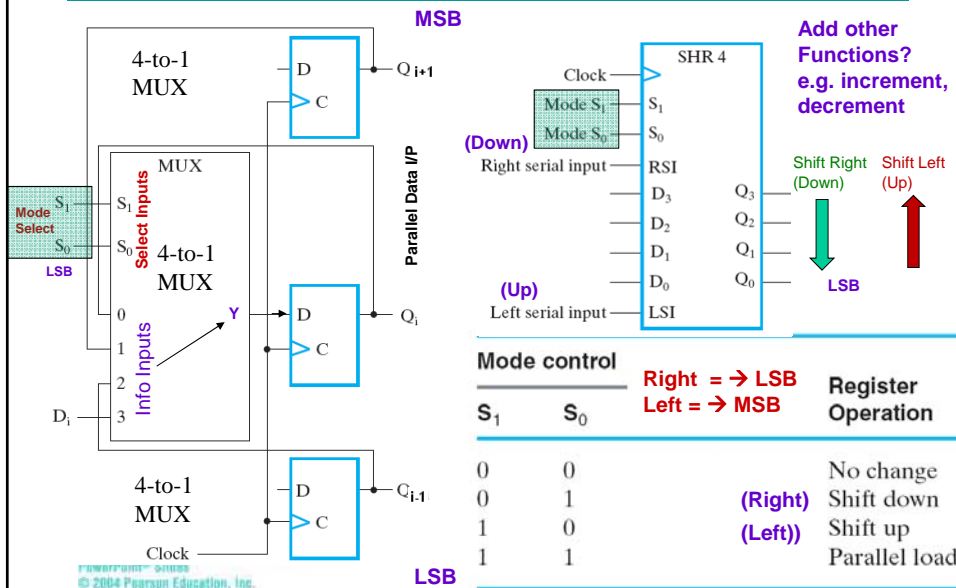
## Universal (Multi-purpose) Shift Register with 4 Functions: - Parallel Load - Shift left - Shift Right - No Change




# Serial (bit-by-bit) adder
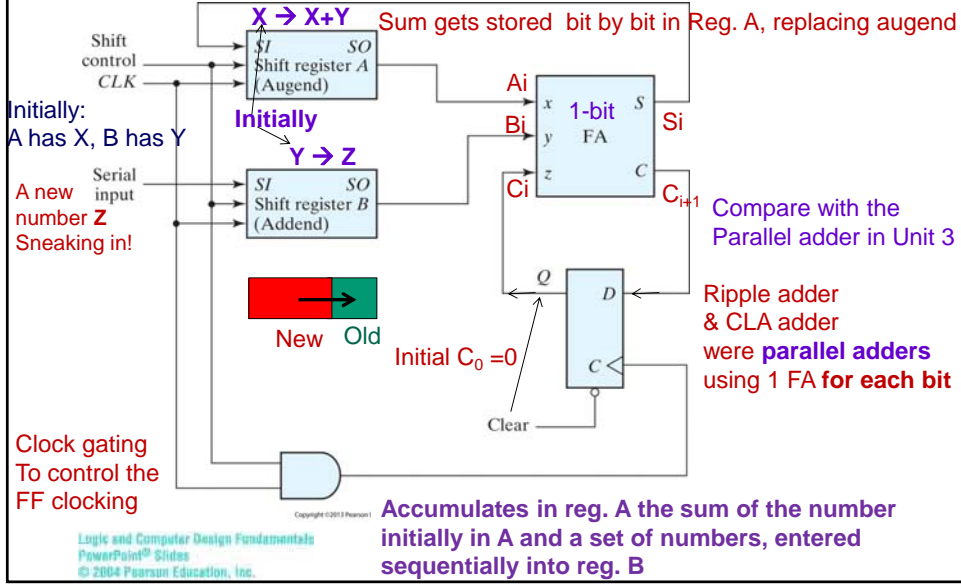
## 1. Using shift registers, 1 Full Adder, and 1 FF



# Serial Adder (bit-by-bit addition)
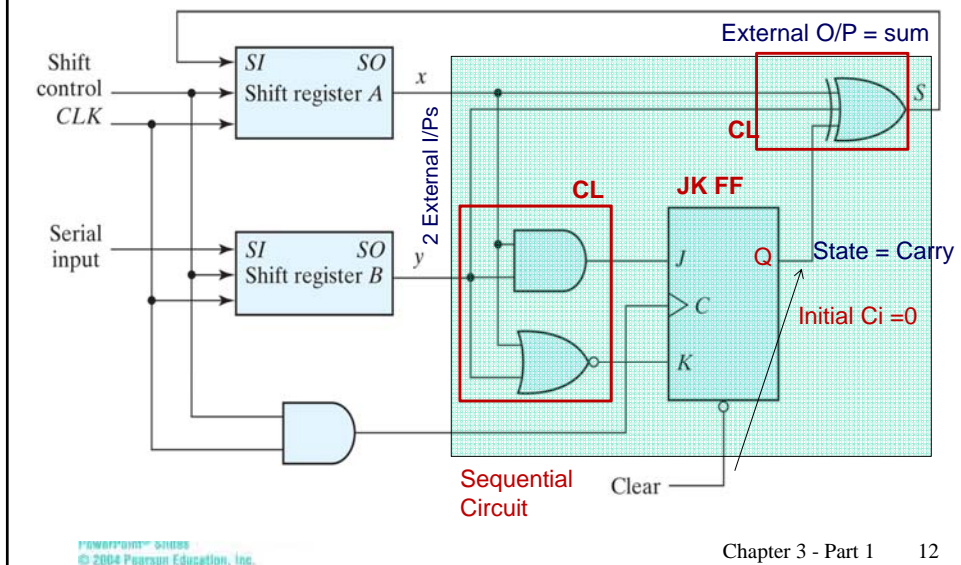
## 2. Using shift regs. and a sequential circuit



# Serial Adder (bit-by-bit addition)

## Using shift regs. and a sequential circuit

3 K-maps → CL on previous slide

Table 6.2  
State Table for Serial Adder

Present State	Inputs		Next State	Output	Flip-Flop Inputs	
Q	x	y	Q	S	J <sub>Q</sub>	K <sub>Q</sub>
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

Carry IN →

Carry Out

Sum

JK Excitation

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Part 1 13

## Counters

- A counter is a register that has its parallel outputs go through a specific count sequence as clock pulses arrive
- Counting sequences can be binary, BCD, etc.
- Counting can be up, down
- A modulo-n counter has n different counting states, e.g. it goes through counts 0,1,2, ..., (n-1),0,1,...
- e.g. a modulo-10 up counter may count: 0,1,...,9,0,1,...
- Modulo n counter divides the clock frequency by n (show waveforms)

Some Applications of counters:

- Counting events
- Timers
- Frequency division

Repeated counting cycle  
# of clock pulses sent = ?  
# of pulses at MSB (A) = ?

This is a modulo-?  
Up/Down? Counter

Successive Clock Pulses	ABC (LSB)
000	
001	
010	
011	
100	
101	
000	
001	

# Implementing Counters

## Two Basic Approaches: 1. Async (Ripple) & 2. Sync.

### 1. Asynchronous (Ripple) Counters

- The **external clock** is connected **only** to the clock input of the LSB bit flip-flop (first counter stage)
- Then the **output of a stage provides the clock I/P to the next stage**
- i.e. circuit is **not synchronous** - (since no common clock to **all** stages)
- Advantage:
  - Simple circuit
- Disadvantages:
  - Output changes are delayed further for each stage toward the LSB (Ripple Effect)
  - This ripple propagation delay limits the maximum clock frequency that can be used (same factor that limited speed of the **ripple adder**)

## Ripple (asynchronous) Counters

### Modulo-16 binary counter (n = 4) using D FFs

**Every Stage is wired to always Toggle with clock & we connect the suitable clock signal to it!**

Counting Up				Counting Down			
Upward Counting Sequence				Downward Counting Sequence			
Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	1	1	1	1
0	0	0	1	1	1	1	0
0	0	0	1	1	1	0	1
0	0	0	1	1	0	0	1
0	0	1	0	1	0	1	0
0	0	1	0	1	0	0	1
0	0	1	1	0	0	0	1
0	0	1	1	0	0	0	0
0	1	0	0	0	1	1	1
0	1	0	0	0	1	1	0
0	1	0	1	0	1	0	1
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	0	0	0	1	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	0	1
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	0	0	0	1	1
1	1	0	0	0	0	1	0
1	1	0	1	0	0	0	1
1	1	0	1	0	0	0	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	0
1	1	1	1	0	0	0	0

Annotations in the diagram and table:  
 - **In-stage Toggling link**: Connects Q to C of the same flip-flop.  
 - **Inter-stage Clocking links**: Connects Q of one flip-flop to C of the next.  
 - **16 clk cycles Repeat Cycle**: Indicated by a red bracket on the table.  
 - **Toggle at +ive edge on Q0**: Indicated by a purple arrow pointing to the first row of the downward sequence.  
 - **Toggle at +ive edge on Q0**: Indicated by a purple arrow pointing to the first row of the downward sequence.  
 - **Connect Q to next C of a +ive Edge FF**: Indicated by a purple arrow pointing to the clock input of the next flip-flop.  
 - **Toggle at -ive edge on Q0**: Indicated by a green arrow pointing to the first row of the upward sequence.  
 - **Connect Q to next C of a +ive Edge FF**: Indicated by a red arrow pointing to the clock input of the next flip-flop.


fc/16 fc/8 fc/4 fc/2 fc = Clock Frequency

How to make an Up/Down ripple counter by adding MUXs?

Frequency Division Properties



 **With T FFs- Toggling obtained with  $T = 1$   
(no need to externally connect  $Q'$  to D for each FF)**



**Binary Up Counter  
0000 → 1111 (16 Counts)**


T FF Advantage: No need for an external  $Q'$  to D connection for each FF to toggle

But for Up counting, Clock is taken from Previous Q not  $Q'$ - Why?

Reset Logic 1

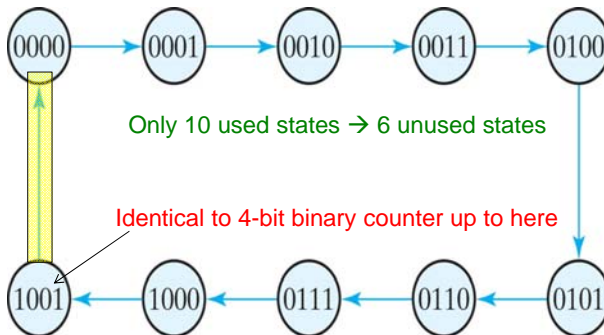**BCD UP (Decade) Ripple Counter**

- Counts 0, 1, ...8, 9, 0 (modulo 10)
- 4-bits → 4 FFs



Upward Counting Sequence

Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

6 unused states

Copyright © 2011 Pearson Education, publishing as Prentice Hall

# BCD (Decade) UP Ripple Counter with JK FF

↓ edge triggered FFs

↓ at Q1, Q8=1 → Q2 to 0\*

↓ at Q1:\*\*  
- (Q4 Q2)=11: Toggle  
- Else: reset to 0

Next pulse at end count

JK Characteristic

J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	$\bar{Q}(t)$	Toggle

Upward Counting Sequence

Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

Toggles on ↓ at Q2 (As usual)

Toggles on ↓ at Q1 if Q8 = 0, otherwise Reset

Toggles Always

Logic 1

Copyright ©2013 Pearson Education, publishing as Prentice Hall

19

# Cascading Ripple Counters 3-Decade Ripple Up Counter (000-999)

Starting with stages Cleared to all 0s

100s

10s

1s

Q<sub>8</sub> Q<sub>4</sub> Q<sub>2</sub> Q<sub>1</sub>

Q<sub>8</sub> Q<sub>4</sub> Q<sub>2</sub> Q<sub>1</sub>

Q<sub>8</sub> Q<sub>4</sub> Q<sub>2</sub> Q<sub>1</sub>

On 1000th clock pulse

On 100th clock pulse

On 10th clock pulse

Count pulses (clock)

10<sup>2</sup> digit

10<sup>1</sup> digit

10<sup>0</sup> digit

Divide-by-1000 Counter


Each stage is a BCD up Decade Counter (last slide)

Clock Rippling at 2 levels:  
- Within each decade stage  
- and also between the stages


Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.
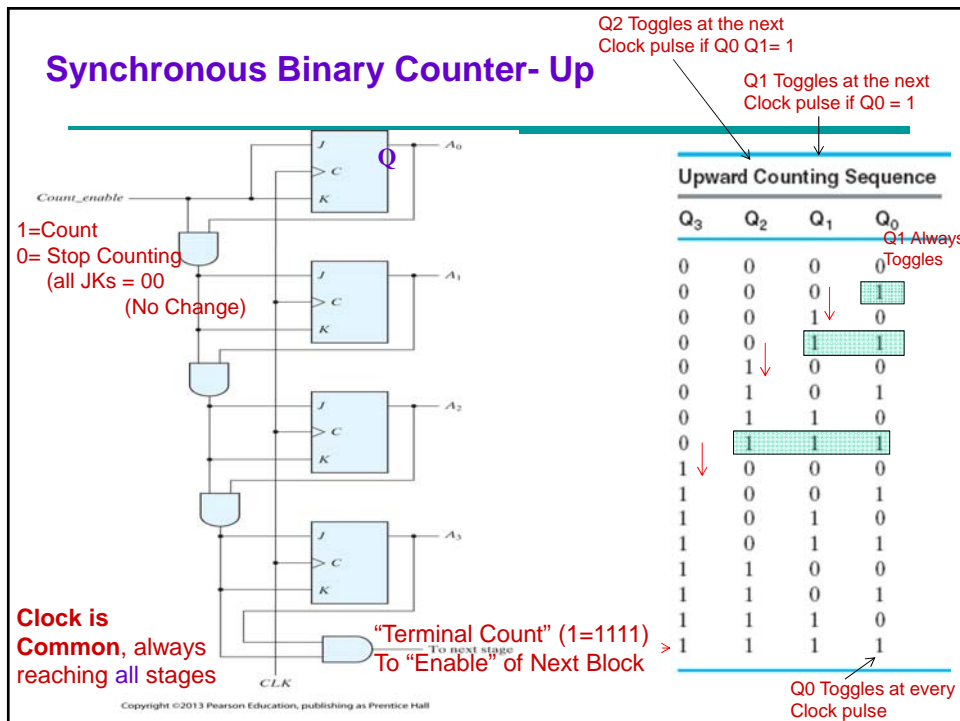
## 2. Synchronous Counters


- The same System clock is connected **directly** to the clock inputs of **ALL flip-flop stages** (→ truly synchronous)
- **No fiddling with clock-** instead, we control operation of individual FFs through data or control inputs e.g. D, JK, T
- **Any counter can be systematically designed as a sequential cct** – see Unit 4
  - A **combinational logic circuit** is used to implement the desired state sequencing through inputs to the Ds of the flip-flop stages
- But simpler **ad hoc** approaches can be used for **regular counting patterns** e.g. binary up or down



## Synchronous Binary Counter- Down

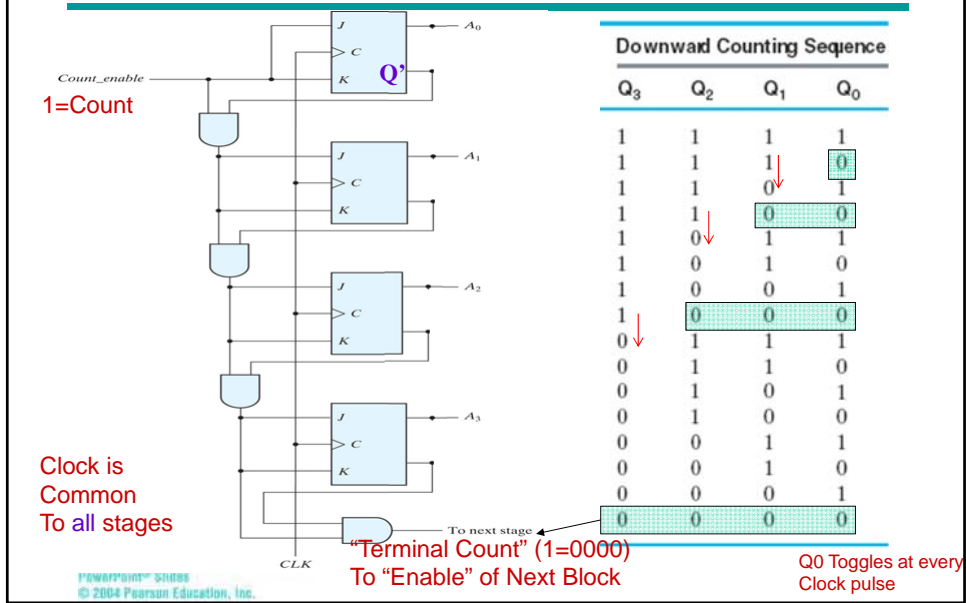
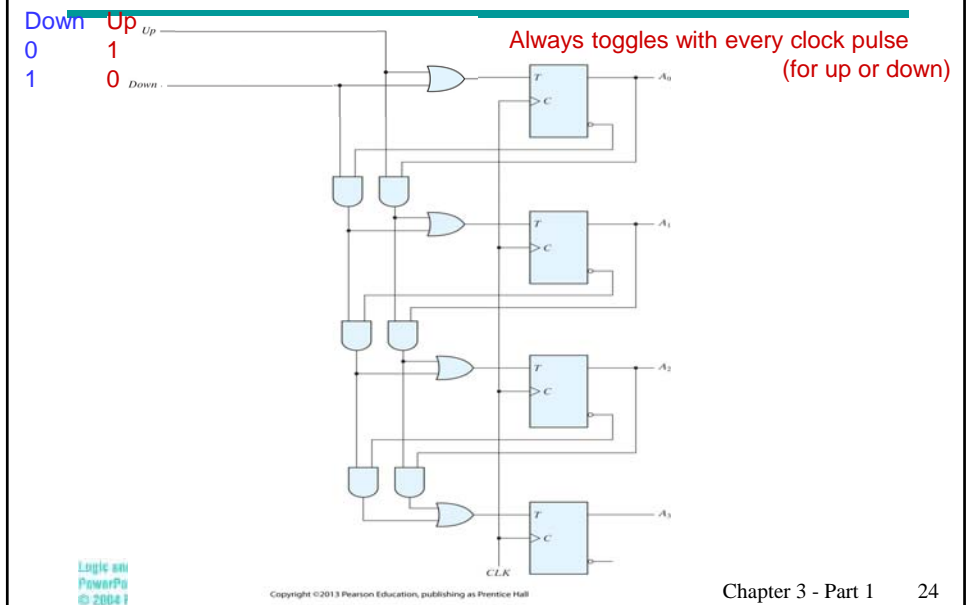
## Synchronous Binary Counter- Up/Down With T Flip Flop



For a binary counter: Irregular counting pattern here

## BCD UP Counter: ...8 9 0 1 ... with T FFs

Table 6.5  
State Table for BCD Counter

Present State				Next State				Output	Flip-Flop Inputs			
Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>	y	TQ <sub>8</sub>	TQ <sub>4</sub>	TQ <sub>2</sub>	TQ <sub>1</sub>
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	1	0	1	1	0	0	1

Additional O/P with 1 pulse of 1 clock period duration every counting cycle (divide by 10)

A more systematic approach to Design, compared to slide 19 (Async)

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Copyright © 2012 Pearson Education, publishing as Prentice Hall

Toggles when Q<sub>1</sub>=1 & Q<sub>8</sub>=0

Toggles Always

$$\begin{aligned}
 T_{Q1} &= 1 \\
 T_{Q2} &= Q_8 Q_1 \\
 T_{Q4} &= Q_2 Q_1 \\
 T_{Q8} &= Q_4 Q_2 Q_1 + Q_8 Q_1 \\
 y &= Q_8 Q_1
 \end{aligned}$$

From T K-maps (use Xs)

25

## Binary UP Counter with Parallel Load (Functional Block)

Count Enable (1)  
Synchronous Load Enable (1)

Function Table

Clear (async)	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next
1	↑	0	0	No change

Note: JK FF is more cumbersome than D For loading data!


Direct Clear (asynchronous)  
Active Low (1 for normal operation)

1 at "terminal count" (1111) to enable Next 4-bit stage (for cascading)

Logic and Computer Design Fundamentals  
PowerPoint® Slides  
© 2004 Pearson Education, Inc.

Copyright © 2012 Pearson Education, publishing as Prentice Hall


6

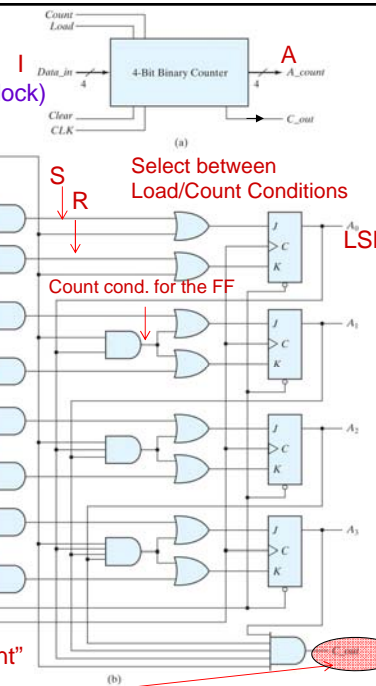

## Designing Larger Counters by **cascading** smaller ones Using the **Cout** (**Terminal Count**) to **EN** of next stage

- Given two 2-bit (modulo-4) counter, how to design a 4-bit (modulo-16) counter?

MS Part		LS Part		
A	B	C	D (LSB)	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

 


LS Part generates a single **Cout** pulse (lasting for 1 clk Cycle only) every time it finishes its counting cycle

MS Part is enabled to increment only once when it receives this pulse at its EN I/P

Example: Design a 16-bit (0-255) binary counter using two of the 4-bit (0-15) universal binary counters on the previous slide

## Using this count/load/clr functional block to implement a modulo-n Counter
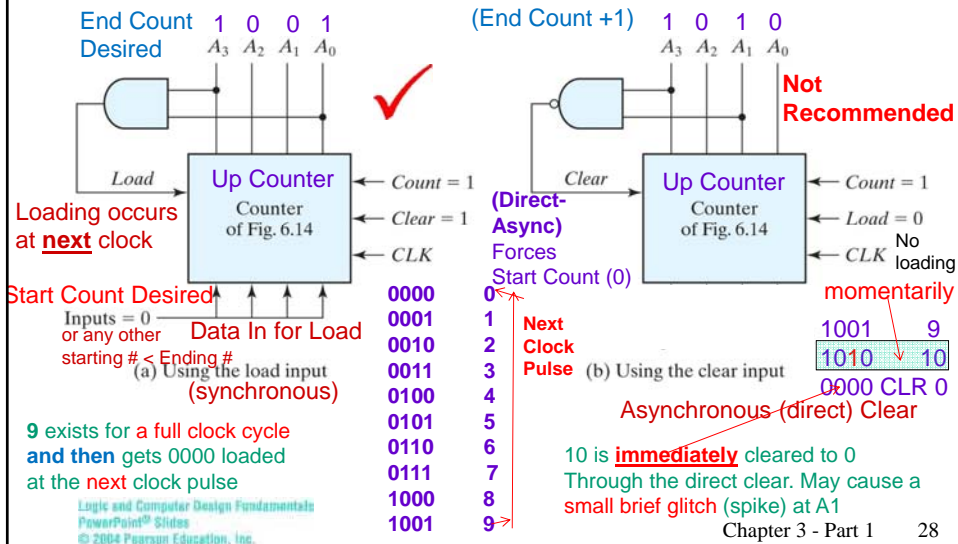
### Two Approaches for a BCD (0 to 9) Counter



## Modulo 6 Counter with Arbitrary Counting Sequence:

### Investigate Effect of Unused States on performance

Unused State 011 → X X X  
 Unused State 111 → X X X

Present State			Next State		
A	B	C	DA	DB	DC
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	0	0	0

Modulo?   
 At O/P A, Divide by ?

Count Sequence?   
 Number of FFs Needed?   
 Used states?   
 Unused states?

Three 3-variable K-maps for CL Optimization, with Xs

Derive these transitions from The D eqns.

Two Unused states: Determine transitions from circuit or eqns and ensure safe return to normal counting seq.

Logic and Computer Design Fundamentals  
 PowerPoint® Slides  
 © 2004 Pearson Education, Inc.

29

## Generating a sequence of non-overlapping timing signals

### 1. Ring counter (Shift-Right with Rotate - D-type FFs)

T 0 1 2 3  
 0 0 0 1 Initially loaded by direct S/R  
 1 0 0 0 Pulse 1  
 0 1 0 0 Pulse 2  
 0 0 1 0 ...  
 0 0 0 1 0 0 0 1 Q  
 1 0 0 0

4 different states

(a) Ring-counter (initial value = 0001)  
 Inserted directly with Set/Reset

Shift right register with 4 D-type FFs (i.e. Q to next RHS D),  
 + Rotate Feedback: Q<sub>3</sub> → D<sub>0</sub>

CLK

T = clock period

n intervals  
 Need n FFs

4 non-overlapping Timing signals


(b) Sequence of four timing signals

Initially loaded through directly Set-Reset of the D FFs

Logic and Computer Design Fundamentals  
 PowerPoint® Slides  
 © 2004 Pearson Education, Inc.


Chapter 3 - Part 1 30
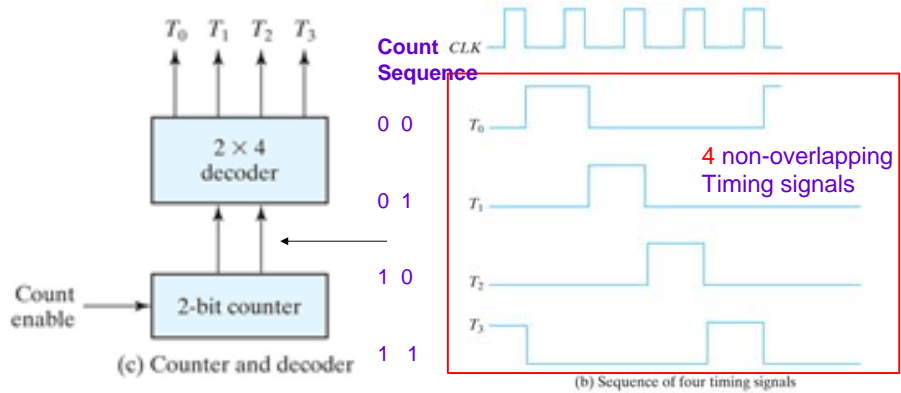
## Generating a sequence of timing signals: 2. Counter-Decoder Implementation


 
## Johnson Counter: 8 non-overlapping signals from 4-bit shift register with rotate - but E' instead of E!

n intervals  
Need only n/2 FFs  
- More efficient cct!



8 non-overlapping  
timing signals are  
produced by the  
8 AND gates shown  
In the table opposite

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	A'E'
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	A'B
7	0	0	1	1	B'C
8	0	0	0	1	C'E

8 additional 2-input ANDs

8 non-overlapping  
Timing signals

8 different states  
not 4 as on normal ring counter!

(b) Count sequence and required decoding