

# EE 200: Digital Logic Circuit Design

Dr Radwan E Abdel-Aal, COE

## Unit 6

### 1. Random Access Memory (RAM)

(Sections 7.2- 7.3)

### 2. Programmable Logic

(Sections 7.5-7.7)

Charles Kime & Thomas Kaminski


© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)
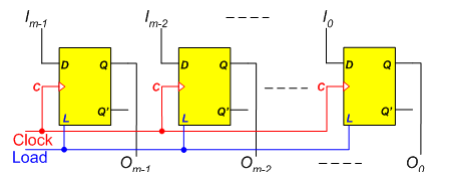
## 1. Random Access Memory (Read/Write)

- Storage element → Memory device for data storage
- A latch or a flip flop stores **one** bit
- A **register** of **m** such flip flops stores **m** bits



$m = 8$ : Byte,  $m = 16$ : Word,  
 $m = 32$ : double words,  $m = 64$ : Quad words, etc.

Over the years, **Processors** have used larger and larger **registers** to store/ process data:  $m = 4, 8, 16, 32, 64, 128$  bits

# Computer Storage

The computer needs to store **programs and data**

## Primary Storage

Solid State (Semiconductor) Memory  
**(Random Access)**

- Faster Speed
- More Costly (per bit)
- Smaller Capacity
- Closer to processor

## Secondary (Mass) Storage

Discs, tapes, CDs  
**(Sequential Access)**

Now new mass storage devices are Solid State (semiconductor)!

### Volatile

Read/Write (RAM)\*

### Non Volatile (e.g. for booting)

Read Only (ROM)

Static

- SRAM

ROM

PROM

EPROM

EEPROM?

Dynamic

- DRAM:

- Larger Capacity
- Cheaper per bit
- Lower power
- But needs continuous refreshing to maintain data

\* Misnomer – Why?

The Read/Write becoming a misnomer as well!

## Random Access (Read/Write) Memory (RAM)

Example: 1024 (1 k) locations × 16-bit each

- A RAM memory Chip **effectively** contains a number of registers

- Why “**random access**”?

Time taken to transfer data to or from **any** address (storage location) **is the same** regardless of the address


- This is different from **sequential storage**, e.g. Disc, CD, or tape

Memory address	Binary	Decimal	Memory content
	000000000	0	1011010101011101
	000000001	1	1010101110001001
	000000010	2	0000110101000110
		⋮	⋮
	111111101	1021	1001110100010100
	111111110	1022	0000110100011110
	111111111	1023	1101111000100101

## Size or Storage Capacity of a Memory Device
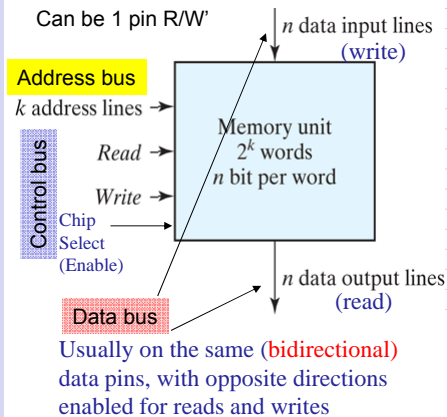
# of storage locations  $\times$  width of each location (bits)

- Address =  $k$  bits, Data width =  $n$   
Number of registers (storage locations) =  $2^k$  locations
- Each location is  $m$ -bit wide
- Memory size is  $2^k$  locations  $\times$   $n$  bits each
- Total storage Capacity in bits:  
Number of storage locations  $\times$  width of data in each location
- Example:  $k = 10$ ,  $n = 8$   
 → Size:  $2^{10}$  locations  $\times$  8 bits each  
 → 1K Bytes of storage  
 = 1 K Bytes = 8 K bits



What is  $k$ ,  $n$  for a 64 K x Byte memory?


## RAM Memory

### Read and Write Operations

- Write:
  - Enable the memory device (Chip Select)
  - Apply the **address** of the location you want to write to
  - Apply the **data** to be written to data I/P pins
  - Activate the **WRITE** Control input → Data on the input pins are **written** into addressed location


Chip Select	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

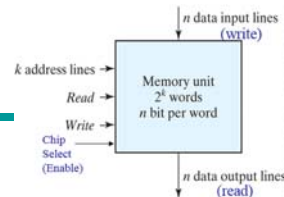- READ:
  - Enable the memory device (Chip Select)
  - Apply the **address** of the location you want to write to
  - Activate the **READ** Control input  
 → Data stored at addressed location appears at the Data O/P pins (are read) **after** some propagation delay (access time)




# Memory

## Write and Read Cycles

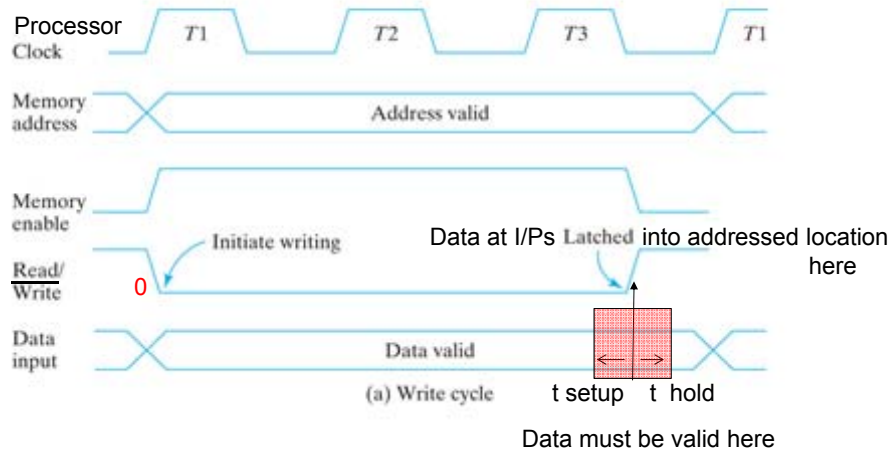

# Memory

## Write and Read Cycles


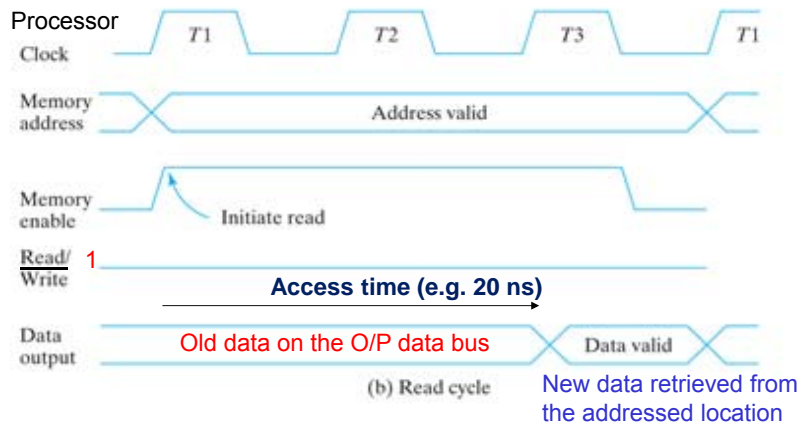


# Types of RAM (Read/Write) Memories

Two Basic Types:

- **Static RAM (SRAM):** Data stored in latch (1 latch per bit) and remains as long as power remains ON
- **Dynamic (DRAM):** Data stored as a charge on a capacitor – can be lost due to leakage, needs to be periodically refreshed, otherwise data will be lost even with power ON

1-bit Cell  $\approx$  4 Transistors

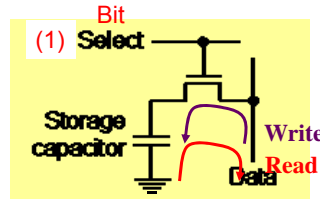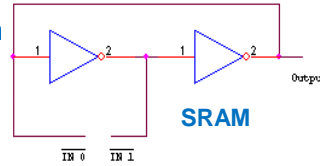


Only 1 Transistor Per 1-bit cell DRAM

Comparison: Speed, Cost, Density, Applications

Bare Circuits (Storage Only)


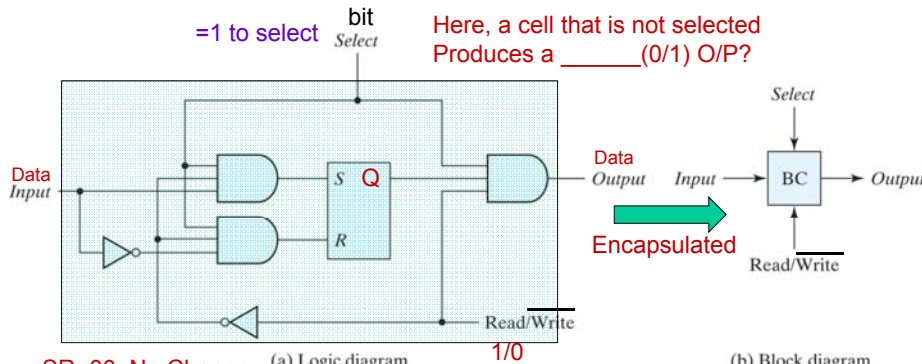
## Modeling a Complete bit circuit (BC) with controls



SR=00: No Change (Read)

Copyright ©2013 Pearson Education, publishing as Prentice Hall

Memory Enable	Read/ $\overline{\text{Write}}$	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

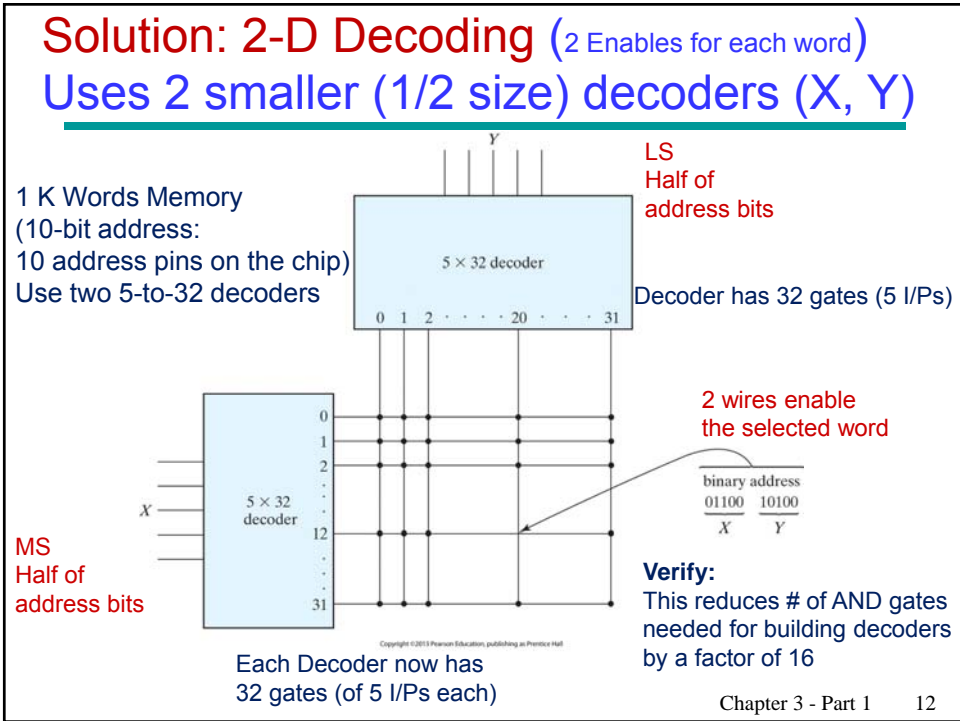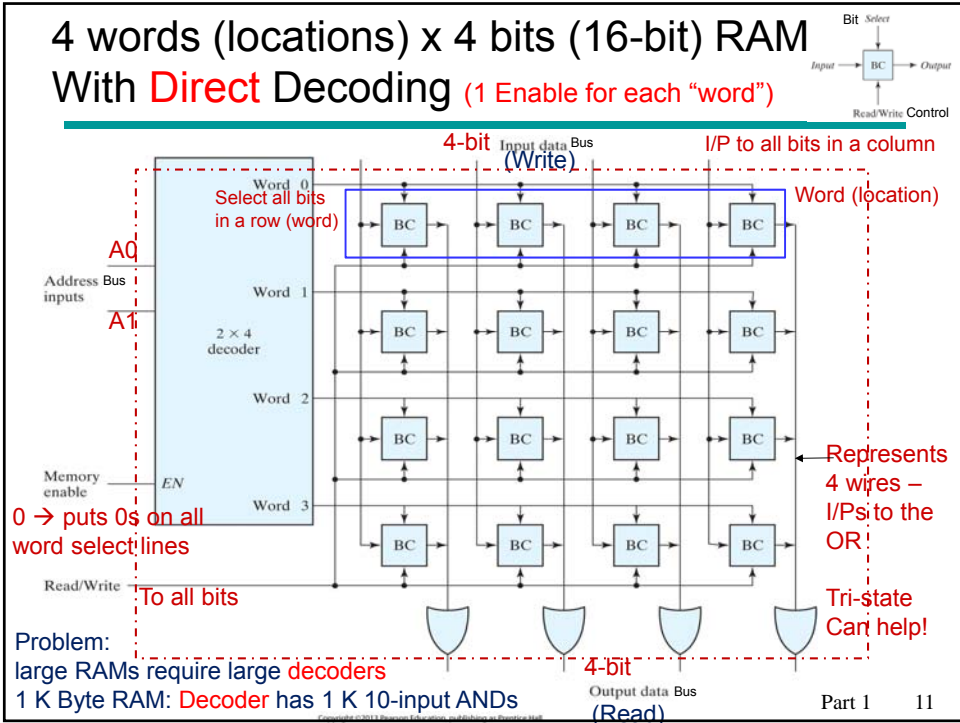

## Further Improvements for DRAM ... Address Multiplexing (reduced the # of address pins)

DRAMs are large in capacity

Their large address needs a  
Large number of pins on the chip


We can half the number of pins  
If we use separate registers for the row and column  
Addresses on the chip

64K =  $2^{16}$  locations (16-bit address)

The 16 bit address is  
Supplied to the chip  
on only 8-pins:

1. Row part with the RAS signal
2. Column part with the CAS signal

Helps reduce the physical size of  
DRAM chips

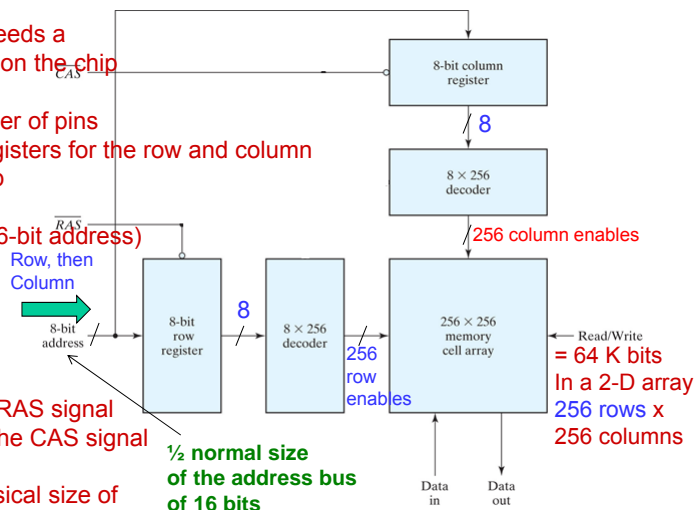

Chapter 3 - Part 1 13

## 2. Programmable Logic Implementation Technologies Overview

- Why programmable logic?
- Programmable logic:  
**Technologies** and **Configurations**
- Examples of Programmable Logic Devices:
  - Read-Only Memory (ROM)
  - Programmable Array Logic (PAL)
  - Programmable Logic Array (PLA)
  - VLSI Programmable Logic Devices  
(Field Programmable Gate Arrays- FPGA)

Chapter 3 - Part 1 14

## The Rationale: Why Programmable Logic?

---

- Facts: (Economy of Scale)
  - It is most economical to produce ICs in **large volumes**
  - But:
    - In many situations users require:
      - ICs in **smaller volumes**
      - **Frequent changes to be done** in the field, e.g. on the **Firmware** of a product under development
- A **programmable logic device** can be a **good compromise**:
  - **Produced** in large quantities
  - But also allows users to **program it** many times\* (in the field) to accommodate changes on small volumes


Integrated  
Circuits

(\*nowadays: erasable, reprogrammable, etc.)

15

## Programmable Logic Concept

---

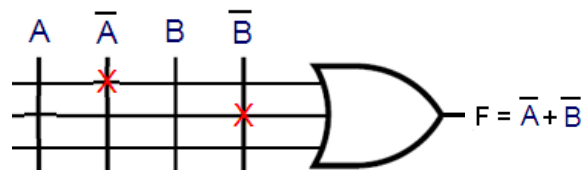

**Locations of connections inserted/removed by user determine the logic function implemented**




# Hardware Programming Technologies

## How connections are made: The ROM case




- **ROM:** In the Factory (not user-programmable)
  - Cannot be erased or reprogrammed by user
    - “Programmed” permanently through the VLSI mask during manufacturing of the chip
- **PROM:** Programmable only once,
  - e.g. using fusible links (metal connections)
- Programmable many times (Erase & then Re-program)
  - **Ultra-Violet (UV)** Erasable, e.g. **EPROMs** (off situ)
  - **Electrically** Erasable, (in situ) e.g.
    - **EEPROMs**
    - **Flash Memory**
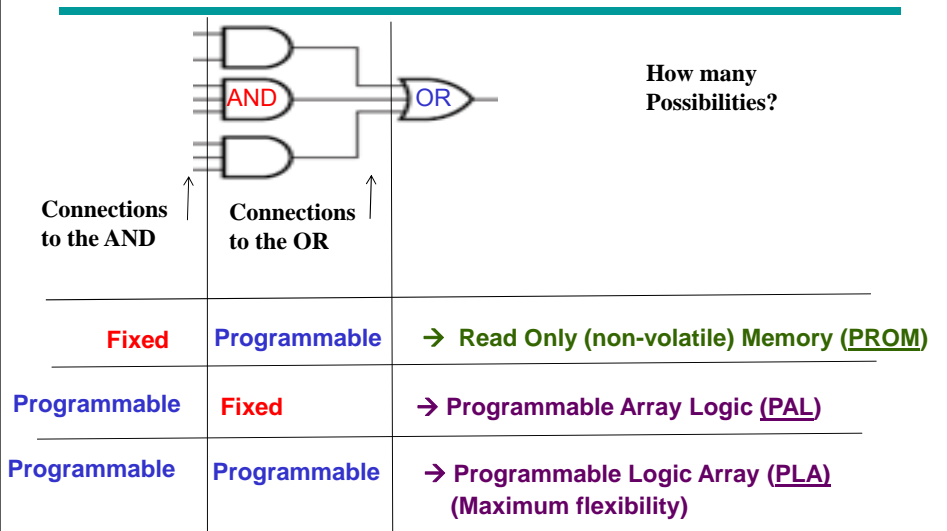
### Programmable Logic Configurations: (SOM or SOP)

All use AND-OR structure- differ in which is programmable




## ROM, PAL and PLA Configurations

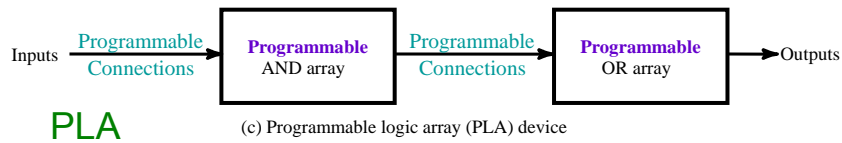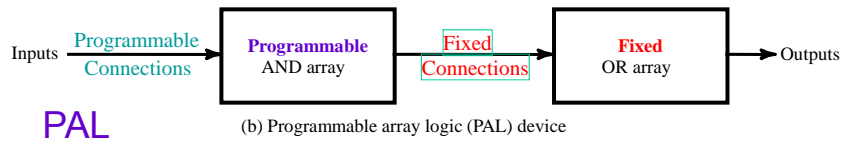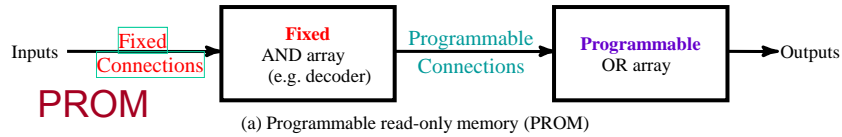
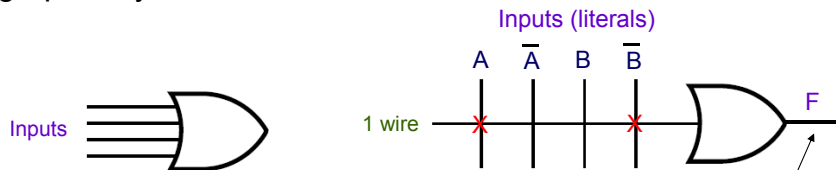
## Wiring Conventions for Programmable Logic

- We deal with a large number of gates and gate inputs
- Need a more **concise** way of expressing gate circuits graphically



(a) Conventional symbol

(b) Array logic symbol

X marks a connection, i.e. an input to the OR

For the connections shown,  
F = ?

## a. Read Only Memory (ROM): & Fixed- OR: Programmable sum of fixed minterms


- Example: 8 X 4 PROM (n = 3 i/p (address) lines, m = 4 o/p lines)

- The fixed "AND" array is in a 3-to-8 "decoder" giving all 8 minterms

- Programmable "OR"s. We use a single line to represent all inputs to an OR gate. An "X" in the array indicates connecting the minterm to the OR

- Example: For input (A,B,C) = 010: output is (F<sub>3</sub>,F<sub>2</sub>,F<sub>1</sub>,F<sub>0</sub>) = 1001.

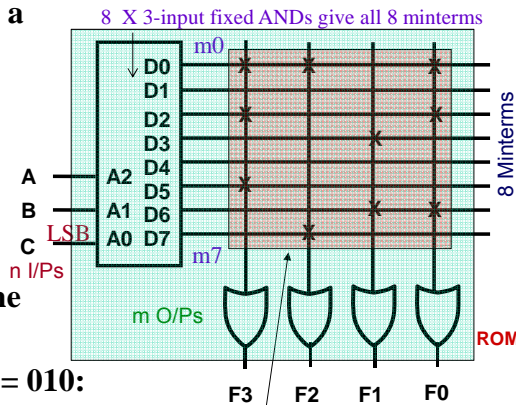- Exercise: Express the F<sub>1</sub> as -  $\sum m()$




2<sup>n</sup> x m Programmable Connections

3-input 4-output CL cct seen differently

- an algebraic expression in A,B,C

## This ROM implements this truth table

A	B	C	F3	F2	F1	F0
0	0	0	1	1	0	1
0	0	1	0			
0	1	0	1			
0	1	1	0			
1	0	0	0			
1	0	1	1			
1	1	0	0			
1	1	1	0			

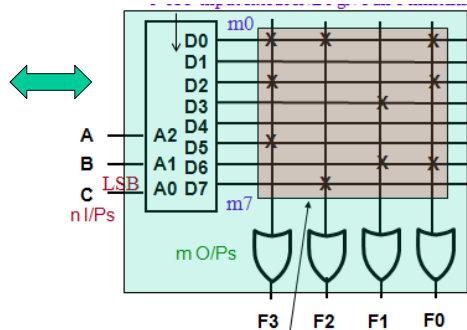

Can look at it in several ways:

- As an 8 words x 4-bit memory: at address 000 we permanently stored data 1101 (non volatile)
- As a look-up table: Enter I/P 000 you get corresponding O/P 1101
- As an implementation of 3-I/P 4 O/P Combinational Logic (Using a decoder and 4 OR gate- Unit 3)

## Read Only Memory (ROM): $n$ i/ps to $m$ o/ps $2^n$ permanent storage locations x $m$ bits each

- A Read Only Memory (ROM) has:
  - $n$  input (address) lines  $\rightarrow 2^n$  storage locations,  $2^n$  minterms
  - $m$  output lines (word width for each storage location)
- A Fixed array of  $2^n$  AND gates implements all the  $n$ -input minterms  
 Obtained from an  $n$ -to- $2^n$  decoder
- Programmable Array of  $m$  OR gates to form  $m$  Som outputs.
- The program for a PROM is simply the multiple-output truth table to be implemented
  - For a 1 at an output in the table, a connection is made from the corresponding minterm to the corresponding OR gate
  - For a 0 entry, no connection is made
- Can be viewed as a memory with the  $m$  inputs as addresses of data (output values), hence ROM or PROM names!  
 Device on previous slide is an  $8 \times 4$  memory (8 locations x 4-bit wide)
- Truth table is a listing of the memory contents at each input address

## Read Only Memory (ROM) Advantages/Limitations

Q. For 1 M (Mega) Byte PROM Device  
 (1M locations x 8 bits)

# of Input (address) lines  $n = ?$

# of Output lines  $m = ?$



- Advantages of ROMs: (= advantages of the canonical form)
  - Can implement any function (since all minterms of the input variables are available!)
  - PROM Program is derived **directly** from the truth table specifying the information to be stored
- Disadvantages:
 

(disadvantages of the canonical form- No SOP optimization)  
 As  $n$  increases  $\rightarrow$  Large Decoders needed ( $2^n$  AND gates, each having  $n$  inputs)

Example: 4-Output memory? Size?


## ROM-based Designs (Canonical Form), Som for **Combinational & Sequential** circuits

- For **Combinational Circuits**:

ROMs can be used to implement a combinational circuit given its truth tables

- Example: Look up table**

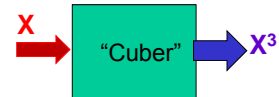example:  $X \rightarrow X^3$ ;  $X$  is a 4-bit unsigned integer



You should be able to determine the **minimum ROM size** (# of locations  $\times$  "word" size) required for a given problem

- For **Sequential Circuits**:


Use ROMs to implement the **combinational part** of the sequential circuit

## ROM-based Designs: **Combinational Circuits: Individual O/Ps**

Example 1: Implement the following two combinational functions using a ROM

$$F_1(X,Y) = \sum m(1,2,3)$$

$$F_2(X,Y) = \sum m(0,2)$$

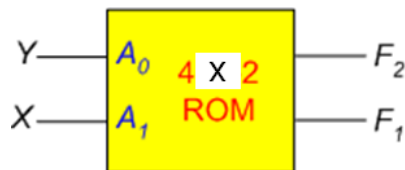

Solution should:

- Specify the smallest ROM required:  
ROM has  $n = 2$  inputs ( $\rightarrow 2^2 = 4$  locations)  
and  $m = 2$  outputs ( $\rightarrow$  Each location has 2 bits) ...i.e. a 4 x 2 bit ROM
- Specifying the ROM data content (to be programmed into the ROM):  
Directly from the truth table of the two functions

Show the connection diagram for this ROM (Decoder + ORs)

Index	ROM Address		Stored Information	
	$A_1$	$A_0$	$F_1$	$F_2$
0	0	0	0	1
1	0	1	1	0
2	1	0	1	1
3	1	1	1	0

Give Logic Diagram

ROM Programming Table

## ROM-based Design Examples: Combinational Circuits: Look-up Tables

Example 2:  $X^2$  look-up table, X is 3-bit binary number

→ Specification: Use a ROM to implement a combinational circuit that accepts a 3-bit unsigned binary number at the input and generates its **squared value** at the output.

→ Formulation:  
8 x 6 bits ROM, Truth Table →

→ Observations on the truth table:  
1. Output  $B_0$  = Input  $A_0$   
2. Output  $B_1$  = Always 0

No need to 'store' data for  $B_0$  and  $B_1$

This reduces the size of the ROM required from 8 x 6 bits to 8 x 4 bits

X			X <sup>2</sup>						
Inputs			Outputs						
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	Decimal
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49


## ROM-based Designs: Combinational Circuits : Look-up Tables

Example 2, Continued

Truth Table for Reduced ROM


ROM Address			Stored Information			
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

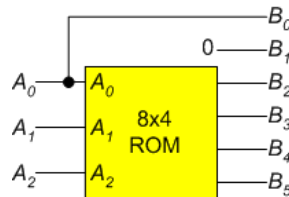Implementations of the  $X^2$  Look-up Table:




# ROM-based Designs: Sequential Circuits

## Conventional Design

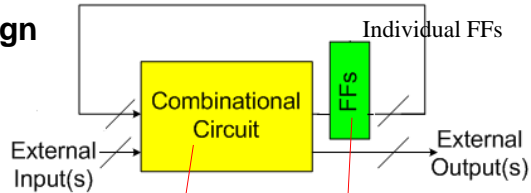

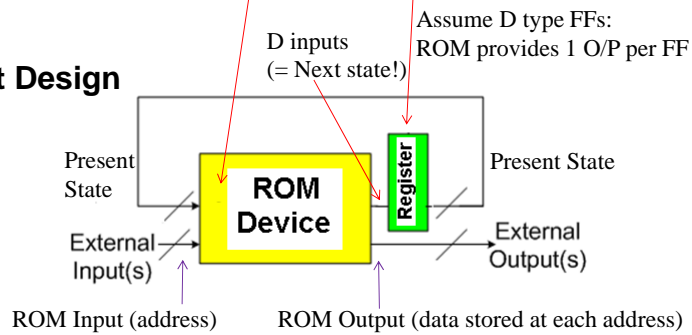
## ROM-Register Sequential Cct Design Very compact!



# ROM-based Designs: Sequential Circuit- D FF

## The ROM Required

Inputs to FFs  
D- FF: 1 per FF

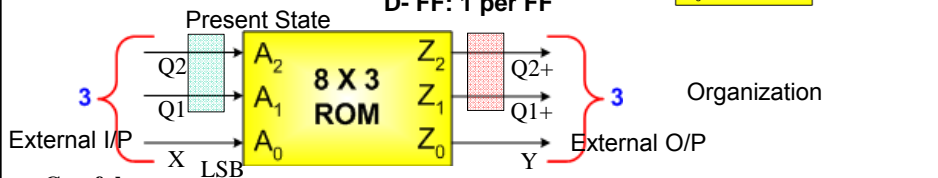

Careful  
with order  
of inputs


ROM Address			Stored Information		
$A_2$	$A_1$	$A_0$	$Z_2$	$Z_1$	$Z_0$
0	0	0	0	0	0
0	0	1	0	1	0
1	0	0	0	1	0
1	0	1	0	0	1
0	1	0	1	0	0
0	1	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

Present State I/P      Next State      O/P

Assume D type FFs:  
ROM provides 1 O/P per FF


ROM Truth Table

 Derive the state diagram  
For this sequential circuit




## Programmable Array Logic (PAL)

- PAL is the opposite of the ROM, having a set of programmable ANDs combined with a set of fixed ORs-  
(Programmable = has selectable I/Ps)
- PAL has some outputs from OR terms that can be fed back (as **internal inputs**) to all **other** AND terms, allowing implementation as **multi-level (>2)** logic circuits
- Some PALs have outputs that can be **complemented**, allowing F implementation as a POS:

$$F = \overline{F}$$

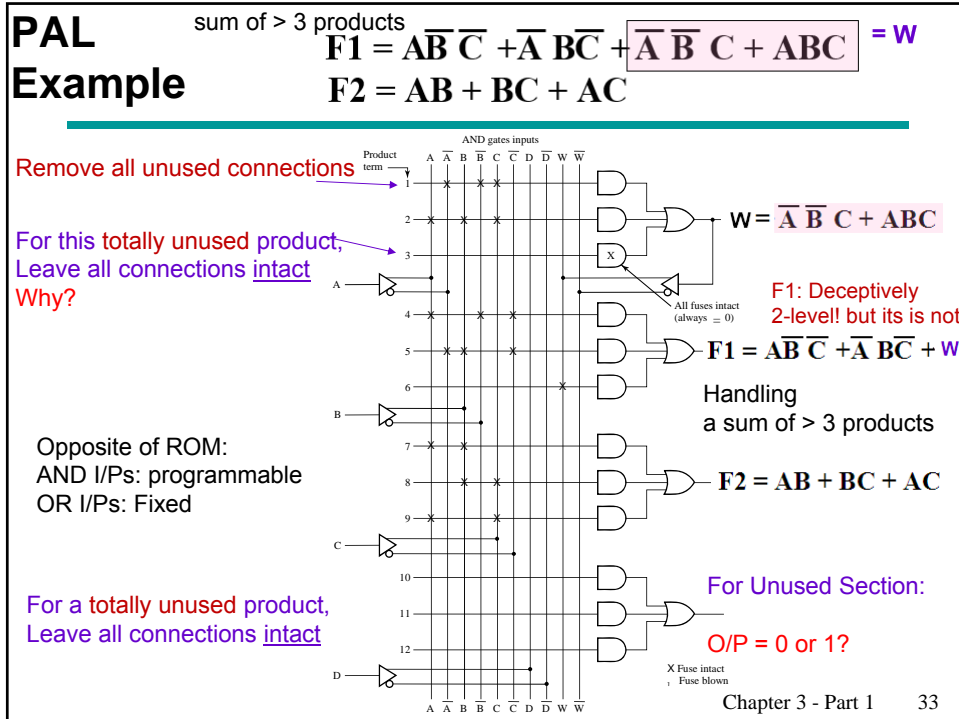
- Advantages **over** ROM
  - Allows **optimized** implementation as Sum of a few Products (usually not all minterms would be available)
  - For a given total # of gates, a PAL can support **larger n and m** than a ROM
- Limitation: 1. Functions with many products: may not be possible
- 2. Sharing of products between sections is not possible!
- multiple generation!





## PAL Programming Table

- Equations:  $F1 = \overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + \overline{A} \overline{B} C + ABC = W$   
 $F2 = AB + BC + AC$

- F1 was **factored** - has four terms (> 3)
- Factor out last two terms as W

PAL Programming Table


Product term	AND Inputs					Outputs
	A	B	C	D	W	
1	0	1	—	—	—	$W = \overline{A} \overline{B} \overline{C} + ABC$
2	1	1	—	—	—	
3	*	*	*	*	*	
4	1	0	0	—	—	
5	0	1	0	—	—	
6	—	—	—	—	1	$F2 = Y = AB + BC + AC$
7	1	1	—	—	—	
8	—	1	1	—	—	
9	1	—	1	—	—	
10	Unused Section					
11	Keep All Connections → 0 O/P					
12						

PAL comes with all Connections made. Connections that are not needed should be removed

How many connections are removed for product 1?, for product 3? 34
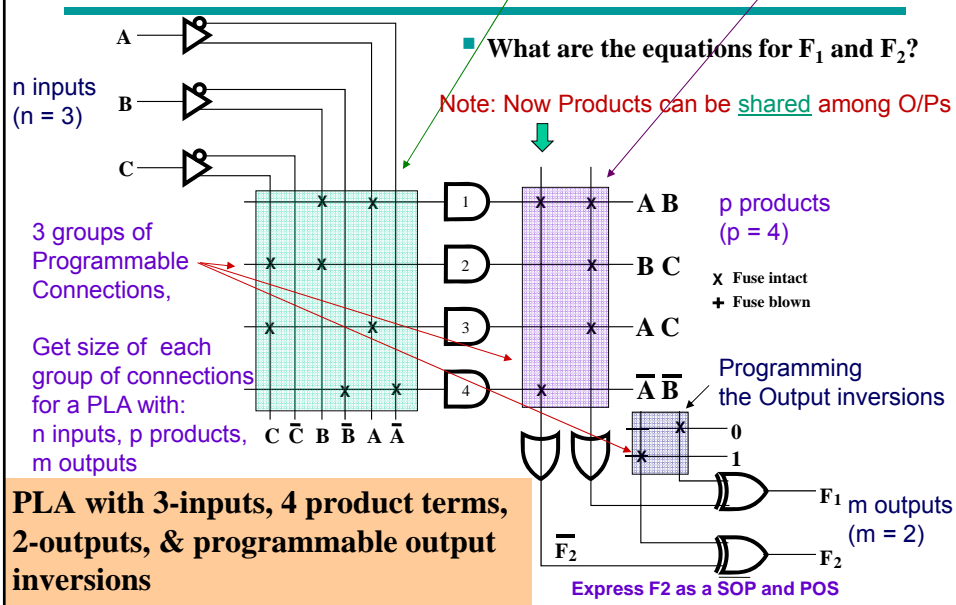
### c. Programmable Logic Array (PLA)

Programming at both the **product** and the **sum** levels



## Programmable Logic Array (PLA)

- Compared to ROMs and PALs, PLA is the **most flexible & economical programmable device**: having programmable ANDs, programmable ORs, and even programmable output inversions!
- Advantages
  - More concise implementations than ROM – Uses K-map optimized products
  - Allows larger 2-level sums than with PALs: All product terms are **available for sharing by all summing Ors**
  - You do not have to generate a product more than once as in PAL
  - PLAs have outputs that can be complemented, so a SOP can be that of either  **$F$  or  $F'$** , whichever proves more optimal - globally
- But still
  - The limited **# of product terms** can limit the application of a PLA.  
Solution: → Use global multiple-output optimization to reduce the number of product terms required to fit it into the PLA.

## PLA Global Optimization Example

F1(A,B,C), F2(A,B,C), PLA: (3 inputs, 4 products, 2 outputs with programmable o/p inversion)

- K-map specifications**
- How can this be implemented with only four products?**
- Complete the programming table**
- Choose implementations (F or  $\bar{F}$ ) that has the largest # of shared products!**
- Is this PLA enough if we choose to implement F1 & F2 directly?**

F1 map

BC \ A	00	01	11	10
0	0	1	0	1
1	1	0	0	0

$F_1 = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$   
 $F_1 = AB + AC + BC + \bar{A}\bar{B}C$

F2 map

BC \ A	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$F_2 = AB + AC + BC$   
 $F_2 = \bar{A}C + \bar{A}B + \bar{B}C$

Product term	Inputs			Outputs	
	A	B	C	F1	F2
1	1	1	-	1	1
2	1	-	1	1	1
3	-	1	1	1	1
4	0	0	0	1	-

SUM (OR) Programming (Vertically)  
Product (AND) Programming (horizontally)

## Programmable Logic Array (PLA) Example, Contd.

