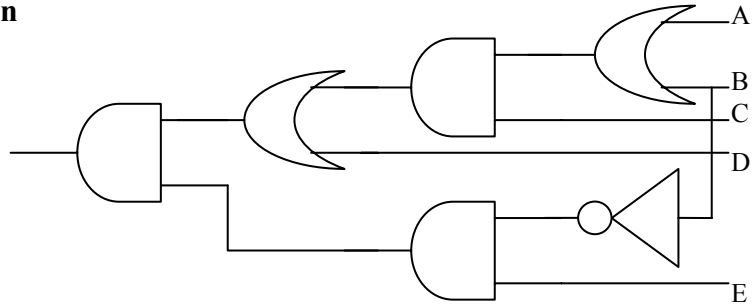


Q.1. Convert the following logic diagram to:

- (a) **NAND Only implementation**
- (b) **NOR Only implementation**



Q.2. Implement the following functions, assuming the inputs are only available in true format and using the specified conditions:

- (i) $F = \overline{(XY + Z)}(Y + XZ)$ Using minimum number of logic levels and using NANDs only
- (ii) Repeat (i) above using minimum number of NAND gates
- (iii) $F = \overline{(XY + ZY')} X'Z'$ Using minimum number of logic levels and using NORs only
- (iv) Repeat (iii) above using minimum number of NOR gates

Q.3. A combinational circuit has 4 inputs (X, Y, W and Z) and one output. The output is 1 if the majority of inputs are equal to 1 and it is 0 otherwise. Show the implementation of this circuit using:

- (i) An 8-to-1 Multiplexer,
- (ii) Minimum number of 3-to-8 decoders,
- (iii) Minimum number of 2-input NAND gates.

Q.4. It is required to design a circuit that has two 4-bit inputs $A=A_3A_2A_1A_0$ and $B=B_3B_2B_1B_0$ and one 5-bit output $C=C_4C_3C_2C_1C_0$. The circuit implements the following four functions based on the values of the two selection inputs, S1 and S0.

S1 S0	Function
0 0	$C=A - B$
0 1	$C=A + B$
1 0	$C=-A$
1 1	$C=2A$

Implement the circuit using any components you like (including MSI components).

