


COE 200, Term 042
Fundamentals of Computer Engineering
HW# 10

Memory Elements Design & Operation

- Q.1.** Draw the logic diagram of a clocked D-Latch using NOR gates only.
- Q.2.** Show the design of the following flip-flops using SR latches and external gates:
- (i) A negative-edge triggered D-FF.
 - (ii) A negative edge-triggered JK-FF.
 - (iii) A positive-edge triggered T-FF.
- Q.3.** A set-dominant flip-flop has set and reset inputs. It differs from a conventional SR flip-flop in that, when both S and R are equal to 1, the flip-flop is set.
- (i) Obtain the characteristic table of the set-dominant flip-flop.
 - (ii) Derive the excitation table for the set-dominant flip-flop.
 - (iii) Design a positive-edge triggered set-dominant flip-flop using D-FF.
 - (iv) Design a positive-edge triggered set-dominant flip-flop using JK-FF.

Synchronous Sequential Circuit Design

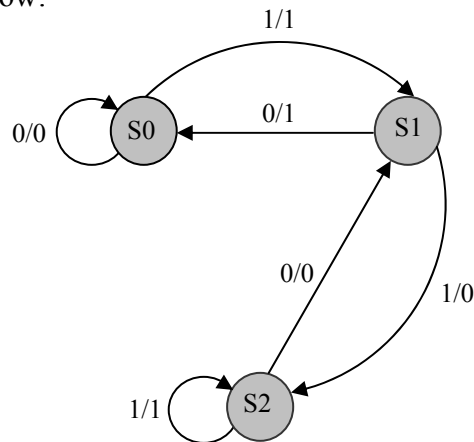- Q.4.** It is required to design a sequential circuit that receives a serial input X, and produces a serial output Z, equivalent to $3 \cdot X$, i.e., $Z = 3 \cdot X$. The state diagram for this circuit is shown below:



- (i) Implement the sequential circuit using D-FFs and the smallest number of gates possible assuming the state assignment: S0=00, S1=01, and S2=10.

- (ii) Implement the sequential circuit using D-FFs and the smallest number of gates possible assuming the state assignment: $S_0=11$, $S_1=01$, and $S_2=10$.
- (iii) Implement the sequential circuit using JK-FFs and the smallest number of gates possible assuming the state assignment: $S_0=00$, $S_1=01$, and $S_2=10$.

- Q.5.** You are to design a serial adder (**Add3**) that computes the sum of three separate serial input streams rather than the usual two. The adder has three primary inputs X_1 , X_2 , X_3 , and a single primary output Z . Draw the state diagram, construct the state table, and use D flip-flops and show the detailed design of the **Add3**.
- Q.6.** A sequential circuit **MON** is to be designed to monitor the condition of a patient in a hospital bed. The input to **MON** is a binary number n that ranges in value from 1 to 7 and indicates the patient's condition. The expected value of n is sent to **MON** automatically every five seconds. If n goes below 2 or above 4 on *two or more* occasions, the machine should activate an alarm at a nurse's station. The nurse responds by administering medication to the patient and resetting the monitor. *Using JK flip-flops and NOR gates only*, carry out the logic design of **MON**. Obtain a state table, a state assignment, and a complete logic diagram.

Synchronous Sequential Circuit Analysis

- Q.7.** A sequential circuit uses 2 flip-flops. The first (**A**) is a **D-FF** while the second (**B**) is a **JK-FF**. The circuit has 2 inputs X and Y , and one output Z . The circuit is specified by the following input equations:

$$D_A = X' Y + X A \qquad J_B = X' B + X A \qquad K_B = X' A + X B \qquad Z = B$$

(i) Draw the logic diagram of the circuit.

(ii) Derive the state table.

Additional Design Problem

- Q.8.** Design a sequential circuit with two flip-flops A and B and two inputs E and X . If $E=0$, the circuit remains in the same state, regardless of the value of X . When $E=1$ and $X=1$, the circuit goes through the state transitions from 00 to 01 to 10 to 11, back to 00, and then repeats. When $E=1$ and $X=0$, the circuit goes through the state transitions from 00 to 11 to 10 to 01, back to 00, and then repeats. Design the circuit using the following types of FFs:
- (i) Positive-edge-triggered D-FF.
 - (ii) Positive-edge-triggered JK-FF.
 - (iii) Positive-edge-triggered T-FF.