

COE 200, Term 042
Fundamentals of Computer Engineering
HW# 6

Q.1. Show that the NAND and NOR operations are not associative.


Q.2. Given the function $F(w, x, y, z) = \Sigma(2,3,6, 10, 11)$ with a set of don't cares at $\Sigma(1,5, 9, 12, 13, 14, 15)$, obtain a simplified expression and two alternative 2-level implementations for the function in the following forms

- (i) SOP
- (ii) POS
- (iii) AOI
- (iv) OAI







Q.3. Algebraically, prove the following

- (i) $X \oplus 1 = X'$
- (ii) $X \oplus 0 = X$
- (iii) $(X + Y) \odot (X+Z) = X + (Y \odot Z)$
- (iv) $X \odot Y \odot (X+Y) = X Y$

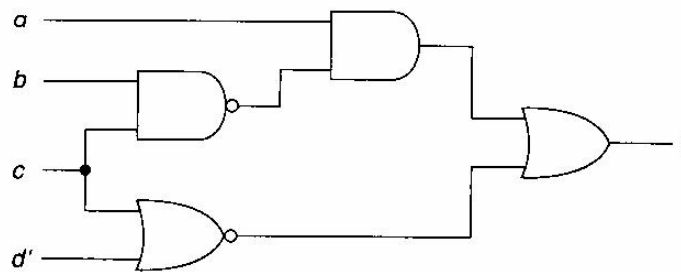Q 4 For each of the following circuits, find the expression of the output function then put it in a SOP form.



a.

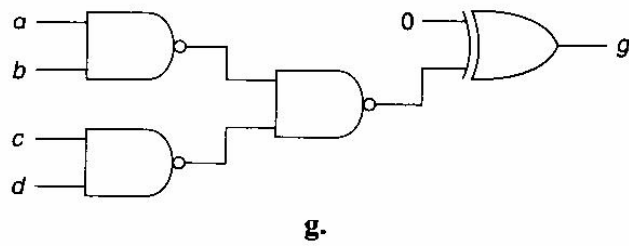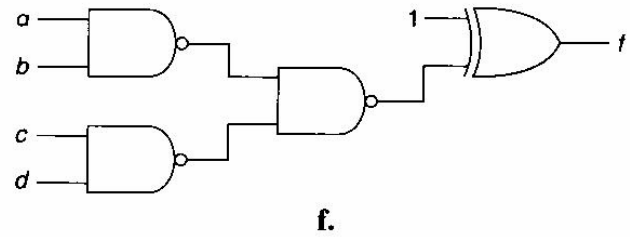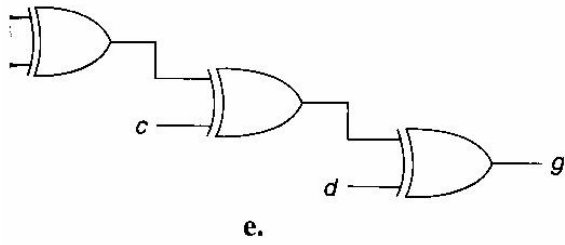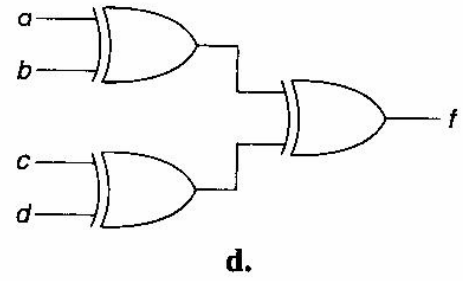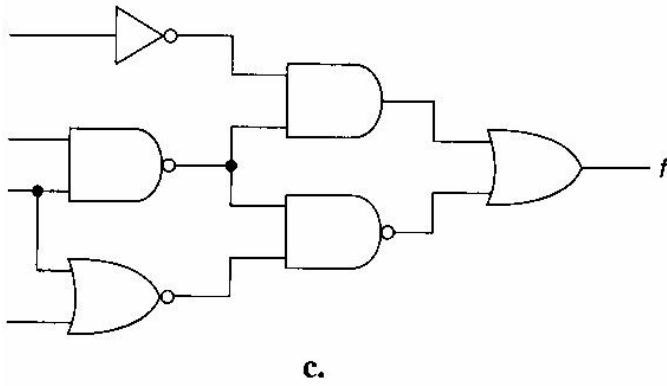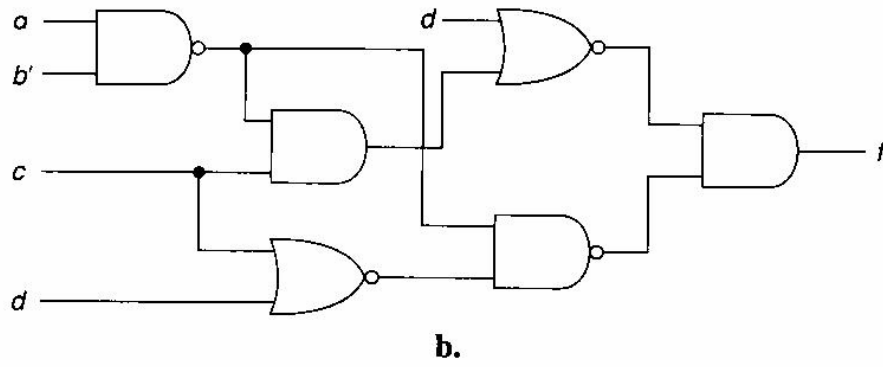

- Q5) Convert the following to:
 (a) NAND-only implementation
 (b) NOR-only implementation

