

COE360 – Assignment # 3
Dr. M. Elrabaa (051)

Q1) For the circuits shown, assume $V_{tn} = |V_{tp}| = 0.8V$ for the enhancement MOS, and make any other reasonable assumptions you need to calculate V_o .

$$C_{ox} = 2 \text{ fF}/\mu\text{m}^2, \mu_n = 600 \text{ and } \mu_p = 250$$

