


**COE 561 Digital System Design and Synthesis, Term 071**  
**Assignment # 5, Due Sunday, January 13th, 2008**

**Q.1.** Consider the incompletely-specified FSM represented by the following state table:

Input	Present State	Next State	Output
0	S1	S1	0
1	S1	S4	*
0	S2	S2	0
1	S2	S1	1
0	S3	S4	0
1	S3	S5	1
0	S4	S6	0
1	S4	S5	1
0	S5	S6	1
1	S5	S1	0
0	S6	S3	*
1	S6	S5	1

- (i) Replace the don't-care conditions by 0's and minimize the obtained state table.
- (ii) Replace the don't-care conditions by 1's and minimize the obtained state table.
- (iii) Minimize the state table of the incompletely specified FSM.

 **Q.2.** Consider the synchronous sequential circuit given below-specified FSM represented by the following state table:



- (i) Draw the synchronous network graph corresponding to the given circuit. In the graph, vertices represent inputs, outputs, gates, and fanout stems.
- (ii) Assume that delay of each gate is 1. Retime the graph to reduce the cycle time. Draw the resulting circuit.
- (iii) Read the library **synch.genlib** using the command **read\_library synch.genlib**. Then, map your design to the library using the command **map -s**. Then, retime the circuit using the command **retime**. Compare the maximum arrival time before and after retiming. Compare the obtained solution to the solution you obtained in (ii).

**Q.3.** Solve problems 4.1 and 4.2 in the text book.