


COE360 Course Project

Dr. Muhammad Elrabaa

Choose one of the following projects depending on your group size. For all projects use AMI's 0.5 μm technology (5V supply) and assume 2 pF load capacitance at all your circuit's outputs. Also, all gates should have symmetrical noise margins and rise and fall times

I. Projects for Groups of 3:

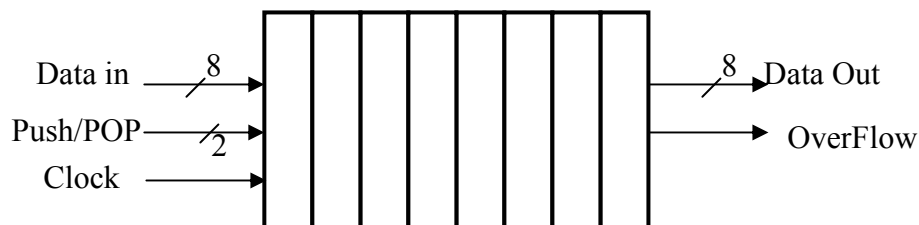1. Design an 8-bit X 8 FIFO buffer that can be read and written simultaneously with a buffer full/empty indicators and operating frequency of 500 MHz.



2. Design a digital filter that implement the function at 500 MHz:

$$Y = \sum 2^i X_i , \quad i=1,2,3$$

The input data (X) are 6-bit signed-integers. Round the results to produce an 8-bit signed-integer result.

3. Design a small look-up table (4 lines, 24-bits wide). An 8-bit word is read with a 16-bit tag, if the entry exists, otherwise a miss indicator is asserted. New entries are always written over the oldest-read entry. Operating frequency is 250 MHz.

