

COE360: Dr. M. Elrabaa

Take Home Quiz # 4 (due 12 noon, Sat. 13/12)

Problem#1:

Implement the following function in static CMOS using minimum number of transistors:

$$F = A(\overline{B} + C) + \overline{D}E$$

Assume that the inputs are only available in true format.

Problem #2:

Show the CMOS implementation of a positive edge-triggered D-FF with asynchronous input R and S that affect the FF as shown in the table below:

Clk	R	S	Q <sup>+</sup>
0	0	0	Q
⌈	0	0	D
X	0	1	1
X	1	0	0
X	1	1	Q <sup>~</sup>

Problem #3:

Design the following circuit in static CMOS using minimum number of transistors. The maximum input frequency is 4 GHz, minimum channel length is 1 μm,  $t_{ox}=20$  nm,  $V_{tn}=V_{tp}=0.8V$ ,  $I_{Dsat}(nmos) = 500 \mu A/\mu m$

