

WEEK 5 (LECTURES)

MOS Digital Circuits:


-Digital means \rightarrow I/Ps & O/Ps are binary (0 OR 1) represented by 2 voltages: V_{OL} = (V output Low) = Logic Zero;
 V_{OH} = (V output High) = Logic One.

-The input voltage at which the output voltage is in the middle of its range is called the logical threshold V_{thlog} .

▪ How can we make Digital circuits using switches?

 1. Inverters

-Using a single NMOS switch and inverter.




I/P	I*	V _{out}	O/P
0	0A	V _{DD}	1
V _{DD}	I	V _{DD} -IR*	0

*Where I is the current through the resistor and the NMOS switch, R is the resistance and IR is the voltage drop across the resistor

This is called NMOS inverter

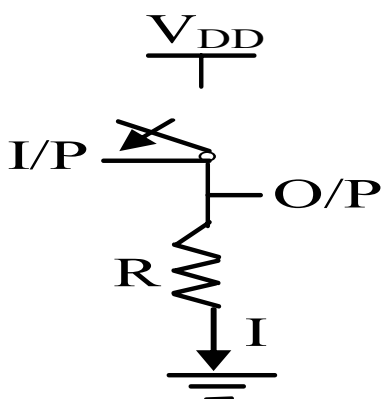
- Another way, using a single PMOS switch and a resistor:



I/P	I	V _{out}	O/P
0	I	IR	1
V _{DD}	0A	0V	0

This is called a PMOS inverter.

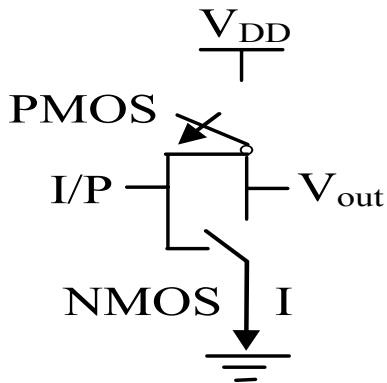- A 3rd way using 2 switches(an NMOS and a PMOS):



<i>I/P</i>	<i>I*</i>	<i>V_{out}</i>	<i>O/P</i>
0	0A	V_{DD}	1
V_{DD}	0A	0V	0
*I is the current through the two switches			


This is called CMOS (Complementary MOS) inverter.

Other gates;

ex. 2 I/P NAND?


- **NMOS NAND:**

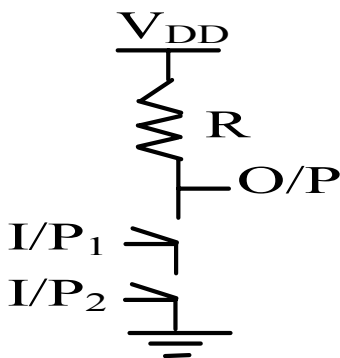O/P = 0 only If both I/P are 1 & O/P =1 otherwise




<i>I/P₁</i>	<i>I/P₂</i>	<i>O/P</i>
0	0	1
0	1	1
1	0	1
1	1	0


- **PMOS NAND:**

 

- **CMOS NAND:**

 


▪ **NMOS 2 I/P NOR:**

 


Modeling The MOSFET as a Switch:

 We will utilize the fact that in digital circuits all transistors will have either a 1 or 0 input to simplify the way we do calculations. So transistors are either ON or OFF. Hence we can model them as shown below:



 - **We model the NMOS switch (or the PMOS switch) as an ideal switch in series with a resistance.**
- **The ideal switch has no voltage drop across it when it is ON or closed and is an open circuit when it is OFF or open.**
- **This means that the transistor is Open Circuit when OFF (zero current through it) and has a resistance R_{eq} when it is ON ($I/P = V_{OH}$)**




R_{eq} = the resistance of the MOS channel in the ON state.

We will approximate this resistance as (see the graph below):

$$R_{eq} = V_{DD} / 2I_{Dsat}$$

$$I_{Dsat} (@ V_{DS} = V_{GS} = V_{DD}) = \frac{1}{2} M_n C_{ox} (w/L) (V_{DD} - V_{th})^2$$
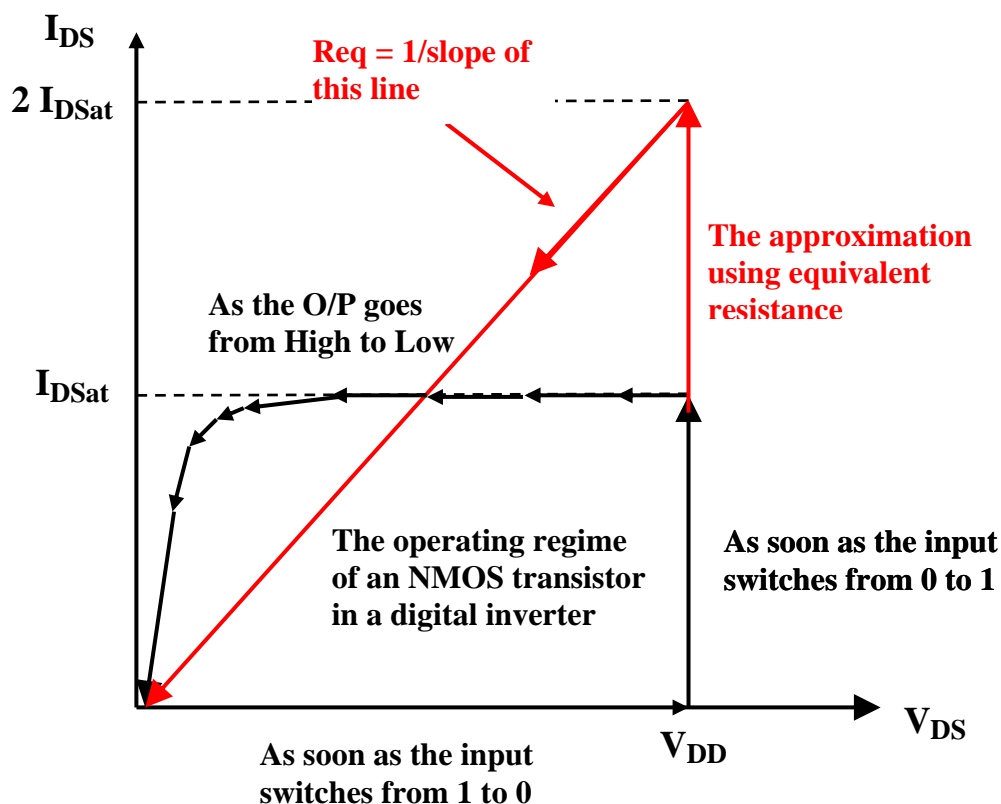
$$R_{eq} = V_{DD} / M_n C_{ox} (w/L) (V_{DD} - V_{th})^2 = 1 / M_n C_{ox} (w/L) (V_{DD} - V_{th})$$



• Usually IC manufacturers provide designers with device parameters such as L_{min} , V_{DD} , V_{th} , C_{ox} & $I_{Dsat/\mu m}$.

$$I_{Dsat/Mm} = I_{DS} \text{ with } L = L_{min}, w = 1 \mu m, V_{DS} = V_{GS} = V_{DD}$$

→ R_{eq} of a MOSFET with width w :


$$R_{eq} = (V_{DD} - V_{th}) / (2 I_{Dsat/\mu m} * w)$$

$$= 1 / (\mu_n C_{ox} (w/L_{min}) (V_{DD} - V_{th}))$$

NMOS Inverter:

Basic structure

The load is always ON

 


→ 3 types are possible depending on the load:


1- Resistive Load:

$$V_{OH} = V_{DD}$$
 
$$V_{OL} = V_{DD} - IR = (V_{DD} * R_{eq}) / (R_{eq} + R_L)$$



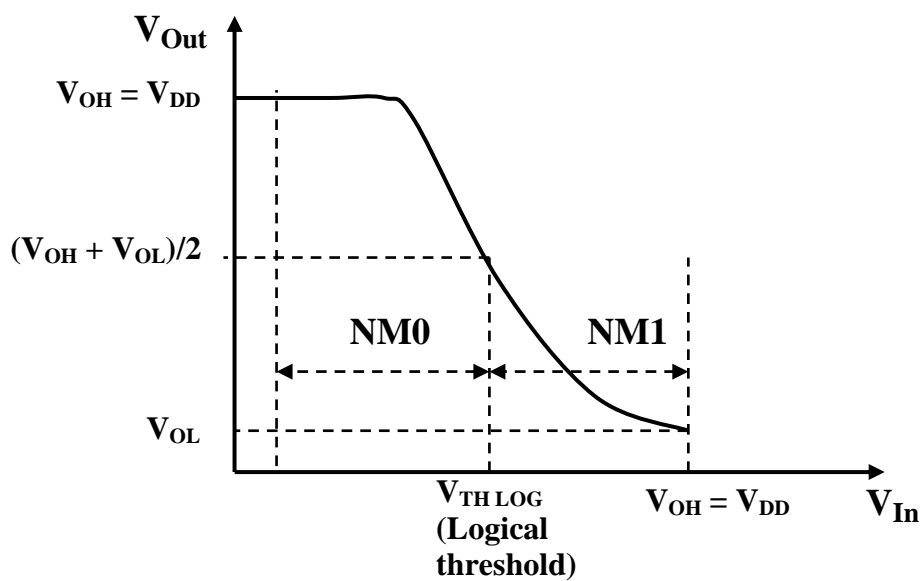-Voltage Characteristics and noise margins:



→ **Average static Power:**

$$P_{DC\text{average}} = \frac{1}{2} V_{DD} I = \frac{1}{2} (V_{DD}^2 / (R_{eq} + R_L))$$

Noise Margins (NMs):

NMs can be approximated as:

$$NMO = V_{thlog} - V_{OL}$$

$$NM1 = V_{OH} - V_{thlog}$$


Average Propagation Delay:

When I/P = V_{OL}

The rising Delay T_r = time From I/P = 50% of its final value to rising O/P reaching 50% of its final value ($\approx 0.5 V_{DD}$)

T_r is approximated as $R_L C_L$

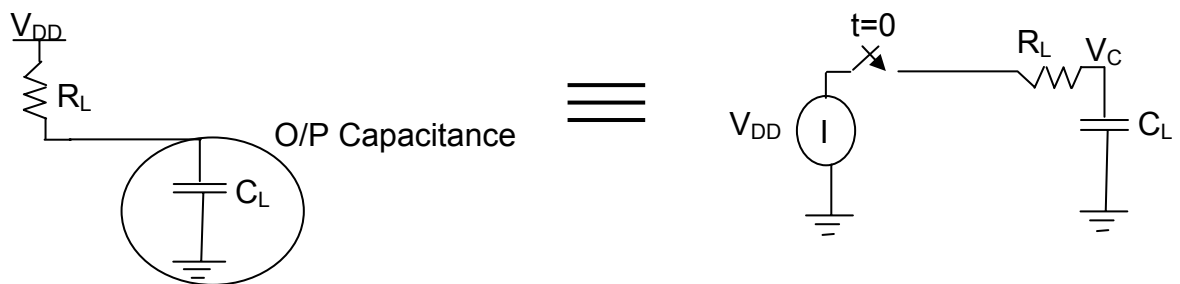
This is obtained as follows: We are charging the output capacitance C_L through a resistance R_L as shown in the figure below. Hence



$$V_C(t) = V_{DD} (1 - \exp(-t / R_L C_L))$$

$$\text{@ } t = R_L C_L; \quad V_C = V_{DD} (1 - \exp(-1)) = 0.69 V_{DD} \approx 0.5 V_{DD}$$

 Fall Delay T_f = time From I/P = 50% of its final value to falling O/P reaching 50% of its final value ($\approx 0.5 V_{DD}$)



$$T_f = R_{eq} C_L$$

$$\therefore T_{D_{ave}} \text{ (average Prob. Delay)} = \frac{1}{2} (T_f + T_r) = \frac{1}{2} C_L (R_L + R_{eq})$$


$$\longrightarrow \text{The max. possible I/P freq. : } F_{I/P_{max}} = \frac{1}{2T_{D_{ave}}}$$

$$\longrightarrow \text{Dynamic Power: } P_{D_{ynave}} = F_{I/P} C_L V_{DD}^2$$

Ex. Design an NMOS inverter with the following specifications $V_{OH} = V_{DD}$; $V_{OL} = 0.1 V_{DD}$; $P_{DC_{ave}} = 10 \mu W$. Assume a ($1 \mu m$, 5V) technology, $I_{D_{sat}/Mm(NMOS)} = 500 \mu A/\mu m$ & $V_{th} = 0.8V$.

Ans.

1. Circuit

 

2. Using resistive load:

$$V_{OH} = V_{DD}$$

$$V_{OL} = (V_{DD} R_{eq}) / (R_{eq} + R_L) = 0.1 V_{DD}$$

$$\longrightarrow R_{eq} = 0.1(R_L + R_{eq}) \rightarrow R_L = 9 R_{eq} \text{ ----- } 1$$

$$\longrightarrow P_{DCave} = 10 \cdot 10^{-6} = \frac{1}{2} (V_{DD}^2 / (R_{eq} + R_L))$$

$$\longrightarrow R_L + R_{eq} = 12.5 / 10 \cdot 10^{-6} = 1.25 M\Omega \text{ ----- } 2$$

Sub. 1 in 2:

$$10 R_{eq} = 1.25 \cdot 10^6 \quad R_{eq} \longrightarrow = 0.125 M\Omega = 125 K\Omega$$

$$\longrightarrow R_L = 9 \cdot 125 K\Omega = 1.125 M\Omega$$

For the NMOS assuming $L = L_{min}$

$$R_{eq} = (V_{DD} - V_{th}) / 2 I_{Dsat/Mm} * w \quad \rightarrow$$

$$w = 4.2 / 2 * 500 * 10^{-6} * 125 * 10^3 = 0.034 \mu m$$

However we are using a $1 \mu m$ technology \rightarrow This means nothing can be less than $1 \mu m$.

\longrightarrow This w was calculated assuming $L = L_{min} = 1 \mu m$

\longrightarrow The required $w/L = 0.034/1$, let $w = 1 \mu m$

$\longrightarrow 1/L = 0.034 \longrightarrow L = 1/0.034 = 30 \mu m$

Ex. For the inverter design in last example, calculate the noise margins & maximum I/P freq. at a load of $100ff$ ($100 \cdot 10^{-15} F$).

Ans.


$$NM0 \approx V_{thlog} - V_{OL}$$

$$NM1 \approx V_{OH} - V_{thlog}$$

V_{thlog} (logical + threshold) is the input voltage that would make $V_{out} \approx V_{DD}/2$.

In this case:

Assuming that the NMOS is in saturation:

 

$$I_{DS} = (V_{DD} - (V_{DD}/2)) / R_L = 2.5 / 1.125 M\Omega$$

$$= 2.22 \cdot (10^{-6}) = \frac{1}{2} M_n C_{ox} (w/L) (V_{GS} - V_{th})^2$$

$$= \frac{1}{2} \mu_n C_{ox} (w/L) (V_{thlog} - V_{th})^2$$

To find $\mu_n C_{ox}$, we use $I_{Dsat/\mu m}$ given in example.

$$I_{Dsat/Mm} = 500 \mu A = \frac{1}{2} \mu_n C_{ox} (1/1) (V_{DD} - V_{th})^2$$

$$\longrightarrow \mu_n C_{ox} = (100 \cdot 10^{-6}) / 4.2^2$$

Sub. In 1:

$$2.22 \cdot 10^{-6} = \frac{1}{2} ((1000 \cdot 10^{-6}) / (4.2^2)) \cdot 0.034 (V_{thlog} - 0.8)^2$$

$$\sqrt{(4.44 \cdot 4.2^2) / 34} = (V_{thlog} - 0.8)$$

$$\longrightarrow V_{thlog} = 2.318V \longrightarrow V_{GS} = 2.318 < 2.5 = V_{DS}$$

So, our assumption was correct.

$$\therefore NM0 = 2.318 - 0.5 = 1.818V$$

$$NM1 = 5 - 2.318 = 2.692V$$

$$F_{I/Pmax} = 1/2 T_{Dave} = 1/(T_r + T_f)$$

$$\longrightarrow T_r = C_L \cdot R_L = 100ff \cdot 1.125 \cdot 10^6 = 112.5ns$$

$$\longrightarrow T_f = C_L \cdot R_{eq} = 100ff \cdot 125K\Omega = 12.5ns$$

$$\longrightarrow F_{I/Pmax} = 1/125ns = 8MHz$$

2- Enhancement NMOS Load:

$$V_{OH} = V_{DD} - V_{th}$$

$$V_{OL} = V_{DD} (R_L / (R_L + R_{eq}))$$

R_L : equivalent resistance of the load transistor.

(Reduced noise margins, but smaller area than the resistive load)



3- Depletion NMOS Load:

The depletion load has $V_{th} < 0$

$$V_{OH} = V_{DD}$$

$$V_{OL} = V_{DD} (R_L / (R_L + R_{eq}))$$
  
$$\longrightarrow P_{DCave} = \frac{1}{2} (V_{DD}^2) / (R_L + R_{eq})$$



EX. Design a depletion load NMOS inverter such that $V_{OL} = 0.1V_{DD}$ $P_{DCave} = 10M$ W. Use the 1Mm, 5V technology. Assume V_{th} for the depletion NMOS = -2V.

Ans.

$$V_{OH} = 5V = V_{DD}$$

$$V_{OL} = V_{out} \text{ when } V_{in} = 5V$$

The driver NMOS is in linear region

The load NMOS is in sat.

$$I_{DSload} = I_{DSdriver} \rightarrow$$

$$\frac{1}{2} \mu_n C_{ox} (w/L)_L (0 - (-2))^2 = \mu_n C_{ox} (w/L)_D ((5 - 0.8)0.5 - \frac{1}{2} (0.5)^2)$$

$$\rightarrow (w/L)_L = 0.49 (w/L)_D \text{ -----1}$$

$$\text{Also, } P_{DCave} = 10 * 10^{-6} = 0.49/2 @ V_{in} = V_{OH} * V_{DD}$$

$$\rightarrow I_{DS} \text{ when } V_{in} = 5V = 20 * 10^{-6} / 5 = 4 \mu A$$

$$= \frac{1}{2} \mu_n C_{ox} (w/L)_L (4) \rightarrow \text{this gives us } (w/L)_L \text{ and then}$$

from 1 we get $(w/L)_D$

