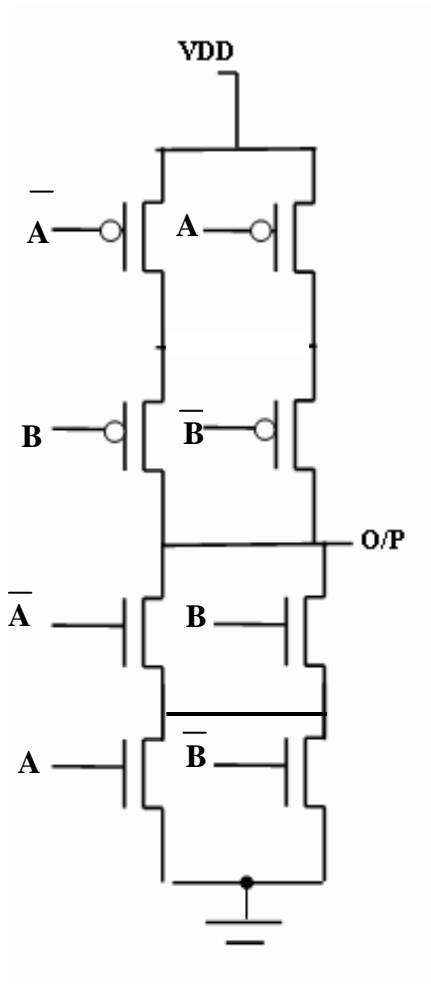


Ex4: Implement a 2 I/P XOR in CMOS

Sol: $F = A\bar{B} + \bar{A}B$


F is not complemented and some of the I/P's are complemented.
we need to do some logic transformations:

$$F = [\overline{A\bar{B} + \bar{A}B}] \quad (\text{expand the 1}^{\text{st}} \text{ complement}) \rightarrow F = \overline{(\bar{A}+B)(A+\bar{B})}$$



- # of transistors = 12 T
- # of logic levels = 2
- # of gates = 3 (including two inverters for the inputs)

Another XOR implementation (basically as the complement of the XNOR i.e. $\overline{\overline{A}\overline{B}+AB}$)

 

Ex5) Implement $F = \overline{A} (B + C + D) + \overline{E}$ Using minimum # of transistors.

Sol : F is not complemented and some I/P are complemented .

2 choices for logic transformation

$$F = \overline{\overline{A} (B + C + D) + \overline{E}}$$

F has five literals (the occurrence of each variable in the Boolean expression is a literal whether the variable is in true or complemented form). E.g. the 2 I/P XOR had 4 literals.

1) implement \overline{F} then invert

→ the # of T = 4 T (to invert A & E)
 + 10T (to implement the expression with “5literals”)
 + 2T to invert the O/P = 16T


3 logic levels , 4 Gates

2) Expand the 1st complement then implement $F = [A + \overline{C} \overline{B} \overline{D}] \cdot E$

of T = 6 T for I/P : C, B & D inversions
 + 10T for expression = 16 T

of gates = 4 gates
 # of logic levels = 2

choose 2) since it has lower # of logic levels

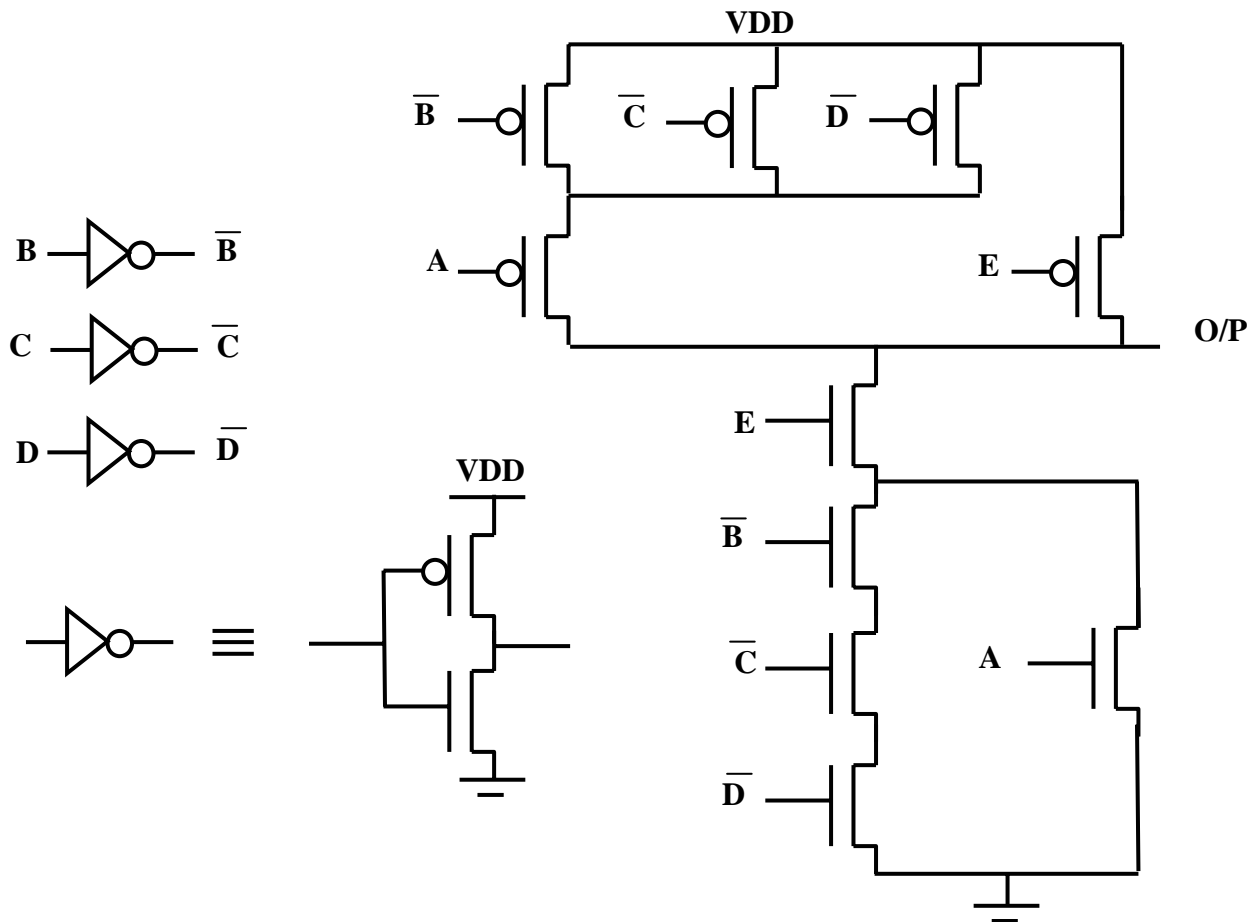


Ex6) Redo Ex5 assuming that inputs are available in true and complement form

Sol: first choice # of transistors = 10 T for expression
 + 2 T for O/P inverters

→ 12 transistors → 2 gates → 2 logic levels


Second choice # of transistors = 10 T and 1 logic level (1 gate)
 So we choose 2nd choice with no need for input inverters..

 Ex7) in the following PD block of a CMOS Gate, find the function of this circuit
 & obtain the pull up (PU) block



$$F = \overline{[(AB + C)D + E]G + H}$$

PU:

 


Ex8) implement the following function in CMOS using minimum number of logic levels

$$F = \{ [(\bar{A} + \bar{B}) C + D] \cdot E + G \} H$$

Sol:

$$F = \{ [(\bar{A} + \bar{B}) C + D] \cdot E + G \} H$$

$$= (((AB + C) \cdot \bar{D}) + E) \bar{G} + \bar{H} \quad \rightarrow 2 \text{ logic levels (function + input inverters)}$$

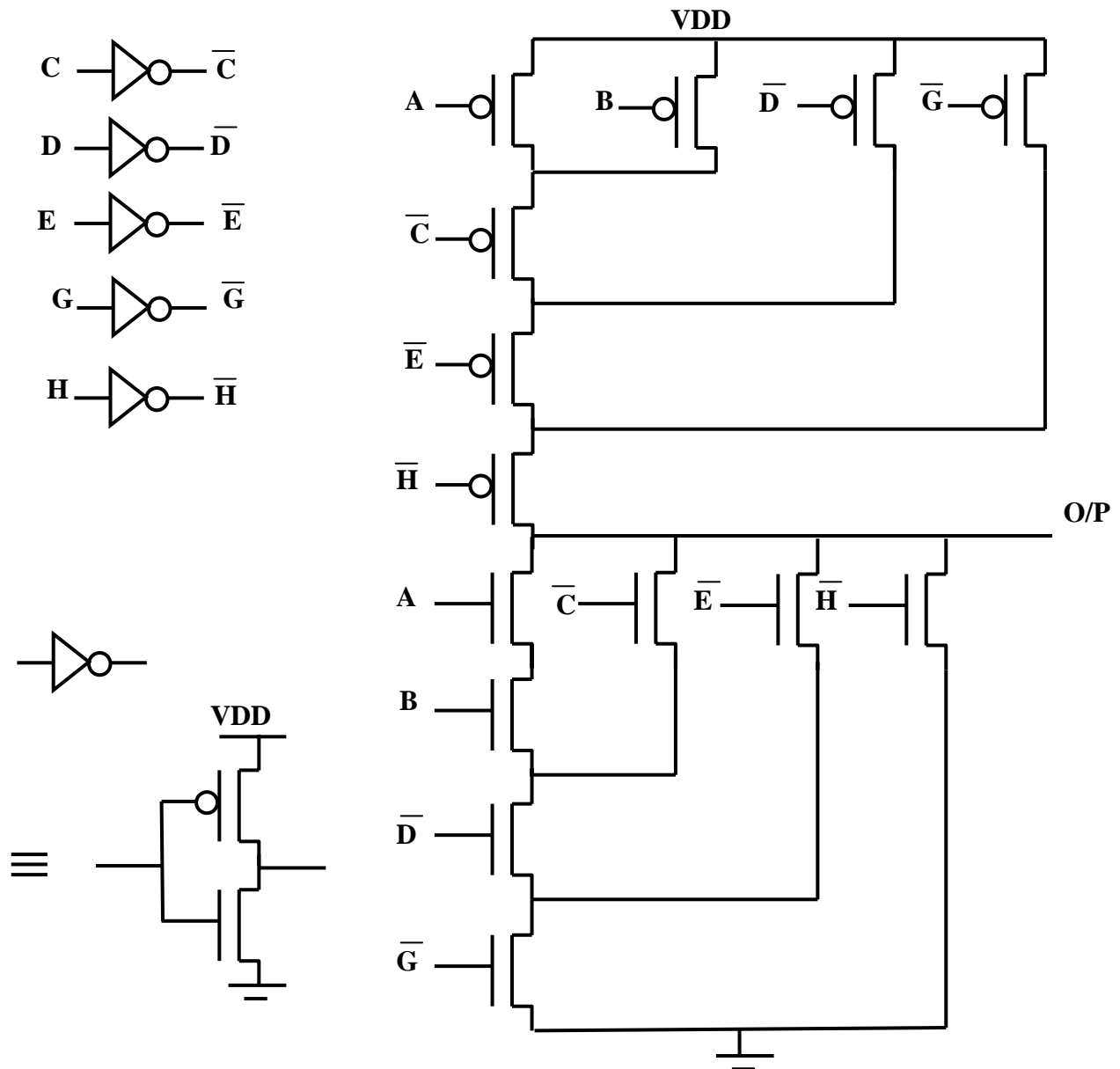

Ex9) Redo Ex8 to obtain minimum number of T

Sol: now we will implement \overline{F} & invert the output

→ the # of T = 4 T to invert A & B

+ 14T to implement the expression

+ 2 to invert the output

= 20 T

→ 20 Transistors → 3 logic levels

$\overline{F} = \overline{(((\overline{A} + \overline{B}) \cdot C + D) \cdot E) + G} \cdot H$ so implement \overline{F} then invert

(to obtain the circuit schematic exchange the PMOS and NMOS blocks in the previous circuit, and invert all I/Ps, e.g. A becomes \overline{A} and \overline{C} becomes C)