

Standard Naming of Logic Functions:

A combination of letters and numbers are used to describe the function and the number of I/Ps.

Letters: A = AND , O = OR , I = Invert

Ex1. AOI 222 : 3 AND terms, that are ORed then Inverted
 ↘ We have 3 logic terms each has 2 I/Ps.

$$F = \overline{(1.2) + (3.4) + (5.6)}$$

$\underbrace{\hspace{100px}}_{A}$

 $\underbrace{\hspace{100px}}_{A}$

 $\underbrace{\hspace{100px}}_{A}$

$\underbrace{\hspace{100px}}_{OR}$

Ex2. OAI 123 → 3 OR terms that are ANDed then Inverted

$$F = \overline{1.(2+3).(4+5+6)}$$


Ex3. AO 223

$$F = \overline{(1.2) + (3.4) + (5.6.7)}$$

CMOS Logic Circuit Design:


Delay Calculation for CMOS Gate:

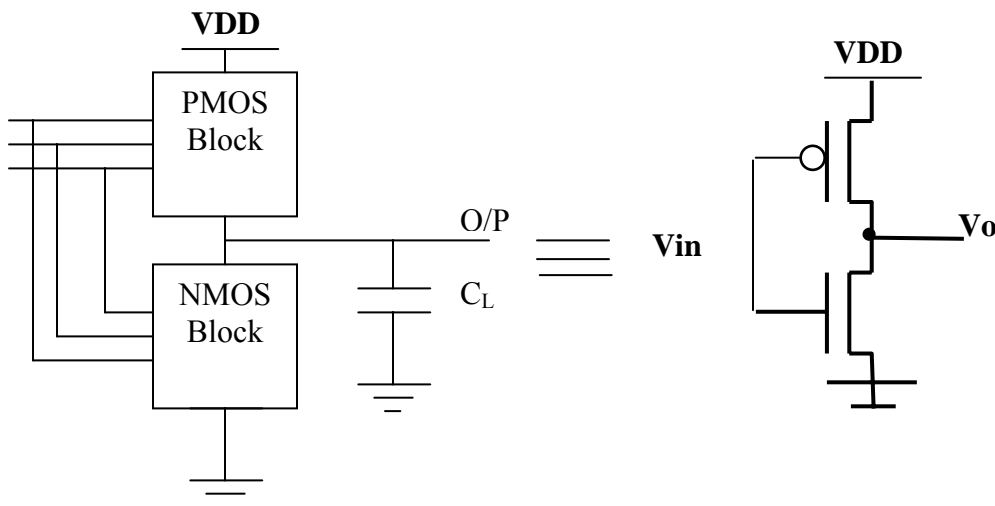In order to calculate the delay of the CMOS gate, we find an equivalent inverter (with equivalent pull-up and pull-down resistances) and calculate $T_D = 0.5 C_L (R_P + R_N)$




Where T_r and T_f of the equivalent inverter = worst case T_r and T_f of the gate.

 - Worst case T_r occur when the O/P is charged (or pulled-up) through the longest chain of series PMOS transistors: e.g. for the PU block below, worst case charging is when $B = D = H = 1$ And $A = C = E = 0$ i.e. charging through A,C, & E.



 - Similarly, worst case T_f occurs when discharging the output through the longest discharging path. For the PD block below, Worst case : 1,4,6 are ON or 2,4,6 or 3,4,6 while every other transistor is off



$$R_{P_{\text{eff}}} = \frac{V_{DD} - V_{th}}{2 I_{DSat}/U_m * W_{P_{\text{eff}}}} \quad , \quad R_{N_{\text{eff}}} = \frac{V_{DD} - V_{th}}{2 I_{DSat}/U_m * W_{N_{\text{eff}}}}$$

W_{eff} of any series connected transistors is obtained as follows:


$$R_{eq1} + R_{eq2} + R_{eq3} = R_{\text{eff}} \rightarrow$$

$$(V_{DD} - V_{th} / 2 \cdot I_{DSat}) \cdot (1/W_1 + 1/W_2 + 1/W_3)$$

$$= (V_{DD} - V_{th} / 2 \cdot I_{DSat} \cdot W_{\text{eff}})$$

$$\rightarrow 1/W_{\text{eff}} = 1/W_1 + 1/W_2 + 1/W_3 \dots$$

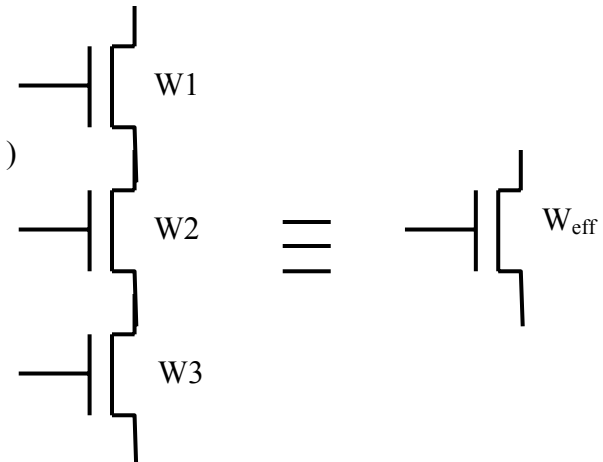If $W_1 = W_2 = W_3 = W_N \rightarrow W_{\text{eff}} = W_N/3$



Ex1. Calculate the maximum frequency of operation of an AOI 222 CMOS gate with a 100 fF load, assuming that all NMOS transistor are 9 μm wide and 1 μm long. All PMOS transistors are 10/1 μm use the 1 μm technology.

$$I_{DSat} = 200 \mu\text{A}/\mu\text{m} , V_{tN} = |V_{tP}| = 0.8\text{V} , V_{DD} = 5\text{V}$$

$$T_{D_{\text{avg}}} = 0.5 C_L (R_P + R_N)$$

$$R_{P_{\text{eff}}} = V_{DD} - |V_{tP}| / (2 \cdot I_{DSat} \cdot W_{P_{\text{eff}}}) \quad , \text{from the circuit schematic below:}$$

$$W_{P_{\text{eff}}} = W_P / 3 = 10/3 = 3.33 \mu\text{m}$$

$$R_{P_{\text{eff}}} = 4.2 / (400 \times 10^{-6} \times 3.33) = 34 \text{ K}\Omega$$

$$R_{N_{\text{eff}}} = (V_{DD} - V_{tN}) / (2 \cdot I_{DSat} \cdot W_{N_{\text{eff}}}) , W_{N_{\text{eff}}} = W_N/2 = 2.5 \mu\text{m}$$

$$R_{N_{\text{eff}}} = 4.2 / (100 \times 10^{-6} \times 2.5) = 1.6 \text{ K}\Omega$$

$$F_{\text{max}} = 1/T_{D_{\text{avg}}} = 1 / (T_r + T_f) = 1 / C_L (R_{P_{\text{eff}}} + R_{N_{\text{eff}}})$$

$$F_{l/P_{\text{max}}} = 1 / (100 \times 10^{-15} \cdot (3.4 + 1.6) \times 10^3)$$

